RRB JE (CBT-2) — Electronics & Allied Engineering — Complete Weighted Book

Exam: RRB Junior Engineer, CEN No. 05/2025 (JE/DMS/CMA)

Exam Group: Electronics & Allied Engineering (Annexure-VII C)

Stage: CBT-2 (Second Stage) — 150 Questions / 150 Marks / 120 min / −⅓ negative marking

This book was built **weighted to the actual exam** — every chapter's depth is proportional to how heavily the topic is tested, derived from the official syllabus **and** a question-by-question analysis of the real 22-04-2025 CBT-2 Electronics paper. Every syllabus line item is covered; nothing is skipped.

How to use this book

- **Technical Abilities is 100 of 150 marks** — it is the whole ball game. Chapters 1–10 below cover it completely.
- The **three heaviest chapters** (Ch2 Devices & Circuits, Ch3 Digital Electronics, Ch7 Communication) carry ~16% each. Master these first.
- General Abilities (50 marks) is covered in the `general-abilities/` capsules, built on **NCERT** for Physics & Chemistry.
- For CBT-1 non-technical (Maths & Reasoning), the `pyq-research/` folder holds a curated PYQ bank instead of full theory, as requested.

Exam Pattern (CBT-2)

Section	Questions	Marks
General Awareness	15	15
Physics & Chemistry	15	15
Basics of Computer Applications	10	10
Basics of Environment & Pollution Control	10	10
Technical Abilities (Electronics)	**100**	**100**
Total	**150**	**150**

Negative marking: −1/3 mark per wrong answer.

Technical Abilities — Chapter Weightage

Ch	Chapter	Weight	Priority
2	Electronic Devices & Circuits	~16%	★★★
3	Digital Electronics	~16%	★★★
7	Communication Engineering	~16%	★★★
1	Electronic Components & Materials	~10%	★★
9	Computer Programming (C/C++, DS, DBMS)	~10%	★★
5	Microprocessor & Microcontroller (8085/8051)	~8%	★★
8	Data Communication & Networks	~8%	★★
10	Basic Electrical Engineering (+ Protection, Earthing)	~8%	★★
4	Linear Integrated Circuits (Op-amp, 555, PLL)	~4%	★
6	Electronic Measurements	~4%	★

Contents

Technical Abilities

1. Electronic Components & Materials
2. Electronic Devices & Circuits
3. Digital Electronics
4. Linear Integrated Circuits
5. Microprocessor & Microcontroller
6. Electronic Measurements
7. Communication Engineering
8. Data Communication & Networks
9. Computer Programming
10. Basic Electrical Engineering

General Abilities (NCERT-based)

- Physics (NCERT)
- Chemistry (NCERT)
- Basics of Computer Applications
- Environment & Pollution Control
- General Awareness Capsule

PYQ Research (CBT-1 non-technical)

- CBT-1 Mathematics & Reasoning PYQ Bank

Blueprint & methodology: see 00_Blueprint_and_Weightage.md.

RRB JE — Electronics & Allied Engineering Book — Blueprint & Weightage

Source documents (in `RRB/Rrb/`):

- `official-syllabus.pdf` — CEN 05/2025 Annexure-VII C (Electronics & Allied Engineering Exam Group, CBT-2)
- `Electronics-and-Allied-Engineering-Shift-02.pdf` — actual CBT-2 paper (22/04/2025), 100 Q analysed
- Screenshot (Adda247) — CBT-2 marks distribution
- CBT-1 answer keys (19-02-2026 S1/S2) — for CBT-1 pattern reference

CBT-2 Exam Pattern (150 Q / 150 marks, 2 hrs, −1/3 negative)

Section	Questions	Marks
General Awareness	15	15
Physics & Chemistry	15	15
Basics of Computer Applications	10	10
Basics of Environment & Pollution Control	10	10
Technical Abilities (Electronics)	**100**	**100**

> Note: In the analysed Shift-2 paper, Q1–50 covered General Abilities and Q51–100 Technical (shift-level variation exists); the official pattern above is the planning basis.

Technical Abilities — observed distribution (50 technical Q of Shift-2, scaled ×2 to 100)

#	Syllabus Unit (Annexure-VII C)	Observed Q (of 50)	Weight %	Book pages target
2	Electronic Devices & Circuits	8	16%	~40
3	Digital Electronics	8	16%	~40
7	Communication Engineering	8	16%	~40
1	Electronic Components & Materials	5	10%	~25
9	Computer Programming (C/C++, DS, DBMS)	5	10%	~25
5	Microprocessor & Microcontroller (8085/8051)	4	8%	~20
8	Data Communication & Networks	4	8%	~20
10	Basic Electrical Engg. (incl. relays/protection)	4	8%	~20
4	Linear Integrated Circuits (Op-amp, 555, PLL)	2	4%	~12
6	Electronic Measurements	2	4%	~12

Chapter depth follows this weightage — heavier chapters get more solved examples and practice MCQs — but **every syllabus line item is covered**, no topic skipped.

Chapter files

File	Chapter
`chapters/Ch01_Electronic_Components_Materials.md`	Components & Materials
`chapters/Ch02_Electronic_Devices_Circuits.md`	Devices & Circuits
`chapters/Ch03_Digital_Electronics.md`	Digital Electronics
`chapters/Ch04_Linear_Integrated_Circuits.md`	Linear ICs
`chapters/Ch05_Microprocessor_Microcontroller.md`	µP & µC
`chapters/Ch06_Electronic_Measurements.md`	Measurements
`chapters/Ch07_Communication_Engineering.md`	Communication
`chapters/Ch08_Data_Communication_Networks.md`	Data Comm & Networks
`chapters/Ch09_Computer_Programming.md`	Programming
`chapters/Ch10_Basic_Electrical_Engineering.md`	Basic Electrical
`general-abilities/GA01_Physics_NCERT.md`	Physics (NCERT-based)
`general-abilities/GA02_Chemistry_NCERT.md`	Chemistry (NCERT-based)
`general-abilities/GA03_Computer_Applications.md`	Computer basics
`general-abilities/GA04_Environment_Pollution.md`	Environment & Pollution
`general-abilities/GA05_General_Awareness.md`	GA capsule
`pyq-research/CBT1_PYQ_Maths_Reasoning.md`	CBT-1 Maths + Reasoning PYQs

Chapter format standard (every chapter)

1. **Weightage box** — Q expected, PYQ trend
2. **Concept sections** — NCERT-grounded first-principles explanations, every syllabus line item
3. **Worked examples** — numerical + conceptual
4. **PYQ-style solved questions** — including the actual 2025 CBT-2 questions from this unit with solutions
5. **Practice MCQs with answer key**
6. **Rapid-revision formula/fact sheet**

Chapter 1 — Electronic Components & Materials

RRB JE CBT-2 · Electronics & Allied Engineering (CEN 05/2025, Annexure-VII C, Unit 1)

> **Syllabus text (Unit 1):** *Electronic Components & Materials: Conductors, Semi-conductor & Insulators; Magnetic materials; Jointing & Cleaning materials for U/G copper cable & OFC; Cells and Batteries (chargeable and non-chargeable); Relays, Switches, MCB & Connectors.*

📊 Weightage & Trend Box

Parameter	Value
Weight in Technical section	**~10 %** (5 of 50 technical Q in the actual 22-04-2025 CBT-2 Shift-2 paper; ≈ 10 of 100 on the official pattern)
Difficulty level	Easy–Moderate (definition + property-based; almost no lengthy numericals)
Best scoring strategy	Memorise property tables (resistivity, dielectric strength, battery chemistry, insulation classes) — these convert directly into marks

Questions actually observed in the 22-04-2025 CBT-2 paper from this unit:

1. **Dielectric strength** — definition (maximum electric field an insulator withstands without breakdown, kV/mm).
2. **Conductor material choice** — why **copper** is preferred (high conductivity **and** corrosion resistance).
3. **Mineral insulating materials** — their applications (used where **mechanical strength + insulation** are both needed: e.g., porcelain/ceramic line insulators, mica in heating appliances).
4. **Nickel–Iron (Edison) cell** — discharge chemistry ($NiOOH/Ni(OH)_3$ positive plate reduced to $Ni(OH)_2$; iron negative plate oxidised to $Fe(OH)_2$; KOH electrolyte concentration essentially unchanged).
5. **Resistor rating** — what decides the rating of a resistor (**permissible power dissipation** — wattage).

Trend takeaway: The board tests *definitions, material selection logic and cell chemistry* — exactly the content of the tables and boxed definitions in this chapter. Every one of the five 2025 questions is solved in the **PYQ Corner** (Section 12).

---

1. Classification of Materials — Conductors, Semiconductors, Insulators

1.1 On the basis of conductivity / resistivity

Class	Resistivity ρ (Ω·m)	Conductivity σ (S/m)	Examples
Conductor	10^{-8} – 10^{-6}	10^{6} – 10^{8}	Ag, Cu, Al, Fe
Semiconductor	10^{-5} – 10^{6}	10^{-6} – 10^{5}	Ge, Si, GaAs, InP
Insulator	10^{8} – 10^{18}	negligible	Mica, glass, PVC, porcelain, quartz

1.2 Energy-band explanation (the *why*)

In a solid, discrete atomic levels broaden into **bands**. The two bands that matter:

- **Valence band (VB)** — highest band filled with electrons at 0 K.
- **Conduction band (CB)** — the next higher band; electrons here are free to conduct.
- **Forbidden energy gap (E_g)** — separation between VB top and CB bottom.

Material	Band picture	Energy gap E_g	Behaviour
Conductor	VB and CB **overlap** (no gap)	$E_g \approx 0$ eV	Enormous free-electron density (~10^{28}–10^{29} /m^3); conducts at all temperatures
Semiconductor	Small gap	**Si ≈ 1.12 eV, Ge ≈ 0.72 eV, GaAs ≈ 1.43 eV** (at 300 K)	Insulator at 0 K; thermal energy at room temperature lifts some electrons into CB → moderate conduction; conductivity **rises** with temperature (negative temperature coefficient of resistance)
Insulator	Large gap	$E_g > 3$ eV (diamond ≈ 5.5 eV, SiO_2 ≈ 9 eV)	Practically no electrons reach CB; negligible conduction

Key contrasts (exam favourites):

- Conductors have a **positive** temperature coefficient of resistance (resistance ↑ with T); semiconductors and insulators have a **negative** one.
- In semiconductors current is carried by **electrons and holes**; in metals by electrons only.
- **Intrinsic** semiconductor = pure ($n_i = p_i$); **extrinsic** = doped. Pentavalent donor (P, As, Sb) → **n-type** (electrons majority); trivalent acceptor (B, Al, Ga, In) → **p-type** (holes majority). Typical doping ≈ 1 impurity atom per 10^6–10^8 host atoms.
- Fermi level: middle of the gap (intrinsic); near CB (n-type); near VB (p-type).

---

2. Conductor Materials

2.1 Desirable properties of a conductor material

High conductivity (low ρ), low temperature coefficient, good **corrosion resistance**, adequate mechanical strength/ductility, solderability, availability and low cost.

2.2 Resistivity table (memorise — direct questions)

Material	ρ at 20 °C (Ω·m ×10^{-8})	Temp. coeff. α (/°C)	Chief uses
Silver (Ag)	1.59 (lowest of all)	0.0038	Contact plating, precision contacts, fuses
Copper (Cu)	1.68–1.72	0.00393	Windings, cables, busbars, PCB tracks
Gold (Au)	2.44	0.0034	Connector plating (does not tarnish)
Aluminium (Al)	2.65–2.82	0.0039	Overhead lines (ACSR), light busbars
Tungsten (W)	5.6	0.0045	Lamp filaments (m.p. 3422 °C — highest of metals)
Iron (Fe)	9.7	0.005	Earth wires, structural
Nichrome (80Ni-20Cr)	≈ 100–112	0.0001	Heating elements (high ρ, oxidation-resistant up to ~1150 °C)
Manganin (Cu-Mn-Ni)	≈ 44–48	≈ 0.00001 (almost zero)	Precision/standard resistors, shunts
Constantan / Eureka (55Cu-45Ni)	≈ 49	≈ 0.00002	Thermocouples, precision resistors, strain gauges

Why copper is the standard electrical conductor (2025 PYQ): second-highest conductivity (only silver beats it) **plus** excellent **corrosion resistance**, high ductility/malleability (drawn into fine wires), good mechanical strength, easy soldering, and reasonable cost. Silver is better electrically but too costly and tarnishes (Ag_2S); iron corrodes and has ~6× the resistivity.


Copper vs Aluminium:

Property	Copper	Aluminium
Conductivity	100 % IACS reference	≈ 61 % of Cu
Density	8.96 g/cm^3	2.70 g/cm^3 (≈ ⅓ of Cu) — for equal conductance an Al conductor is ~50 % lighter though ~1.6× thicker
Solderability / jointing	Easy	Difficult (oxide film Al_2O_3); needs special flux/crimping
Uses	Machine windings, U/G cables, house wiring	Long-span overhead transmission (ACSR)

2.3 Solid vs stranded conductors; ACSR

- **Solid conductor:** single wire — cheapest, most rigid; used in short fixed wiring, PCB jumpers.
- **Stranded conductor:** many thin wires twisted together — **flexible**, resists fatigue from vibration/bending; standard strandings 7, 19, 37, 61 … (formula $3n^2 + 3n + 1$ layers). Used in cables, appliance cords, overhead lines.
- **ACSR (Aluminium Conductor Steel Reinforced):** central galvanised-steel strand(s) give **tensile strength** (long spans, less sag), outer aluminium strands carry the current (skin effect makes the periphery carry most AC current anyway). Standard for HV overhead transmission.
- **Bundled conductors** (2/3/4 sub-conductors per phase) at EHV reduce corona and line reactance.
- **Skin effect:** at AC, current crowds to the surface; effective resistance rises with frequency — another reason hollow/stranded/bundled conductors are used at high frequency/EHV.

3. Resistors

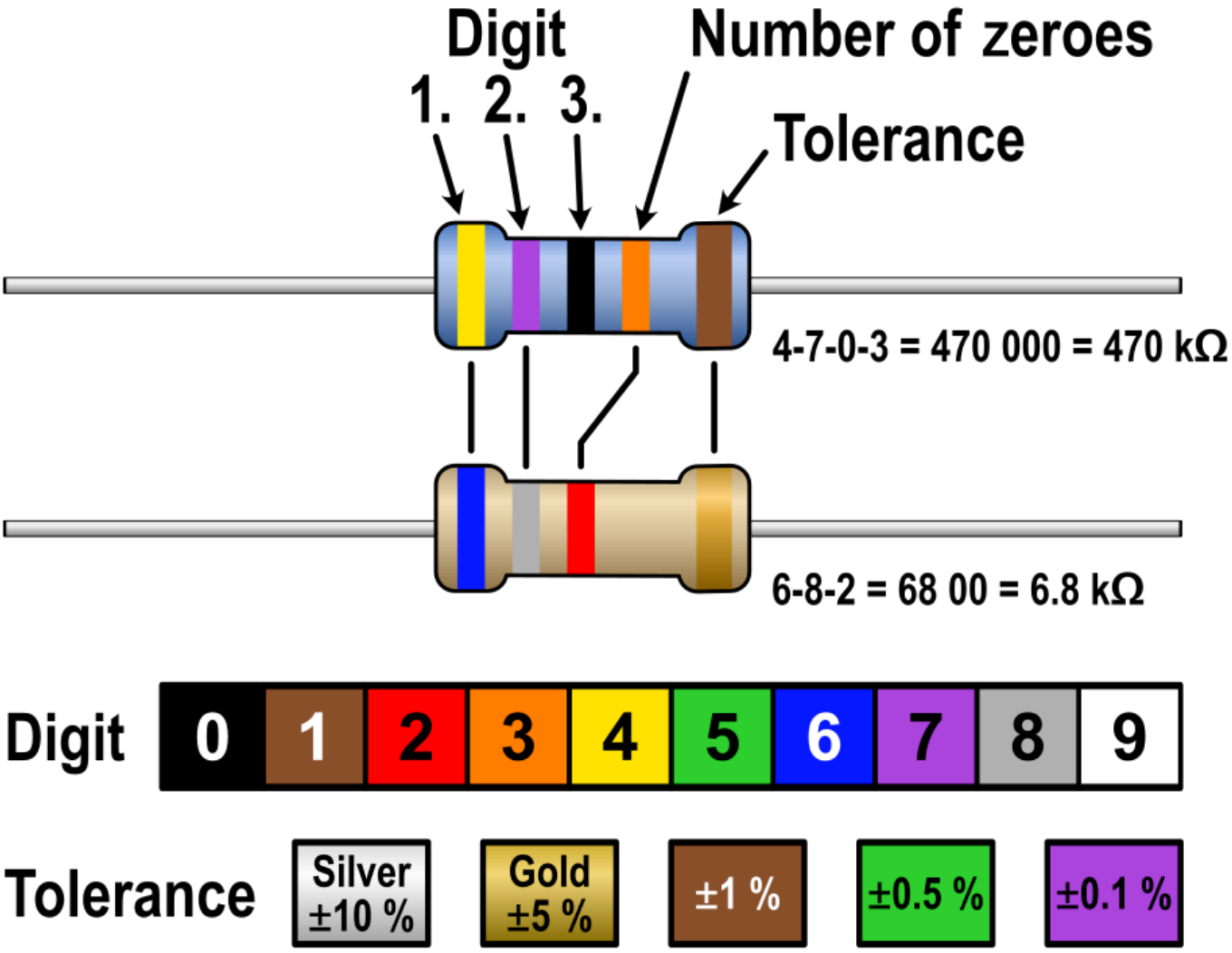

Resistor colour-code chart.

A resistor opposes current: $V = IR$; power dissipated $P = I^2R = V^2/R$.

3.1 Types

Type	Construction	Tolerance	Features
Carbon composition	Carbon + binder rod	±5 to ±20 %	Cheap, high noise, poor stability; withstands pulses
Carbon film	Carbon film spiralled on ceramic	±2 to ±5 %	General purpose, low cost
Metal film	Ni-Cr film on ceramic	±0.1 to ±2 %	Low noise, precise, stable — precision circuits
Metal oxide film	Tin-oxide film	±1 to ±5 %	Higher power & temperature capability
Wire-wound	Nichrome/manganin wire on ceramic former	±0.05 to ±5 %	Highest power (to hundreds of W) & precision, but **inductive** — unsuitable at high frequency (non-inductive Ayrton–Perry winding used for RF)
SMD (chip) resistor	Thick/thin film on ceramic chip (0402, 0603, 0805, 1206 sizes)	±1, ±5 %	Marked with 3/4-digit code (e.g., **472 = 47 × 10^2 = 4.7 kΩ**; 1002 = 100 × 10^2 = 10 kΩ); "0R0" = zero-ohm link
Fusible / fusistor	Designed to open safely on overload	—	Combined resistor + fuse

3.2 Colour code

B B ROY of Great Britain had a Very Good Wife →

Colour	Digit	Multiplier	Tolerance
Black	0	10^0	—
Brown	1	10^1	±1 %
Red	2	10^2	±2 %
Orange	3	10^3	—
Yellow	4	10^4	—
Green	5	10^5	±0.5 %
Blue	6	10^6	±0.25 %
Violet	7	10^7	±0.1 %
Grey	8	10^8	±0.05 %
White	9	10^9	—
Gold	—	10^{-1}	±5 %
Silver	—	10^{-2}	±10 %
No band	—	—	±20 %

- **4-band:** digit-digit-multiplier-tolerance.
- **5-band (precision):** digit-digit-digit-multiplier-tolerance.
- A 6th band, when present, gives the temperature coefficient (ppm/°C).


3.3 Power rating — what decides a resistor's "rating" (2025 PYQ)

> **The rating (wattage) of a resistor is determined by the maximum power it can safely dissipate as heat without its temperature exceeding the permissible limit** — i.e., by **permissible power dissipation**, which depends on physical size, surface area, materials and ambient temperature. Common ratings: ⅛ W, ¼ W, ½ W, 1 W, 2 W, 5 W, 10 W… Bigger body ⇒ higher wattage. Design rule: choose a rating ≥ 2× the expected dissipation (derating), because rated power falls at high ambient temperature.

3.4 Non-linear / special resistors

Device	Behaviour	Material	Applications
LDR (light-dependent resistor / photoresistor)	Resistance **falls** as illumination rises (MΩ dark → few hundred Ω bright)	CdS, CdSe	Street-light control, light meters, alarms
Thermistor NTC	Resistance **falls** with temperature (exponential; $R = R_0 e^{\beta(1/T - 1/T_0)}$)	Sintered Mn/Ni/Co oxides	Temperature sensing, inrush-current limiting
Thermistor PTC	Resistance **rises sharply** above a switch temperature	Doped $BaTiO_3$	Over-current/over-temperature protection, self-regulating heaters, CRT degaussing
Varistor (VDR / MOV)	Resistance falls steeply above a threshold voltage (symmetrical, $V = kI^{\beta}$)	ZnO (metal-oxide)	Surge/transient (lightning) protection across supply lines
Potentiometer / preset / rheostat	Manually variable	Carbon/cermet/wire	Volume controls, calibration, current control

4. Capacitors

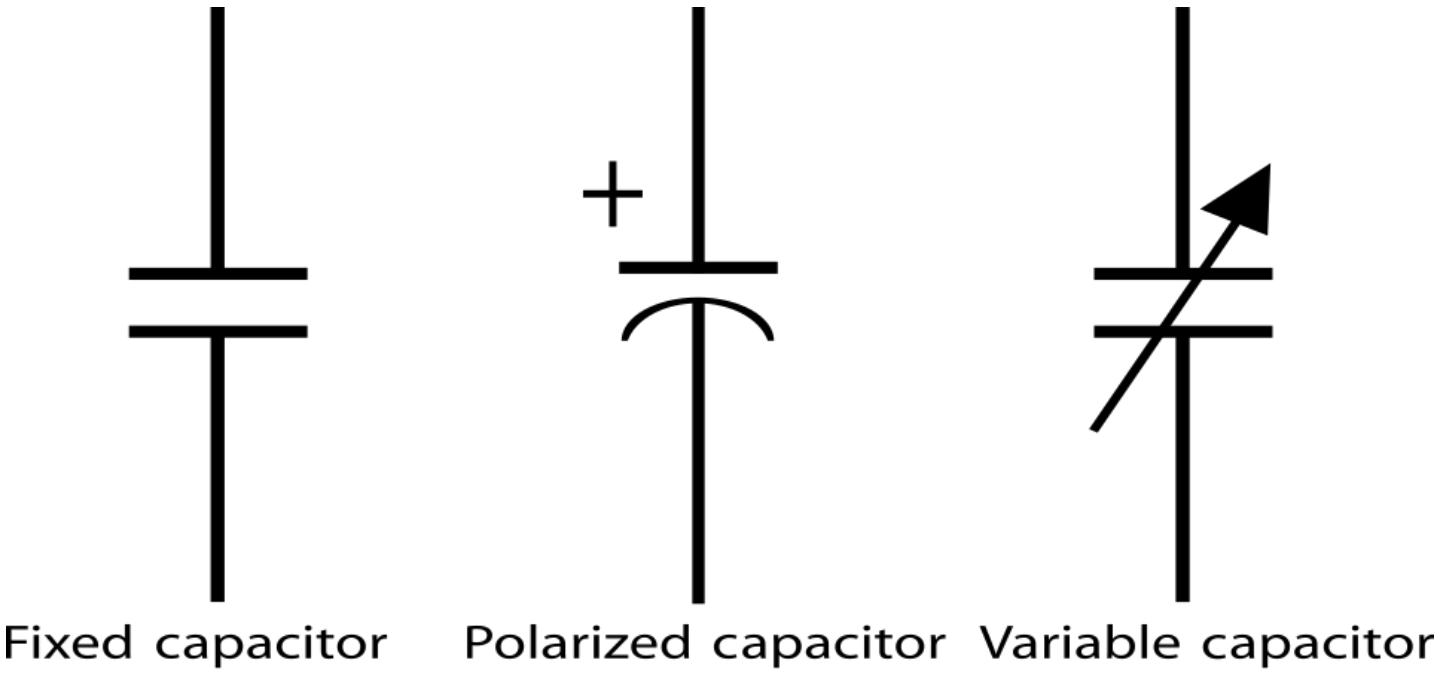

Common capacitor types.

A capacitor stores charge/energy in the electric field between plates: **$C = \varepsilon A/d = \varepsilon_0\varepsilon_r A/d$**; Q = CV.

Energy stored: $W = \frac{1}{2}CV^2 = \frac{1}{2}QV = Q^2/2C$ (joules).

4.1 Two definitions you must not confuse (2025 PYQ)

> **Dielectric constant (relative permittivity, ε_r):** the ratio of the permittivity of the dielectric to that of free space ($\varepsilon/\varepsilon_0$); equivalently, the factor by which capacitance increases when the dielectric replaces vacuum. Dimensionless. (Air ≈ 1.0006, paper ≈ 2–4, mica ≈ 5–7, ceramic 6 → several thousand, water ≈ 80.)

> **Dielectric strength:** the **maximum electric field (potential gradient) an insulating material can withstand without breakdown**, i.e., without losing its insulating property. Units **kV/mm** (or V/m). It is a *breakdown* property, not a *storage* property.

Typical dielectric strengths: **air ≈ 3 kV/mm**, transformer oil ≈ 10–15 kV/mm (test ≥ 30 kV across a 2.5 mm gap), paper (impregnated) ≈ 15–25 kV/mm, porcelain ≈ 10–15 kV/mm, glass ≈ 20–30 kV/mm, **mica ≈ 50–120 kV/mm (among the highest)**, polyethylene/XLPE ≈ 20–40 kV/mm, PVC ≈ 15–30 kV/mm, ceramic ≈ 5–10 kV/mm, SF_6 gas ≈ 8–9 kV/mm at 1 atm (≈ 2.5–3× air).

4.2 Capacitor types

Type	Dielectric	Range	Polarity	Key features / uses
Ceramic (disc / MLCC)	Ceramic (Class 1 NP0/C0G stable; Class 2 X7R/Y5V high-k)	pF → µF	Non-polar	Cheap, small, RF decoupling/bypass; Class 2 values drift with V & T
Mica (silvered)	Mica sheets	pF → nF	Non-polar	Very stable, precise, low loss, high dielectric strength — RF tuned circuits, HV
Paper	Kraft paper impregnated with oil/wax	nF → µF	Non-polar	Older motor/power-factor use; superseded by film
Plastic film	Polyester (Mylar), polypropylene, polystyrene, PTFE	nF → µF	Non-polar	Low loss, self-healing (metallised film), timing, audio, snubbers, AC motor-run
Aluminium electrolytic	Al_2O_3 film formed on etched Al foil, wet electrolyte	1 µF → 10^4 µF+	**Polarised** (reverse connection destroys it)	Huge C/volume; power-supply filtering/smoothing; high leakage & tolerance (−20/+80 %); limited life (electrolyte dries)
Tantalum	Ta_2O_5 on sintered tantalum	0.1 → few hundred µF	**Polarised**	Smaller, stabler, lower leakage than Al electrolytic; low ESR; fails short if reversed/over-volted
Supercapacitor (EDLC)	Electric double layer on activated carbon	0.1 F → 1000s F	Polarised	Memory backup, energy buffering; low voltage/cell (~2.5–2.7 V)
Variable (gang / trimmer)	Air / mica / plastic	pF	Non-polar	Radio tuning, circuit alignment

4.3 Combinations

- **Parallel:** C_eq = $C_1 + C_2 + \ldots$ (capacitances add; same V).
- **Series:** 1/C_eq = $1/C_1 + 1/C_2 + \ldots$ (same Q; voltage divides inversely as C). Two in series: C_eq = $C_1C_2/(C_1+C_2)$.
- (Note this is the **opposite** of resistors.)

4.4 Practical parameters

Working voltage (choose ≥ 1.5–2× circuit voltage), tolerance, leakage current, **ESR** (equivalent series resistance — low ESR needed in SMPS filters), dissipation factor tan δ, temperature coefficient. Capacitor 3-digit code like resistor SMD: **104 = 10 × 10^4 pF = 100 nF = 0.1 µF**.

Applications recap: filtering/smoothing (electrolytic), coupling/DC-blocking, decoupling/bypass (ceramic 0.1 µF), tuning (variable/mica), timing (film, with R: τ = RC), power-factor correction, motor start/run, energy storage (photo-flash, defibrillator), snubbers.

---

5. Inductors & Transformers as Components

5.1 Inductors

Store energy in a magnetic field: **$W = \frac{1}{2}LI^2$**; v = L di/dt. Unit **henry (H)**.

- **Inductance of a solenoid:** $L = \mu_0\mu_r N^2 A/l$ — increases with turns^2 and core permeability.
- **Types:** air-core (RF, no saturation), iron-core laminated (AF/power chokes), **ferrite-core** (SMPS, RF — low eddy loss), toroidal (self-shielding, high efficiency), moulded/SMD chip inductors, variable (slug-tuned).
- **Series:** $L_{eq} = L_1 + L_2$ (+2M if mutually coupled aiding, −2M opposing). **Parallel:** $1/L_{eq} = 1/L_1 + 1/L_2$ (no coupling).
- **Quality factor Q = ωL/R** — figure of merit; higher Q ⇒ sharper tuning.
- Applications: filters/chokes, tuned circuits ($f_0 = 1/2\pi\sqrt{LC}$), SMPS energy storage, RFI suppression (ferrite beads).

5.2 Transformers (component view)

Static device transferring AC power by mutual induction: **$V_2/V_1 = N_2/N_1 = I_1/I_2$** (ideal).

- EMF equation: **$E = 4.44\, f\, N\, \Phi_m$**.
- Small-signal component types: mains (50 Hz laminated **CRGO** core), audio (impedance matching: $Z_1/Z_2 = (N_1/N_2)^2$), pulse, RF/IF (ferrite/air core), isolation (1:1, safety), auto-transformer (single tapped winding — no isolation), current transformer (CT — never open-circuit the secondary while energised).
- Losses: **core/iron losses** (hysteresis + eddy — constant) and **copper loss I^2R** (load-dependent); maximum efficiency when copper loss = iron loss.

---

6. Insulating Materials

6.1 Required properties

High resistivity, high **dielectric strength**, low dielectric loss (tan δ), adequate mechanical strength, thermal endurance, resistance to moisture/chemicals/ageing.

6.2 Thermal classification of insulation (IS/IEC 60085) — memorise

Class	Max. operating temp.	Typical materials
Y	90 °C	Un-impregnated paper, cotton, silk
A	105 °C	Impregnated paper/cotton, oil-immersed insulation
E	120 °C	Enamelled wire coverings, polyester film
B	130 °C	Mica, glass fibre, asbestos with organic binder
F	155 °C	Mica/glass fibre with epoxy/alkyd binders
H	180 °C	Mica/glass fibre with silicone binder; silicone rubber
C	> 180 °C	Mica, porcelain, ceramics, glass, quartz, PTFE


(Trick: **Y-A-E-B-F-H-C = 90-105-120-130-155-180-above 180**.)

6.3 Important insulating materials & applications

Material	Nature	Key properties	Applications
Mica (muscovite/phlogopite)	Mineral	Splits into thin flexible sheets; dielectric strength up to ~50–120 kV/mm; heat-proof to ~600 °C+; low loss	Commutator segment separation, capacitor dielectric, **heating-appliance element support (iron/toaster)**, insulation washers
Porcelain / ceramic	Mineral (fired clay + quartz + feldspar)	**High mechanical (compressive) strength + insulation together**; weather/arc resistant; brittle in tension	**Overhead-line insulators (pin, disc/suspension, strain, shackle)**, bushings, fuse bodies, resistor formers
Steatite / alumina ceramics	Mineral	High-frequency low loss; hard	RF coil formers, spark-plug insulators (alumina), substrates
Glass (toughened)	Mineral	Transparent (cracks visible), dielectric strength 20–30 kV/mm	Suspension-line insulators, lamp envelopes, glass-fibre insulation
Asbestos *(legacy)*	Mineral fibre	Heat-proof	Older heater/arc-chute insulation (now avoided — health hazard)
Rubber (natural/synthetic, silicone)	Organic/polymer	Flexible	Wire covering, gloves/mats (safety), silicone for class-H
PVC	Thermoplastic polymer	Cheap, tough, flame-retardant, moisture-proof; but max ~70–105 °C	LT cable and house-wiring insulation & sheathing
Polyethylene (PE) / XLPE	Polymer (XLPE = cross-linked)	Very low loss; XLPE withstands 90 °C continuous (250 °C short-circuit)	**HV/EHV underground cable insulation (XLPE)**, coaxial-cable dielectric (PE)
PTFE (Teflon)	Fluoropolymer	$\varepsilon_r \approx 2.1$, works −200…+260 °C, chemically inert	RF coax, aerospace wiring, non-stick bushings
Bakelite (phenolic)	Thermoset	Hard, machinable	Switch/plug bodies, terminal boards, older PCBs (FR-2); FR-4 = glass-epoxy
Transformer (mineral) oil	Liquid	Dielectric strength ≥ 30 kV per 2.5 mm gap (BDV test); also a **coolant**	Transformer/CB insulation & cooling; tested for BDV, moisture, acidity
SF_6 gas	Gas	Electronegative; dielectric strength ≈ 2.5–3× air; excellent arc quenching	Gas-insulated switchgear (GIS), HV circuit breakers *(strong greenhouse gas — handled in closed cycle)*
Air / vacuum / N_2	Gas	Air ≈ 3 kV/mm	Overhead-line spacing, vacuum interrupters (MV breakers), capacitors

Mineral insulating materials (2025 PYQ): mica, porcelain/ceramics, glass, steatite, marble, slate, asbestos, quartz. They are chosen **where the part must simultaneously insulate and bear mechanical load and/or high temperature** — overhead-line insulators and bushings (porcelain/glass), heating appliances and commutators (mica), panel boards (marble/slate legacy), high-temperature class-C insulation. Also the basis of **MICC (mineral-insulated copper-clad) cable** — copper conductors in compressed **magnesium-oxide (MgO)** powder inside a copper sheath — used for fire-survival circuits (alarms, emergency lighting).

7. Magnetic Materials

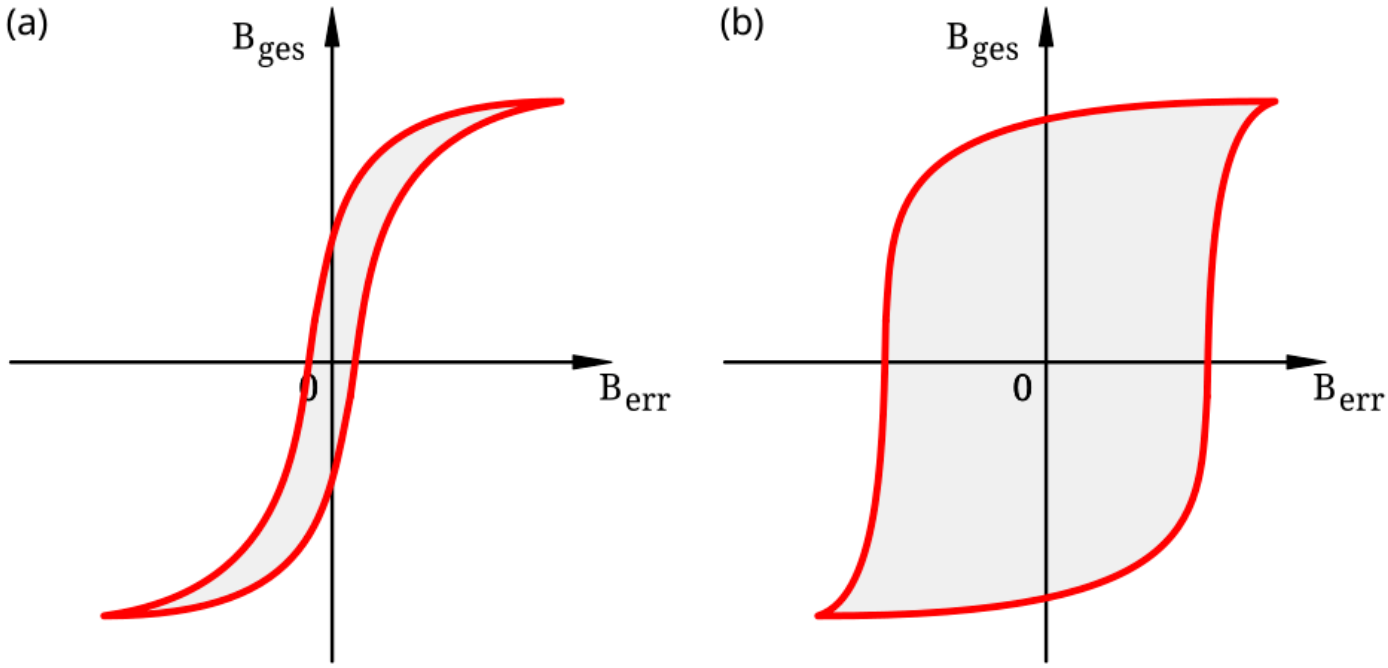

B–H hysteresis loops: soft vs hard magnetic material.

7.1 Classification by magnetic behaviour

Class	Relative permeability μ_r	Susceptibility χ	Behaviour	Examples
Diamagnetic	Slightly < 1	Small negative	Weakly **repelled** by field; magnetisation opposes H; independent of temperature	Cu, Ag, Au, Bi, Zn, water, superconductors (perfect diamagnets, $\chi = -1$)
Paramagnetic	Slightly > 1	Small positive	Weakly attracted; obeys **Curie law** $\chi \propto 1/T$	Al, Pt, Mn, Cr, O_2, Na
Ferromagnetic	$\gg 1$ ($10^2 - 10^5$)	Large positive	Strongly attracted; domains; spontaneous magnetisation; hysteresis; becomes paramagnetic above **Curie temperature** (Fe 770 °C, Ni 358 °C, Co 1131 °C)	Fe, Ni, Co, and alloys
Antiferromagnetic	≈ 1	small	Adjacent moments antiparallel, cancel	MnO, Cr
Ferrimagnetic (ferrites)	high	large	Antiparallel but unequal moments → net magnetisation; **high resistivity**	Fe_3O_4, Mn-Zn & Ni-Zn ferrites

7.2 B–H (hysteresis) loop terms

- **B** lags **H** → loop. **Retentivity/remanence (B_r):** flux density remaining when H → 0. **Coercivity (H_c):** reverse H needed to bring B to zero. **Saturation (B_sat):** further H gives no extra B.
- **Hysteresis loss per cycle ∝ loop area**; Steinmetz: **P_h = η B_max^1.6 f V** (watts).
- **Eddy-current loss:** $P_e = K_e B_{max}^2 f^2 t^2 V$ — reduced by **laminating** the core (thin varnish-insulated 0.35–0.5 mm sheets) or using high-resistivity **ferrites** at high frequency.

7.3 Soft vs hard magnetic materials

Property	Soft magnetic	Hard magnetic
Hysteresis loop	**Narrow/thin** (small area)	**Broad/fat** (large area)
Coercivity	Low (easy to demagnetise)	High (hard to demagnetise)
Retentivity usable?	Not required	High — retains magnetism
Permeability	Very high	Lower
Use	**Temporary magnets / AC cores** — transformer & motor cores, relay armatures, electromagnet cores, chokes	**Permanent magnets** — loudspeakers, PMMC meters, magnetos, small PM motors, holding magnets
Examples	Pure (soft) iron, **CRGO silicon steel**, permalloy (Ni-Fe), mumetal (shielding), amorphous metal, soft ferrites (Mn-Zn, Ni-Zn)	Carbon/tungsten/cobalt steels, **Alnico** (Al-Ni-Co-Fe), hard ferrites (barium/strontium ferrite), Sm-Co, **Nd-Fe-B (strongest)**

CRGO silicon steel: cold-rolled grain-oriented steel with ~3–4 % silicon. Silicon **raises resistivity (cuts eddy loss)** and reduces hysteresis loss; grain orientation gives highest permeability along rolling direction. Standard for **power/distribution transformer cores** (CRNGO — non-oriented — for rotating machines, where flux direction changes).

Ferrites: ceramic ferrimagnetic oxides MFe_2O_4. Very high resistivity ⇒ negligible eddy loss ⇒ ideal **above ~1 kHz to hundreds of MHz**: SMPS transformer cores, antenna rods, RFI beads, deflection yokes, memory cores (historical). Soft ferrites = Mn-Zn (to ~1 MHz), Ni-Zn (to ~100 MHz); hard ferrites = ceramic permanent magnets (cheap fridge/speaker magnets).

Alnico: cast/sintered Al-Ni-Co-Fe permanent-magnet alloy; high retentivity and best temperature stability (usable to ~500 °C); used in instruments, loudspeakers, guitar pickups.

---

8. Jointing & Cleaning Materials — U/G Copper Cable & OFC

(Railway S&T context: underground jelly-filled telecom copper cables and optical-fibre cables along the track.)

8.1 Soldering materials

- **Solder** = fusible alloy that joins metals below their melting points.
- **Tin-lead (soft solder):** 60Sn-40Pb (m.p. ≈ 188 °C, electronics standard) and **63Sn-37Pb eutectic (183 °C — melts/freezes at a single temperature, no plastic/pasty range → best joints)**; 50/50 and 40/60 (plumber's, wiping joints on lead-sheathed cables).
- **Lead-free (RoHS):** SAC305 = 96.5Sn-3Ag-0.5Cu, m.p. ≈ 217 °C.
- **Hard solder / brazing:** silver solder, spelter — > 450 °C, stronger joints.
- **Flux** removes/prevents oxide so solder wets the metal:
- **Rosin (colophony)** — non-corrosive, for **electronics/telecom conductors** (RA/RMA grades).
- **Zinc chloride ("killed spirits") / acid flux** — active, for sheet-metal/galvanised work — **never on electronic joints** (corrosive residue).
- Water-soluble and no-clean fluxes in modern assembly.

- A good soldered joint is bright, concave-filleted; a **dry (cold) joint** is dull grey, high-resistance, unreliable.

8.2 Underground copper-cable jointing materials

Item	Purpose
Jelly-filled cable (PIJF) — polythene-insulated, petroleum-jelly-filled	The jelly blocks longitudinal water ingress in U/G telecom cable
Crimp/wire connectors (UY/UR/UG "B-wire"/3M Scotchlok type), jelly-filled	Splice individual copper pairs without soldering; jelly inside keeps moisture out
Cable jointing kit	Complete set: joint sleeve/closure, sealing tapes, resin or heat-shrink, connectors, abrasive strip, instructions
Heat-shrink sleeves/tubes (cross-linked polyolefin, often with hot-melt adhesive lining)	Shrink to ~½ diameter on heating (torch/hot-air) forming a sealed, insulated cover over the joint
Epoxy/polyurethane resin compound (two-part, poured into mould)	Fully encapsulates LT power-cable joints — waterproof and mechanically solid
Cold-shrink / push-on sleeves	Pre-stretched EPDM/silicone tube that contracts when the holdout is removed — no flame needed
Insulating & self-amalgamating tapes	PVC tape for covering; self-amalgamating (self-fusing) rubber tape fuses into a solid waterproof mass
Cable lugs (copper/aluminium, tinned; crimped or soldered) & **ferrules**	Terminate a conductor for bolting to equipment; bimetallic (Cu-Al) lugs stop galvanic corrosion between dissimilar metals
Cable glands (brass/nylon, with armour clamp)	Seal and anchor the cable where it enters an enclosure; earth the armour
Joint closure boxes (mechanical, re-enterable)	Protect telecom splices in manholes/pits
Denso (petrolatum) tape / bitumen compound	Corrosion protection of buried metallic sheaths

8.3 OFC (optical fibre cable) splicing & jointing

Method	How	Loss	Use
Fusion splicing	Fibre ends cleaved, aligned, welded by an **electric arc** in a fusion-splicing machine; protected by a heat-shrink **splice-protection sleeve** with steel strength member	**Lowest, ~0.01–0.1 dB**, permanent	Standard for route joints — Railways/telecom backbone
Mechanical splicing	Cleaved fibres butt-aligned in a precision V-groove/gel-filled element; **index-matching gel** fills the gap	~0.1–0.5 dB	Temporary/emergency restoration
Connectorised joints	Field/factory connectors — SC, LC, FC, ST (E2000, MPO) with PC/UPC/APC polish	0.2–0.5 dB per mated pair	Patch panels, FDMS, equipment ends

Supporting materials: **fibre cleaver** (precision 90° cleave is critical), **Kevlar/aramid-yarn scissors**, buffer/coating **stripper**, **splice closure (dome/inline)** with cable-seal heat-shrink and splice trays, loose-tube **thixotropic gel** inside the cable (water blocking), FRP/steel central strength member, HDPE outer sheath, armouring for direct burial.

8.4 Cleaning materials & agents

- **Isopropyl alcohol (IPA, ≥ 99 %)** — the standard cleaning agent for **bare fibre before splicing**, connector end-faces, and flux-residue removal on electronic joints. Fast-evaporating, residue-free.
- **Lint-free wipes / lens tissue** and **one-click connector cleaners / cleaning cassettes** for ferrule end-faces (inspect with a fibre microscope — a dirty end-face is the #1 cause of optical loss).
- **D-Gel / jelly-cleaning solvent** — removes petroleum jelly from PIJF copper pairs and cable-filling gel from loose tubes before jointing.
- **Emery/abrasive strip, wire brush, knife** — brighten copper conductors and sheath before soldering/crimping.
- **Contact cleaner sprays** (for connectors/relays), compressed air (dust), **carbon tetrachloride is obsolete/banned** (toxic, ozone-depleting) — IPA replaces it.
- Never touch or re-use a cleaned bare fibre end; always clean → cleave → splice immediately.

---

9. Cells & Batteries

Cell = single electrochemical unit; **battery** = cells in series/parallel.

Primary (non-chargeable): reaction irreversible — use once. **Secondary (chargeable/accumulator):** reaction reversible by charging.

9.1 Primary cells

Cell	Anode (−)	Cathode (+)	Electrolyte	EMF	Notes
Leclanché / zinc-carbon (dry cell)	Zinc can	Carbon rod + **MnO_2 depolariser**	NH_4Cl (+ $ZnCl_2$) paste	**1.5 V**	Cheapest; polarisation (H_2 at cathode) removed by MnO_2; shelf-life short; sal-ammoniac = NH_4Cl
Alkaline (Zn-MnO_2)	Zinc powder	MnO_2	**KOH**	1.5 V	3–5× capacity of zinc-carbon, better shelf life & leak resistance
Mercury (Zn-HgO) *(phased out)*	Zn	HgO	KOH	**1.35 V — exceptionally flat/stable**	Was used as a voltage reference & in hearing aids; banned (Hg toxicity)
Silver-oxide (Zn-Ag_2O)	Zn	Ag_2O	KOH/NaOH	1.55 V	Watch button cells; very flat discharge
Zinc-air	Zn	O_2 from air	KOH	1.4 V	Highest energy density of common primaries; hearing aids
Lithium coin/cylindrical (Li-MnO_2 "CR"; Li-$SOCl_2$)	Li metal	MnO_2 (or $SOCl_2$)	Organic/non-aqueous	**3.0 V** (Li-$SOCl_2$ 3.6 V)	10-year shelf life; CMOS/RTC backup (CR2032), meters, memory retention

9.2 Secondary cells

(a) Lead-acid cell — the workhorse (Railway train lighting, telecom exchanges, substations, inverters, vehicles)

- **Construction:** positive plate **PbO_2** (chocolate brown), negative plate **spongy Pb** (grey); plates interleaved (always one more negative), separated by PVC/glass-mat separators; electrolyte **dilute H_2SO_4**; container of hard rubber/PP; vent plugs; Pb-Sb or Pb-Ca grids. Types: flooded, tubular (traction), **SMF/VRLA (sealed maintenance-free — AGM or Gel)**.
- **Overall (double-sulphation) reaction:**

$Pb + PbO_2 + 2H_2SO_4 \rightleftharpoons 2PbSO_4 + 2H_2O$ (→ discharge; ← charge)

On **discharge** both plates convert to **whitish $PbSO_4$**, acid is consumed, water is formed ⇒ **specific gravity falls**.

- **Specific gravity of electrolyte:** fully charged ≈ **1.26–1.28** (1.21–1.23 tropical/telecom float); discharged ≈ 1.13–1.18. Measured with a **hydrometer** — the best state-of-charge indicator.
- **Voltages:** nominal **2.0 V/cell**; open-circuit charged ≈ 2.1–2.2 V; **discharge cut-off 1.75–1.8 V/cell (never below)**; gassing voltage ≈ 2.4 V; float 2.15–2.25 V; equalising ≈ 2.5 V. 12 V battery = 6 cells.
- **Efficiency:** ampere-hour (quantity) efficiency ≈ 90–95 %; watt-hour (energy) efficiency ≈ 70–80 %.
- **Sulphation:** if left discharged/undercharged, $PbSO_4$ hardens into large inert crystals that will not reconvert — capacity is permanently lost. Prevention: never store discharged; recharge promptly; trickle/float charge; keep electrolyte level topped **with distilled water only** (acid is added only to correct s.g. after confirmed loss of acid).
- Other ailments: **buckling** of plates (over-discharge/heavy charge), **shedding** of active material (sediment → internal short), internal short, over-gassing (loss of water).

(b) Nickel-Cadmium (Ni-Cd)

- Positive **NiOOH**, negative **Cd**, electrolyte **KOH (≈ 21 %, s.g. ~1.2)** — *electrolyte concentration does not change* (it only transports OH^-).
- $Cd + 2NiOOH + 2H_2O \rightleftharpoons Cd(OH)_2 + 2Ni(OH)_2$. Nominal **1.2 V/cell**.
- Rugged, long life (~2000 cycles), high discharge currents, works at low temperature, flat discharge; drawbacks — **memory effect**, cadmium toxicity (restricted), lower energy density. Uses: railway coach/emergency lighting, aircraft/engine starting, power tools (legacy).

(c) Nickel-Iron (Edison) cell — ★2025 PYQ★

- **Positive electrode:** nickel oxyhydroxide **NiOOH** (often written as hydrated $Ni(OH)_3$ in older texts), in nickel-plated steel tubes with graphite/nickel flakes for conductivity.
- **Negative electrode: iron (Fe)** powder in perforated steel pockets.
- **Electrolyte: KOH ≈ 21 % (s.g. ≈ 1.2), with a little LiOH** added to improve capacity/life. As in all alkaline cells, the **electrolyte concentration/specific gravity stays practically constant** — a hydrometer cannot indicate state of charge.
- **Discharge chemistry:**
- Negative (oxidation): $Fe + 2OH^- \rightarrow Fe(OH)_2 + 2e^-$
- Positive (reduction): $2NiOOH + 2H_2O + 2e^- \rightarrow 2Ni(OH)_2 + 2OH^-$
- **Overall: $Fe + 2NiOOH + 2H_2O \rightleftharpoons Fe(OH)_2 + 2Ni(OH)_2$** (→ discharge; ← charge)
- **Voltages:** EMF charged ≈ **1.4 V**, nominal **1.2 V/cell**, discharge cut-off ≈ 1.0–1.1 V.
- **Features:** almost indestructible mechanically and electrically — tolerates overcharge, over-discharge, short-circuit and standing discharged **without sulphation-type damage**; very long life (20–30 years, thousands of cycles). Drawbacks: low energy density, heavy, poor charge retention (self-discharge 20–40 %/month), low efficiency (~65 % Wh), poor low-temperature performance, higher internal resistance and cost than lead-acid.
- Historic uses: railway train lighting & signalling, mine locomotives, standby supplies — wherever ruggedness beats efficiency.

(d) Nickel-Metal Hydride (Ni-MH)

Positive NiOOH, negative **hydrogen-absorbing alloy (MH)**, KOH electrolyte, **1.2 V/cell**; ~40 % more capacity than Ni-Cd, no cadmium, little memory effect; higher self-discharge (LSD types like Eneloop fixed this). Uses: AA/AAA rechargeables, older hybrid-car packs.

(e) Lithium-ion (Li-ion) / Li-polymer

- **Chemistry:** during **discharge**, Li^+ ions move from the graphite (LiC_6) negative through the organic electrolyte ($LiPF_6$ in carbonate solvents) and **intercalate** into the metal-oxide positive ($LiCoO_2$, NMC, $LiFePO_4$ …); electrons flow through the external circuit; charging reverses this ("rocking-chair" cell).
- Overall (LCO): $LiC_6 + CoO_2 \rightleftharpoons C_6 + LiCoO_2$.
- **Nominal 3.6–3.7 V/cell** ($LiFePO_4$ 3.2 V); charge to 4.2 V/cell with **CC-CV** method only, protection circuit (BMS) mandatory.
- **Advantages:** highest energy density (150–250 Wh/kg), light, no memory effect, low self-discharge (~2–5 %/month), long cycle life (500–2000+), high cell voltage → fewer cells.
- **Cautions:** thermal runaway if overcharged/punctured; capacity fades with age/heat. Uses: phones, laptops, EVs, modern railway applications, grid storage.

9.3 Battery terms & calculations

- **Capacity (Ah):** current × time it can deliver to cut-off at a stated rate (e.g., C_{10} = 10-hour rate, standard for lead-acid; C_{20} for automotive). Faster discharge yields **less** than rated Ah (Peukert effect).
- **C-rate:** discharge/charge current relative to capacity. For 100 Ah: 1C = 100 A, C/10 (0.1C) = 10 A, 2C = 200 A.
- **Energy (Wh) = Ah × nominal V. Energy density** = Wh/kg (gravimetric) or Wh/L (volumetric); **power density** = W/kg.
- **Cycle life:** number of charge-discharge cycles to a stated depth of discharge (DoD) before capacity falls to 80 % of rated.
- **Self-discharge, internal resistance, memory effect** (Ni-Cd), **depth of discharge (DoD)** vs state of charge (SoC).
- **Series connection:** voltages add, Ah same. **Parallel:** Ah add, voltage same.
- **Charging methods:** constant-current (Ni-Cd/Ni-MH, with −ΔV/temperature end detection), constant-voltage/**CC-CV** (lead-acid, Li-ion), taper charge, **trickle charge** (compensates self-discharge, C/50–C/100), **float charge** (battery permanently across load + charger — telecom/substation), **boost/equalising charge** (periodic controlled overcharge of flooded lead-acid to balance cells and stir electrolyte), pulse/fast charging.
- **Lead-acid maintenance drill:** keep terminals clean and petroleum-jelly-coated, electrolyte 10–15 mm above plates (top up with distilled water), check s.g. and cell voltages, keep vents clear, never leave discharged, charge in ventilated area (H_2 + O_2 evolved — explosion risk), never place metal tools across terminals.

---

10. Relays

An **electromagnetic relay** is an electrically operated switch: a small coil current controls one or more contact sets switching an independent (usually larger) circuit — providing **isolation** between control and load.

10.1 Construction & operation (attracted-armature type)

Coil on an iron core + yoke; a hinged **armature** carries the moving contact against a return spring. Coil energised → magnetic pull exceeds spring force → armature attracted → contacts change over. De-energised → spring restores. Key parts: coil, core, yoke, armature, spring, contacts (silver / silver-cadmium-oxide / gold-flashed), **freewheeling diode** across a DC coil to absorb the inductive kick.

- **Pick-up (operate) value:** minimum coil current/voltage at which the relay just operates.
- **Drop-out (release/reset) value:** value at which it releases (< pick-up — hysteresis).
- **Operating time:** typically 5–20 ms (electromechanical).

10.2 Contacts, poles & throws

- **NO (normally open / make, form A):** open when de-energised, closes on operation.
- **NC (normally closed / break, form B):** closed when de-energised, opens on operation.
- **CO/changeover (form C):** one common with one NC + one NO (break-before-make).

- **Pole** = number of separate circuits switched; **throw** = positions per pole. SPST, SPDT, DPDT, 4PDT etc. — a **DPDT relay switches two independent circuits between two positions each**.

10.3 Types of relays

Type	Principle	Typical use
Attracted-armature (hinged/clapper, plunger)	Electromagnetic attraction; works on **AC or DC**; fast, instantaneous	General switching, railway signalling line/track relays, instantaneous overcurrent
Induction type (disc/cup)	Torque from two AC fluxes on an Al disc (like energy-meter); **AC only**; inherent time delay (IDMT — inverse definite minimum time)	Classic overcurrent & directional **protection** relays
Thermal relay	Bimetallic strip bends on I^2R heating	Motor **overload** protection (with contactor starters); time-lagged
Reed relay	Ferromagnetic reed contacts sealed in inert-gas glass tube, operated by coil/magnet around it	Fast (<1 ms), sealed, low-level signal switching, proximity sensing
Latching (bistable) relay	Permanent magnet/second coil holds either state with no coil power	Memory/energy-saving switching
Solid-state relay (SSR)	No moving parts — optocoupler + triac/thyristor (AC) or MOSFET (DC); zero-crossing switching versions	Silent, fast, million-cycle life, heater/PLC loads; needs heat-sink, has leakage & on-state drop
Buchholz relay	Gas-actuated float switch in transformer oil pipe	Incipient-fault protection of oil-filled transformers
Numerical/static relays	Microprocessor-based measurement	Modern substation protection

10.4 Ratings & applications

Coil rating (V, DC/AC, resistance), **contact rating (max switching V & A, AC/DC — always separately specified)**, contact resistance (mΩ), electrical/mechanical life (10^5/10^7 operations), dielectric strength coil-to-contact, operate/release time. **Applications:** control & interlocking, motor starters, **power-system protection** (overcurrent, earth-fault, differential, distance), railway signalling (track circuits, point control — where fail-safe relay logic is standard), automotive, telecom exchanges, timers/flashers.

---

11. Switches

A switch makes/breaks a circuit mechanically. Described by **poles (P)** and **throws (T)** and its actuator.

Configuration	Meaning	Example use
SPST	1 circuit, on-off	Simple light switch
SPDT	1 circuit, 2 positions (common + 2 ways)	**Two-way staircase wiring** (two SPDTs), source selection
DPST	2 circuits switched together on-off	Switching line + neutral together
DPDT	2 circuits, 2 positions each	**Motor reversing**, changeover (mains/inverter)
Intermediate	Cross-over switch	Middle switch of 3-location staircase control

Actuator/mechanism types

- **Toggle switch** — lever, snap action; panel on-off.
- **Push-button** — momentary (push-to-make like a doorbell, or push-to-break) or alternate-action/latching; START (NO, green) & STOP (NC, red) in motor control.
- **Rotary switch** — one shaft, many positions/decks (e.g., multimeter range selector, fan regulator, band selector).
- **Slide switch** — small equipment on/off, mode select.
- **Rocker switch** — see-saw action; appliance mains switches.
- **Micro-switch** — snap-action switch needing tiny force/movement via lever/roller; door interlocks, limit sensing, mouse buttons; very high repeat accuracy.
- **Limit switch** — rugged micro-switch package operated by a machine part reaching a position — end-of-travel protection in cranes, lifts, machine tools.
- **DIP switch** — row of tiny slide/rocker switches in a dual-in-line package; PCB configuration/address setting.
- **Key/keypad, tactile switches** — momentary dome switches on PCBs.
- **Proximity/reed switches** — non-contact position sensing (magnetically operated reed with door magnets in alarms).
- **Selector/cam switches** — e.g., ammeter/voltmeter phase selectors, star-delta rotary starters.

Switch ratings: current & voltage (AC and DC separately — DC arcs are harder to break), contact resistance, insulation resistance, mechanical/electrical life, IP rating. Contact bounce (few ms) must be **debounced** in digital circuits (RC/flip-flop/software).

---

12. MCB — Miniature Circuit Breaker

An MCB automatically disconnects a circuit on **overload** and **short-circuit**, and doubles as a manual switch. Standard: IS/IEC 60898.

12.1 Working — two tripping mechanisms in one

1. **Thermal tripping (overload):** load current heats a **bimetallic strip**; on sustained overload it bends enough to release the trip latch. Inverse-time characteristic — bigger overload trips faster (seconds→minutes).
2. **Magnetic tripping (short-circuit):** a **solenoid/electromagnet** in series; a heavy fault current instantly (< 10 ms) attracts the plunger and trips the latch.
3. The **arc** drawn at the contacts is driven by magnetic action into **arc-chute splitter plates**, split, cooled and extinguished. A trip-free mechanism ensures it trips even if the toggle is held ON.

12.2 Trip-curve classes (magnetic-trip threshold, × rated current I_n)

Curve	Instantaneous trip at	Application
B	3–5 × I_n	Resistive/lighting circuits, domestic sockets — low inrush
C	5–10 × I_n	Mixed/mildly inductive loads — motors, fluorescent banks, ACs; the general-purpose choice
D	10–20 × I_n	High-inrush loads — transformers, welding sets, large motors, X-ray
(K ≈ 8–12×, Z ≈ 2–3× — special: motor and semiconductor/instrument protection respectively)		

12.3 Ratings

- **Rated current I_n:** 0.5–125 A (common 6, 10, 16, 20, 25, 32, 40, 63 A) at 30 °C reference.
- **Poles:** SP, SP+N, DP, TP, TP+N, 4P.

- **Rated voltage** 240/415 V AC; **breaking (short-circuit) capacity:** 3, 6, 10 kA (marked in a rectangle, e.g., "10000"); **energy-limiting class 3** typical.

12.4 MCB vs rewireable fuse

Point	MCB	Fuse
Action	Trips — **reusable**, just switch back ON	Element melts — must be **replaced/rewired**
Restoration time	Seconds	Minutes + skill; risk of wrong wire size
Characteristic	Precise, factory-set thermal-magnetic	Deteriorates with age; rewireable fuse imprecise
Phase indication & safety	Clear ON/OFF/trip, no live parts touched	Live parts exposed while rewiring
Cost	Higher initial	Cheap
Speed on huge faults	~ms	HRC fuse can be even faster (current-limiting, cuts off before first peak) — hence fuses still back up breakers

12.5 Related breakers — one-liners

- **MCCB (moulded-case circuit breaker):** bigger brother — 16 A to 1600 A, breaking capacity 10–100 kA, often adjustable thermal/magnetic or electronic trip; industrial feeders.
- **ELCB (earth-leakage CB, voltage-operated):** old type tripping on voltage rise of earthed metalwork; needs sound earth connection; obsolete.
- **RCCB/RCD (residual-current CB, current-operated):** core-balance CT compares phase and neutral currents; trips when the **residual (leakage) difference exceeds 30 mA (shock protection) / 100–300 mA (fire protection)** within ~30 ms — protects against electrocution; does **not** protect against overload (combine with MCB).
- **RCBO:** RCCB + MCB overload/short-circuit protection in one module.
- **Isolator:** off-load disconnector for maintenance isolation — never open on load; a **switch-disconnector-fuse (SDF)** adds fuses.

---

13. Connectors

A connector provides a **separable** electrical joint between cables, boards and equipment. Merits are judged by contact resistance, insertion/withdrawal force, mating cycles, current/voltage rating and environmental sealing.

13.1 Families

Family	Examples	Notes / uses
Audio	6.35 mm (¼") phone jack, **3.5 mm TRS/TRRS** (tip-ring-sleeve: L, R, ground, +mic), RCA/phono, **XLR (3-pin, balanced, locking)**, banana plugs	Headphones, line audio, professional mics (XLR), test leads (banana, 4 mm)
RF / coaxial	**BNC** — bayonet lock, 50/75 Ω, to ~4 GHz: oscilloscopes, video, LAN (legacy 10BASE2); **SMA** — threaded, 50 Ω, precision to ~18 GHz: antennas, RF modules; TNC (threaded BNC); **N-type** (to 11 GHz, weatherproof, base stations); UHF (PL-259/SO-239, HF radio); F-type (TV/satellite, 75 Ω); MCX/MMCX/U.FL (miniature, GPS/Wi-Fi boards)	Maintain characteristic impedance (50 Ω instruments/comms, 75 Ω video/CATV) to avoid reflections
Card-edge connectors	PCB edge fingers into a slot — PCI/PCIe, DIMM/RAM sockets	Gold-plated fingers ("goldfinger"); polarising key slot
D-subminiature (DB/DE)	**DB-9 (DE-9): RS-232 serial**; DB-25: parallel/serial legacy; DB-15/HD-15 = **VGA** (3-row)	Trapezoidal D-shell polarises the mating; screw locks
RJ family (modular)	**RJ45 (8P8C): Ethernet LAN** — T568A/T568B colour codes, ≤ 100 m Cat5e/6; RJ11/RJ12 (6P2C/6P4C): telephone	Crimped with modular crimping tool; keystone jacks
USB	Type-A, Type-B, Mini, Micro, **Type-C (reversible, 24-pin)** — USB 2.0 (480 Mb/s, 4-pin) → 3.x (extra pairs) → USB4; also powers loads (5 V; USB-PD up to 100–240 W over Type-C)	Universal peripheral/data/charging connector
Terminal blocks	Screw-clamp (barrier/PCB), spring-cage, **DIN-rail** terminals, pluggable (Phoenix) types	Panel wiring & field terminations; ferrules on stranded wire
Power & board-level	IEC 60320 C13/C14 mains inlet, Anderson, XT60, header pins/Berg, FRC/IDC ribbon (insulation-displacement), JST, ZIF/FFC for flex cables	IDC = insulation-displacement contact — no stripping needed
Circular/military & industrial	M8/M12 sensor connectors, MIL-C-5015/38999	Vibration-proof threading, IP67 sealing
Optical-fibre connectors	SC (push-pull, square), **LC (small form-factor — most common now)**, ST (bayonet), FC (threaded), MPO (multi-fibre); polish grades PC/UPC (blue) & **APC (green, 8° angle — lowest back-reflection)**	Patch panels, FTTH, transceivers (SFP uses LC)

13.2 Contact materials & plating

- **Base contact metal:** brass, phosphor bronze or beryllium copper (best spring properties).
- **Plating: gold** (flash over nickel) — does not oxidise, lowest and most stable contact resistance — for low-level signal contacts and edge fingers; **silver** — best conductivity, used in power contacts (tarnish film breaks down easily at power levels); **tin** — cheap, general power/consumer contacts (avoid mating tin with gold — fretting corrosion); **nickel** — hard barrier/underplate; palladium-nickel as gold substitute.

- Design points: wiping action self-cleans contacts on insertion; polarisation/keying prevents wrong mating; strain relief and locking (bayonet/screw/latch) preserve the joint; rated mating cycles (tin ~100s, gold ~1000s).

---

14. Worked Examples (8)

Example 1 — 4-band colour code.

Bands: **Red-Violet-Orange-Gold**.

Red = 2, Violet = 7, Orange = $\times 10^3$, Gold = ±5 %.

R = 27 × 10^3 = **27 kΩ ± 5 %** (i.e., 25.65–28.35 kΩ).

Example 2 — 5-band colour code.

Bands: **Brown-Black-Black-Red-Brown**.

Digits 1, 0, 0; multiplier $\times 10^2$; tolerance ±1 %.

R = 100 × 10^2 = **10 kΩ ± 1 %**.

Example 3 — Reverse colour code.

What are the bands of a 470 Ω ± 10 % resistor (4-band)?

470 = 4, 7 × 10^1 → **Yellow-Violet-Brown-Silver**.

Example 4 — Resistor power rating (2025-PYQ style).

A 100 Ω resistor must carry 100 mA continuously. What minimum standard wattage should be chosen?

P = I^2R = $(0.1)^2$ × 100 = **1 W**. With the ×2 derating rule, select a **2 W** resistor. (Rating is set by permissible power dissipation, not by resistance value.)

Example 5 — Capacitor energy.

Energy stored in a 470 µF capacitor charged to 25 V:

W = ½CV^2 = ½ × 470×10^{-6} × 25^2 = ½ × 470×10^{-6} × 625 = **0.147 J** (≈ 147 mJ).

If voltage doubles to 50 V, energy becomes 4× = 0.587 J ($W \propto V^2$).

Example 6 — Dielectric strength.

A 0.2 mm mica sheet is to insulate 6 kV. Is it adequate if mica's dielectric strength is 50 kV/mm?

Applied stress = 6 kV / 0.2 mm = **30 kV/mm < 50 kV/mm** → withstands, with safety factor 50/30 ≈ 1.67. (For a design safety factor of 2.5, thickness needed = 6/(50/2.5) = 0.3 mm.)

Example 7 — Battery backup time.

A 12 V, 150 Ah (C_{10}) battery feeds an inverter delivering 400 W at 90 % efficiency. Estimate backup (to 100 % DoD, ideal).

Battery output power = 400/0.9 = 444.4 W → current = 444.4/12 = **37 A**.

Ideal time = 150 Ah / 37 A ≈ **4.05 h** (~4 hours). *Practically less — Peukert effect at above-C_{10} current and usable DoD limit (~80 % ⇒ ≈ 3.2 h).*

Example 8 — Cells in series-parallel.

How are 2 V, 100 Ah lead-acid cells arranged to build a 48 V, 300 Ah battery bank?

Series for voltage: 48/2 = **24 cells per string**. Parallel for capacity: 300/100 = **3 strings**. Total = 24 × 3 = **72 cells**. Energy = 48 × 300 = 14.4 kWh.

Bonus check — capacitors in series. Two capacitors 6 μF and 3 μF in series across 90 V: C_eq = (6×3)/(6+3) = 2 μF; Q = 2 μF × 90 = 180 μC on each; V_6 = 180/6 = 30 V, V_3 = 180/3 = 60 V (larger voltage across the smaller capacitor).

---

15. PYQ Corner — Actual CBT-2 (22-04-2025) Questions Solved

PYQ 1. Dielectric strength of an insulating material is defined as —

(a) the ratio of its permittivity to that of free space

(b) **the maximum electric field (voltage per unit thickness) it can withstand without electrical breakdown**

(c) the resistance offered per unit volume

(d) the energy stored per unit volume

Answer: (b). Dielectric strength = maximum potential gradient the insulator sustains without losing its insulating property (breakdown). Measured in **kV/mm**. Option (a) defines *dielectric constant* — the classic distractor. Representative values: air 3 kV/mm, transformer oil ~10–15, porcelain ~10–15, mica 50+ kV/mm.

PYQ 2. Copper is widely preferred as an electrical conductor material because it has —

(a) the lowest resistivity of all metals

(b) **high electrical conductivity along with good corrosion resistance**

(c) very high resistivity and high melting point

(d) magnetic properties useful in machines

Answer: (b). Silver actually has the lowest resistivity (1.59×10^{-8} Ω·m vs copper's ~1.7×10^{-8}), so (a) is false. Copper wins on the *combination*: near-best conductivity, excellent corrosion resistance (protective oxide, no destructive tarnish problem in service), ductility for wire-drawing, strength, solderability and economy.

PYQ 3. Mineral insulating materials (mica, porcelain, glass, etc.) are chiefly used where —

(a) only flexibility is required

(b) **both good mechanical strength/heat withstand and electrical insulation are required**

(c) the operating temperature is below 90 °C only

(d) a conducting path must be provided

Answer: (b). Minerals are class-B/C insulation: porcelain/toughened glass carry the full mechanical load of overhead conductors while insulating them (pin/disc insulators, bushings); mica supports red-hot heating elements in irons and toasters and separates commutator bars; MgO fills fire-survival MICC cables. Organic insulators (class Y, ~90 °C) cannot survive these duties.

PYQ 4. In a Nickel-Iron (Edison) cell, during discharge —

(a) the positive plate PbO_2 changes to $PbSO_4$

(b) the KOH electrolyte is consumed and its specific gravity falls sharply

(c) **the nickel oxyhydroxide positive plate is reduced to $Ni(OH)_2$ while the iron negative plate is oxidised to $Fe(OH)_2$; the KOH concentration remains practically unchanged**

(d) lithium ions intercalate into a cobalt-oxide cathode

Answer: (c). Discharge reactions: $Fe + 2OH^- \rightarrow Fe(OH)_2 + 2e^-$ (negative); $2NiOOH + 2H_2O + 2e^- \rightarrow 2Ni(OH)_2 + 2OH^-$ (positive); overall **$Fe + 2NiOOH + 2H_2O \rightarrow Fe(OH)_2 + 2Ni(OH)_2$**. The KOH merely ferries OH^- ions — its specific gravity (~1.2) stays constant, so a hydrometer cannot show the state of charge (unlike lead-acid, option (b)/(a) territory). Nominal 1.2 V/cell; famously rugged — survives overcharge, deep discharge and idle-discharged storage.

PYQ 5. The rating (wattage) of a resistor is decided by —

(a) its resistance value

(b) its tolerance

(c) **the maximum power it can safely dissipate as heat (permissible power dissipation)**

(d) its temperature coefficient

Answer: (c). Two resistors of identical resistance can have very different ratings (¼ W chip vs 10 W wire-wound): the rating depends on how much heat ($P = I^2R = V^2/R$) the body can shed without exceeding its temperature limit — governed by physical size, surface area, construction material and ambient temperature, not by the ohmic value itself.

---

16. Practice MCQs (25)

Q1. The forbidden energy gap of silicon at room temperature is approximately —

(a) 0.3 eV (b) 0.72 eV (c) 1.12 eV (d) 5.5 eV

Q2. The material having the lowest electrical resistivity is —

(a) copper (b) silver (c) aluminium (d) gold

Q3. Manganin is used for making standard resistances mainly because of its —

(a) high resistivity only (b) low cost (c) **very low temperature coefficient of resistance** (d) high melting point

Q4. In an ACSR conductor, the steel core primarily provides —

(a) higher conductivity (b) mechanical/tensile strength (c) corona reduction (d) lower skin effect

Q5. A resistor has bands Green-Blue-Red-Gold. Its value is —

(a) 56 kΩ ± 5 % (b) 5.6 kΩ ± 5 % (c) 560 Ω ± 5 % (d) 6.5 kΩ ± 10 %

Q6. An NTC thermistor's resistance —

(a) rises with temperature (b) falls with temperature (c) is independent of temperature (d) falls with light intensity

Q7. A MOV (metal-oxide varistor) connected across a supply protects equipment against —

(a) overload current (b) earth leakage (c) voltage surges/transients (d) low voltage

Q8. Which capacitor is polarised and must never be connected in reverse?

(a) mica (b) ceramic disc (c) aluminium electrolytic (d) polypropylene film

Q9. Two capacitors of 4 μF and 12 μF are connected in series. The equivalent capacitance is —

(a) 16 μF (b) 8 μF (c) 3 μF (d) 48 μF

Q10. The energy stored in a 100 μF capacitor charged to 200 V is —

(a) 0.2 J (b) 2 J (c) 4 J (d) 0.02 J

Q11. Class F insulation permits a maximum operating temperature of —

(a) 105 °C (b) 130 °C (c) 155 °C (d) 180 °C

Q12. XLPE is widely used as —

(a) transformer-core material (b) HV underground-cable insulation (c) fuse element (d) contact plating

Q13. A material weakly repelled by a magnetic field (μ_r slightly less than 1) is —

(a) ferromagnetic (b) paramagnetic (c) diamagnetic (d) ferrimagnetic

Q14. Transformer cores are made of CRGO silicon steel because silicon —

(a) raises permeability by lowering resistivity (b) raises resistivity, reducing eddy-current loss (c) makes the steel a permanent magnet (d) increases hysteresis loss

Q15. A permanent magnet should be made of a material having —

(a) low retentivity, low coercivity (b) high retentivity, high coercivity (c) high permeability, narrow B-H loop (d) low retentivity, high permeability

Q16. Ferrite cores are preferred for SMPS/high-frequency transformers because they have —

(a) very high electrical resistivity, hence negligible eddy loss (b) the highest saturation flux density (c) zero hysteresis (d) high mechanical strength

Q17. Eutectic tin-lead solder (63Sn-37Pb) is preferred in electronics because it —

(a) melts at the highest temperature (b) melts/solidifies at a single temperature with no pasty range (c) needs no flux (d) is mechanically strongest of all alloys

Q18. The flux recommended for soldering electronic/telecom copper joints is —

(a) zinc chloride (killed spirits) (b) hydrochloric acid (c) rosin (d) caustic soda

Q19. The splicing method giving the lowest loss (~0.01–0.05 dB) for optical fibre is —

(a) mechanical splice (b) fusion splice (c) connectorised joint (d) twisted joint

Q20. The standard cleaning agent for fibre ends and connector faces before splicing is —

(a) kerosene (b) carbon tetrachloride (c) isopropyl alcohol (d) soap water

Q21. In a fully charged lead-acid cell, the specific gravity of the electrolyte is about —

(a) 1.00 (b) 1.13 (c) 1.28 (d) 1.80

Q22. "Sulphation" in a lead-acid battery is caused by —

(a) overcharging at high rate (b) adding excess distilled water (c) leaving the battery in a discharged state for long periods (d) too high electrolyte level

Q23. The nominal voltage per cell of Ni-Cd, Ni-Fe and Ni-MH cells is —

(a) 2.0 V (b) 1.5 V (c) 1.2 V (d) 3.6 V

Q24. A C-type MCB provides instantaneous (magnetic) tripping at —

(a) 1–2 × I_n (b) 3–5 × I_n (c) 5–10 × I_n (d) 10–20 × I_n

Q25. The connector normally used for terminating an Ethernet LAN cable is —

(a) BNC (b) DB-9 (c) RJ45 (d) SMA

Answer key with brief explanations

Q	Ans	Why
1	c	Si gap ≈ 1.12 eV (Ge 0.72 eV, diamond 5.5 eV).
2	b	Silver 1.59×10^{-8} Ω·m — lowest of all metals; Cu next.
3	c	Manganin's α ≈ 10^{-5}/°C — resistance almost constant with temperature (also low thermo-EMF with Cu).
4	b	Steel = strength (long spans, low sag); outer Al strands carry the current.
5	b	5,6 × 10^2 = 5600 Ω = 5.6 kΩ; gold = ±5 %.
6	b	NTC: negative temperature coefficient — R falls exponentially as T rises.
7	c	Varistor resistance collapses above threshold voltage, clamping surges/spikes.
8	c	Electrolytics (Al, Ta) are polarised — reverse polarity destroys the oxide film.
9	c	Series: (4×12)/(4+12) = 3 µF — less than the smallest.
10	b	$W = ½CV^2 = ½\times100\times10^{-6}\times(200)^2 = ½\times10^{-4}\times4\times10^4$ = 2 J.
11	c	Y-A-E-B-F-H-C = 90-105-120-130-**155**-180->180 °C.
12	b	Cross-linked polyethylene: 90 °C continuous, low loss — standard HV U/G cable insulation.
13	c	Diamagnetics (Cu, Bi, water) are feebly repelled; χ small negative.
14	b	~3–4 % Si multiplies resistivity → eddy loss ↓ (also hysteresis ↓); grain orientation boosts µ.
15	b	Permanent magnet = hard material: broad loop, high B_r and H_c (Alnico, ferrite, Nd-Fe-B).
16	a	Ferrites are ceramic semicon/insulators — eddy currents negligible even at MHz.
17	b	Eutectic point 183 °C: no plastic range ⇒ no disturbed/dry joints while freezing.
18	c	Rosin is non-corrosive; acid/$ZnCl_2$ fluxes corrode fine conductors.
19	b	Arc-fusion welds the glass — lowest, permanent loss; mechanical ~0.1–0.5 dB.
20	c	≥99 % IPA with lint-free wipes — residue-free; CCl_4 banned/toxic.
21	c	Charged 1.26–1.28 (falls to ~1.15 discharged); read by hydrometer.

Q	Ans	Why
22	c	Standing discharged lets $PbSO_4$ harden into large non-convertible crystals — permanent capacity loss.
23	c	All three alkaline nickel systems: 1.2 V nominal (lead-acid 2.0 V, Li-ion 3.6–3.7 V).
24	c	B: 3–5×, **C: 5–10×**, D: 10–20× I_n.
25	c	RJ45 (8P8C modular) on Cat5e/6 twisted pair; BNC was for legacy coax LAN.

17. Rapid-Revision Fact Sheet

A. Energy gaps & resistivities

Item	Value
E_9: Ge / Si / GaAs	0.72 / 1.12 / 1.43 eV
E_9 insulator (diamond)	> 3 eV (≈ 5.5 eV)
ρ: Ag / Cu / Au / Al / W	1.59 / 1.7 / 2.44 / 2.7 / 5.6 ($\times 10^{-8}$ Ω·m)
ρ: Manganin / Constantan / Nichrome	≈ 45 / 49 / 100–112 ($\times 10^{-8}$ Ω·m)
Lowest ρ metal / conductor % IACS of Al	Silver / ≈ 61 %
α of manganin	~10^{-5} /°C (near zero)

B. Colour code & component formulas

Item	Value
Colour order 0→9	Black Brown Red Orange Yellow Green Blue Violet Grey White
Tolerance	Gold ±5 %, Silver ±10 %, none ±20 %, Brown ±1 %, Red ±2 %
Resistor rating decided by	**Permissible power dissipation (wattage)**
Capacitor energy / inductor energy	$W = \frac{1}{2}CV^2$ / $W = \frac{1}{2}LI^2$
Caps: series / parallel	$1/C_{eq} = \Sigma 1/C$ / $C_{eq} = \Sigma C$
SMD "472", cap "104"	4.7 kΩ; 100 nF

C. Dielectric strengths (kV/mm) & insulation classes

Material	kV/mm
Air	3
Transformer oil	10–15 (BDV ≥ 30 kV/2.5 mm)
Porcelain	10–15
Glass	20–30
XLPE / PE	20–40
Mica	**50–120 (highest common)**
SF_6 (1 atm)	≈ 8–9 (2.5–3 × air)

Class	Y	A	E	B	F	H	C
°C max	90	105	120	130	155	180	>180

D. Magnetic quick facts

Item	Fact
Soft magnetic	Narrow B-H loop, low Hc — CRGO, permalloy, soft ferrite → transformer/machine cores
Hard magnetic	Broad loop, high B_r & Hc — Alnico, hard ferrite, Nd-Fe-B → permanent magnets
Hysteresis loss	∝ f · B_max^1.6 (Steinmetz), ∝ loop area
Eddy loss	∝ f^2 B^2 t^2 — cut by lamination / ferrites
Curie temp Fe / Ni	770 °C / 358 °C
Diamagnetic examples	Cu, Ag, Bi, water (μ_r < 1)

E. Battery chemistries & voltages

Cell	Type	Nominal V	Electrolyte	Key point
Zinc-carbon (Leclanché)	Primary	1.5	NH_4Cl paste	MnO_2 = depolariser
Alkaline Zn-MnO_2	Primary	1.5	KOH	3–5× capacity of Zn-C
Mercury / Silver-oxide	Primary	1.35 / 1.55	KOH	Flat voltage (reference/watches)
Lithium CR coin	Primary	3.0	Organic	10-yr shelf life, RTC backup
Lead-acid	Secondary	**2.0**	dil. H_2SO_4, s.g. 1.26–1.28 charged	s.g. falls on discharge; sulphation if left discharged; cut-off 1.75 V
Ni-Cd	Secondary	1.2	KOH (const. s.g.)	Rugged, memory effect, Cd toxic
Ni-Fe (Edison)	Secondary	1.2 (EMF 1.4)	KOH + LiOH (const. s.g.)	$Fe + 2NiOOH + 2H_2O \rightleftharpoons Fe(OH)_2 + 2Ni(OH)_2$; 20–30 yr life; abuse-proof; high self-discharge
Ni-MH	Secondary	1.2	KOH	MH negative; no Cd; AA rechargeables
Li-ion	Secondary	3.6–3.7 (charge 4.2)	$LiPF_6$ organic	Li^+ intercalation; highest energy density; CC-CV charge; BMS needed
C-rate for 100 Ah	—	—	—	1C = 100 A; C/10 = 10 A

F. Relays, switches, MCB, connectors

Item	Fact
Relay contacts	NO (form A) / NC (form B) / changeover (form C); pick-up > drop-out
Relay types	Attracted-armature (AC/DC, instantaneous), induction (AC only, IDMT protection), thermal (motor overload), reed (sealed, fast), SSR (no moving parts), Buchholz (transformer gas)
DC relay coil must have	Freewheeling diode across it
Switch configs	SPST on-off; SPDT two-way staircase; DPDT reversing/changeover; intermediate = 3rd location
Micro/limit switch	Snap action, position sensing / end-of-travel
MCB tripping	Thermal (bimetal, overload, inverse-time) + magnetic (solenoid, short-circuit, instantaneous)
MCB curves	**B: 3–5×, C: 5–10×, D: 10–20× I_n**
MCB breaking capacity	3/6/10 kA (IS/IEC 60898)
RCCB sensitivity	30 mA (shock) / 300 mA (fire); no overload protection
RCBO	RCCB + MCB combined
BNC / SMA	Bayonet coax to ~4 GHz / threaded 50 Ω to ~18 GHz
DB-9 / HD-15 / RJ45	RS-232 serial / VGA / Ethernet 8P8C
Best contact plating (signal)	Gold (no oxide, stable low resistance); silver for power; tin economy
Fibre splice loss	Fusion ~0.01–0.1 dB < mechanical ~0.1–0.5 dB < connector ~0.2–0.5 dB
Fibre/joint cleaning	≥ 99 % isopropyl alcohol + lint-free wipes; D-Gel for jelly-filled cable

---

End of Chapter 1. Next: Chapter 2 — Electronic Devices & Circuits.

Chapter 2 — Electronic Devices and Circuits

Syllabus coverage (Unit 2, CEN 05/2025 Annexure-VII C): PN Junction diodes, thyristor; Diode and triode circuits; Junction Transistors; Amplifiers; Oscillator; Multivibrator, counters; Rectifiers; Inverter and UPS.

📊 Weightage & Trend Box

Parameter	Detail
Observed weight (CBT-2, 22-04-2025 shift)	**8 out of 50 technical questions ≈ 16%** — the single highest-weight unit
Expected marks contribution	14–18 out of 100 technical marks
Difficulty band	Easy–Moderate; mostly formula-recall, statement-verification and one-step numericals

Topics actually asked in the 22-04-2025 CBT-2 paper (recreated in the PYQ Corner of this chapter):

1. Rectifier comparison — statement question involving **TUF** (Transformer Utilisation Factor)
2. **BJT current relation** IE = IC + IB and α–β conversions
3. **Half-wave rectifier fed through a transformer** — turns-ratio / output-voltage numerical
4. **Bridge vs centre-tapped** full-wave rectifier — comparative statement question
5. **Colpitts oscillator** — pick-the-incorrect-statement
6. **n-type semiconductor** — majority carriers
7. **Ideal diode circuit** with input V(t) = $\sin^2 t + \cos^2 t$ (a disguised 1 V DC source!)
8. **Oscillator / Barkhausen criterion** — pick-the-false-statement

Preparation strategy: Master the rectifier comparison table (ripple factor, efficiency, PIV, TUF, form factor) until you can reproduce it from memory; memorise every oscillator frequency formula and its identification trick; drill α/β/γ conversions; and never forget the trigonometric identity $\sin^2\theta + \cos^2\theta = 1$ — RRB literally tested it.

2.1 Semiconductor Physics — The Foundation

2.1.1 Energy bands and classification of materials

Electrons in an isolated atom occupy discrete energy levels. When atoms come close in a crystal, these levels split into closely spaced **energy bands**. The two bands that decide electrical behaviour are:

- **Valence band (VB):** highest band filled with electrons at 0 K.
- **Conduction band (CB):** the next higher band; electrons here are free to conduct.
- **Forbidden energy gap (Eg):** separation between the top of VB and bottom of CB.

Material	Energy gap Eg	Behaviour
Conductor (Cu, Al)	Bands overlap, Eg ≈ 0	Abundant free electrons
Semiconductor (Ge, Si, GaAs)	Ge ≈ 0.72 eV, Si ≈ 1.1 eV, GaAs ≈ 1.43 eV	Conduction possible with thermal/optical energy
Insulator (diamond, mica)	Eg > 3 eV (diamond ≈ 6 eV)	Practically no conduction

Key facts repeatedly asked:

- Silicon (Z = 14) and Germanium (Z = 32) are **tetravalent** (4 valence electrons), Group-14 (IV-A) elements forming a diamond-cubic covalent lattice.
- Resistivity order: conductor (10^{-8} Ω·m) < semiconductor (10^{-5}–10^{6} Ω·m) < insulator (10^{11}–10^{19} Ω·m).
- Semiconductors have a **negative temperature coefficient of resistance** — resistance *decreases* as temperature rises because carrier concentration increases exponentially.

2.1.2 Intrinsic semiconductors

A chemically pure semiconductor is **intrinsic**. At 0 K it behaves as a perfect insulator. At room temperature, thermal energy breaks some covalent bonds, generating **electron–hole pairs (EHP)**:

- Free electron → jumps to conduction band.
- **Hole** → the vacancy left in the valence band; behaves as a mobile positive charge carrier.

In an intrinsic semiconductor:

$n = p = n_i$

where n_i is the intrinsic carrier concentration (Si: $n_i \approx 1.5 \times 10^{16}$ /m^3; Ge: $n_i \approx 2.5 \times 10^{19}$ /m^3 at 300 K).

Intrinsic concentration rises steeply with temperature:

$n_i^2 = A_0\, T^3\, e^{\wedge}(-Eg/kT)$

Total current = electron current + hole current. Conductivity of an intrinsic sample:

$\sigma_i = n_i\, e\, (\mu_n + \mu_p)$

where μ_n, μ_p are electron and hole mobilities (for Si: $\mu_n \approx 0.135$ m^2/V·s, $\mu_p \approx 0.048$ m^2/V·s — electrons are roughly 2–3 times more mobile than holes).

2.1.3 Extrinsic semiconductors — doping

Adding a controlled impurity (≈ 1 part in 10^6) enormously increases conductivity. Two types:

n-type (donor doping)

- Dopant: **pentavalent** atom — P, As, Sb, Bi (Group 15/V-A).
- Four electrons bond covalently; the fifth is loosely bound (~0.01–0.05 eV below CB) and is easily donated → **donor level just below the conduction band**.
- **Majority carriers: electrons. Minority carriers: holes.** ← *asked verbatim in the 2025 paper*
- n ≈ N_D (donor concentration); the crystal remains **electrically neutral** overall.

p-type (acceptor doping)

- Dopant: **trivalent** atom — B, Al, Ga, In (Group 13/III-A).
- Only three bonds complete; the vacancy accepts an electron → **acceptor level just above the valence band**.
- **Majority carriers: holes. Minority carriers: electrons.**
- p ≈ N_A.

Mass-action law (holds for both intrinsic and extrinsic material at thermal equilibrium):

$n \cdot p = n_i^2$

So doping that raises one carrier type suppresses the other proportionally.

Charge neutrality: p + N_D = n + N_A.

2.1.4 Drift and diffusion currents

Two transport mechanisms exist in semiconductors:

Drift current — carriers move under an applied electric field E:

- Drift velocity: v_d = μE
- Drift current density: **$J_{drift} = (n e \mu_n + p e \mu_p) E = \sigma E$** (Ohm's law in point form)

Diffusion current — carriers move from high to low concentration (no field needed); unique to semiconductors:

- **$J_n(diff) = +e D_n (dn/dx)$ $J_p(diff) = -e D_p (dp/dx)$**

D_n, D_p are diffusion coefficients linked to mobility by the **Einstein relation**:


$D/\mu = kT/e = V_T$ (thermal voltage; **$V_T \approx 26$ mV at 300 K**, ≈ T/11600 volts)

Total current density: J = J_drift + J_diffusion for each carrier type.

Hall effect (quick recall): when a current-carrying semiconductor is placed in a transverse magnetic field, a voltage develops perpendicular to both — used to find carrier type and concentration. Hall voltage V_H = BI/(n e t). The polarity of V_H tells whether the sample is n-type or p-type.

2.2 The PN Junction Diode

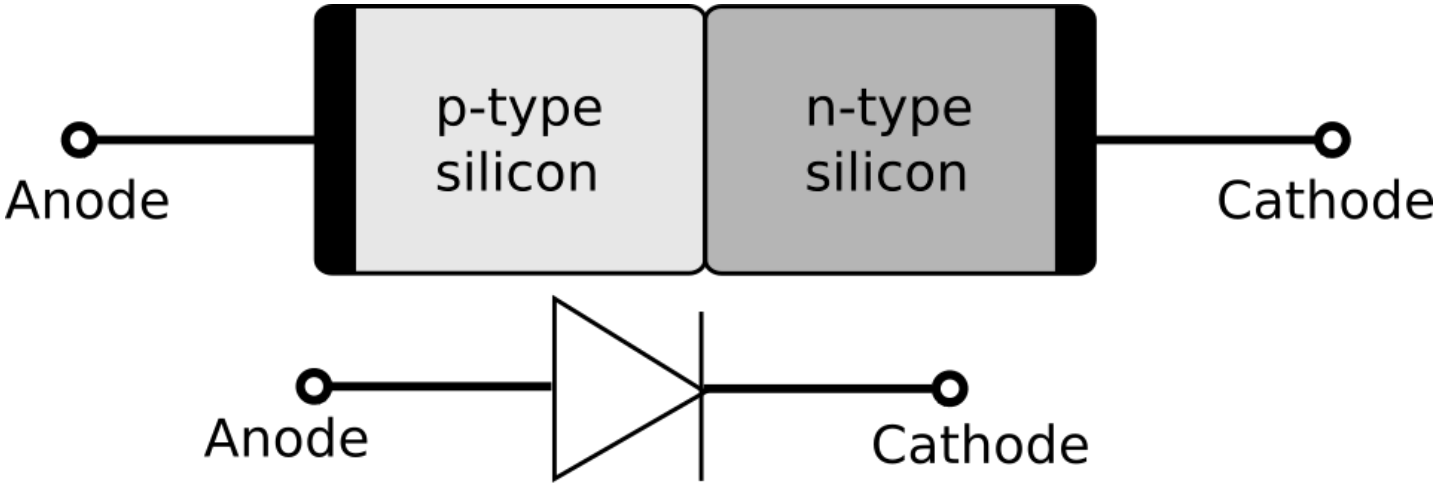2.2.1 Junction formation and the depletion region



PN-junction diode: depletion region and circuit symbol.

When p-type and n-type regions are formed in a single crystal:

1. Electrons diffuse from n → p; holes diffuse from p → n (concentration gradients).
2. Near the junction, they recombine, leaving **immobile ions**: negative acceptor ions on the p-side, positive donor ions on the n-side.
3. This carrier-free zone is the **depletion (space-charge) region**, width ≈ 0.1–0.5 μm.
4. The ionic charges create an internal electric field (n → p) and a **barrier potential V_B**:

- **Si: ≈ 0.7 V, Ge: ≈ 0.3 V** (at 25 °C); GaAs ≈ 1.2 V.

- V_B decreases by about **2 mV per °C rise** in temperature.

1. Equilibrium: diffusion current is exactly balanced by drift of minority carriers — net current zero.

Built-in potential (Boylestad/Millman level):

$V_0 = V_T \ln(N_A N_D / n_i^2)$

Depletion width $W \propto \sqrt{(V_0 \pm V)}$ — widens under reverse bias, narrows under forward bias. The region penetrates deeper into the **lightly doped side** ($W \propto 1/N$).

2.2.2 Biasing


Forward bias (p to +, n to −):

- Applied field opposes barrier; depletion narrows.
- Significant current flows once V > cut-in (knee) voltage **$V_\gamma \approx 0.7$ V (Si) / 0.3 V (Ge)**.
- Current is due to **majority carriers**; grows exponentially.

Reverse bias (p to −, n to +):

- Barrier increases; depletion widens.
- Only a tiny **reverse saturation current I_0 (I_s)** flows, due to **minority carriers**; nearly independent of voltage.
- I_0 **doubles for every 10 °C rise** in temperature (both Si and Ge). I_0 is of order nA for Si, μA for Ge.

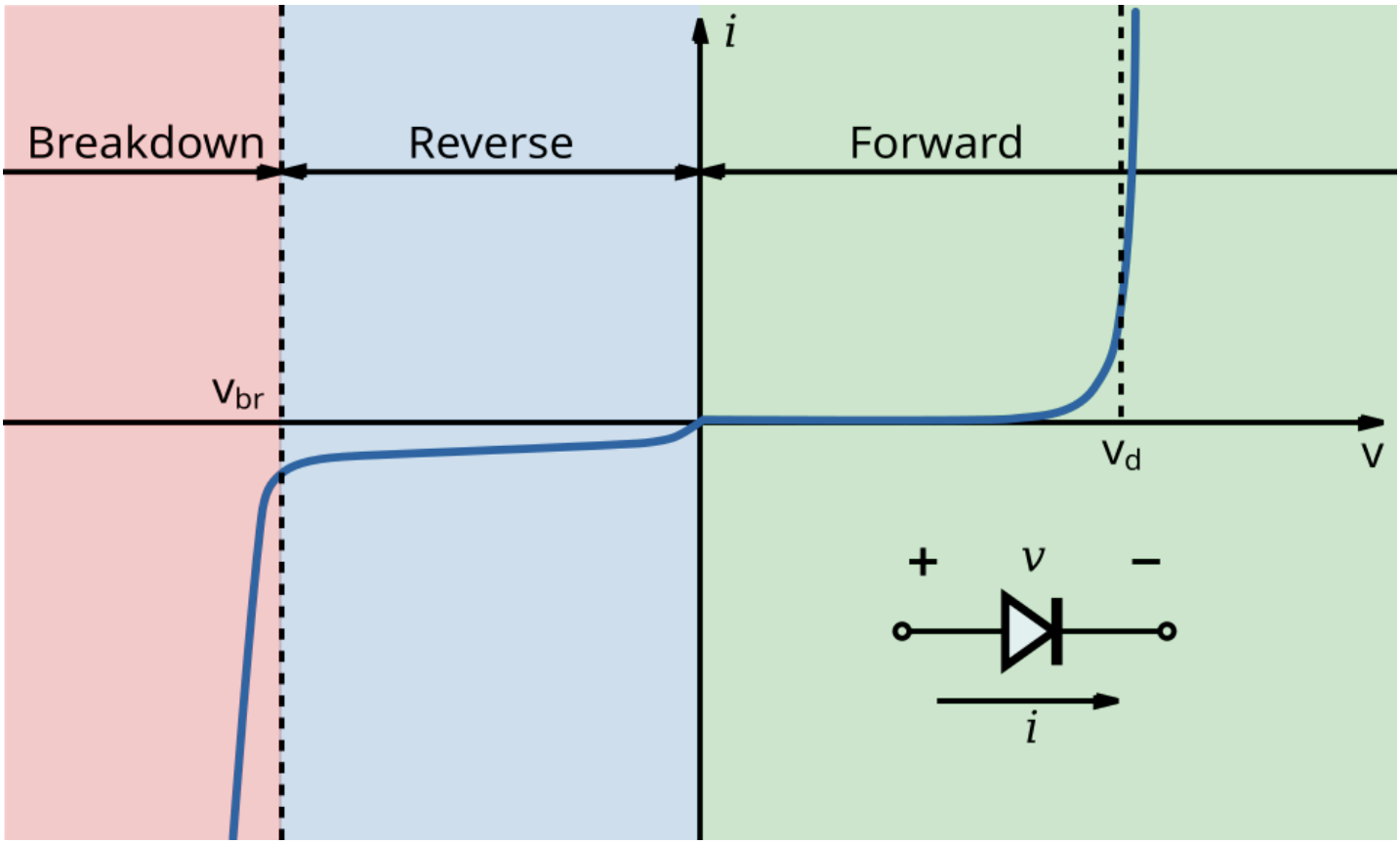2.2.3 Diode equation and V-I characteristics



Diode forward/reverse V–I characteristic.

Shockley diode equation:

$I = I_0 (e^{(V/\eta V_T)} - 1)$

- η (ideality factor) = 1 for Ge, ≈ 2 for Si at low currents (often taken as 1 in problems unless stated).
- $V_T = kT/e \approx 26$ mV at 300 K.

The forward characteristic is exponential after the knee; the reverse characteristic is a flat $-I_0$ line until breakdown.

Diode resistances:

- **Static (DC) resistance:** $R_D = V/I$ at the operating point.
- **Dynamic (AC) resistance:** $r_d = \Delta V/\Delta I = \eta V_T / I$ → the famous **$r_d \approx 26$ mV / I(mA) ohms** (for η = 1).
- Bulk/body resistance of semiconductor material adds in series at high currents.

2.2.4 Diode equivalent models

Model	Description	Use
Ideal diode	Short when forward, open when reverse; $V_\gamma = 0$, $r_f = 0$	Quick circuit analysis, exam "ideal diode" questions
Constant-voltage / practical (2nd approx.)	Battery V_γ (0.7 V Si) in series with ideal diode	Most numericals
Piecewise-linear (3rd approx.)	V_γ + forward resistance r_f in series	Accurate rectifier calculations

2.2.5 Breakdown — Zener vs Avalanche

Under sufficient reverse voltage, the diode conducts heavily — **breakdown**. Not destructive if current is limited.

Feature	Zener breakdown	Avalanche breakdown
Mechanism	High field (~10^7 V/m) directly ruptures covalent bonds — quantum-mechanical tunnelling of electrons	Minority carriers accelerated by field cause impact ionisation → carrier multiplication (chain reaction)
Doping	**Heavily doped**, thin depletion layer	Lightly doped, wide depletion layer
Breakdown voltage	Low: **V_Z < ~5–6 V**	Higher: **V_Z > ~6–8 V**
Temperature coefficient	**Negative** (V_Z falls as T rises)	**Positive** (V_Z rises as T rises)
V-I knee	Sharp	Softer

Around 5–6 V both mechanisms coexist and the temperature coefficient is nearly zero — hence 5.6 V Zeners are the most temperature-stable.

2.2.6 Zener diode as voltage regulator

A Zener operated in reverse breakdown maintains nearly constant voltage V_Z across itself. Standard shunt-regulator circuit: unregulated V_{in} → series resistor R_S → Zener (in reverse) in parallel with load R_L.

Analysis (Zener ON when the open-circuit voltage across it ≥ V_Z):

- Voltage across load: **$V_L = V_Z$**
- Series-resistor current: **$I_S = (V_{in} - V_Z)/R_S$**
- Load current: **$I_L = V_Z/R_L$**
- Zener current: **$I_Z = I_S - I_L$** (must satisfy $I_{Z(min)} \le I_Z \le I_{Z(max)} = P_Z/V_Z$)

Regulation works against both **line variations** (changing V_{in}) and **load variations** (changing R_L). Worst cases: I_Z is maximum when V_{in} is max and I_L is min; I_Z is minimum when V_{in} is min and I_L is max.

2.2.7 Special-purpose diodes

Diode	Bias used	Principle	Applications / key point
LED	Forward	Electroluminescence — radiative recombination of injected carriers	Made from **GaAs (IR), GaAsP (red/yellow), GaP (green)** — never plain Si/Ge (indirect band gap). λ = 1240/Eg(eV) nm. Cut-in ≈ 1.8–2.4 V
Photodiode	**Reverse**	Light generates EHPs in depletion region → photocurrent ∝ illumination	Light detectors, optocouplers; faster than LDR
Solar cell	No external bias	Photovoltaic effect at unbiased junction	Large area junction; open-circuit voltage ≈ 0.5–0.6 V per Si cell
Varactor (varicap)	**Reverse**	Depletion width (hence junction/transition capacitance $C_T \propto 1/\sqrt{V_R}$) varies with reverse voltage	Electronic tuning, VCOs, AFC
Schottky (hot-carrier)	Forward	**Metal–semiconductor** junction; conduction by majority carriers only — no minority-carrier storage	Very fast switching, low forward drop ≈ 0.2–0.3 V; used in SMPS, clamping in TTL (Schottky TTL)
Tunnel (Esaki) diode	Forward	Very heavy doping ($1:10^3$) → extremely thin junction → quantum tunnelling	Exhibits **negative resistance region** between peak ($V_P \approx 65$ mV) and valley ($V_V \approx 350$ mV Ge); microwave oscillators, high-speed switching
PIN diode	Reverse/RF	Intrinsic layer between p and n	RF switch/attenuator

Diode capacitances: transition (depletion) capacitance C_T dominates in **reverse** bias (varactor); diffusion (storage) capacitance C_D dominates in **forward** bias and limits switching speed (reverse recovery time t_{rr}).

2.3 Diode Circuits — Rectifiers

Rectification = conversion of AC into unidirectional (pulsating) DC. Input: $v = V_m \sin \omega t$ from the transformer secondary.

2.3.1 Half-wave rectifier (HWR)

One diode conducts only in the positive half-cycle; output is zero for the negative half.

Derivations (ideal diode, resistive load R_L):

- DC (average) load current: $I_{dc} = \frac{1}{2\pi}\int_0^{\pi} I_m \sin\theta \, d\theta = \mathbf{I_m/\pi}$
- DC output voltage: $\mathbf{V_{dc} = V_m/\pi \approx 0.318\ V_m}$
- RMS load current: $I_{rms} = \sqrt{\frac{1}{2\pi}\int_0^{\pi} I_m^2 \sin^2\theta \, d\theta} = \mathbf{I_m/2}$
- **Form factor** $= I_{rms}/I_{dc} = (I_m/2)/(I_m/\pi) = \mathbf{\pi/2 = 1.57}$
- **Ripple factor** $\gamma = \sqrt{FF^2 - 1} = \sqrt{1.57^2 - 1} = \mathbf{1.21}$
- **Rectification efficiency** $\eta = P_{dc}/P_{ac} = (I_{dc}^2 R_L)/(I_{rms}^2(r_f + R_L)) \rightarrow$ max $\mathbf{\eta = 4/\pi^2 = 40.6\ \%}$ (ideal diode)
- **PIV = V_m**


- **TUF = 0.287** (secondary); because DC flows through the secondary, the transformer core suffers **DC saturation** — a major drawback.
- Ripple (lowest/fundamental) frequency = **f** (same as supply, e.g. 50 Hz).

2.3.2 Full-wave centre-tapped rectifier (FWR-CT)

Two diodes + centre-tapped secondary; each half of the secondary drives one diode alternately, so **both half-cycles** appear across the load in the same direction.

- **$I_{dc} = 2I_m/\pi$, $V_{dc} = 2V_m/\pi \approx 0.636\ V_m$** ($V_m$ = peak of *half* secondary)
- **$I_{rms} = I_m/\sqrt{2}$**
- **Form factor = $(I_m/\sqrt{2})/(2I_m/\pi) = \pi/(2\sqrt{2}) = 1.11$**
- **Ripple factor $\gamma = \sqrt{(1.11^2 - 1)} = 0.482 \approx 0.48$**
- **$\eta(max) = 8/\pi^2 = 81.2\ \%$**
- **PIV = $2V_m$** ← the big penalty of the centre-tap topology
- **TUF = 0.693** (average of primary 0.812 and secondary 0.574)
- Ripple frequency = **2f** (100 Hz on 50 Hz mains).

2.3.3 Bridge rectifier

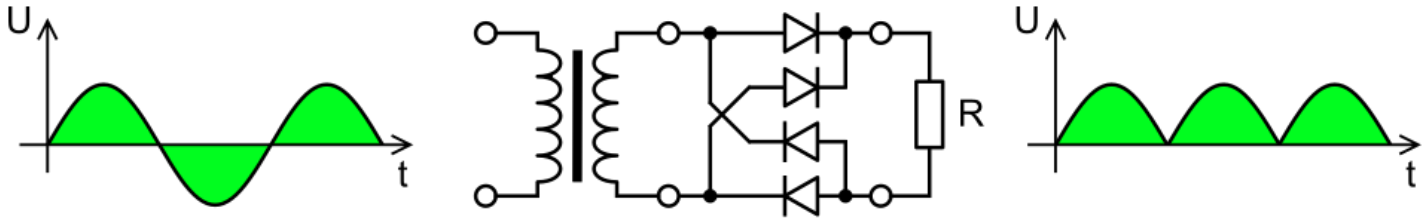

Full-wave bridge rectifier (Graetz bridge).

Four diodes in a bridge; no centre tap required. In each half-cycle two diagonal diodes conduct in series.

- Same waveform maths as FWR-CT: $V_{dc} = 2V_m/\pi$, FF = 1.11, γ = 0.48, $\eta(max)$ = 81.2 %
- **PIV per diode = V_m only** (half that of centre-tap for the same output)
- **TUF = 0.812** — best transformer utilisation
- Two diode drops (≈ 1.4 V for Si) in series each half-cycle — slight disadvantage at low voltages
- Ripple frequency = **2f**.

2.3.4 Master comparison table (memorise completely)

Parameter	Half-wave	Full-wave centre-tap	Bridge
No. of diodes	1	2	4
V_{dc} (ideal)	$V_m/\pi = 0.318\ V_m$	$2V_m/\pi = 0.636\ V_m$	$2V_m/\pi = 0.636\ V_m$
I_{rms}	$I_m/2$	$I_m/\sqrt{2}$	$I_m/\sqrt{2}$
Form factor	**1.57**	**1.11**	**1.11**
Ripple factor	**1.21**	**0.482**	**0.482**
Max efficiency	**40.6 %**	**81.2 %**	**81.2 %**
PIV per diode	V_m	**$2V_m$**	**V_m**
TUF	0.287	0.693	**0.812**
Ripple frequency	f	2f	2f
Centre-tapped transformer?	No	**Yes**	No
Diode drops in path	1	1	2
DC core saturation	Yes	No	No

Bridge vs centre-tap (statement questions love these):

1. Bridge needs no centre-tapped transformer (cheaper, smaller transformer).
2. PIV rating of bridge diodes is half → suits **high-voltage** applications.
3. Bridge has the **highest TUF (0.812)**.
4. Centre-tap wins only where the two extra diode drops matter (very low output voltages) since it has one diode drop per path.

2.3.5 Transformer Utilisation Factor (TUF) — asked in 2025

TUF = P_{dc} delivered to load / AC (VA) rating of the transformer

It measures how effectively transformer VA capacity is converted into DC power. TUF is always < 1. Ranking: **Bridge (0.812) > FW centre-tap (0.693) > Half-wave (0.287)**. Low TUF of HWR means a much bigger transformer is needed for the same DC output.

2.3.6 Filters

The pulsating rectifier output = DC + ripple harmonics. Filters pass DC and block ripple.

Filter	Connection	Behaviour	Ripple factor (FWR)	Best at
Shunt capacitor (C)	C across load	C charges to V_m, feeds load during diode-off time	$\gamma = 1/(4\sqrt{3}\, f\, C\, R_L)$	Light loads (small I_{dc}). Surge current on diodes is high
Series inductor (L)	L in series	L opposes changes in current	$\gamma = R_L/(3\sqrt{2}\,\omega L)$	Heavy loads (large I_{dc})
LC (L-section)	L series + C shunt	Combines both; ripple independent of load	$\gamma = \sqrt{2}/(12\,\omega^2 LC)$	Good regulation; needs bleeder resistor & critical inductance $L_C = R_L/3\omega$
π (CLC)	C–L–C	Highest DC output (≈ V_m), best smoothing	Higher than LC at same L,C values? No — lowest ripple, but **poor regulation**	Low-current, low-ripple loads

Capacitor-filter DC output ≈ $V_m - I_{dc}/(4fC)$ for full-wave. Peak-to-peak ripple $V_{r(pp)} = I_{dc}/(2fC)$ (full-wave), $I_{dc}/(fC)$ (half-wave).

2.3.7 Clippers and clampers

Clipper (limiter): removes part of the waveform above/below a reference level using a diode ± bias battery. Series clipper (diode in series with load) or shunt clipper (diode across load). Output amplitude is *changed*; DC level essentially unchanged. Applications: wave shaping, protection, TV sync separation.

- Positive clipper: removes positive peaks. Biased clipper: clips beyond $V_\gamma + V_{bias}$.
- Two-level (slicer/zener) clipper: clips both peaks — makes an approximate square wave from a sine.

Clamper (DC restorer): shifts the entire waveform up or down **without changing its shape or peak-to-peak value**, using a capacitor + diode (+ optional bias). $RC \gg T$ (typically $\geq 10T$).

- Positive clamper: pushes waveform up (diode conducts on negative peak, charging C to V_m).
- Negative clamper: pushes it down.
- Total swing after clamping = same $2V_m$; new peak = $2V_m$ (voltage doubler principle builds on this).

Rule of thumb: clipper *cuts*, clamper *shifts*.

2.4 Junction Transistor (BJT)


2.4.1 Construction

A Bipolar Junction Transistor = two PN junctions back-to-back sharing a common middle region: **NPN** or **PNP**.

Region	Doping	Width	Role
Emitter (E)	Heaviest	Moderate	Injects (emits) majority carriers
Base (B)	Lightest	**Thinnest** (~μm)	Passes carriers through; small recombination
Collector (C)	Moderate	**Largest area**	Collects carriers; large area to dissipate heat

"Bipolar" = both electrons **and** holes take part in conduction. NPN is preferred: electron mobility > hole mobility → faster, higher gain.

2.4.2 Operation (active region, NPN)

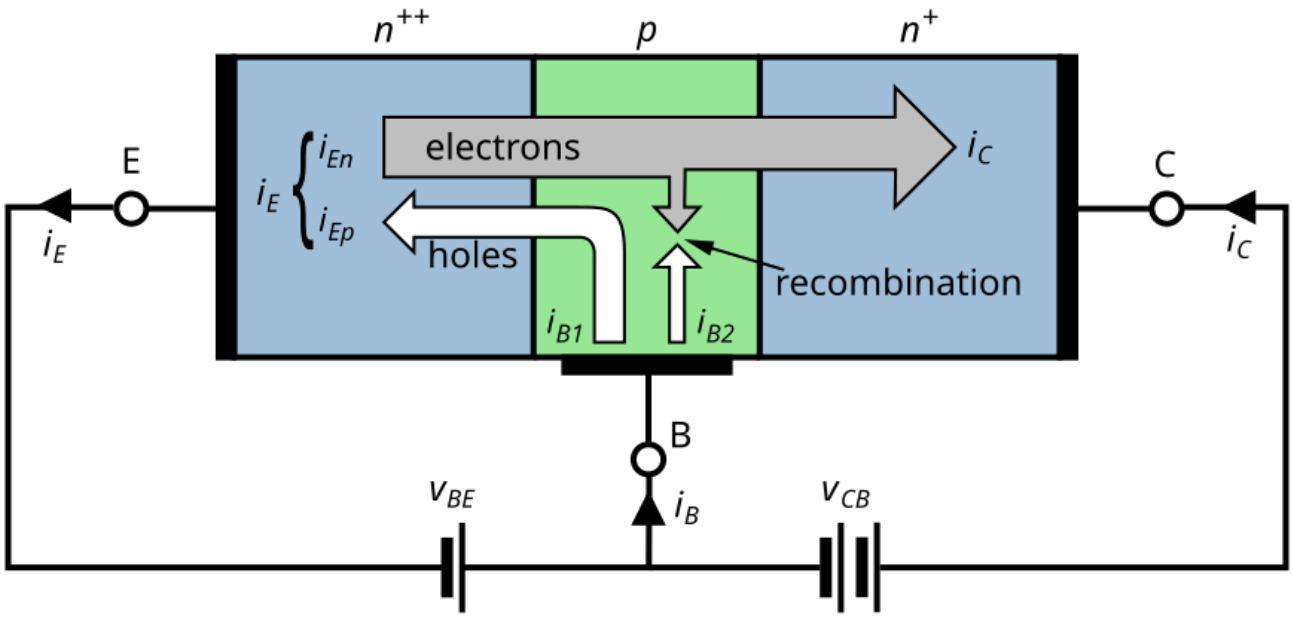

NPN BJT carrier flow in the active region.

Bias for amplifier action: **emitter–base junction forward biased, collector–base junction reverse biased.**

1. Forward-biased EB junction injects electrons from emitter into the base.
2. Base is thin and lightly doped → only ~1–5 % recombine (forming I_B).
3. ~95–99 % diffuse across and are swept into the collector by the reverse-biased CB field → I_C.

Fundamental current relation (KCL on the device):

I_E = I_C + I_B ← asked directly in 2025

Including leakage: I_C = αI_E + I_CBO, and in CE form I_C = βI_B + I_CEO where **I_CEO = (1+β) I_CBO**.

2.4.3 Current gains α, β, γ

- **α (CB current gain)** = I_C/I_E (0.95–0.998, always < 1)
- **β = h_FE (CE current gain)** = I_C/I_B (20–500)
- **γ (CC current gain)** = I_E/I_B = **1 + β**

Conversions (drill these):

β = α/(1−α) α = β/(1+β) γ = 1 + β = 1/(1−α)

2.4.4 Configurations — comparison table

Property	Common Base (CB)	Common Emitter (CE)	Common Collector (CC)
Input between	E–B	B–E	B–C
Current gain	$\alpha < 1$	**β (high)**	$\gamma = 1+\beta$ (highest)
Voltage gain	High	**High**	< 1 (≈ 0.95–0.99)
Power gain	Moderate	**Highest**	Lowest
Input impedance	Very low (20–100 Ω)	Moderate (~1 kΩ)	**Very high (~100s of kΩ)**
Output impedance	Very high (~MΩ)	Moderate (~50 kΩ)	**Very low (~50 Ω)**
Phase shift (in–out)	0°	**180°**	0°
Applications	HF amplifier, impedance step-up	**General amplifier** (most used)	Buffer / emitter follower, impedance matching

2.4.5 CE output characteristics and regions of operation

Plot of I_C vs V_{CE} for steps of I_B shows three regions:

Region	EB junction	CB junction	Behaviour	Use
Cut-off	Reverse	Reverse	$I_C \approx 0$ (only leakage)	Switch OFF
Active	Forward	Reverse	$I_C = \beta I_B$, nearly flat curves	**Amplifier**
Saturation	Forward	Forward	$V_{CE} \approx 0.2$ V (Si), I_C limited by external circuit	Switch ON

Early effect (base-width modulation): increasing V_{CE} slightly narrows the base → curves have small upward slope in active region.

2.4.6 DC load line and Q-point

For a CE stage with collector supply V_{CC} and collector resistor R_C (plus R_E if present), KVL gives:

$V_{CE} = V_{CC} - I_C (R_C + R_E)$

This straight line on the output characteristics is the **DC load line**:

- V_{CE}-axis intercept (cut-off point): $V_{CE} = V_{CC}$ ($I_C = 0$)
- I_C-axis intercept (saturation point): $I_{C(sat)} = V_{CC}/(R_C + R_E)$

The **quiescent (Q) point** is the intersection of the load line with the $I_B = I_{BQ}$ characteristic. For maximum symmetrical swing in class-A: place Q at the **middle** of the load line ($V_{CEQ} \approx V_{CC}/2$).

AC load line has slope $-1/(R_C \parallel R_L)$ and passes through Q; it is steeper than the DC load line.

2.4.7 Biasing methods and stability factor

Bias circuits must hold Q fixed against temperature (I_{CBO} doubles/10 °C, V_{BE} −2 mV/°C, β spread).

Stability factor $S = \partial I_C / \partial I_{CBO}$ (smaller is better; ideal = 1).

Method	Circuit essence	S	Comment
Fixed bias (base bias)	Single R_B from V_CC to base	**S = 1 + β** (worst)	Simplest; thermally unstable; risk of thermal runaway
Collector-to-base bias	R_B from collector to base	S = (1+β)/(1 + β·R_C/(R_C+R_B))	Negative feedback improves stability; reduces gain
Emitter bias (fixed + R_E)	R_B + emitter resistor R_E	Between fixed and voltage-divider	R_E gives current-series feedback
Voltage-divider (self) bias	R_1–R_2 divider + R_E	**S = (1+β)·(1 + R_B/R_E)/(1 + β + R_B/R_E) ≈ 1 + R_B/R_E** (best practical)	Industry standard; Q nearly independent of β

Voltage-divider analysis: V_B = V_CC·R_2/(R_1+R_2) (if divider stiff, i.e. I_divider ≫ I_B); V_E = V_B − 0.7; I_C ≈ I_E = V_E/R_E; V_CE = V_CC − I_C(R_C + R_E).

Thermal runaway: rise in T → I_CBO↑ → I_C↑ → junction power ↑ → T↑ … cumulative destruction. Prevented by R_E (self-bias), heat sinks, and ensuring V_CE < V_CC/2 condition for thermal stability.

2.4.8 BJT as a switch

- **OFF:** base open/reverse biased → cut-off → V_out ≈ V_CC.
- **ON:** enough base drive to saturate (I_B > I_C(sat)/β) → V_CE(sat) ≈ 0.2 V.

Used in logic gates, relay/LED drivers, choppers. Switching speed is limited by storage time (charge stored in base during saturation).

2.5 Field-Effect Transistors — JFET and MOSFET (basics)

FETs are **unipolar** (conduction by one carrier type only), **voltage-controlled** devices with very high input impedance.

2.5.1 JFET

- Structure: n-channel (or p-channel) bar with two p^+ (or n^+) gate regions; terminals **Source, Gate, Drain**.
- Gate–channel junction always **reverse biased**; input impedance ~10^8 Ω.
- Increasing |V_GS| widens depletion, narrows channel; at **pinch-off voltage V_P**, channel closes and I_D saturates.
- Transfer (Shockley) equation: **$I_D = I_{DSS}(1 - V_{GS}/V_P)^2$** — square-law device (low intermodulation distortion).
- Transconductance: **$g_m = \partial I_D/\partial V_{GS} = g_{m0}(1 - V_{GS}/V_P)$**, where $g_{m0} = 2I_{DSS}/|V_P|$.
- Amplification factor: **μ = g_m × r_d**.
- JFET is a **depletion-mode-only** device; normally ON at V_GS = 0.

2.5.2 MOSFET

Metal-Oxide-Semiconductor FET: gate insulated from channel by SiO_2 → input impedance 10^{10}–10^{15} Ω; handle with anti-static care (gate oxide punctures easily).

Type	State at V_GS = 0	Control
Depletion MOSFET (D-MOSFET)	ON (channel built in)	Can be operated in both depletion and enhancement modes
Enhancement MOSFET (E-MOSFET)	**OFF** (no channel)	Conducts only when V_GS > threshold V_T; $I_D = k(V_{GS} - V_T)^2$

E-MOSFETs (NMOS/PMOS) are the basis of **CMOS** digital ICs — negligible static power. Power MOSFETs (VDMOS) dominate SMPS and motor drives.

BJT vs FET quick contrast: BJT — bipolar, current-controlled, low input Z, higher gain, cheaper; FET — unipolar, voltage-controlled, very high input Z, better thermal stability (negative temperature coefficient of I_D prevents thermal runaway), lower noise.

2.6 Transistor Amplifiers

2.6.1 Small-signal CE amplifier

The workhorse voltage amplifier: voltage-divider-biased CE stage with coupling capacitors (block DC) and emitter bypass capacitor (restores AC gain).

- AC emitter resistance: **$r_e' = 26\ mV / I_{E(mA)}$**
- Voltage gain (bypassed R_E): **$A_v \approx -(R_C \parallel R_L)/r_e'$** (minus = 180° phase inversion)
- Input impedance: $Z_{in} = R_1 \parallel R_2 \parallel \beta\, r_e'$
- Removing the bypass capacitor: $A_v \approx -R_C/(r_e' + R_E)$ — lower but stabler gain (swamping).

2.6.2 h-parameters (hybrid model) — basics

For any two-port: $v_1 = h_i\, i_1 + h_r\, v_2$; $i_2 = h_f\, i_1 + h_o\, v_2$.

Symbol (CE)	Name	Typical value	Unit
h_ie	Input impedance (output shorted)	1–2 kΩ	Ω
h_re	Reverse voltage ratio	2.5×10^{-4}	—
h_fe (= β_ac)	Forward current gain	50–300	—
h_oe	Output admittance (input open)	25 µS	siemens (℧)

Note the mixed units → "hybrid". Approximate CE results: $A_i = -h_{fe}/(1 + h_{oe} R_L) \approx -h_{fe}$; $Z_{in} \approx h_{ie}$; $A_v = -h_{fe} R_L/h_{ie}$.

2.6.3 Multistage & RC-coupled amplifier frequency response

Cascading raises gain: overall $A = A_1 \times A_2 \times \ldots$; in dB, gains add. Coupling methods: RC (cheapest, audio), transformer (impedance matching, power), direct (DC amplifiers, drift problem).

RC-coupled amplifier response (the classic curve):

- **Low-frequency roll-off:** coupling & bypass capacitors' reactance rises → gain falls.
- **Mid-band:** capacitors ≈ shorts, strays ≈ open → flat maximum gain.
- **High-frequency roll-off:** shunt/stray/junction capacitances (and Miller capacitance $C_M = C_{bc}(1+|A_v|)$) short the signal.
- **Cut-off frequencies f_1 (lower), f_2 (upper):** gain = $A_{mid}/\sqrt{2}$ = **−3 dB points** (half-power points).
- **Bandwidth $BW = f_2 - f_1$; Gain × Bandwidth = constant** (figure of merit f_T).

2.6.4 Amplifier classes (power amplifiers)

Class	Conduction angle	Q-point location	Max theoretical efficiency	Distortion	Use
A	360°	Centre of load line	**25 %** (series-fed), **50 %** (transformer-coupled)	Lowest	Small-signal, hi-fi
B	180°	At cut-off	**78.5 % (π/4)**	Crossover distortion in push-pull	Push-pull output stages
AB	180°–360°	Slightly above cut-off	50–78.5 %	Removes crossover distortion	Audio power amps
C	< 180°	Below cut-off	> 90 % (up to ~99 %)	Very high — needs tuned tank	RF tuned amplifiers, oscillators

Push-pull class-B: two transistors handle alternate half-cycles; even harmonics cancel. Complementary-symmetry version (NPN + PNP) eliminates transformers. Crossover distortion (dead zone ±0.7 V) removed by class-AB pre-bias (diode biasing).

2.6.5 Distortion & noise (one-liners)

- Amplitude (harmonic) distortion — nonlinearity of characteristics; measured by THD.
- Frequency distortion — unequal gain at different frequencies.
- Phase distortion — unequal phase shift vs frequency.
- Noise figure NF = (S/N)_in / (S/N)_out in dB; ideal amplifier NF = 0 dB.

2.7 Feedback in Amplifiers

Feedback returns a fraction β_f (feedback factor) of the output to the input.

Closed-loop gain: A_f = A / (1 + Aβ_f) (negative feedback; loop gain = Aβ_f)

If |1 + Aβ_f| > 1 → **negative (degenerative)**; if < 1 → positive (regenerative); if 1 + Aβ_f = 0 → oscillation.

Effects of negative feedback (all by the factor D = 1 + Aβ_f):

Quantity	Effect
Gain	Decreases: A_f = A/D
Gain stability	Improves: dA_f/A_f = (1/D)(dA/A)
Bandwidth	**Increases**: BW_f = D × BW (gain × BW constant)
Distortion & noise (in loop)	Decreases by D
Input impedance	↑ for **series** mixing; ↓ for shunt mixing
Output impedance	↓ for **voltage** (shunt) sampling; ↑ for current (series) sampling

Four topologies:

Topology (sampling–mixing)	Alt name	Z_in	Z_out	Stabilised gain	Example
Voltage-series	Series-shunt	↑	↓	Voltage gain	Emitter follower, non-inverting op-amp
Voltage-shunt	Shunt-shunt	↓	↓	Transresistance	Collector-to-base bias, inverting op-amp
Current-series	Series-series	↑	↑	Transconductance	Unbypassed R_E stage
Current-shunt	Shunt-series	↓	↑	Current gain	Two-stage feedback pair

When $A\beta_f \gg 1$: **$A_f \approx 1/\beta_f$** — gain set only by (passive, stable) feedback network.

2.8 Oscillators

An oscillator converts DC into AC of desired frequency **without any external input signal** — it is an amplifier with **positive feedback** satisfying:

2.8.1 Barkhausen criterion — asked in 2025

For sustained oscillations:

1. **Loop gain magnitude $|A\beta_f| = 1$** (in practice slightly > 1 to start; amplitude then self-limits), and
2. **Total loop phase shift = 0° or 360°** (i.e. $2n\pi$).

The starting "input" is internal noise/switching transient — no external signal is required. If $|A\beta| < 1$ oscillations die out; if held $\gg 1$ the output distorts/clips.

2.8.2 RC oscillators (audio frequency)


RC phase-shift oscillator

- CE amplifier (180°) + three-section RC ladder giving another 180° (60° per section).
- **$f = 1/(2\pi RC\sqrt{6})$** (FET/ideal version); with BJT loading: $f = 1/[2\pi RC\sqrt{(6 + 4R_C/R)}]$.
- Requires amplifier gain **$|A| \geq 29$** ($\beta_f = 1/29$).

Wien bridge oscillator

- Series RC + parallel RC (lead–lag) network in a bridge; two-stage/non-inverting amplifier (0° amplifier phase, 0° network phase at f_0).
- **$f = 1/(2\pi RC)$** (equal R, C).
- Network attenuation = 1/3 → requires **gain ≥ 3** (so in op-amp form $R_f = 2R_1$).
- Amplitude stabilised by a thermistor/sensistor or lamp. Excellent low-distortion sine source; standard in audio signal generators.

2.8.3 LC oscillators (radio frequency)

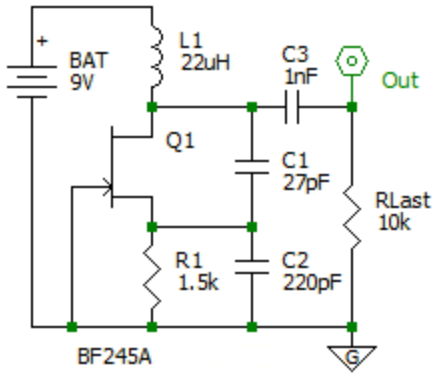

Colpitts oscillator (capacitive tap — an LC oscillator).

General form: tank circuit of reactances X_1, X_2 (across the two amplifier input/output nodes) and X_3 (feedback). Oscillation needs X_1, X_2 same type and X_3 opposite type.

Hartley oscillator — **tapped inductor** (two inductors L_1, L_2, may be mutually coupled M) + one capacitor:

$f = 1/(2\pi\sqrt{(L_{eq} C)})$, $L_{eq} = L_1 + L_2 + 2M$; feedback fraction $\beta_f = L_2/L_1$ (gain needed ≈ L_1/L_2).

Colpitts oscillator — **tapped capacitor** (C_1, C_2 in series) + one inductor:

$f = 1/(2\pi\sqrt{(L\, C_{eq})})$, $C_{eq} = C_1C_2/(C_1 + C_2)$; feedback fraction = C_1/C_2 (voltage divider across capacitors); gain condition ≈ C_2/C_1 (using amplifier input side C_2). Better frequency stability than Hartley at high f; capacitors are cheaper/purer than tapped coils.

Clapp oscillator — Colpitts + small capacitor **C_3 in series with L**; $C_3 \ll C_1$, C_2 dominates the frequency:

$f = (1/2\pi)\sqrt{[(1/L)(1/C_1 + 1/C_2 + 1/C_3)]} \approx 1/(2\pi\sqrt{(LC_3)})$

Frequency almost independent of transistor junction capacitances → improved stability.

Identification trick: Colpitts → **C**apacitive divider; **H**artley → tapped **H**enries (inductor); Clapp → Colpitts + extra series C.

2.8.4 Crystal oscillator

Quartz crystal = electromechanical resonator (piezoelectric effect). Equivalent circuit: series R-L-C (motional arm) in parallel with mount capacitance C_M.

- **Series resonance $f_s = 1/(2\pi\sqrt{(LC)})$**; parallel (antiresonance) f_p slightly above f_s; crystal is **inductive between f_s and f_p** — the region used in oscillator circuits (e.g. Pierce = crystal Colpitts).
- Extraordinary **Q (10^4–10^6)** → frequency stability ~1 ppm or better.
- Used wherever accuracy matters: clocks, microprocessors, transmitters, watches.

Frequency-stability ranking: Crystal ≫ Clapp > Colpitts ≈ Hartley > RC types.

2.8.5 Negative-resistance & relaxation oscillators

- Tunnel-diode and UJT oscillators exploit negative-resistance/relaxation action (UJT covered in §2.10.6).
- Relaxation oscillators produce **non-sinusoidal** (sawtooth/square) outputs via RC charge–discharge.

2.9 Multivibrators and Counters

Multivibrators are two-stage regenerative (positive-feedback) switching circuits producing square/rectangular waves. Each stage drives the other; the transistors act as switches, alternately cut-off and saturated.

2.9.1 The three types

Type	Stable states	Coupling (classic BJT circuit)	Output	Also called	Applications
Astable	**0** (free-running)	Both stages **capacitor (AC)** coupled	Continuous square wave	Free-running MV	Clock generation, flashers
Monostable	**1**	One capacitive + one resistive (DC) coupling	Single pulse of fixed width per trigger	One-shot	Pulse-width generation, timing/delay
Bistable	**2**	Both stages **resistive (DC)** coupled	Toggles state on each trigger, holds indefinitely	Flip-flop, Eccles–Jordan, binary	Memory, **counters**, frequency division

2.9.2 Timing formulas (BJT collector-coupled circuits)

- Half-period of astable per side: T_1 = **$0.693\ R_1C_1$** (time for the capacitor to bring the off transistor's base up through V_BE); total **$T = 0.693(R_1C_1 + R_2C_2)$**; symmetric case **$T = 1.386\ RC$**, f = 1/T ≈ **$0.72/RC$**.
- Monostable pulse width: **$T = 0.693\ RC$**.
- (IC 555 versions: astable T = 0.693(R_A + 2R_B)C; monostable T = 1.1 RC — useful cross-checks.)

2.9.3 Schmitt trigger

An emitter-coupled bistable with **hysteresis**: two different threshold voltages, Upper Trip Point (UTP) and Lower Trip Point (LTP). Converts any slowly varying/noisy waveform into a clean square wave — a "squaring circuit"/level detector. Hysteresis width = UTP − LTP gives noise immunity.


2.9.4 Counters (as required by the syllabus keyword)

A **counter** is a chain of bistable multivibrators (flip-flops). Each flip-flop **divides frequency by 2** (one output pulse for every two input triggers).

- **n flip-flops → modulus up to 2^n** (counts 0 to $2^n - 1$). For MOD-m: n = $\lceil \log_2 m \rceil$ flip-flops; unwanted states skipped by reset logic (e.g. decade counter MOD-10 uses 4 FFs, resets at 1010).
- **Asynchronous (ripple) counter:** clock ripples through FFs; simple but slow (delays add: t_total = n·t_pd).
- **Synchronous counter:** common clock to all FFs; faster, glitch-free.
- **Ring counter:** n FFs → MOD-n; **Johnson (twisted-ring):** n FFs → MOD-2n.
- Applications: digital clocks, frequency division/measurement, event counting. (Full digital treatment appears in the Digital Electronics chapter; here remember the multivibrator–counter link: **bistable = 1-bit memory = divide-by-2**.)

2.10 Thyristor Family

2.10.1 SCR — construction

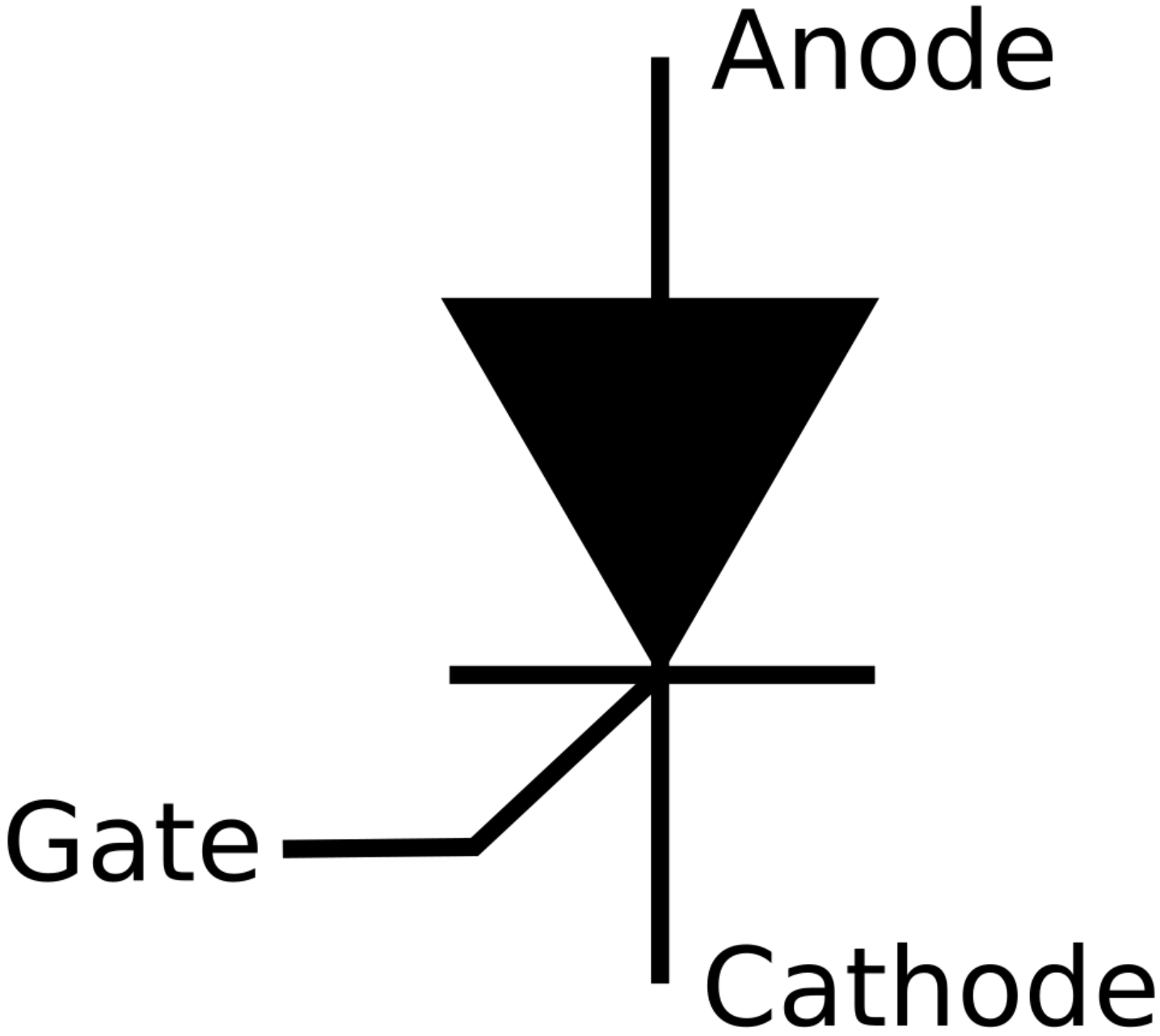

SCR / thyristor symbol.

The Silicon Controlled Rectifier is a **four-layer (P-N-P-N), three-junction (J_1, J_2, J_3), three-terminal** device: **Anode (A), Cathode (K), Gate (G — attached to the inner p-layer near the cathode)**. It is a unidirectional, latching power switch (ratings to several kA / kV).

2.10.2 V-I characteristic

- **Reverse blocking (A negative):** J_1, J_3 reverse biased → tiny leakage until reverse breakdown V_BR. SCR must never be gated here.
- **Forward blocking (A positive, no gate):** J_2 reverse biased → only leakage flows (OFF state) until the **forward break-over voltage V_BO**.
- **Forward conduction (ON):** once triggered (gate pulse or V > V_BO), J_2 collapses; device latches like a closed switch, drop ≈ 1–2 V. **Increasing gate current lowers the break-over voltage.**

- **Latching current I_L:** minimum anode current to latch ON just after triggering (gate may then be removed).
- **Holding current I_H:** minimum anode current below which the SCR turns OFF. **I_L > I_H** (typically I_L ≈ 2–3 × I_H).

2.10.3 Two-transistor analogy

Split the PNPN structure into a PNP (Q_1) and an NPN (Q_2) transistor: collector of each feeds the base of the other. Anode current:

$I_A = (\alpha_1 + \alpha_2) I_A + I_{leak} \rightarrow I_A = I_{leak} / [1 - (\alpha_1 + \alpha_2)]$

When gate/leakage current raises $\alpha_1 + \alpha_2 \rightarrow 1$, $I_A \rightarrow \infty$ (limited only by external circuit) — **regenerative latching**. This explains: (i) why the gate loses control after turn-on, and (ii) dv/dt false triggering (junction capacitance current mimics gate current).

2.10.4 Triggering (turn-on) and commutation (turn-off)

Turn-on methods:

1. **Gate triggering** (normal method — small gate pulse while forward biased)
2. Forward-voltage triggering (exceeding V_BO — avoided in practice)
3. **dv/dt triggering** (fast anode voltage rise — unwanted; suppressed by RC **snubber**)
4. Temperature triggering (leakage rise — unwanted)
5. Light triggering (**LASCR** — used in HVDC valves)

Turn-off (commutation) — anode current must fall below I_H and reverse bias/zero bias held for the turn-off time t_q:

- **Natural (line) commutation:** AC supply reverses every half-cycle — free of cost; used in phase-controlled rectifiers, AC regulators.
- **Forced commutation:** in DC circuits an auxiliary L-C circuit forces current to zero (classes A–F) — used in choppers and (older) inverters.

Gate protection & firing: series resistor limits gate current, R-C across gate for noise, pulse-transformer/optocoupler isolation; R-firing, RC-firing and UJT-firing circuits give 0–90°, 0–180°, and precise wide-range control respectively.

2.10.5 TRIAC and DIAC

TRIAC = two SCRs in inverse parallel integrated in one 5-layer chip; terminals **MT_1, MT_2, Gate**. Conducts in **both directions**; can be triggered by positive or negative gate pulses (four triggering modes; quadrants I+ and III− are most sensitive). Used in AC phase control: fan regulators, lamp dimmers, temperature control. Drawback vs two SCRs: lower dv/dt rating, less sensitive in some quadrants.

DIAC = gateless bidirectional trigger diode (3-layer/5-layer symmetric). Blocks until break-over (≈ 30–35 V) in either polarity, then exhibits negative resistance. Almost always used in the gate circuit of a TRIAC (dimmers) to deliver sharp symmetric trigger pulses.

Other members (one-liners): GTO — gate turn-off thyristor (negative gate pulse turns it OFF; no forced-commutation circuit needed); SCS — silicon controlled switch (two gates); PUT — programmable UJT; MCT/IGBT covered in Power Electronics.

2.10.6 UJT and the relaxation oscillator

UJT (Uni-Junction Transistor): lightly doped n-type silicon bar with base contacts B_1, B_2 and a single p-emitter part-way along — one PN junction, hence the name; also called *double-base diode*.

- **Intrinsic stand-off ratio: $\eta = R_{B1}/(R_{B1} + R_{B2})$**, typically **0.5–0.8**.
- Emitter peak (firing) voltage: **$V_P = \eta V_{BB} + V_D$** ($V_D \approx 0.7$ V).
- Once $V_E \geq V_P$, the E–B_1 region floods with carriers → R_{B1} collapses → **negative-resistance region** between peak and valley points — the key to oscillation.

UJT relaxation oscillator: R_T charges C_T toward V_BB; at V_P the UJT fires and rapidly discharges C_T through B_1 (sharp pulse across R_1); C_T recharges and the cycle repeats.

$T \approx R_T C_T \ln[1/(1-\eta)]$, $f = 1/T$

(For $\eta = 0.63$, $T \approx R_T C_T$.) Output: sawtooth at the emitter, sharp spikes at B_1 — ideal, well-synchronised **trigger pulses for SCR/TRIAC firing**.

2.11 Triode and Vacuum-Tube Basics (brief — syllabus item)

Before semiconductors, thermionic vacuum tubes did every electronic job.

- **Diode valve (Fleming, 1904):** heated cathode (thermionic emission — Richardson's law) + anode (plate). Conducts only when plate is positive → rectifier. Space-charge-limited current follows **Child–Langmuir 3/2-power law: $I_P \propto V_P^{(3/2)}$**.
- **Triode (De Forest, 1906):** adds a **control grid** between cathode and plate. A small negative grid voltage strongly throttles plate current → **amplification**.

Triode constants (defined at constant third variable):

Constant	Definition	Typical
Amplification factor **μ**	$-\partial V_P/\partial V_G$ at constant I_P	10–100
Plate (dynamic) resistance **r_p**	$\partial V_P/\partial I_P$ at constant V_G	5–50 kΩ
Transconductance (mutual conductance) **g_m**	$\partial I_P/\partial V_G$ at constant V_P	1–10 mA/V

Master relation: $\mu = g_m \times r_p$

Triode amplifier gain: **$A = \mu R_L/(r_p + R_L)$** (approaches μ as $R_L \to \infty$).

Later tubes: **tetrode** (screen grid — but has negative-resistance kink from secondary emission), **pentode** (adds suppressor grid — removes the kink; higher gain). Tubes survive today in high-power RF transmitters, magnetrons (microwave ovens), CRTs and boutique audio. Triode ↔ semiconductor analogy: cathode↔emitter/source, grid↔base/gate, plate↔collector/drain.

2.12 Inverters and UPS

2.12.1 Inverter

An **inverter converts DC into AC** of desired voltage and frequency (the inverse of a rectifier). Power devices used: MOSFET/IGBT (modern), thyristors with forced commutation (legacy).

Classification:

Basis	Types
Source	**VSI** (Voltage Source Inverter — stiff DC voltage, capacitor at input) / **CSI** (Current Source Inverter — stiff DC current, large series inductor)
Phases	Single-phase (half-bridge: 2 switches, output ±V_dc/2; full-bridge/H-bridge: 4 switches, output ±V_dc) / Three-phase (6 switches; 120°- or 180°-conduction modes)
Output waveform	**Square wave** (simple, high harmonic content), **modified/quasi sine** (stepped), **pure sine** (PWM + LC filter — best for motors and sensitive loads)
Control	PWM — **sinusoidal PWM (SPWM)** compares a sine reference with a high-frequency triangular carrier; modulation index m_a = V_ref/V_carrier controls the fundamental output; harmonics pushed to high frequency, easily filtered

Square-wave full-bridge output: RMS = V_dc; fundamental RMS = (4V_dc/π)/√2 = **0.9 V_dc**; only odd harmonics present (3rd = 1/3 amplitude, 5th = 1/5 …). Harmonic quality measured by **THD** (square wave THD ≈ 48.3 %).

Applications: solar/battery power systems, UPS, variable-frequency drives (VFD), induction heating, HVDC receiving stations, electric traction auxiliaries.

2.12.2 UPS — Uninterruptible Power Supply

A UPS delivers continuous, conditioned AC power to critical loads (computers, servers, medical, railway signalling) during mains failure or disturbances.

Core blocks: Rectifier/charger (AC→DC), **Battery bank** (energy storage), **Inverter** (DC→AC), **Static transfer switch/bypass**.

Three standard topologies:

Type	Normal-path operation	Transfer time	Protection quality	Typical use
Offline (standby)	Load fed **directly from mains**; inverter idle, battery on float charge. On failure, static switch transfers load to inverter	~4–10 ms (brief break)	Basic — voltage sags/noise pass through in normal mode	PCs, home use; cheapest, most efficient in standby
Line-interactive	Mains feeds load through an **AVR (buck–boost autotransformer)**; the bidirectional inverter/charger sits across the line and corrects sags/swells without draining the battery	~2–4 ms	Good — regulates voltage without battery use	Small servers, network gear
Online (double-conversion)	Load is fed **always from the inverter**: mains → rectifier → DC bus (battery floats here) → inverter → load. Mains failure causes **zero transfer time** — battery is already in the path	**0 ms (no break)**	Best — total isolation from all mains disturbances; output frequency/voltage fully regenerated	Data centres, hospitals, railway signalling & telecom

Block-diagram memory aid (online UPS): Mains → [Rectifier/Charger] → DC bus ← [Battery] → [Inverter] → [Static bypass switch] → Load. The bypass carries the load if the inverter itself fails or during overload/maintenance.

2.12.3 Battery sizing basics

- **Battery Ah capacity required ≈ (Load power in W × backup time in h) / (Battery voltage × inverter efficiency × depth-of-discharge)**
- Example: 600 W load, 1 h backup, 24 V bank, η_inv = 0.85, DoD = 0.8:

Ah = 600 × 1 / (24 × 0.85 × 0.8) ≈ **36.8 Ah → choose 40–42 Ah bank (e.g. two 12 V, 42 Ah in series)**.

- **VA vs W:** UPS rating in VA; usable watts = VA × power factor (typically 0.6–0.8 for small UPS; unity for premium online units).
- Battery types: flooded/tubular lead-acid (long life, needs topping-up), **SMF/VRLA** (sealed maintenance-free — standard in UPS), Li-ion (modern, light, costly). Float charge ≈ 2.25 V/cell, boost ≈ 2.4 V/cell (lead-acid, 2 V nominal per cell → 6 cells = 12 V battery).
- Backup time ∝ Ah / load current; runtime doubles (roughly) when load halves.

2.13 Worked Numerical Examples (12)

Example 1 — Diode dynamic resistance.

A Si diode carries a forward DC current of 2 mA at 300 K. Find its dynamic resistance (η = 1).

Solution: r_d = ηV_T/I = 26 mV / 2 mA = **13 Ω**.

Example 2 — Zener regulator.

V_in = 20 V, R_S = 1 kΩ, V_Z = 10 V, R_L = 5 kΩ. Find I_S, I_L, I_Z and power dissipated in the Zener.

Solution:

I_S = (20 − 10)/1k = 10 mA; I_L = 10/5k = 2 mA; I_Z = 10 − 2 = **8 mA**.

P_Z = V_Z × I_Z = 10 × 8 mA = **80 mW**.

Example 3 — Half-wave rectifier with transformer.

A HWR is fed from 230 V, 50 Hz mains through a 10:1 step-down transformer. Diode ideal, R_L = 100 Ω. Find V_dc, I_dc, PIV and ripple frequency.

Solution:

Secondary RMS = 230/10 = 23 V → V_m = 23√2 ≈ 32.5 V.

V_dc = V_m/π = 32.5/3.1416 ≈ **10.35 V**; I_dc = 10.35/100 ≈ **103.5 mA**.

PIV = V_m ≈ **32.5 V**; ripple frequency = **50 Hz**.

Example 4 — Full-wave centre-tap numbers.

A centre-tapped FWR has 30-0-30 V (RMS) secondary, ideal diodes, R_L = 1 kΩ. Find V_dc, I_dc, PIV, and ripple factor.

Solution:

V_m (per half) = $30\sqrt{2} \approx 42.43$ V.

$V_{dc} = 2V_m/\pi = 2 \times 42.43/\pi \approx$ **27 V**; I_{dc} = 27 mA.

PIV = $2V_m \approx$ **84.85 V**; $\gamma =$ **0.482**.

Example 5 — Rectifier efficiency with diode resistance.

A half-wave rectifier uses a diode of forward resistance $r_f = 20\ \Omega$ with $R_L = 480\ \Omega$. Find the rectification efficiency.

Solution:

$\eta = 0.406/(1 + r_f/R_L) = 0.406/(1 + 20/480) = 0.406/1.04167 \approx$ **0.39 → 39 %**.

Example 6 — Capacitor filter ripple.

A bridge rectifier (50 Hz mains) delivers 20 mA DC to a load with a 1000 µF filter capacitor. Find peak-to-peak ripple voltage.

Solution:

Full-wave: $V_{r(pp)} = I_{dc}/(2fC) = 0.02/(2 \times 50 \times 1000\times10^{-6}) = 0.02/0.1 =$ **0.2 V**.

Example 7 — α to β conversion.

A transistor has $\alpha = 0.98$ and $I_E = 5$ mA. Find β, I_C and I_B.

Solution:

$\beta = \alpha/(1-\alpha) = 0.98/0.02 =$ **49**.

$I_C = \alpha I_E = 0.98 \times 5 =$ **4.9 mA**; $I_B = I_E - I_C =$ **0.1 mA** (check: $I_C/I_B = 49$ ✓).

Example 8 — Voltage-divider bias Q-point.

V_{CC} = 12 V, R_1 = 40 kΩ, R_2 = 8 kΩ, R_C = 2 kΩ, R_E = 1 kΩ, Si transistor (V_{BE} = 0.7 V), β large. Find I_C and V_{CE}.

Solution:

$V_B = 12 \times 8/(40+8) = 2$ V; $V_E = 2 - 0.7 = 1.3$ V.

$I_C \approx I_E = 1.3/1k =$ **1.3 mA**.

$V_{CE} = 12 - 1.3\text{ mA} \times (2k + 1k) = 12 - 3.9 =$ **8.1 V**. Q-point = (8.1 V, 1.3 mA).

Example 9 — Load line end-points.

For V_{CC} = 10 V, R_C = 2 kΩ (no R_E), state the DC load-line intercepts and the mid-point Q for maximum swing.

Solution:

Cut-off point: (V_{CE}, I_C) = (**10 V, 0**). Saturation point: $I_C = 10/2k =$ **5 mA** at $V_{CE} = 0$.

Mid-point Q: $V_{CEQ} = 5$ V, $I_{CQ} =$ **2.5 mA**.

Example 10 — CE amplifier gain.

A CE amplifier has I_E = 1.3 mA, R_C = 3 kΩ, R_L = 6 kΩ (capacitively coupled), emitter fully bypassed. Estimate the voltage gain.

Solution:

$r_e' = 26/1.3 = 20\ \Omega$. $R_{ac} = R_C \parallel R_L = 3k \times 6k/9k = 2\ k\Omega$.

$A_v = -R_{ac}/r_e' = -2000/20 =$ **−100** (gain 100 with 180° inversion).

Example 11 — Colpitts frequency.

A Colpitts oscillator uses C_1 = 100 pF, C_2 = 400 pF and L = 50 µH. Find the oscillation frequency.

Solution:

$C_{eq} = C_1C_2/(C_1+C_2) = 100 \times 400/500 = 80$ pF.

$f = 1/(2\pi\sqrt{(LC_{eq})}) = 1/(2\pi\sqrt{(50\times10^{-6} \times 80\times10^{-12})})$

$= 1/(2\pi\sqrt{(4\times10^{-15})}) = 1/(2\pi \times 6.325\times10^{-8}) \approx$ **2.52 MHz**.

Example 12 — UJT relaxation oscillator.

A UJT with η = 0.63 is used with R_T = 10 kΩ, C_T = 0.1 µF, V_{BB} = 12 V. Find the firing voltage and oscillation frequency (V_D = 0.7 V).

Solution:

$V_P = \eta V_{BB} + V_D = 0.63 \times 12 + 0.7 =$ **8.26 V**.

$T = R_T C_T \ln[1/(1-\eta)] = 10^4 \times 10^{-7} \times \ln(1/0.37) = 10^{-3} \times 0.994 \approx 1$ ms.

$f = 1/T \approx$ **1 kHz**.

Bonus Example 13 — Wien bridge.

R = 10 kΩ, C = 0.01 µF in a Wien bridge oscillator. $f = 1/(2\pi RC) = 1/(2\pi \times 10^4 \times 10^{-8}) = 1/(2\pi \times 10^{-4}) \approx$ **1.59 kHz**; minimum amplifier gain required = **3**.

Bonus Example 14 — Class-B efficiency check.

A class-B push-pull amplifier with V_{CC} = 20 V drives a load to a peak output of 20 V (full swing). Maximum efficiency = π/4 = **78.5 %**. If the swing is only 10 V peak, $\eta = (\pi/4)(V_{peak}/V_{CC}) = 0.785 \times 0.5 \approx$ **39.3 %**.

2.14 PYQ Corner — 22-04-2025 CBT-2 (recreated & fully solved)

PYQ 1 (TUF statement). *Which statement about Transformer Utilisation Factor is correct?*

(a) TUF of a half-wave rectifier is 0.812

(b) TUF = DC power delivered to load ÷ AC rating of transformer secondary

(c) TUF of a bridge rectifier is less than that of a half-wave rectifier

(d) TUF is always greater than 1

Solution: TUF is defined as P_dc/(transformer VA rating) — option **(b)**. Values: HWR 0.287, FW-CT 0.693, bridge 0.812 (highest); TUF < 1 always. Hence (a), (c), (d) are all wrong. **Answer: (b)**

PYQ 2 (BJT current relation). *For a junction transistor, which of the following is always true?*

(a) $I_C = I_E + I_B$ (b) $I_B = I_C + I_E$ (c) **$I_E = I_C + I_B$** (d) $I_E = I_C - I_B$

Solution: KCL at the device: the emitter current splits into collector and base components: **$I_E = I_C + I_B$**. Numerically I_E is the largest, I_B the smallest ($I_B \approx$ 1–5 % of I_E). **Answer: (c)**

PYQ 3 (HWR with transformer — numerical). *A half-wave rectifier is supplied from 220 V, 50 Hz mains through a step-down transformer of turns ratio 10:1. Assuming an ideal diode, the DC output voltage is approximately:*

(a) 22 V (b) 9.9 V (c) 31.1 V (d) 14 V

Solution: Secondary RMS = 220/10 = 22 V → $V_m = 22\sqrt{2} = 31.11$ V.

$V_{dc} = V_m/\pi = 31.11/3.1416 \approx$ **9.9 V**. **Answer: (b)**

(Trap options: 22 V is the RMS, 31.1 V is the peak, 14 V ≈ 0.636×22 is the *full-wave* value.)

PYQ 4 (Bridge vs centre-tap). *Which of the following is NOT an advantage of the bridge rectifier over the centre-tapped full-wave rectifier?*

(a) No centre-tapped transformer is required

(b) PIV rating required per diode is half

(c) Higher transformer utilisation factor

(d) Only one diode drop occurs in the conduction path

Solution: In a bridge, **two** diodes conduct in series each half-cycle (≈ 1.4 V total drop); the centre-tap circuit has only one. So (d) is false — it is actually a *disadvantage*. (a), (b), (c) are genuine advantages. **Answer: (d)**

PYQ 5 (Colpitts — incorrect statement). *Which statement about the Colpitts oscillator is INCORRECT?*

(a) It uses a capacitive voltage divider for feedback

(b) Its frequency is $f = 1/(2\pi\sqrt{(LC_{eq})})$ with $C_{eq} = C_1C_2/(C_1+C_2)$

(c) It uses a tapped inductor for feedback

(d) It is an LC (tuned) oscillator suitable for RF generation

Solution: The tapped-**inductor** feedback belongs to the **Hartley** oscillator; Colpitts uses the tapped-**capacitor** pair C_1–C_2. Mnemonic: **C**olpitts–**C**apacitor, **H**artley–**H**enry. **Answer: (c)**

PYQ 6 (n-type majority carriers). *In an n-type semiconductor, the majority charge carriers are:*

(a) Holes (b) **Electrons** (c) Protons (d) Negative ions

Solution: Pentavalent donor atoms (P, As, Sb) contribute one free electron each → electrons are majority carriers, holes minority. The crystal remains electrically neutral. **Answer: (b)**

PYQ 7 (Ideal diode, V(t) = $\sin^2 t + \cos^2 t$). *An ideal diode is connected in series with a 1 kΩ load across a source V(t) = $\sin^2 t + \cos^2 t$ volts. The current through the load is:*

(a) Zero (b) 1 mA DC (c) 1 mA AC at 1 rad/s (d) 0.5 mA pulsating

Solution: Trigonometric identity: $\sin^2 t + \cos^2 t$ = **1** for all t → the source is a pure **1 V DC** supply. The ideal diode (zero drop) is forward biased permanently, so I = 1 V / 1 kΩ = **1 mA steady DC**; output voltage across the load = 1 V DC. **Answer: (b)**

Lesson: RRB hides a mathematics identity inside an electronics question — always simplify the source expression first.

PYQ 8 (Oscillator — false statement). *Which statement about oscillators is FALSE?*

(a) The Barkhausen criterion requires |Aβ| = 1 and total loop phase shift of 0° or 360°

(b) An oscillator needs an external AC input signal to sustain its output

(c) Oscillations start from internal noise or the switching transient

(d) If |Aβ| < 1, the oscillations die out

Solution: An oscillator is precisely a circuit that generates AC **without** any external input — positive feedback recycles a fraction of the output as its own input, with internal noise providing the seed. Statement (b) is false; (a), (c), (d) are correct. **Answer: (b)**

2.15 Practice MCQs (30)

Q1. The forbidden energy gap of silicon at room temperature is about:

(a) 0.3 eV (b) 0.72 eV (c) 1.1 eV (d) 6 eV

Q2. The barrier potential of a germanium PN junction at 25 °C is approximately:

(a) 0.7 V (b) 0.3 V (c) 1.1 V (d) 0.1 V

Q3. With every 10 °C rise in temperature, the reverse saturation current of a diode:

(a) halves (b) doubles (c) stays constant (d) becomes zero

Q4. In a p-type semiconductor, the Fermi level lies:

(a) closer to the conduction band (b) closer to the valence band (c) exactly at mid-gap (d) inside the conduction band

Q5. Zener breakdown (as distinct from avalanche) occurs in diodes that are:

(a) lightly doped (b) heavily doped with thin depletion layers (c) undoped (d) metal–semiconductor junctions

Q6. A varactor diode is operated in:

(a) forward bias (b) reverse bias (c) breakdown (d) zero bias only

Q7. The negative-resistance region in a tunnel diode lies between:

(a) zero and peak point (b) peak and valley points (c) valley point and infinity (d) it has no such region

Q8. The ripple factor of an ideal full-wave rectifier is:

(a) 1.21 (b) 0.482 (c) 0.812 (d) 1.11

Q9. For a half-wave rectifier with peak input V_m, the PIV rating of the diode must be at least:

(a) $V_m/2$ (b) V_m (c) $2V_m$ (d) πV_m

Q10. The lowest ripple frequency at the output of a bridge rectifier on 50 Hz mains is:

(a) 25 Hz (b) 50 Hz (c) 100 Hz (d) 150 Hz

Q11. A shunt-capacitor filter gives the best performance when:

(a) load current is large (b) load current is small (c) frequency is very low (d) capacitor is very small

Q12. A clamper circuit changes the:

(a) peak-to-peak value (b) waveshape (c) DC level of the waveform (d) frequency

Q13. In a BJT, the emitter region compared to base and collector is:

(a) most lightly doped (b) most heavily doped (c) largest in area (d) thinnest

Q14. If $\alpha = 0.99$, β equals:

(a) 9 (b) 49 (c) 99 (d) 100

Q15. The configuration with voltage gain less than unity but highest input impedance is:

(a) CB (b) CE (c) CC (d) all equal

Q16. For a transistor used as an amplifier, the junction bias condition is:

(a) both junctions forward (b) both reverse (c) EB forward, CB reverse (d) EB reverse, CB forward

Q17. The stability factor of a fixed-bias circuit is:

(a) 1 (b) $1 + \beta$ (c) $1/(1+\beta)$ (d) β

Q18. In a voltage-divider-biased amplifier, the emitter bypass capacitor is used to:

(a) increase DC stability (b) prevent AC degeneration and restore gain (c) block collector DC (d) reduce input impedance

Q19. The device with the highest input impedance among these is:

(a) BJT-CE (b) JFET (c) MOSFET (d) BJT-CB

Q20. Shockley's equation $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$ applies to:

(a) BJT (b) JFET (c) SCR (d) UJT

Q21. Maximum theoretical efficiency of a class-B push-pull amplifier is:

(a) 25 % (b) 50 % (c) 78.5 % (d) 100 %

Q22. Crossover distortion is associated with class:

(a) A (b) B (c) C (d) AB

Q23. Negative feedback in an amplifier:

(a) increases gain and decreases bandwidth (b) decreases gain and increases bandwidth (c) increases both (d) decreases both

Q24. An RC phase-shift oscillator using three identical RC sections needs each section to provide a phase shift of:

(a) 30° (b) 45° (c) 60° (d) 90°

Q25. The minimum amplifier gain required for a Wien bridge oscillator is:

(a) 1 (b) 3 (c) 29 (d) 10

Q26. The oscillator with the best frequency stability is:

(a) Hartley (b) Colpitts (c) RC phase-shift (d) crystal

Q27. A monostable multivibrator has:

(a) no stable state (b) one stable state (c) two stable states (d) three stable states

Q28. An SCR is a:

(a) 2-layer, 1-junction device (b) 3-layer, 2-junction device (c) 4-layer, 3-junction device (d) 5-layer, 4-junction device

Q29. The relation between latching current I_L and holding current I_H of an SCR is:

(a) $I_L = I_H$ (b) $I_L < I_H$ (c) $I_L > I_H$ (d) unrelated

Q30. In an online (double-conversion) UPS, the transfer time on mains failure is:

(a) 10 ms (b) 4 ms (c) 25 ms (d) zero

Answer Key with one-line explanations

Q	Ans	One-line reason
1	c	Si Eg ≈ 1.1 eV (Ge 0.72 eV, diamond ≈ 6 eV)
2	b	Ge barrier ≈ 0.3 V; Si ≈ 0.7 V
3	b	I_0 doubles per 10 °C rise (minority-carrier generation)
4	b	Acceptor level/holes pull the Fermi level toward the valence band
5	b	Heavy doping → thin depletion → field tunnelling (Zener), V_Z < ~5–6 V
6	b	Reverse bias varies depletion width → voltage-variable capacitance
7	b	Current falls from peak (~65 mV) to valley → negative resistance
8	b	$\gamma(FW) = \sqrt{(1.11^2 - 1)} = 0.482$; 1.21 is half-wave
9	b	HWR diode blocks only the peak V_m; 2V_m applies to centre-tap FWR
10	c	Full-wave ripple frequency = 2f = 100 Hz
11	b	$\gamma = 1/(4\sqrt{3}\, fCR_L)$: small I_dc (large R_L) → low ripple
12	c	Clamper shifts the DC level; shape and p-p value unchanged
13	b	Emitter is doped heaviest to inject carriers efficiently
14	c	$\beta = \alpha/(1-\alpha) = 0.99/0.01 = 99$
15	c	CC (emitter follower): A_v < 1, very high Z_in — buffer
16	c	Active region: EB forward, CB reverse
17	b	Fixed bias: S = 1 + β — the worst stability
18	b	Bypassing R_E removes AC negative feedback → full gain, DC stability kept
19	c	MOSFET's insulated gate: 10^{10}–10^{15} Ω
20	b	JFET square-law transfer characteristic
21	c	η_{max}(class B) = π/4 = 78.5 %
22	b	Class B dead zone near ±0.7 V; class AB cures it
23	b	$A_f = A/(1+A\beta)$; BW multiplies by (1+Aβ) — G×BW constant
24	c	3 × 60° = 180° from network + 180° from CE amplifier = 360°
25	b	Lead–lag network attenuates by 3 → gain ≥ 3

Q	Ans	One-line reason
26	d	Quartz Q ~10^4–10^6 → ppm-level stability
27	b	Monostable = one-shot: one stable + one quasi-stable state
28	c	SCR = PNPN: 4 layers, 3 junctions, 3 terminals
29	c	I_L (to latch ON) ≈ 2–3 × I_H (to stay ON)
30	d	Inverter is always in the load path → zero-break transfer

2.16 Rapid-Revision Formula Sheet

Semiconductors & diode

- Mass action: $n \cdot p = n_i^2$ $\sigma = e(n\mu_n + p\mu_p)$ Einstein: $D/\mu = V_T = kT/e \approx$ **26 mV @ 300 K**
- Diode: $I = I_0(e^{(V/\eta V_T)} - 1)$; $r_d = \eta V_T/I \approx 26$ mV/I(mA)
- Barrier: Si 0.7 V, Ge 0.3 V; falls ≈ 2 mV/°C; I_0 doubles per 10 °C
- Zener breakdown: heavy doping, $V_Z < 5$–6 V, −ve temp-coeff; Avalanche: light doping, $V_Z > 6$ V, +ve temp-coeff
- LED wavelength: λ(nm) = 1240/Eg(eV)

Rectifiers (V_m = peak input)

	HW	FW-CT	Bridge
V_{dc}	V_m/π (0.318V_m)	$2V_m/\pi$ (0.636V_m)	$2V_m/\pi$
I_{rms}	$I_m/2$	$I_m/\sqrt{2}$	$I_m/\sqrt{2}$
FF	1.57	1.11	1.11
γ	1.21	0.482	0.482
η_{max}	40.6 %	81.2 %	81.2 %
PIV	V_m	$2V_m$	V_m
TUF	0.287	0.693	0.812
f_{ripple}	f	2f	2f

- η(HW) = 0.406/(1 + r_f/R_L); η(FW) = 0.812/(1 + r_f/R_L)
- γ = $\sqrt{(FF^2 - 1)}$; C-filter: γ = $1/(4\sqrt{3}\, fCR_L)$ (FW); $V_{r(pp)} = I_{dc}/(2fC)$ (FW)

BJT

- **$I_E = I_C + I_B$**; α = I_C/I_E; β = I_C/I_B; γ = 1 + β
- **β = α/(1−α); α = β/(1+β)**; $I_{CEO} = (1+\beta)I_{CBO}$
- Load line: $V_{CE} = V_{CC} - I_C(R_C + R_E)$; $I_C(sat) = V_{CC}/(R_C+R_E)$
- $r_e' = 26$ mV/I_E(mA); CE gain $A_v = -(R_C \parallel R_L)/r_e'$
- Stability: fixed bias S = 1+β (worst); voltage-divider S ≈ 1 + R_B/R_E (best)

FET

- $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$; $g_m = g_{m0}(1 - V_{GS}/V_P)$; $g_{m0} = 2I_{DSS}/|V_P|$; $\mu = g_m r_d$

Amplifier classes

- A: 25 % (50 % transformer) — 360°; B: **78.5 %** — 180°; AB: between; C: > 90 % — < 180°
- Feedback: A_f = A/(1+Aβ); BW_f = (1+Aβ)BW; distortion ÷ (1+Aβ)

Oscillators

- Barkhausen: |Aβ| = 1, phase = 0°/360°
- RC phase-shift: f = 1/(2πRC√6), gain ≥ 29
- Wien: f = 1/(2πRC), gain ≥ 3
- Hartley: f = 1/(2π√((L₁+L₂+2M)C)) — tapped inductor
- Colpitts: f = 1/(2π√(L·C₁C₂/(C₁+C₂))) — tapped capacitor
- Clapp: f ≈ 1/(2π√(LC₃)), C₃ smallest
- Crystal: f_s = 1/(2π√(LC)); inductive between f_s and f_p; Q ~ 10^4–10^6

Multivibrators / UJT / SCR

- Astable (BJT): T = 0.693(R_1C_1 + R_2C_2); symmetric T = 1.386RC
- Monostable: T = 0.693RC; n flip-flops → MOD 2^n counter (÷2 per FF)
- UJT: V_P = ηV_BB + 0.7; T = RC ln[1/(1−η)]; η = R_B1/(R_B1+R_B2) ≈ 0.5–0.8
- SCR: I_A = I_leak/[1 − (α₁+α₂)]; latches when α₁+α₂ → 1; I_L > I_H

Triode

- **μ = g_m × r_p**; gain A = μR_L/(r_p + R_L); Child's law I_P ∝ V_P^(3/2)

Inverter / UPS

- Square-wave fundamental (full-bridge): V_1(rms) = 0.9 V_dc; odd harmonics only
- UPS transfer times: offline 4–10 ms > line-interactive 2–4 ms > **online 0 ms**
- Battery Ah = (W × hours)/(V_batt × η_inv × DoD); Watts = VA × pf

---

End of Chapter 2. Next: Chapter 3 — Digital Electronics.

Chapter 3 — Digital Electronics

RRB JE CBT-2 · Electronics & Allied Engineering (CEN 05/2025, Annexure-VII C) · Syllabus Unit 3

> **Unit coverage:** Number System & Binary codes · Boolean Algebra & Logic gates · Combinational & Sequential logic circuits · A/D & D/A converters, Counters · Memories

📊 Weightage & Trend Box

Parameter	Detail
Share of technical marks	**≈ 16 %** — the single heaviest technical unit
Questions in 22-04-2025 CBT-2 paper	**8 / 50** technical questions
Difficulty profile	Mostly formula/definition recall + 1-step numericals
Time you should budget	~45–60 s per question

Actual question themes observed in the 22-04-2025 paper:

1. Behaviour of a **priority encoder** (highest-priority input wins).
2. **XOR gate** symbol / gate-combination identification.
3. **Half-adder carry** expression (C = A·B).
4. **T flip-flop** output after 3 clock pulses with T = 1.
5. **2's complement** of 101110.
6. **EX-OR output** when both inputs are 1.
7. **Asynchronous (ripple) counter** — how flip-flops are clocked.
8. **3-to-8 decoder** — number of active outputs at a time.
9. **SRAM vs DRAM** — which needs refreshing / uses capacitor storage.

Preparation strategy: Master (i) complement arithmetic, (ii) all flip-flop truth/excitation tables, (iii) counter MOD logic, (iv) MUX/decoder/encoder behaviour, (v) ADC/DAC resolution formulas, (vi) SRAM–DRAM–ROM comparison. These six blocks alone historically cover 90 % of the questions from this unit.

3.1 Number Systems

A number system is defined by its **radix (base) r** and its digit set {0, 1, …, r−1}. Any number is a weighted sum of powers of the radix:

$N = d_n \cdot r^n + \ldots + d_1 \cdot r^1 + d_0 \cdot r^0 + d_{-1} \cdot r^{-1} + d_{-2} \cdot r^{-2} + \ldots$

System	Base r	Digits	Typical use
Binary	2	0, 1	All digital hardware
Octal	8	0–7	Compact binary (3-bit groups)
Decimal	10	0–9	Human interface
Hexadecimal	16	0–9, A–F	Compact binary (4-bit groups), addresses

With **n bits** you can represent **2^n distinct values**: unsigned range 0 to $2^n - 1$.

3.1.1 Conversions between bases

(a) Binary → Decimal — multiply each bit by its positional weight and add.

$(1\ 0\ 1\ 1\ 0\ 1)_2 = 1{\cdot}32 + 0{\cdot}16 + 1{\cdot}8 + 1{\cdot}4 + 0{\cdot}2 + 1{\cdot}1 = \mathbf{45_{10}}$

(b) Decimal → Binary — repeated division by 2 for the integer part (remainders read bottom-up); repeated multiplication by 2 for the fraction part (integer carries read top-down).

Convert 45_{10}:

```
45 ÷ 2 = 22 rem 1
22 ÷ 2 = 11 rem 0
11 ÷ 2 =  5 rem 1
 5 ÷ 2 =  2 rem 1
 2 ÷ 2 =  1 rem 0
 1 ÷ 2 =  0 rem 1   → read up: 101101₂ ✓
```

Convert 0.625_{10}: 0.625×2 = 1.25 → 1; 0.25×2 = 0.5 → 0; 0.5×2 = 1.0 → 1 ⇒ $\mathbf{0.101_2}$

(c) Binary ↔ Octal — group bits in **threes** from the radix point outward.

$101\ 110_2 \rightarrow 5\ 6 \Rightarrow \mathbf{56_8}$ | Reverse: $7\ 4_8 \rightarrow 111\ 100_2$

(d) Binary ↔ Hexadecimal — group bits in **fours**.

$1011\ 0110_2 \rightarrow B\ 6 \Rightarrow \mathbf{B6_{16}}$ | Reverse: $2F_{16} \rightarrow 0010\ 1111_2$

(e) Octal ↔ Hexadecimal — always go **via binary** (regroup 3-bit ↔ 4-bit).

Example: $375_8 = 011\ 111\ 101_2 = 1111\ 1101_2 = \mathbf{FD_{16}}$

(f) Decimal ↔ any base r — same division/multiplication method with divisor r.

Example: 250_{10} → hex: 250 ÷ 16 = 15 rem 10(A); 15 ÷ 16 = 0 rem 15(F) ⇒ $\mathbf{FA_{16}}$

✍ Worked Example 1 — Multi-base conversion

Convert 156.25_{10} to binary, octal and hexadecimal.

Integer: $156 = 128 + 16 + 8 + 4 = 10011100_2$

Fraction: 0.25 × 2 = 0.5 → 0; 0.5 × 2 = 1.0 → 1 ⇒ $.01_2$

Binary: $\mathbf{10011100.01_2}$

Octal (3-bit groups): 010 011 100 . 010 = $\mathbf{234.2_8}$

Hex (4-bit groups): 1001 1100 . 0100 = $\mathbf{9C.4_{16}}$

3.1.2 Signed number representations

For an n-bit word, three schemes represent negative numbers:

Scheme	−N formed by	Range (n bits)	Zeros	Arithmetic
Sign-magnitude	sign bit 1 + magnitude	$-(2^{n-1}-1)$ … $+(2^{n-1}-1)$	two (+0, −0)	awkward
1's complement	invert every bit	$-(2^{n-1}-1)$ … $+(2^{n-1}-1)$	two	end-around carry
2's complement	invert + add 1	**-2^{n-1} … $+(2^{n-1}-1)$**	**one**	**simple — used in all CPUs**

For 8 bits, 2's complement range = **−128 to +127**.

Finding the 2's complement quickly: starting from the LSB, **copy bits up to and including the first 1, then invert all remaining bits**.

✍ Worked Example 2 — 2's complement (2025 PYQ pattern)

Find the 2's complement of 101110.

Method 1: 1's complement = 010001; add 1 → **010010** ✓

Method 2 (shortcut): copy from right up to first 1 → "...10"; invert the rest (1011 → 0100) → **010010** ✓

3.1.3 Complement arithmetic

1's-complement subtraction (A − B): add A to the 1's complement of B; if an **end-around carry** appears, add it back to the LSB (result positive); if no carry, result is negative and in 1's-complement form.

2's-complement subtraction (A − B): add A to the 2's complement of B; **discard** any final carry (positive result); no carry ⇒ negative result in 2's-complement form.

✍ Worked Example 3 — 2's-complement subtraction

Compute $43_{10} - 25_{10}$ using 6-bit 2's-complement arithmetic.

$43 = 101011_2$, $25 = 011001_2$

2's complement of 25 = 100111_2

101011 + 100111 = 1 010010 → discard carry ⇒ **$010010_2 = 18_{10}$** ✓

Compute 25 − 43 (6-bit): 2's comp of 43 = 010101; 011001 + 010101 = 101110 (no carry ⇒ negative). Magnitude = 2's comp of 101110 = 010010 = 18 ⇒ answer **−18** ✓

✍ Worked Example 4 — Overflow detection

Add +90 and +70 in 8-bit 2's complement. Comment.

90 = 01011010, 70 = 01000110. Sum = 10100000 = −96 (wrong sign!).

Two positives yielding a negative ⇒ **overflow** (160 > +127 limit). Rule: overflow occurs when **carry into MSB ≠ carry out of MSB**.

Key facts to memorise

- r's complement = (r−1)'s complement + 1.
- 9's complement of a decimal digit d = 9 − d; 10's complement = 9's complement + 1.
- In 2's complement the MSB has weight **-2^{n-1}** (so 101110_2 as a signed 6-bit number = −32+8+4+2 = −18).

3.2 Binary Codes

A binary **code** assigns bit patterns to symbols. Two families:

- **Weighted codes** — each bit position has a fixed weight: 8421 (natural BCD), 2421, 5211, 84-2-1.
- **Non-weighted codes** — Excess-3, Gray code.

3.2.1 BCD (8421 code)

Each **decimal digit** is coded separately in 4 bits (0000–1001). Codes 1010–1111 are **invalid (6 unused states)**.

Example: 59_{10} = **0101 1001**(BCD) — note this is *not* binary 59 (111011_2).

BCD addition rule: add 4-bit groups; if a group > 1001 **or** produces a carry, **add 0110 (6)** to correct it.

✍ Worked Example 5 — BCD addition

Add 48 + 39 in BCD.

0100 1000 + 0011 1001:

Units: 1000 + 1001 = 1 0001 (carry) → add 0110 → 0111, carry 1 to tens.

Tens: 0100 + 0011 + 1 = 1000 (valid).

Result = 1000 0111 = **87** ✓

3.2.2 Excess-3 (XS-3) code

XS-3 = BCD + 0011. It is **non-weighted** and **self-complementing**: the 9's complement of a digit is obtained by simply **inverting all bits**.

Digit	BCD	XS-3
0	0000	0011
4	0100	0111
5	0101	1000
9	1001	1100

(Check: XS-3 of 4 = 0111; invert → 1000 = XS-3 of 5 = 9−4 ✓.) 2421 and 5211 are self-complementing **weighted** codes.

3.2.3 Gray code (reflected code)

A **unit-distance / cyclic** code — successive values differ in **exactly one bit**. Used in shaft encoders, K-map ordering, asynchronous interfaces (avoids transition glitches).

Binary → Gray: G(MSB) = B(MSB); $G_i = B_{i+1} \oplus B_i$.

Gray → Binary: B(MSB) = G(MSB); $B_i = B_{i+1}$(binary) $\oplus G_i$.

✍ Worked Example 6 — Gray conversions

(a) Binary 1011 → Gray: keep 1; 1⊕0=1; 0⊕1=1; 1⊕1=0 ⇒ **1110**.

(b) Gray 1110 → Binary: keep 1; 1⊕1=0 — careful, XOR previous *binary* bit with current *Gray* bit: B_3=1; B_2=1⊕1=0; B_1=0⊕1=1; B_0=1⊕0=1 ⇒ **1011** ✓ (round-trip consistent).

4-bit Gray sequence begins: 0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100, …

3.2.4 Alphanumeric codes

- **ASCII** — 7-bit code, 2^7 = **128 characters** (often stored in 8 bits with a parity/0 bit). 'A' = 41_{16} = 65_{10}, 'a' = 61_{16} = 97_{10}, '0' = 30_{16} = 48_{10}.
- **EBCDIC** — 8-bit IBM code (256 symbols).
- **Unicode/UTF-8** — modern multi-byte superset of ASCII.

3.2.5 Error detection & correction

Parity: append one bit so the total number of 1s is even (even parity) or odd (odd parity). Detects any **odd number of bit errors**; cannot correct, cannot detect double errors. A parity generator/checker is a tree of **XOR gates** (XOR of all bits = 1 ⇔ odd number of 1s).

Hamming code: k parity bits protect m data bits when **$2^k \geq m + k + 1$**. Parity bits sit at positions 1, 2, 4, 8, …; the syndrome (recomputed checks) directly gives the **position of a single-bit error**, which is then flipped — Single Error Correction. With one extra overall parity bit → SEC-DED (corrects 1, detects 2).

- For m = 4 data bits ⇒ k = 3 (the classic **Hamming (7,4)** code).
- **Hamming distance** d of a code: detects (d − 1) errors, corrects $\lfloor (d-1)/2 \rfloor$ errors.

✍ Worked Example 7 — Hamming bits

How many parity bits are needed to protect 16 data bits?

Need $2^k \geq 16 + k + 1$. Try k = 5: 32 ≥ 22 ✓ (k = 4 gives 16 ≥ 21 ✗). **Answer: 5 parity bits** (21-bit codeword).

3.3 Boolean Algebra

Boolean algebra (George Boole, 1854; applied to switching by Claude Shannon, 1938) manipulates variables that take only values **0 and 1** with operations AND (·), OR (+), NOT ($\bar{}$).

3.3.1 Postulates and theorems

#	Law	OR form	AND form
1	Identity	$A + 0 = A$	$A \cdot 1 = A$
2	Null (domination)	$A + 1 = 1$	$A \cdot 0 = 0$
3	Idempotent	$A + A = A$	$A \cdot A = A$
4	Complement	$A + \bar{A} = 1$	$A \cdot \bar{A} = 0$
5	Involution	$(\bar{A})\bar{} = A$	—
6	Commutative	$A + B = B + A$	$AB = BA$
7	Associative	$(A+B)+C = A+(B+C)$	$(AB)C = A(BC)$
8	Distributive	$A(B + C) = AB + AC$	**$A + BC = (A+B)(A+C)$**
9	Absorption	$A + AB = A$	$A(A + B) = A$
10	Redundancy	$A + \bar{A}B = A + B$	$A(\bar{A} + B) = AB$
11	Consensus	$AB + \bar{A}C + BC = AB + \bar{A}C$	$(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

De Morgan's theorems (the exam favourite):

- $(A + B)\bar{} = \bar{A} \cdot \bar{B}$ — *complement of a sum = product of complements*
- $(A \cdot B)\bar{} = \bar{A} + \bar{B}$ — *complement of a product = sum of complements*

Generalises to any number of variables. Hardware meaning: **NOR = bubbled AND, NAND = bubbled OR**.

Duality principle: in any valid identity, swapping (+ ↔ ·) and (0 ↔ 1) — leaving variables unchanged — yields another valid identity. (The dual of $A + \bar{A}B = A + B$ is $A(\bar{A} + B) = AB$.) The **complement** of a function is found by taking the dual **and** complementing every literal.

✍ Worked Example 8 — Simplification

Simplify $F = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}$.

$= \bar{A}C(\bar{B} + B) + A\bar{B} = \bar{A}C + A\bar{B}$. **$F = \bar{A}C + A\bar{B}$** (3 literals fewer; verify with a truth table if unsure).

3.3.2 Standard forms — SOP, POS, minterms, maxterms

- **Minterm m_i** — an AND term containing **every** variable once (true for exactly one input row). For (A,B,C), $m_5 = A\,\bar{B}\,C$ (101).
- **Maxterm M_i** — an OR term containing every variable once (false for exactly one row). $M_5 = \bar{A} + B + \bar{C}$.
- Relationship: **$M_i = \bar{m}_i$**.
- **Canonical SOP:** F = Σm(list of rows where F = 1). **Canonical POS:** F = ΠM(rows where F = 0). The two lists are complementary: for n variables, Σ-list ∪ Π-list = {0 … 2^n-1}.

Example: F(A,B,C) = Σm(1, 3, 5, 7) = C (all odd rows have C = 1); equivalently F = ΠM(0, 2, 4, 6).

Any function of n variables is one of **$2^{(2^n)}$** possible functions (n = 2 → 16 functions).

3.4 Karnaugh Maps (K-maps)

A K-map is a truth table redrawn so that **adjacent cells differ in one variable** (Gray-code ordering: 00, 01, 11, 10). Grouping adjacent 1s in powers of two (1, 2, 4, 8, …) eliminates the variables that change within the group.

Rules

1. Groups must be rectangles of size 2^k.
2. The map is a **torus** — edges and corners wrap around (the four corner cells of a 4-variable map are adjacent).
3. Make groups **as large as possible**, use **as few groups as possible**; every 1 must be covered; overlap is allowed.
4. A group of 2^k cells in an n-variable map gives a product term of **n − k literals**.
5. **Don't-care (×)** cells may be treated as 1 *or* 0 — include them only when they enlarge a group.
6. Grouping 0s instead gives the minimal **POS** (write the complement, then apply De Morgan).

✍ Worked Example 9 — 4-variable K-map

Minimise F(A,B,C,D) = Σm(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14).

Map (rows AB, columns CD, Gray order 00-01-11-10):

AB\CD	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	1	1	0	1
10	1	1	0	0

Groups (all cells listed are 1s in the map):

1. **Octet** — columns CD = 00 and CD = 01 (all 8 cells: m0, m1, m4, m5, m12, m13, m8, m9) → variables A, B, D drop out ⇒ term $\bar{C}$.
2. **Quad** — rows AB = 01, 11 × columns CD = 00, 10 (m4, m6, m12, m14) → term $B\bar{D}$. This is what covers m6 and m14 (the C = 1, D = 0 cells of rows 01 and 11).
3. **Quad** — rows AB = 00, 01 × columns CD = 00, 10 (m0, m2, m4, m6) → term $\bar{A}\bar{D}$. This covers the remaining 1 at m2.

Every 1 is now covered (m10 stays 0 and is in no group).

$F = \bar{C} + B\bar{D} + \bar{A}\bar{D}$ — minimal SOP: 3 terms, 5 literals.

✍ Worked Example 10 — Don't-cares (BCD application)

F(A,B,C,D) = Σm(1, 3, 5, 7, 9) + d(10, 11, 12, 13, 14, 15). Minimise.

Map: 1s at all odd minterms 1–9; don't-cares fill the entire invalid-BCD region 10–15.

- Group all cells with D = 1: m1, m3, m5, m7, m9 plus d11, d13, d15 → the full **D column-pair (8 cells)** → term **D**.

F = D — a single literal. (This is exactly the "BCD digit is odd" detector: a BCD number is odd iff its LSB is 1.)

3.5 Logic Gates

3.5.1 The basic and derived gates

Gate	Symbolic expression	Output = 1 when	Truth table (A B → Y)
NOT	$Y = \bar{A}$	A = 0	0→1, 1→0
AND	$Y = A \cdot B$	all inputs 1	00→0, 01→0, 10→0, 11→**1**
OR	$Y = A + B$	any input 1	00→**0**, 01→1, 10→1, 11→1
NAND	$Y = \overline{(AB)}$	any input 0	00→1, 01→1, 10→1, 11→**0**
NOR	$Y = \overline{(A+B)}$	all inputs 0	00→**1**, 01→0, 10→0, 11→0
XOR	$Y = A \oplus B = \bar{A}B + A\bar{B}$	inputs **differ**	00→0, 01→1, 10→1, **11→0**
XNOR	$Y = \overline{(A \oplus B)} = AB + \bar{A}\bar{B}$	inputs **equal**	00→1, 01→0, 10→0, 11→1

XOR properties (exam-critical):

- $A \oplus 0 = A$ (buffer); $A \oplus 1 = \bar{A}$ (controlled inverter); $A \oplus A = 0$; $A \oplus \bar{A} = 1$.
- Both inputs 1 ⇒ output **0** (2025 PYQ).
- Multi-input XOR = 1 when the number of 1-inputs is **odd** → parity element.
- XOR is associative & commutative; used in adders, comparators, Gray converters, parity circuits.
- XNOR is the **equality/coincidence** gate.

Symbols: AND = D-shape; OR = shield/curved shape; XOR = OR with an **extra curved line** on the input side; a **bubble** on any terminal = inversion. (2025 paper asked to identify the XOR symbol among combinations.)

3.5.2 Universal gates — NAND & NOR

NAND and NOR are **universal**: each alone can realise every Boolean function.

All gates from NAND:

Target	NAND realisation	Count
NOT	A NAND A	1
AND	(A NAND B) then NOT	2
OR	(A NAND A) NAND (B NAND B) — De Morgan	3
NOR	OR then NOT	4
XOR	standard 4-gate network: Y = A NAND (A NAND B), B NAND (A NAND B), then NAND together	**4**
XNOR	XOR + inverter	5

All gates from NOR:

Target	NOR realisation	Count
NOT	A NOR A	1
OR	(A NOR B) then NOT	2
AND	(A NOR A) NOR (B NOR B)	3
NAND	AND then NOT	4
XNOR	4-gate NOR network	4
XOR	XNOR + inverter	5

Bubbled-gate (De Morgan) equivalences — remember as pictures:

- **Bubbled-input AND ≡ NOR** ($\bar{A}\cdot\bar{B} = \overline{(A+B)}$)
- **Bubbled-input OR ≡ NAND** ($\bar{A}+\bar{B} = \overline{(AB)}$)
- Bubbled-input NAND ≡ OR; bubbled-input NOR ≡ AND.
- Two cascaded inverting bubbles cancel — the basis of **NAND-NAND = AND-OR (SOP)** and **NOR-NOR = OR-AND (POS)** two-level realisations.

3.5.3 Common 7400-series IC numbers (frequent one-mark questions)

IC	Function	IC	Function
7400	Quad 2-input **NAND**	7447	BCD → 7-segment decoder/driver (common-anode)
7402	Quad 2-input **NOR**	7474	Dual **D flip-flop** (+ve edge)
7404	Hex **inverter** (NOT)	7476	Dual **JK flip-flop**
7408	Quad 2-input **AND**	7483	4-bit **binary full adder**
7432	Quad 2-input **OR**	7485	4-bit magnitude **comparator**
7486	Quad 2-input **XOR**	7490	**Decade counter** (mod-10)
7410	Triple 3-input NAND	7493	4-bit **ripple counter** (mod-16)
74138	**3-to-8 decoder**	74151	**8:1 MUX**
74147	Decimal **priority encoder** (10-to-4)	74148	Octal **priority encoder** (8-to-3)
74194	4-bit **universal shift register**	555	Timer (clock source; not TTL logic)

3.5.4 Logic families — TTL, CMOS, ECL

Parameter	TTL (74xx)	CMOS (40xx/74HC)	ECL (10K)
Basic element	Bipolar (multi-emitter BJT)	Complementary MOSFET pair	BJT differential pair (non-saturating)
Supply	+5 V fixed	3–15 V (4000 series)	−5.2 V
Propagation delay	~10 ns (74LS)	~50 ns (4000) / ~10 ns (74HC)	**~1–2 ns (fastest)**
Static power/gate	~10 mW (74) / 2 mW (LS)	**~nW–µW (lowest static)**	~25–50 mW (highest)
Fan-out	~10	**≥ 50** (very high, capacitive-limited)	~25
Noise margin	~0.4 V	**~30–45 % of V_DD (best)**	~0.2–0.3 V (worst)
Noise immunity	moderate	**highest**	lowest
Logic swing	0.2 V–3.4 V approx.	rail-to-rail	small (~0.8 V)
Saturation?	Transistors saturate	—	**Never saturates → speed**
Remark	Rugged workhorse	Power-critical & VLSI standard	Supercomputers, RF prescalers

TTL levels (5 V): $V_{IL(max)} = 0.8$ V, $V_{IH(min)} = 2.0$ V, $V_{OL(max)} = 0.4$ V, $V_{OH(min)} = 2.4$ V ⇒ noise margins $NM_L = NM_H = 0.4$ V.

Other memorables:

- **Figure of merit = speed–power product** (pJ); lower is better. 74LS ≈ 2 mW × 10 ns = 20 pJ.
- CMOS dynamic power = $C \cdot V^2 \cdot f$ — rises with frequency; at high f CMOS can exceed TTL power.
- **Fan-in** = number of inputs a gate can accept; **fan-out** = number of standard loads an output can drive.
- Unused CMOS inputs must **never float** (tie to rail); floating TTL inputs read as logic 1 (bad practice but common in questions).
- **Totem-pole outputs must not be wire-ANDed**; use **open-collector** (needs external pull-up; allows wired-AND) or **tri-state** (0, 1, Hi-Z; allows bus sharing).

3.6 Combinational Logic Circuits

Output depends **only on present inputs** — no memory, no feedback, no clock. Design flow: truth table → K-map minimisation → gate realisation.


3.6.1 Half adder (HA)

Adds two bits A, B → Sum S, Carry C.

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$S = A \oplus B$ $C = A \cdot B$ (2025 PYQ: carry = AND of inputs). Hardware: **1 XOR + 1 AND**.

3.6.2 Full adder (FA)

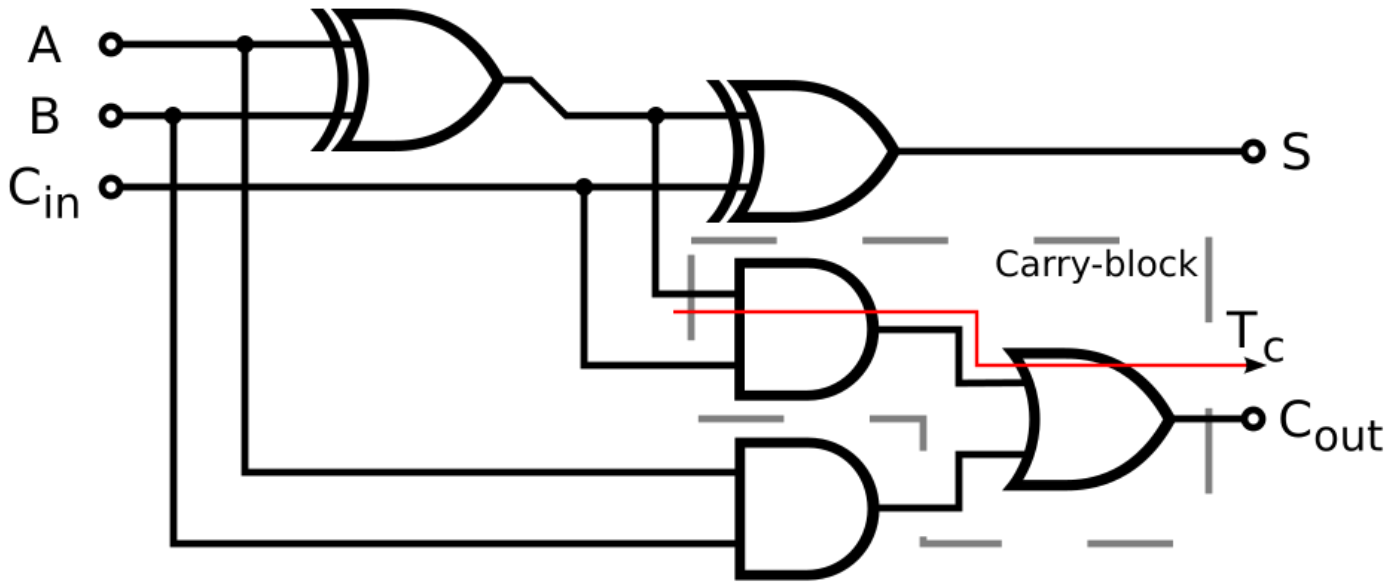

Full-adder logic diagram.

Adds A, B and carry-in Cin → S, Cout.

S = A ⊕ B ⊕ Cin Cout = AB + Cin(A ⊕ B) = AB + BCin + ACin (majority function)

- Built from **2 half adders + 1 OR gate**.
- A full adder needs **min. 2-level logic**; sum is odd-parity of the three inputs.

3.6.3 Half & full subtractor

Circuit	Difference	Borrow
Half subtractor (A − B)	D = A ⊕ B	B_out = **$\bar{A}\cdot B$**
Full subtractor (A − B − Bin)	D = A ⊕ B ⊕ Bin	B_out = $\bar{A}B$ + Bin$\overline{(A \oplus B)}$ = $\bar{A}B$ + $\bar{A}$Bin + B·Bin

Note the symmetry: subtractor = adder with the minuend **complemented in the borrow term**. In practice subtraction is done by **adding the 2's complement** (adder + XOR-controlled inverters + Cin = 1 → a single adder/subtractor unit with mode line M: B-inputs pass through XOR gates with M; M = 0 add, M = 1 subtract).

3.6.4 Parallel (ripple-carry) adder & look-ahead

- **n-bit ripple-carry adder** = n full adders, carry ripples; worst-case delay ∝ n (≈ 2n gate delays).
- **Carry-look-ahead (CLA)** computes all carries in parallel using generate **$G_i = A_iB_i$** and propagate **$P_i = A_i \oplus B_i$**: $C_{i+1} = G_i + P_iC_i$ expanded — delay becomes ~constant (4 gate levels). IC 7483 is a 4-bit adder with internal look-ahead.

3.6.5 Magnitude comparator

Compares two n-bit words → three outputs A>B, A=B, A<B.

- 1-bit: (A>B) = $A\bar{B}$; (A<B) = $\bar{A}B$; (A=B) = $A \odot B$ (XNOR).
- n-bit equality = AND of all bitwise XNORs.
- **IC 7485** = 4-bit comparator, cascadable via expansion inputs.

3.6.6 Multiplexer (MUX) — "many to one"

A 2^n:1 MUX has 2^n data inputs, **n select lines**, 1 output: Y = D_s (the selected input). It is a digitally controlled switch / **data selector**; also called a universal logic element.

- 2:1 MUX: $Y = \bar{S} \cdot D_0 + S \cdot D_1$.
- 4:1 MUX: $Y = \bar{S}_1\bar{S}_0D_0 + \bar{S}_1S_0D_1 + S_1\bar{S}_0D_2 + S_1S_0D_3$.
- 8:1 MUX = IC 74151. Larger MUX from smaller: an 8:1 needs two 4:1 + one 2:1 (or a tree).
- Number of select lines for an N:1 MUX = $\mathbf{\log_2 N}$.

Implementing any n-variable function with a 2^n:1 MUX: connect the n variables to the select lines and hard-wire each data input D_i to the function value (0/1) of minterm i.

Better — 2^{n-1}:1 MUX method: use n−1 variables as selects; each data input then gets one of {0, 1, remaining variable, its complement} read off the folded truth table.

✍ Worked Example 11 — Function on a 4:1 MUX

Implement F(A,B,C) = Σm(1, 2, 6, 7) using a 4:1 MUX with A, B as select lines (S_1 = A, S_0 = B).

Partition minterms by AB:

AB	minterms present	C-column	D_i
00	m1 (C=1) ✓, m0 ✗	F = C	**$D_0 = C$**
01	m2 (C=0) ✓, m3 ✗	F = $\bar{C}$	**$D_1 = \bar{C}$**
10	none (m4, m5 absent)	F = 0	**$D_2 = 0$**
11	m6, m7 both ✓	F = 1	**$D_3 = 1$**

One 4:1 MUX + one inverter realises F. ✓

3.6.7 Demultiplexer (DEMUX) — "one to many"

1 input, n select lines, 2^n outputs; input is routed to the selected output, all others 0. A **DEMUX = decoder with an enable used as the data input**. 1:8 DEMUX ≡ 3-to-8 decoder (74138) with data on $\bar{E}$.

3.6.8 Decoder

An **n-to-2^n decoder** activates **exactly one** output line — the one whose index equals the binary input (2025 PYQ: a 3-to-8 decoder has **only 1 active output at any time**; the other 7 stay inactive). Active-low versions (74138) pull the selected line LOW.

- 2-to-4: 4 AND gates, outputs = the 4 minterms of (A, B).
- **3-to-8 (74138):** outputs = all 8 minterms; has enables (G1, $\bar{G}$2A, $\bar{G}$2B) for cascading — two 74138s + inverter = 4-to-16 decoder.
- **Decoder + OR gates implements any function** (OR the required minterm outputs) — this is how ROMs work.
- **BCD-to-7-segment** (7447/7448) is a code-converter decoder.

3.6.9 Encoder & priority encoder

Encoder = inverse of decoder: 2^n inputs → n-bit binary code of the active input. Simple encoders fail if **two inputs are active simultaneously** (outputs OR together, giving a wrong code) and cannot distinguish "input 0 active" from "no input".

Priority encoder fixes this: when several inputs are active, the output encodes the **highest-priority (highest-numbered) active input**; lower inputs are ignored (2025 PYQ). A **valid/GS output** flags that at least one input is active.

- 74148 = 8-to-3 priority encoder; 74147 = decimal (10-to-4, BCD out) priority encoder.
- Example: inputs I_6 and I_3 both high on a 74148-type encoder → output = **110 (6)**.

3.6.10 Code converters & parity circuits

- **Binary → Gray:** MSB straight, then chain of XORs ($G_i = B_{i+1} \oplus B_i$) — n-bit needs **n−1 XOR gates**.
- **Gray → Binary:** cascaded XORs with feedback of computed binary bits (n−1 XORs, but ripple delay).
- **BCD ↔ XS-3:** add/subtract 0011 with a 4-bit adder or direct K-map design.
- **Even-parity generator** for n bits: XOR tree of all n bits; **checker:** XOR of (n data + parity) — output 1 ⇒ error (odd count).

3.7 Sequential Logic Circuits

Output depends on present inputs **and past history** — the circuit has **memory** (feedback). Classes:

- **Asynchronous** (level/unclocked — latches, ripple counters) vs **Synchronous** (clock-controlled — flip-flops, synchronous counters, registers).

3.7.1 Latch vs flip-flop; triggering

Feature	Latch	Flip-flop
Sensitivity	**Level**-sensitive (transparent while enable active)	**Edge**-triggered (samples only at clock edge)
Clock	Optional enable	Required
Race problems	Transparent — glitches pass	Immune between edges
Example	SR latch (NOR/NAND), gated D latch	7474 D-FF, 7476 JK-FF

Triggering types: positive (rising) edge ↑, negative (falling) edge ↓ (bubble on the clock pin), pulse-triggered (master–slave).
Asynchronous inputs PRESET (Q→1) and CLEAR (Q→0) override the clock.

3.7.2 SR latch / SR flip-flop


NOR-based SR latch (active-high S, R):

S	R	Q(next)	State
0	0	Q (hold)	Memory
0	1	0	Reset
1	0	1	Set
1	1	**Invalid** (Q = $\bar{Q}$ = 0; race on release)	Forbidden

NAND-based ($\bar{S}\bar{R}$) latch is active-low: 11 = hold, **00 = invalid**.

Characteristic equation: $\mathbf{Q^+ = S + \bar{R}Q}$ (with SR = 0 constraint).

3.7.3 JK flip-flop

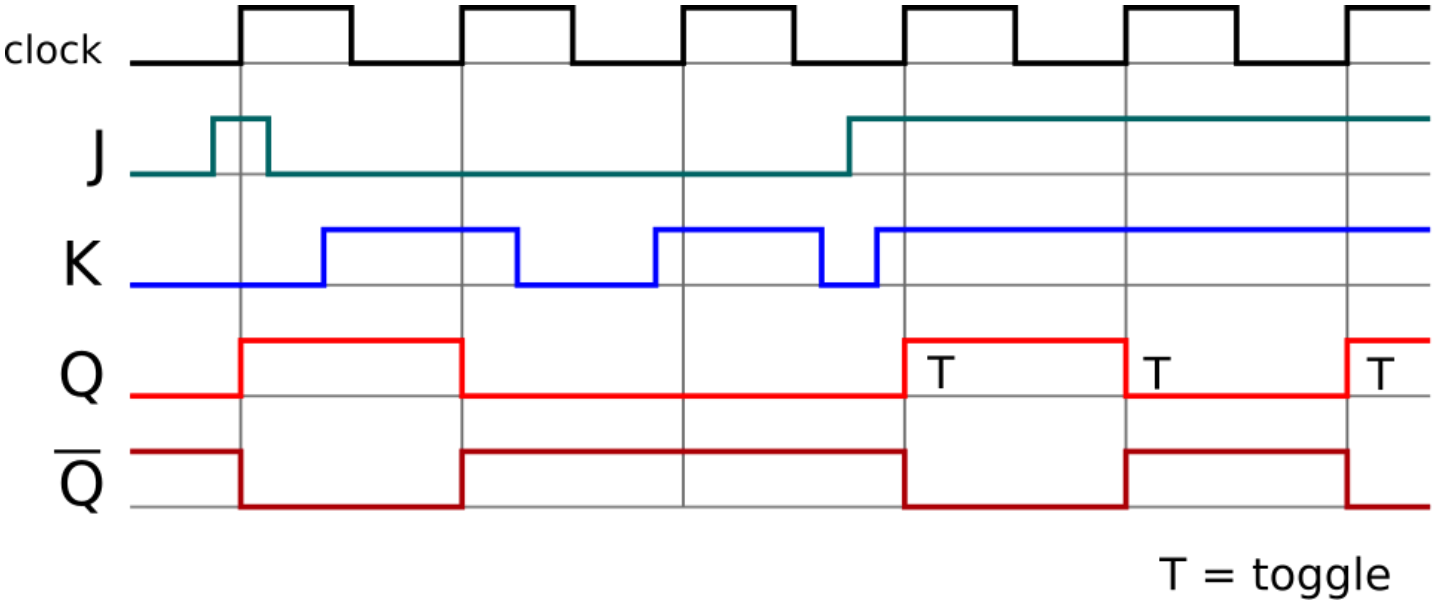

JK flip-flop timing diagram.

Removes the SR forbidden state: J=K=1 **toggles**.

J	K	Q^+	Action
0	0	Q	Hold
0	1	0	Reset
1	0	1	Set
1	1	$\bar{Q}$	Toggle

Characteristic equation: $\mathbf{Q^+ = J\bar{Q} + \bar{K}Q}$.

Race-around condition: in a level-clocked JK with J=K=1, if clock pulse-width t_p > propagation delay t_pd, the output toggles repeatedly during one pulse — final state unpredictable. **Cures:** (i) make t_p < t_pd (impractical), (ii) **edge triggering**, (iii) **master–slave JK**: master latch accepts data while CLK = 1, slave copies it when CLK = 0 → exactly one toggle per pulse ("pulse-triggered"; data changes appear at output on the falling edge). Master–slave JKs can still suffer *ones-catching*; modern parts are pure edge-triggered.

3.7.4 D (data/delay) flip-flop

$Q^+ = \mathbf{D}$ — output follows D at each clock edge (one-clock delay). Built from JK with **$J = D, K = \bar{D}$**, or SR with S = D, R = $\bar{D}$. Used in registers, pipelines, synchronisers. A **gated D latch** (74LS75) is the level-sensitive cousin.

3.7.5 T (toggle) flip-flop

$Q^+ = \mathbf{T \oplus Q}$.

T	Action
0	Hold ($Q^+ = Q$)
1	**Toggle** ($Q^+ = \bar{Q}$)

Built from JK with **$J = K = T$**, or from D with $D = T \oplus Q$. With T = 1 the output is a square wave at **$f_{clk} / 2$** — the frequency-divider element of every binary counter.

2025 PYQ logic: T = 1, $Q_0 = 0$. After clock 1 → Q = 1; clock 2 → Q = 0; clock 3 → **Q = 1** (odd number of toggles inverts the initial state).

3.7.6 Truth (characteristic) & excitation tables — memorise cold

Characteristic equations

FF	Q^+
SR	$S + \bar{R}Q$ ($SR = 0$)
JK	$J\bar{Q} + \bar{K}Q$
D	D
T	$T \oplus Q$

Excitation tables (what inputs produce a desired $Q \rightarrow Q^+$ transition; × = don't care):

$Q \rightarrow Q^+$	S R	J K	D	T
0 → 0	0 ×	0 ×	0	0
0 → 1	1 0	1 ×	1	1
1 → 0	0 1	× 1	0	1
1 → 1	× 0	× 0	1	0

3.7.7 Flip-flop conversions (design with excitation tables)


From → To	Required input logic
JK → D	$J = D,\ K = \bar{D}$
JK → T	$J = K = T$
JK → SR	$J = S,\ K = R$
D → T	$D = T \oplus Q$
D → JK	$D = J\bar{Q} + \bar{K}Q$
T → D	$T = D \oplus Q$
T → JK	$T = J\bar{Q} + KQ$
SR → JK	$S = J\bar{Q},\ R = KQ$
SR → D	$S = D,\ R = \bar{D}$
SR → T	$S = T\bar{Q},\ R = TQ$

Method (works for any pair): write target FF's truth table → for each row use the *source* FF's excitation table → K-map the source inputs.

3.8 Counters

A counter is a register that steps through a fixed sequence of states on clock pulses. **MOD number = number of distinct states**. With n flip-flops, MOD ≤ 2^n, and the required n for MOD-N is **$n = \lceil \log_2 N \rceil$**.

3.8.1 Asynchronous (ripple) counter

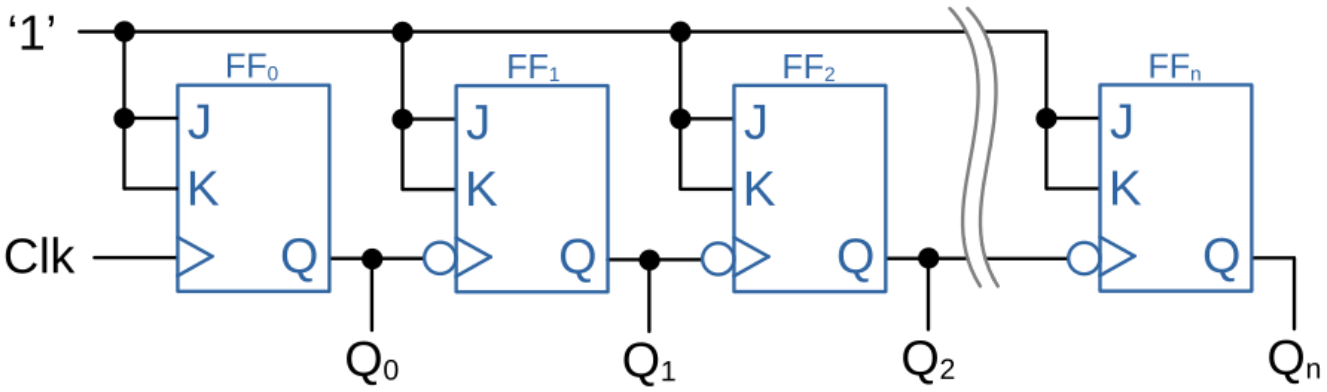

Asynchronous (ripple) counter using JK flip-flops.

- **Only the first flip-flop receives the external clock; each subsequent FF is clocked by the output of the previous stage** (2025 PYQ — this is the defining feature).
- All FFs in toggle mode (T = 1 or JK with J = K = 1).
- **Up counter:** negative-edge FFs clocked from **Q** of the previous stage (or +ve edge from $\bar{Q}$).
- **Down counter:** clock from **$\bar{Q}$** (with −ve edge FFs) — or read outputs from $\bar{Q}$ of an up counter.
- Each stage divides frequency by 2: after n stages, **$f_{out} = f_{in} / 2^n$**.

- **Drawback — ripple delay:** total settling time = n·t_pd; decoded outputs glitch; maximum clock frequency **f_max = 1 / (n·t_pd)**.

Mod-N ripple counter (e.g. decade/7490): detect the first unwanted count with a NAND gate and drive asynchronous CLEAR. Decade (mod-10) counter: NAND of Q_3 and Q_1 fires at count 1010 → resets to 0000 → counts 0–9. Cascading a mod-10 and a mod-6 gives mod-60 (digital clocks).

✍ Worked Example 12 — Ripple counter speed & state

(a) A 4-bit ripple counter uses FFs with t_pd = 25 ns. Maximum clock frequency?

f_max = 1/(n·t_pd) = 1/(4 × 25 ns) = **10 MHz**.

(b) Starting from 0000, what does the counter read after 75 input pulses?

75 mod 16 = 11 → **1011_2**.

(c) Frequency at the MSB output for a 1 MHz clock? 1 MHz / 2^4 = **62.5 kHz**.

3.8.2 Synchronous counters

All flip-flops share the common clock; combinational logic on J/K (or T) inputs decides which FFs toggle. Standard binary up-counter condition: stage i toggles when **all lower stages are 1**: $T_0 = 1$, $T_1 = Q_0$, $T_2 = Q_0Q_1$, $T_3 = Q_0Q_1Q_2$.

- No cumulative delay → **f_max = 1/(t_pd + t_gate)** regardless of length; glitch-free decoding.
- Design procedure for arbitrary sequences: state diagram → state table → excitation table → K-maps → logic. Unused states must be checked for **lock-out** (design them to re-enter the main sequence = self-correcting counter).
- **Up/down counter:** mode input selects whether stage enables come from Q (up) or $\bar{Q}$ (down) — IC 74192/74193.

3.8.3 Ring counter

An n-bit shift register with **Q of the last stage fed back to D of the first**, initialised with a single 1 (e.g. 1000).

- **MOD = n** (n states) — one FF per state, outputs are already decoded (one-hot).
- Sequence for n = 4: 1000 → 0100 → 0010 → 0001 → 1000 …
- Output frequency of each Q = f_clk / n; duty cycle 1/n.

3.8.4 Johnson (twisted-ring / switch-tail) counter

Feedback taken from **$\bar{Q}$ of the last stage** to D of the first.

- **MOD = 2n** with n flip-flops.
- n = 4 sequence: 0000 → 1000 → 1100 → 1110 → 1111 → 0111 → 0011 → 0001 → repeat (8 states).
- Decoding any state needs only a **2-input AND gate**; used for quadrature/multi-phase clocks. Must be protected against the 2^n − 2n unused states.

3.8.5 Counter summary table

Counter (n FFs)	Clocking	MOD	Max freq	Decoding
Ripple (binary)	serial (Q → next CLK)	2^n	1/(n·t_pd) — slowest	glitchy
Synchronous binary	common clock	2^n	1/(t_pd + t_gate) — fast	clean
Ring	common clock (shift)	**n**	fast	none needed (one-hot)
Johnson	common clock (shift)	**2n**	fast	2-input gate

MOD-count quick answers: 3 FF ripple → MOD-8, ÷8 frequency. MOD-10 (decade) needs 4 FFs. MOD-60 = MOD-10 × MOD-6. To divide a clock by 32 → 5 T-FFs in ripple.

3.9 Shift Registers

A cascade of D flip-flops sharing a clock; data moves one stage per clock.

Type	Load	Read	Clocks to move n bits in / out
SISO	serial	serial	n in, n out (n-clock delay line)
SIPO	serial	parallel	n in, 0 (instant read)
PISO	parallel (1 clk)	serial	1 in, n out — parallel→serial converter
PIPO	parallel	parallel	1 and 1 — storage register

- **Universal shift register (74194/74195):** mode controls S_1S_0 select hold / shift-right / shift-left / parallel-load.
- Applications: serial↔parallel conversion, delay lines (SISO delay = n/f_clk), multiplication/division by 2 (left/right shift), ring & Johnson counters, PRBS generators (LFSR).
- Time to fully load an 8-bit SISO register at 1 MHz = 8 µs.

3.10 D/A Converters (DAC)

A DAC converts an n-bit digital word D into an analog output $V_{out} = K \cdot V_{ref} \cdot (D/2^n)$.

Key formulas

- **Resolution (step size) = $V_{FS} / (2^n - 1)$** volts per LSB (V_{FS} = full-scale output). As a fraction/percentage: $1/(2^n - 1) \times 100$ %.
- Number of levels = 2^n; number of steps = $2^n - 1$.
- Analog output for input code D: **$V_{out} = D \times$ step size**.
- Specs: resolution, accuracy, linearity (±½ LSB), monotonicity, settling time, glitch energy.

3.10.1 Weighted-resistor DAC

A summing op-amp whose input resistors are **binary-weighted**: the MSB uses R, the next bit 2R, then 4R, 8R, … (bit of weight 2^i gets resistance halved relative to the next lower bit, so its current is doubled). Output $V_o = -R_f \cdot \Sigma\ (b_i \cdot V_{ref} / R_i)$, i.e. each 1-bit injects a current proportional to its binary weight.

Drawback: an n-bit DAC needs a resistor spread of $2^{n-1} : 1$ (8-bit → 128:1) with matched precision — impractical beyond ~6 bits.

3.10.2 R-2R ladder DAC

Uses **only two resistor values (R and 2R)** regardless of word length — easy to fabricate and match; the industry standard.

$V_{out} = V_{ref} \times D / 2^n$ (inverted-ladder form, unity gain), where D = decimal value of the input word. Each node of the ladder divides by 2 (Thevenin resistance looking into any node = R).

✍ Worked Example 13 — DAC numericals

(a) A 4-bit R-2R DAC has V_{ref} = 16 V. Output for input 1011?

$V_{out} = 16 \times 11/2^4 = 16 \times 11/16 =$ **11 V**.

(b) An 8-bit DAC has full-scale 10 V. Resolution?

Step = $10/(2^8 - 1) = 10/255 =$ **39.2 mV**; % resolution = 1/255 = **0.392 %**.

(c) How many bits for a resolution better than 5 mV on a 10 V range?

$10/(2^n - 1) \le 5$ mV → $2^n - 1 \ge 2000$ → n = 11 (2047 ✓). **11 bits**.

3.11 A/D Converters (ADC)

An ADC samples an analog voltage and outputs an n-bit code. Two-step process: **sample-and-hold**, then **quantise + encode**.

Key formulas

- **Resolution = $V_{FS} / 2^n$** (quantum Q); **quantisation error = ±½ LSB = Q/2** max.
- Dynamic range ≈ 6.02 n dB; SNR (ideal) = 6.02 n + 1.76 dB.
- Nyquist: $f_{sample} \ge 2 f_{max(signal)}$.

3.11.1 Flash (parallel/simultaneous) ADC

- **$2^n - 1$ comparators** + resistor ladder + priority encoder.
- **Fastest** ADC (one comparator delay, ~ns) — video/oscilloscope use.
- Hardware doubles per extra bit → practical only to ~8–10 bits. (3-bit flash → 7 comparators; 8-bit → 255.)

3.11.2 Counter (ramp) ADC

Counter drives a DAC; comparator stops the count when $V_{DAC} \ge V_{in}$.

- Simple; conversion time **variable, up to $2^n - 1$ clocks** (worst case) → slow.
- Tracking (up/down) ADC is the continuous version.

3.11.3 Successive-approximation ADC (SAR)

Binary search: SAR sets each bit MSB→LSB, DAC output compared with V_{in}, bit kept or cleared.

- **Conversion time = n clock cycles — fixed, independent of V_in.**
- Best speed/complexity/cost trade-off → the most widely used general-purpose ADC (8–16 bits). Needs S/H at input.

3.11.4 Dual-slope (integrating) ADC

Integrate V_in for fixed time T_1, then de-integrate with −V_ref and count time T_2: **$V_{in} = V_{ref} \cdot T_2/T_1$** (counts ∝ V_in).

- **Highest accuracy & noise rejection** — errors in R, C, clock cancel (ratiometric).
- Choosing T_1 = k/50 Hz rejects mains hum (excellent NMR).
- Very **slow** (ms) → digital multimeters, panel meters.

3.11.5 ADC comparison table

Type	Conversion time	Hardware	Accuracy	Typical use
Flash	~1 comparator delay (fastest)	2^n-1 comparators (huge)	moderate	video, DSO
SAR	n clocks (fixed)	1 DAC + SAR (moderate)	good	data acquisition, µC
Counter/ramp	≤ 2^n-1 clocks (variable)	minimal	moderate	cheap/slow apps
Dual-slope	2 integration periods (slowest)	integrator + counter	**best**	DMM, instrumentation

✍ Worked Example 14 — ADC numericals

(a) A 10-bit ADC spans 0–10 V. Resolution and max quantisation error?

Q = $10/2^{10}$ = 10/1024 = **9.77 mV**; error = ±Q/2 = **±4.88 mV**.

(b) An 8-bit SAR ADC uses a 1 MHz clock. Conversion time?

t = n/f = 8 × 1 µs = **8 µs** (same for every input voltage).

(c) Comparators in a 6-bit flash ADC? $2^6 - 1$ = **63**.

(d) A 12-bit counter ADC with 1 MHz clock — worst-case conversion time?

($2^{12} - 1$) × 1 µs = 4095 µs ≈ **4.1 ms**.

3.12 Memories

A memory stores binary words. Organisation **M × N** = M words (addresses) × N bits per word; address lines k where **$2^k = M$**; capacity = M × N bits.

3.12.1 Classification

```
Semiconductor memory
├── Volatile — RAM (read/write; loses data at power-off)
│   ├── SRAM  (static)
│   └── DRAM  (dynamic)
└── Non-volatile — ROM family (retains data)
    ├── Mask ROM  (factory-programmed)
    ├── PROM      (one-time, fuse-blown)
    ├── EPROM     (erase: UV light, whole chip; quartz window)
    ├── EEPROM    (erase: electrical, byte-wise)
    └── Flash     (electrical, block/sector-wise; SSDs, pen drives)
```

3.12.2 SRAM vs DRAM (2025 PYQ)

Parameter	SRAM	DRAM
Storage element	**Cross-coupled latch (6 transistors)**	**1 transistor + 1 capacitor**
Refresh needed?	**No** — data held while powered	**Yes** — capacitor leaks; refresh every ~2–64 ms
Speed	Faster (sub-10 ns access)	Slower
Density / cost per bit	Low density, expensive	**High density, cheap**
Power (standby)	Lower	Higher (refresh)
Interface	Simple	Multiplexed row/column address (RAS/CAS)
Use	**Cache memory**, registers	**Main memory**

Both are **volatile**. Exam one-liners: "*Which memory must be refreshed periodically?*" → *DRAM*. "*Which stores data in a capacitor?*" → *DRAM*. "*Which is used for cache?*" → *SRAM*.

3.12.3 ROM family details

Type	Programmed by	Erased by	Granularity
Mask ROM	manufacturer mask	never	—
PROM	user, once (fusible links)	never	—
EPROM	user (high-V pulses)	**UV light ~20 min**	entire chip
EEPROM	user, in-circuit	electrically	**byte**
Flash	user, in-circuit	electrically	**block/sector** (fast bulk erase)

- A ROM = fixed **decoder (AND array) + programmable OR array** → can realise any combinational function (lookup table). Related PLDs: **PROM** (fixed AND, prog. OR), **PAL** (prog. AND, fixed OR), **PLA** (both programmable — most flexible).
- Flash uses **floating-gate MOSFETs**; NAND flash = storage (SSD), NOR flash = code execution.

3.12.4 Memory expansion & address decoding

- **Address lines for M words: k = $\log_2 M$.** 1K = 2^{10} = 1024, 1M = 2^{20}, 1G = 2^{30}.
- **Word-length expansion:** place chips side-by-side, same addresses, data buses concatenated.

- **Word-capacity expansion:** stack chips; extra high-order address bits feed a **decoder driving chip-selects (CS)**.

✍ Worked Example 15 — Memory calculations

(a) Address & data lines for a 4K × 8 memory?

4K = 2^{12} ⇒ **12 address lines, 8 data lines**; capacity = 4096 × 8 = 32 768 bits = 4 KB.

(b) How many 1K × 4 chips build a 4K × 8 memory?

Words: 4K/1K = 4 rows; width: 8/4 = 2 per row ⇒ 4 × 2 = **8 chips**, with a **2-to-4 decoder** on $A_{11}A_{10}$ for chip-select.

(c) A ROM realising any 4-input, 3-output function needs $2^4 \times 3$ = **48 bits** (16 words × 3).

(d) Address range of a 16K block starting at 2000_{16}? 16K = 4000_{16} locations → 2000_{16} to **$5FFF_{16}$**.

3.12.5 Memory hierarchy basics

Registers → **Cache (SRAM)** → Main memory (DRAM) → Secondary (Flash/disk). Moving down: size ↑, cost/bit ↓, speed ↓. Cache exploits **locality of reference**; hit ratio h gives average access time t_avg = h·t_cache + (1−h)·t_main.

3.13 PYQ Corner — the 9 observed questions of 22-04-2025, solved

Q1. In a priority encoder, if two inputs are active simultaneously, the output corresponds to —

The input with the **higher priority** (in 74147/74148, the higher-numbered input); the lower one is ignored. E.g. I_5 and I_2 both high → code for 5. ✓

Q2. Which combination of gates gives an output identical to an XOR gate?

$Y = \bar{A}B + A\bar{B}$ — i.e. **two AND gates + one OR gate + two inverters** (or the 4-NAND network). Recognise the symbol: OR shape with an extra curved input line. Also XOR = $(A + B)\cdot\overline{(AB)}$ — an OR and a NAND feeding an AND. ✓

Q3. The carry output of a half adder is —

C = A · B (AND of the two inputs); Sum = A ⊕ B. ✓

Q4. A T flip-flop has T = 1 and starts with Q = 0. Output after 3 clock pulses?

Toggles every clock: 0 → 1 → 0 → **1**. Answer: **Q = 1** (odd number of pulses inverts the start state; after even pulses it returns to 0). ✓

Q5. The 2's complement of 101110 is —

1's complement 010001 + 1 = **010010**. (Shortcut: copy trailing "10", invert the rest.) ✓

Q6. Output of an EX-OR gate when both inputs are 1 —

1 ⊕ 1 = **0**. (XOR is 1 only for *different* inputs; a multi-input XOR outputs 1 for an odd number of 1s.) ✓

Q7. In an asynchronous (ripple) counter, the flip-flops are clocked —

Only the first FF gets the external clock; every following FF is clocked by the output (Q or $\bar{Q}$) of the preceding FF — hence the count "ripples" through with cumulative delay n·t_pd. (Contrast: synchronous counter — one common clock to all FFs.) ✓

Q8. In a 3-to-8 decoder, how many outputs are active at a time?

Exactly one — the output whose index equals the 3-bit input; the remaining seven are inactive. (Active-low in the 74138: the selected line goes LOW.) ✓

Q9. Which RAM stores data as charge on a capacitor and therefore needs periodic refreshing?

DRAM (1T-1C cell, refresh every few ms). SRAM uses a 6-transistor latch, needs no refresh, is faster, and serves as cache. ✓

3.14 Practice MCQs (30 questions)

1. $(2A9)_{16}$ in decimal is —

(a) 649 (b) 681 (c) 665 (d) 425

2. The octal equivalent of binary 110101011 is —

(a) 653 (b) 565 (c) 635 (d) 6AB

3. The range of signed 2's-complement numbers with 8 bits is —

(a) −127 to +127 (b) −128 to +127 (c) −128 to +128 (d) 0 to 255

4. The 1's complement of 0110 is —

(a) 1010 (b) 1001 (c) 0101 (d) 1110

5. Using 2's-complement addition, 0101 − 0011 (4-bit) equals —

(a) 0010 (b) 0100 (c) 1000 (d) 0001

6. Which code is both weighted and self-complementing?

(a) 8421 (b) Excess-3 (c) 2421 (d) Gray

7. The Gray code for binary 1101 is —

(a) 1011 (b) 1010 (c) 1110 (d) 0111

8. The number of characters in standard ASCII is —

(a) 64 (b) 128 (c) 256 (d) 512

9. A single parity bit can —

(a) correct one error (b) detect any single (odd) error (c) detect two errors (d) correct two errors

10. By De Morgan, $\overline{(\bar{A} + \bar{B})}$ equals —

(a) A + B (b) $\bar{A}\cdot\bar{B}$ (c) A·B (d) $\bar{A} + \bar{B}$

11. Simplify $A + \bar{A}B$ —

(a) A (b) A + B (c) AB (d) B

12. The dual of A·(B + C) = AB + AC is —

(a) A + BC = (A+B)(A+C) (b) A(B+C) = A (c) $\bar{A}(\bar{B}+\bar{C})$ (d) none

13. F(A,B,C) = Σm(0, 2, 4, 6) minimises to —

(a) C (b) $\bar{C}$ (c) $\bar{A}$ (d) $A\bar{B}$

14. In a 4-variable K-map, a group of 8 cells yields a term with —

(a) 1 literal (b) 2 literals (c) 3 literals (d) 4 literals

15. A NAND gate with both inputs joined together acts as —

(a) AND (b) OR (c) NOT (d) buffer

16. Minimum number of NAND gates to build an XOR gate —

(a) 3 (b) 4 (c) 5 (d) 6

17. IC 7402 contains —

(a) quad NAND (b) quad NOR (c) hex NOT (d) quad XOR

18. Which logic family has the highest speed?

(a) TTL (b) CMOS (c) ECL (d) RTL

19. Which family has the lowest static power dissipation?

(a) TTL (b) ECL (c) CMOS (d) DTL

20. The sum output of a full adder with inputs A = 1, B = 1, Cin = 1 is —

(a) 0 (b) 1 with carry 0 (c) 1 with carry 1 (d) 0 with carry 0

21. The borrow output of a half subtractor (A − B) is —

(a) AB (b) $\bar{A}B$ (c) $A\bar{B}$ (d) $A \oplus B$

22. Select lines needed for a 16:1 multiplexer —

(a) 2 (b) 3 (c) 4 (d) 16

23. A DEMUX with 4 select lines has how many outputs?

(a) 4 (b) 8 (c) 16 (d) 32

24. In a JK flip-flop with J = K = 1, each clock pulse causes —

(a) set (b) reset (c) hold (d) toggle

25. The race-around condition is eliminated by —

(a) increasing pulse width (b) master–slave configuration (c) removing the clock (d) J = K = 0 always

26. Flip-flops needed for a MOD-100 counter —

(a) 6 (b) 7 (c) 8 (d) 10

27. A 5-stage Johnson counter has a MOD of —

(a) 5 (b) 10 (c) 25 (d) 32

28. A 4-bit ripple counter with FF delay 20 ns has f_max ≈ —

(a) 50 MHz (b) 25 MHz (c) 12.5 MHz (d) 6.25 MHz

29. An 8-bit DAC with 5 V full scale has step size ≈ —

(a) 19.6 mV (b) 39.2 mV (c) 9.8 mV (d) 5 mV

30. Which ADC gives the best 50 Hz noise rejection?

(a) flash (b) SAR (c) dual-slope (d) counter type

Answer Key with one-line explanations

Q	Ans	Explanation
1	b	$2 \cdot 256 + 10 \cdot 16 + 9 = 512 + 160 + 9 = 681$
2	a	110 101 011 → 6 5 3
3	b	$-2^7 \ldots +2^7-1 = -128 \ldots +127$
4	b	Invert every bit: 0110 → 1001
5	a	0101 + 1101 = 1 0010, drop carry → 0010 (5 − 3 = 2)
6	c	2421 is weighted **and** self-complementing; XS-3 is self-complementing but unweighted
7	a	Keep 1; $1 \oplus 1 = 0$; $1 \oplus 0 = 1$; $0 \oplus 1 = 1$ → 1011
8	b	7 bits → $2^7 = 128$
9	b	Parity detects any odd number of errors; corrects none
10	c	Complement of a sum of complements = AB
11	b	Redundancy law: $A + \bar{A}B = A + B$
12	a	Swap + and ·: the other distributive law
13	b	All even minterms have C = 0 → $F = \bar{C}$
14	a	n − k = 4 − 3 = 1 literal
15	c	$\overline{(A \cdot A)} = \bar{A}$
16	b	Standard 4-NAND XOR network
17	b	7402 = quad 2-input NOR
18	c	ECL never saturates → ~1 ns delays
19	c	CMOS draws only leakage current statically
20	c	$1+1+1 = 11_2$ → Sum 1, Carry 1
21	b	Borrow when A = 0, B = 1 → $\bar{A}B$
22	c	$\log_2 16 = 4$
23	c	$2^4 = 16$ outputs
24	d	J = K = 1 is the toggle mode
25	b	Master–slave (or edge triggering) allows one toggle per pulse
26	b	$2^7 = 128 \geq 100 > 64 = 2^6$ → 7 FFs
27	b	Johnson MOD = 2n = 10
28	c	1/(4 × 20 ns) = 12.5 MHz
29	a	$5/(2^8 - 1) = 5/255 \approx 19.6$ mV
30	c	Dual-slope integrates over a mains period → hum cancels

3.15 Rapid-Revision Sheet

Flip-flop master table

FF	Truth table (inputs → Q^+)	Characteristic eqn	Excitation ($Q \to Q^+$: inputs)
SR	00→Q, 01→0, 10→1, 11→invalid	$Q^+ = S + \bar{R}Q$	0→0: 0×; 0→1: 10; 1→0: 01; 1→1: ×0
JK	00→Q, 01→0, 10→1, 11→**toggle**	$Q^+ = J\bar{Q} + \bar{K}Q$	0→0: 0×; 0→1: 1×; 1→0: ×1; 1→1: ×0
D	$Q^+ = D$	$Q^+ = D$	D = desired Q^+
T	0→hold, 1→**toggle**	$Q^+ = T \oplus Q$	same: 0; change: 1

Conversions: JK→T (J=K=T), JK→D (J=D, K=$\bar{D}$), D→T (D = T⊕Q), T→D (T = D⊕Q).

Counter formulas

- FFs for MOD-N: **$n = \lceil \log_2 N \rceil$**; ripple/sync binary MOD = 2^n; **ring = n; Johnson = 2n**.
- Frequency division: n cascaded toggle stages → **$f/2^n$**; T = 1 FF alone → f/2.
- Ripple counter f_{max} = **$1/(n \cdot t_{pd})$**; synchronous $f_{max} = 1/(t_{pd} + t_{gate})$.
- Count after P pulses (from 0) = **P mod 2^n** in binary.
- Decade counter (7490): resets at 1010 via NAND(Q_3, Q_1); counts 0–9.

ADC / DAC formulas

- **DAC step size = $V_{FS}/(2^n - 1)$**; V_{out} = D × step; % resolution = $100/(2^n - 1)$.
- **ADC resolution Q = $V_{FS}/2^n$**; quantisation error = **±½ LSB**; SNR ≈ 6.02n + 1.76 dB.
- Flash: **$2^n - 1$ comparators**, fastest. SAR: **n clocks**, fixed. Counter: ≤ $2^n - 1$ clocks. Dual-slope: $V_{in} = V_{ref} \cdot T_2/T_1$, most accurate, slowest.
- R-2R DAC: only two resistor values; weighted-resistor DAC: spread 2^{n-1}:1 (impractical for large n).

Number-system nuggets

- n bits → 2^n values; signed 2's-comp range $-2^{n-1} \ldots 2^{n-1} - 1$.
- 2's complement shortcut: copy up to first 1 from LSB, invert the rest.
- Binary→Gray: $G_i = B_{i+1} \oplus B_i$. XS-3 = BCD + 3. BCD fix-up: add 6 if group > 9 or carries.
- Hamming: $2^k \geq m + k + 1$; distance d → detect d−1, correct ⌊(d−1)/2⌋.

Gate one-liners

- XOR: 1 iff inputs differ; **1 ⊕ 1 = 0**; odd-parity function; A ⊕ 1 = $\bar{A}$.
- Universal gates: NAND, NOR. XOR from NANDs: **4**. Bubbled AND = NOR; bubbled OR = NAND.
- HA: S = A⊕B, **C = AB**. FA: S = A⊕B⊕Cin, Cout = AB + BCin + ACin. HS borrow = **$\bar{A}B$**.
- Decoder n→2^n: exactly **1 active output**. MUX N:1 needs $\log_2 N$ selects. Priority encoder: **highest active input wins**.

Logic-family comparison (memorise the extremes)

Property	Winner
Fastest (lowest t_pd)	**ECL** (~1 ns; never saturates)
Lowest static power	**CMOS** (~nW)
Highest power drain	ECL
Highest fan-out / noise immunity	**CMOS** (≥50; margins ~0.3–0.45 V_DD)
Standard supply	TTL: +5 V; ECL: −5.2 V; CMOS: 3–15 V
TTL levels	V_IL 0.8, V_IH 2.0, V_OL 0.4, V_OH 2.4 → NM = 0.4 V

Memory one-liners

- **SRAM**: 6-T latch, no refresh, fast, cache. **DRAM**: 1T-1C, needs refresh, dense/cheap, main memory. Both volatile.
- EPROM erased by **UV (whole chip)**; EEPROM **electrically (byte)**; Flash **electrically (block)**; all non-volatile floating-gate.
- M-word memory needs **$\log_2 M$ address lines**; chips for A×B from a×b = (A/a)×(B/b).
- PROM: fixed AND + prog OR; PAL: prog AND + fixed OR; PLA: both programmable.
- Hierarchy: registers → cache (SRAM) → main (DRAM) → flash/disk; t_avg = h·t_c + (1−h)·t_m.

End of Chapter 3. Next: Chapter 4 — Linear Integrated Circuits.

Chapter 4 — Linear Integrated Circuits

Syllabus (Annexure-VII C, Unit 4): Introduction to Operational Amplifier · Linear applications · Non-linear applications · Voltage regulators · Timers · Phase-Locked Loop

📊 Weightage & Trend Box

Item	Detail
Direct weight (22-04-2025 CBT-2, Shift-2)	**2 / 50 technical Q ≈ 4%** (scales to ~4/100 in full technical section)
Q1 observed	**IC 741 internal stages** — "Which is the *second* (intermediate) stage of IC 741?" → **Intermediate / gain stage** (also described as level-shift + gain stage in some texts)
Q2 observed	**Op-amp integrator** — output is **proportional to the integral of the input** ($V_o = -(1/RC)\int V_{in}\,dt$)
Hidden weight	**PLL** questions appeared under **Communication Engineering** (FM demodulation, AM detection by PLL). So PLL preparation here pays off in the 16%-weight Communication unit too.
Trend	Questions are **conceptual/one-step numerical**: op-amp golden rules, standard gain formulas, 555 timing formulas, 78xx/LM317 identification, PLL block roles, capture vs lock range. Nothing beyond standard formulas has been asked.
Strategy	Memorise the **formula sheet** at the end cold; be able to *draw mentally* the 741 stage order, 555 internal block, and PLL block diagram.

4.1 Integrated Circuit (IC) Basics

An **Integrated Circuit** fabricates an entire circuit (transistors, diodes, resistors, small capacitors) on a single chip of semiconductor (usually silicon).

Classification by fabrication:

Type	Description	Remarks
Monolithic IC	All components fabricated on a *single* silicon chip by diffusion/ion implantation	Cheapest in mass production; IC 741, 555, 7400 are monolithic
Hybrid IC	Separate chips + thin/thick-film passive components interconnected on one insulating substrate	Used for high power / high precision
Thin-film / Thick-film	Passive components deposited as films on glass/ceramic; active devices added separately	Film thickness: thin < 1 µm; thick > 1 µm (screen-printed)

Classification by signal: Linear (analog) ICs — output varies continuously with input (op-amps, regulators, timers in linear mode); **Digital** ICs — two-state output (gates, flip-flops).

Classification by integration level: SSI (< 12 gates), MSI (12–99), LSI (100–9999), VLSI (10^4–10^5), ULSI (> 10^5 gates/components).

Advantages of ICs: small size & weight, low cost in volume, high reliability (fewer solder joints), low power, matched components (excellent for differential pairs), improved speed (short interconnects).

Limitations: inductors and large capacitors cannot be fabricated, limited power dissipation, low voltage ratings, cannot be repaired (replace only).

4.1.1 IC 741 — the classic op-amp

- **Monolithic**, general-purpose, internally frequency-compensated (30 pF on-chip capacitor → no external compensation needed), **8-pin DIP**.
- Supply: typically **±15 V** (range ±5 V to ±18 V).

IC 741 pin diagram (8-pin DIP, top view):

Pin	Function	Pin	Function
1	Offset null	8	NC (no connection)
2	Inverting input (−)	7	+V_{CC}
3	Non-inverting input (+)	6	Output
4	−V_{EE}	5	Offset null

Internal block diagram — four stages in order (★ asked in 2025):

```
Input → [1. Input differential amplifier stage]
      → [2. Intermediate / gain stage]          ← ★ SECOND stage (2025 PYQ)
      → [3. Level-shifting (level translator) stage]
      → [4. Output (push-pull class-AB) stage] → Output
```

Stage	Circuit used	Job
1. Input stage	**Dual-input, balanced-output differential amplifier**	High input resistance, high CMRR, most of the voltage gain begins here
2. Intermediate (gain) stage	**Dual-input, unbalanced (single-ended) output differential amplifier**	Provides the bulk of additional voltage gain
3. Level shifter	**Emitter follower with level translator** (V_{BE}-shift network / current source)	Shifts the DC level down so output can swing symmetrically about 0 V (direct coupling accumulates DC)
4. Output stage	**Complementary-symmetry push-pull (class AB)**	Low output resistance, high current drive, large voltage swing

> **Exam nuance:** Some books club stages 2 and 3 and call the second stage the "**level-shift and gain stage**." The 2025 paper's accepted answer for "second/intermediate stage of 741" was the **intermediate gain stage** — remember both names.

Typical 741 data: open-loop gain A ≈ 2×10^5 (≈ 106 dB), input resistance ≈ 2 MΩ, output resistance ≈ 75 Ω, CMRR ≈ 90 dB, slew rate ≈ **0.5 V/µs**, unity-gain bandwidth ≈ 1 MHz, input offset voltage ≈ 2 mV, input bias current ≈ 80 nA, input offset current ≈ 20 nA.

4.2 Op-Amp Fundamentals

An **operational amplifier** is a very-high-gain, direct-coupled differential amplifier. Name comes from its original use for mathematical *operations* (add, subtract, integrate, differentiate) in analog computers.

Symbol: triangle with two inputs — inverting (−) and non-inverting (+) — and one output.

Output (open loop): **$V_0 = A \cdot (V_+ - V_-)$** where A = open-loop differential gain.

4.2.1 Ideal vs practical (741) characteristics ★

Parameter	Ideal op-amp	Practical (IC 741)
Open-loop voltage gain A	∞	≈ 2×10^5
Input resistance R_{in}	∞	≈ 2 MΩ
Output resistance R_{out}	0	≈ 75 Ω
Bandwidth	∞	≈ 1 MHz (unity-gain)
CMRR	∞	≈ 90 dB
Slew rate	∞	≈ 0.5 V/µs
Input offset voltage/current	0	≈ 2 mV / 20 nA
Output for $V_+ = V_-$ (common-mode gain)	0	small but non-zero
Drift with temperature	0	present

Key definitions:

- **CMRR** = |A_d/A_{cm}|; in dB: CMRR = 20 log(A_d/A_{cm}). Higher CMRR ⇒ better rejection of common-mode noise (hum picked up equally on both wires).
- **Slew rate (SR)** = maximum rate of change of output voltage = $(dV_0/dt)_{max}$, in V/µs. For an undistorted sine output of peak V_m at frequency f: required SR ≥ 2πf·V_m. Max full-power frequency **$f_{max} = SR/(2\pi V_m)$**.
- **Gain–bandwidth product (GBW):** for a single-pole op-amp, $A_{CL} \times f_{CL}$ = constant = unity-gain bandwidth (1 MHz for 741). Closed-loop bandwidth = GBW / closed-loop gain.
- **Input offset voltage V_{io}:** DC voltage that must be applied between inputs to force $V_0 = 0$. Nulled in 741 using a 10 kΩ pot between pins 1 and 5 (wiper to −V_{EE}).
- **PSRR:** change in input offset voltage per unit change in supply voltage (µV/V).

4.2.2 Golden rules, virtual short, virtual ground ★

With **negative feedback** and very large A:

1. **Rule 1 (virtual short):** $V_+ \approx V_-$ — the two input terminals sit at (virtually) the same potential, because V_0 is finite and $V_0/A \to 0$.
2. **Rule 2:** No current enters either input terminal ($R_{in} \to \infty$).

Virtual ground: In the *inverting amplifier* the (+) input is grounded, so by Rule 1 the (−) input is also at ≈ 0 V *without being physically connected to ground* — it is a **virtual ground**: zero voltage, but it can sink/source signal current through the feedback path.

> Virtual short exists **only with negative feedback and the op-amp in its linear region**. In comparators/Schmitt triggers (no negative feedback), there is **no** virtual short.


4.2.3 Open-loop configurations

No feedback ⇒ gain ≈ 2×10^5 ⇒ even a few tens of µV drives the output to saturation (±V_{sat} ≈ ±13 V with ±15 V supplies). Three open-loop modes: differential amplifier, inverting amplifier, non-inverting amplifier — all impractical as linear amplifiers (output slams to ±V_{sat}); the useful open-loop application is the **comparator** (§4.4.1).

4.3 Linear Applications of Op-Amps

"Linear" = output is a linear (proportional / weighted-sum / calculus) function of the input; negative feedback keeps the op-amp in its active region.

4.3.1 Inverting amplifier ★

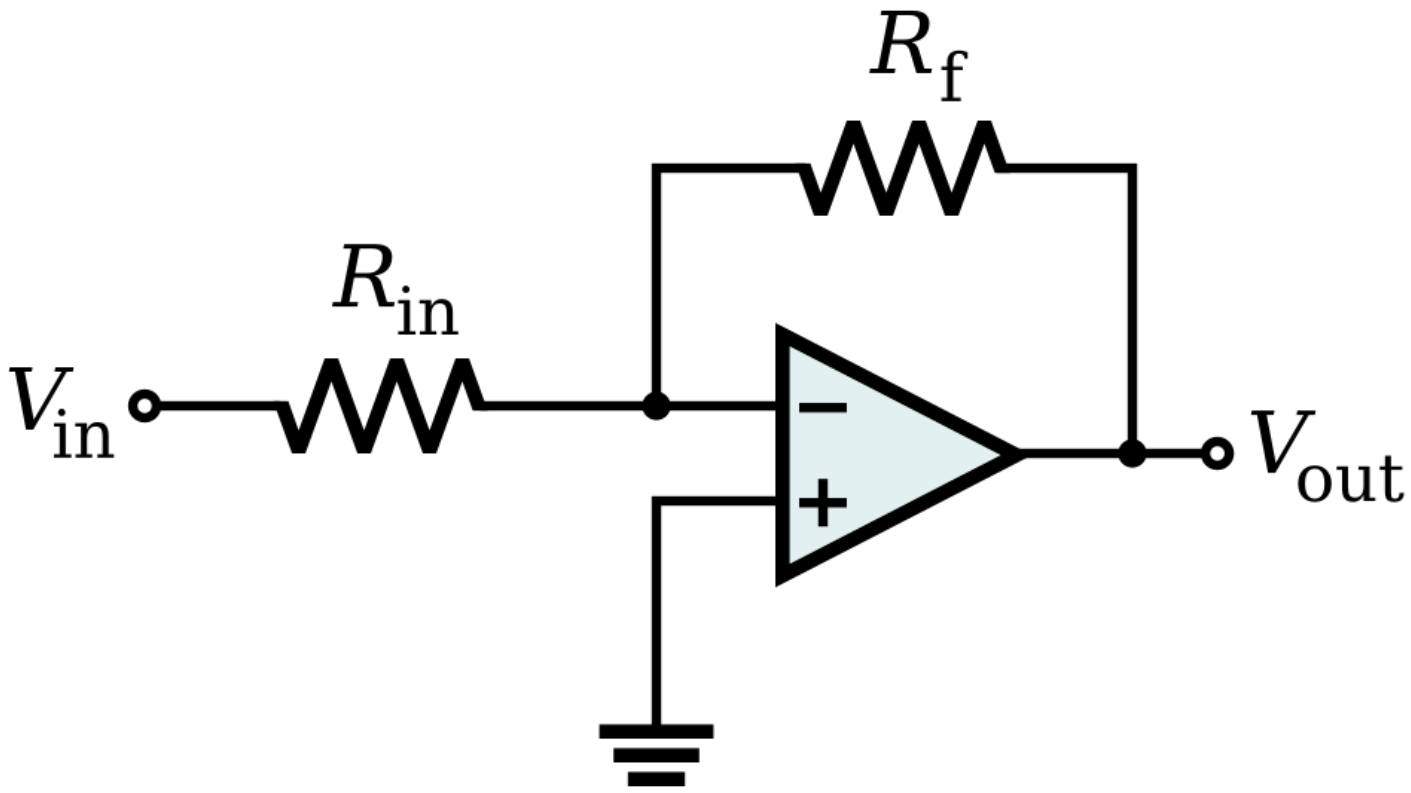

Inverting amplifier (gain −Rf/Rin).


Input via R_{in} (often written R_1) to the (−) terminal; feedback R_f from output to (−); (+) grounded.

Derivation: (−) node is virtual ground ⇒ current through R_1: I = V_{in}/R_1. No current enters op-amp ⇒ same I flows through R_f: 0 − V_0 = I·R_f.

$A_v = V_0/V_{in} = -R_f/R_1$ (180° phase inversion)

Input impedance = R_1 (moderate); output impedance ≈ 0.

4.3.2 Non-inverting amplifier ★

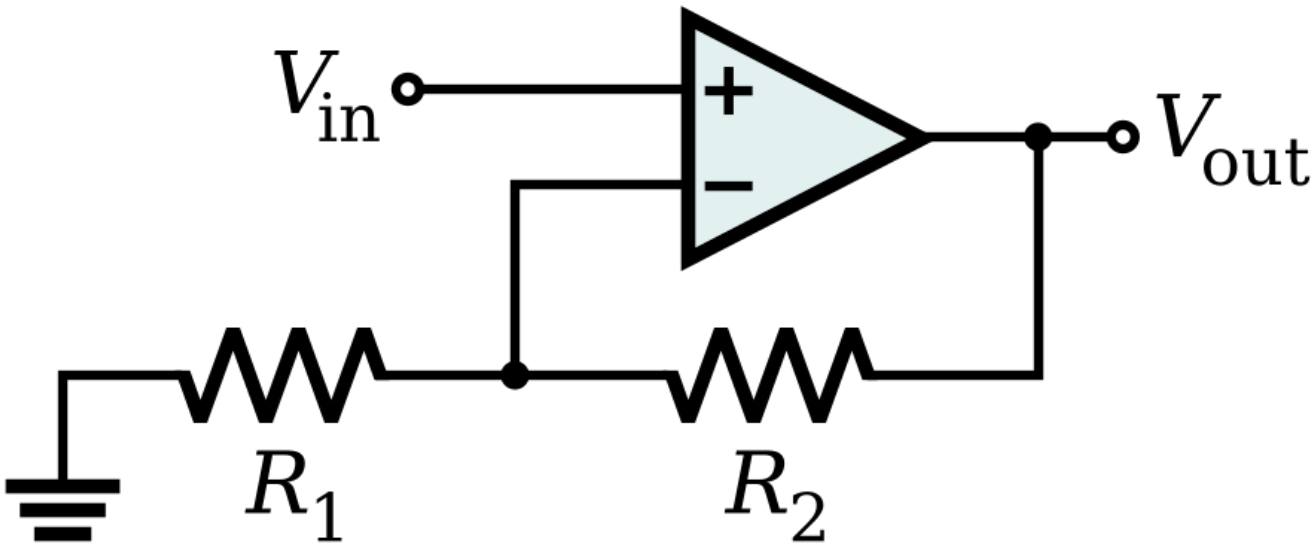

Non-inverting amplifier (gain 1+Rf/Rin).

Signal to (+); feedback divider R_f, R_1 from output to (−) to ground.

Virtual short ⇒ V_- = V_{in}; divider: $V_- = V_0 \cdot R_1/(R_1+R_f)$.

$A_v = 1 + R_f/R_1$ (no phase inversion; gain always ≥ 1)

Very high input impedance (signal sees op-amp's (+) input directly).

4.3.3 Voltage follower (unity-gain buffer)

Non-inverting with $R_f = 0$ (direct wire), $R_1 = \infty$ ⇒ **$A_v = +1$**. Extremely high Z_{in}, near-zero Z_{out} → used for **impedance matching / buffering** (isolating a high-impedance source from a low-impedance load). Best bandwidth of all configurations (BW = full GBW).

4.3.4 Summing amplifier (adder)

Inverting summer: inputs V_1, V_2, V_3 through R_1, R_2, R_3 into the virtual-ground node, feedback R_f:

$V_0 = -R_f(V_1/R_1 + V_2/R_2 + V_3/R_3)$

If $R_1 = R_2 = R_3 = R_f$: $V_0 = -(V_1+V_2+V_3)$. If $R_f = R/3$ with equal Rs: **averager** $V_0 = -(V_1+V_2+V_3)/3$. Weighted summing is the basis of a simple **DAC** (binary-weighted resistor DAC).

Non-inverting summer (two equal inputs): $V_+ = (V_1+V_2)/2$; with gain $(1+R_f/R_1) = 2$ ⇒ $V_0 = V_1+V_2$.

4.3.5 Difference (subtractor) amplifier

Four resistors: V_1 through R_1 to (−) with feedback R_2; V_2 through R_1 to (+) with R_2 to ground (matched pairs).

$V_0 = (R_2/R_1)(V_2 - V_1)$

Rejects common-mode signals *if resistors match perfectly*; mismatch degrades CMRR — hence the instrumentation amplifier.

4.3.6 Instrumentation amplifier

Three op-amps: two non-inverting input buffers sharing gain-set resistor R_G, followed by a difference amplifier.

$V_0 = (1 + 2R/R_G) \cdot (R_3/R_2) \cdot (V_2 - V_1)$ (commonly with $R_3 = R_2$: $V_0 = (1 + 2R/R_G)(V_2 - V_1)$)

Properties: **very high input impedance on both inputs, very high CMRR, gain set by a single resistor R_G**. Used for transducer/bridge signals (strain gauge, thermocouple, biomedical ECG). IC example: AD620.

4.3.7 Integrator ★ (2025 PYQ)

Inverting configuration with feedback **capacitor C** replacing R_f; input through R.

Derivation: virtual ground ⇒ $I = V_{in}/R$; this charges C: $I = -C \cdot dV_0/dt$.

$V_0(t) = -(1/RC) \int_0^t V_{in}\, dt + V_0(0)$

> ★ **Output is proportional to the (negative) integral of the input** — exact 2025 statement.

Input–output waveform pairs (memorise):

Input	Integrator output
Step (DC level)	Negative-going **ramp**
Square wave	**Triangular wave**
Triangular wave	Parabolic segments
Sine wave	**−Cosine** (i.e. sine shifted; gain falls with f)

As a filter, the ideal integrator gain = 1/(ωRC): gain **∞ at DC** (any input offset integrates to saturation — the practical problem) and rolls off at **−20 dB/decade**; phase = +90° (output lags input appropriately as cos → −sin).

Practical (lossy) integrator: a resistor R_f (typically ≈ 10R) is placed **in parallel with C** to give finite DC gain ($-R_f/R$) and prevent saturation. It integrates properly only for **$f \gg f_a = 1/(2\pi R_f C)$**; useful range roughly f_a to $f_b = 1/(2\pi RC)$ (f_b = 0-dB frequency of the ideal response).

4.3.8 Differentiator

Swap R and C of the integrator: input through **C**, feedback **R**.

$I = C \cdot dV_{in}/dt$ through C ⇒ **$V_0 = -RC \cdot (dV_{in}/dt)$**

Input	Differentiator output
Triangular wave	**Square wave**
Square wave	Sharp **spikes/impulses** at edges
Sine	−Cosine (gain rises with f)

Gain = ωRC rises at **+20 dB/decade** ⇒ amplifies high-frequency **noise** and can be unstable. **Practical differentiator:** add series resistor R_1 with the input capacitor (and often a small C_f across R) to limit high-frequency gain; differentiates properly for $f \ll 1/(2\pi R_1 C)$.

4.3.9 V-to-I and I-to-V converters

- **Current-to-voltage (transresistance) converter:** input current I_{in} into the virtual-ground (−) node, feedback R_f ⇒ **$V_0 = -I_{in} R_f$**. Used to read photodiode/photocell currents, DAC output currents.

- **Voltage-to-current (transconductance) converter:** load placed in the feedback path (floating load): **I_L = V_{in}/R₁ — independent of load resistance**. Grounded-load version = **Howland current source**. Used to drive LEDs, deflection coils, 4–20 mA loops.

Worked Examples — linear applications

WE-1 (Inverting gain). R_1 = 10 kΩ, R_f = 100 kΩ, V_{in} = 0.5 V sine peak.

A = −R_f/R_1 = −10 ⇒ output = 5 V peak, phase-inverted. Input impedance = 10 kΩ.

WE-2 (Non-inverting). R_1 = 2 kΩ, R_f = 18 kΩ ⇒ A = 1 + 18/2 = **10**. If V_{in} = 200 mV ⇒ V_0 = 2 V, in phase. Closed-loop bandwidth with a 741 (GBW = 1 MHz): BW = 1 MHz/10 = **100 kHz**.

WE-3 (Summer). R_1 = R_2 = 10 kΩ, R_f = 20 kΩ, V_1 = +1 V, V_2 = −0.5 V.

V_0 = −20k(1/10k − 0.5/10k) = −20k × (0.05 mA) = **−1 V**.

WE-4 (Integrator, step input) ★ pattern of 2025 PYQ. R = 100 kΩ, C = 1 µF, V_{in} = +2 V step at t = 0, $V_0(0)$ = 0.

$V_0(t)$ = −(1/RC)∫2 dt = −(2/0.1)·t = **−20t volts** — a ramp falling at 20 V/s. With ±V_{sat} = ±13 V it saturates at t = 13/20 = **0.65 s**.

WE-5 (Integrator, square input). ±5 V square wave, 1 kHz (T = 1 ms), into R = 10 kΩ, C = 0.1 µF (RC = 1 ms).

During each half-cycle (0.5 ms) the output ramps by ΔV = (1/RC)·V·(T/2) = (1/1 ms)(5)(0.5 ms) = 2.5 V ⇒ **triangular wave of 2.5 V peak-to-peak** (centred, inverted slope sense).

WE-6 (Slew-rate limit). A 741 (SR = 0.5 V/µs) must output a 10 V-peak sine. Max frequency:

f_{max} = SR/(2πV_m) = 0.5×10^6 / (2π×10) ≈ **7.96 kHz**. Above this the sine distorts into a triangle.

4.4 Non-Linear Applications of Op-Amps

Op-amp deliberately driven into saturation (no/positive feedback) or with non-linear feedback elements (diodes).

4.4.1 Comparator & zero-crossing detector

Open-loop op-amp: V_0 = +V_{sat} if $V_+ > V_-$, −V_{sat} if $V_+ < V_-$.

- **Zero-crossing detector:** reference = 0 V; a sine input yields a **square wave** output that switches at every zero crossing. (Basis of frequency measurement, sine-to-square conversion.)
- Non-zero reference V_{ref} on one input ⇒ level detector.
- Weakness: **noise near the threshold causes multiple false transitions (chatter)** — solved by the Schmitt trigger.
- Dedicated comparator ICs (LM311, LM339) have faster response and open-collector outputs.

4.4.2 Schmitt trigger (regenerative comparator) ★

Comparator with **positive feedback**: output fed back to (+) input through divider R_1 (to ground) and R_2 (to output); signal applied to (−).

Two trip points (with symmetric saturation ±V_{sat} and reference ground):

UTP = +V_{sat}·R_1/(R_1+R_2) LTP = −V_{sat}·R_1/(R_1+R_2)

Hysteresis width V_H = UTP − LTP = 2V_{sat}·R_1/(R_1+R_2)

- Rising input must exceed UTP to switch output low; falling input must drop below LTP to switch high (inverting Schmitt). The transfer characteristic is a **hysteresis loop**.
- Noise smaller than V_H cannot cause false triggering — the key advantage over a plain comparator.
- Applications: squaring circuit, noise-immune level detection, relaxation oscillators, debouncing.

4.4.3 Precision rectifiers (super-diode)

An ordinary diode cannot rectify signals below its ~0.7 V drop. Placing the diode **inside the op-amp's feedback loop** divides the effective diode drop by open-loop gain (0.7/A ≈ μV) ⇒ rectification of millivolt signals.

- **Precision half-wave:** op-amp + diode in feedback; output follows input for one polarity, 0 for the other.
- **Precision full-wave (absolute-value circuit):** half-wave stage + summing stage ⇒ $V_0 = |V_{in}|$. Used in AC voltmeters/measurement.

4.4.4 Log and antilog amplifiers (brief)

- **Log amp:** feedback element = diode or transistor (BE junction). Since I = I_se^(V/V_T): **$V_0 = -V_T \cdot \ln(V_{in}/(I_s R))$** — output ∝ logarithm of input.
- **Antilog (exponential) amp:** diode/transistor at the *input*, R in feedback ⇒ output ∝ e^(V_{in}/V_T).
- Cascading log → summer → antilog gives **analog multiplication/division**; also used for dB displays and signal compression.

4.4.5 Op-amp clippers and clampers

- **Active positive/negative clipper:** op-amp with diode + reference V_{ref} clips the waveform precisely at V_{ref} (no 0.7 V error, unlike passive diode clippers).
- **Active clamper (DC restorer):** capacitor in series with input, diode in feedback — shifts the whole waveform so its peak sits at V_{ref}; adds a precise DC level to a signal.
- **Peak detector:** precision half-wave rectifier charging a hold capacitor — output holds the input's peak value.

4.4.6 Waveform generators using op-amps

(a) Square-wave generator (op-amp astable / relaxation oscillator): Schmitt trigger + RC timing network from output to (−) input. The capacitor charges toward ±V_{sat} and the Schmitt flips each time it crosses ±βV_{sat} ($\beta = R_1/(R_1+R_2)$).

$T = 2RC\cdot\ln((1+\beta)/(1-\beta))$; if $R_1 = R_2$ (β = 0.5): **$T \approx 2.2\,RC$**, $f \approx 1/(2.2RC)$, 50% duty cycle.

(b) Triangular-wave generator: square-wave source (Schmitt/comparator) → **integrator** → triangular output; triangle fed back to the comparator closes the loop. Output frequency **$f = R_2/(4R_1 \cdot R\,C)$** for the standard two-op-amp circuit (comparator with divider R_1–R_2 + integrator RC); triangle amplitude = V_{sat}·R_1/R_2. Key idea for exams: **square in → integrator → triangle out**.

(c) Wien-bridge oscillator (sine): op-amp non-inverting amplifier + Wien network (series RC in series with parallel RC) as positive feedback.

$f_0 = 1/(2\pi RC)$; the Wien network's feedback fraction at f_0 = **1/3**, so the amplifier must give gain ≥ 3 ⇒ **R_f = 2R₁** ($1 + R_f/R_1 = 3$). Amplitude stabilised by a thermistor/lamp or diode network. Standard audio-frequency sine source; low distortion.

(Phase-shift oscillator with op-amp: $f_0 = 1/(2\pi RC\sqrt{6})$, required gain 29 — covered fully in the Devices chapter's oscillator section.)

4.4.7 Active filters ★

Active filter = RC network + op-amp: no inductors, provides gain, buffering, easy tuning. (Passive R-L-C filters have no gain and suffer loading.)

Filter	1st-order roll-off	2nd-order roll-off	Cut-off / centre formula
Low-pass (LP)	−20 dB/decade (−6 dB/octave)	−40 dB/decade	f_H = 1/(2πRC) (equal R, C: f = 1/(2πRC))
High-pass (HP)	+20 dB/dec below f_L	+40 dB/dec	f_L = 1/(2πRC)
Band-pass (BP)	—	—	f_0 = √(f_Lf_H); BW = f_H − f_L; Q = f_0/BW
Band-reject (BR/notch)	—	—	Twin-T notch: f_N = 1/(2πRC)

- **First-order LP:** RC to (+) input, op-amp with gain A_F = 1+R_f/R_1; response: |A| = A_F/√(1+(f/f_H)^2); at f = f_H gain is down **3 dB** (0.707A_F).
- **Second-order (Sallen–Key):** two RC sections; equal-component: f_H = 1/(2πRC).
- **Butterworth:** *maximally flat* passband; a 2nd-order Butterworth Sallen–Key needs pass-band gain **1.586** (damping ζ = 0.707, Q = 0.707). Chebyshev = steeper roll-off but ripple; Bessel = best (linear) phase.
- **Wide-band BP** = HP cascaded with LP (f_L < f_H). **Notch** = LP + HP summed, or twin-T; classic use: removing 50 Hz hum.
- **All-pass filter:** flat gain, only phase varies with f — used for phase equalisation/delay.

WE-7 (Filter design). First-order Butterworth LP with f_H = 1 kHz, C = 0.1 µF chosen:

R = 1/(2πf_HC) = 1/(2π×10^3×10^{-7}) ≈ **1.59 kΩ**. For pass-band gain 2, choose R_f = R_1 = 10 kΩ.

4.5 Voltage Regulators

A voltage regulator keeps the DC output constant against **line (input) variation, load variation and temperature**.

- **Line regulation** = $\Delta V_0/\Delta V_{in}$ (output change per volt of input change).
- **Load regulation** = (V_{NL} − V_{FL})/V_{FL} × 100%.

4.5.1 Shunt vs series (linear) regulators

	Shunt regulator	Series regulator
Control element	In **parallel** with load (e.g. zener + R)	In **series** with load (pass transistor)
Simplest example	Zener shunt regulator	Emitter-follower with zener reference
Efficiency	Poor (draws current even at no load)	Better; standard for linear ICs
Short-circuit behaviour	Inherently short-circuit tolerant (series R limits)	Needs added current limiting

A full series regulator = **reference (zener) + error amplifier (op-amp) + series pass transistor + sampling divider** — negative feedback holds V_0 = V_{ref}(1 + R_1/R_2).

4.5.2 Three-terminal fixed IC regulators — 78xx / 79xx ★

Series	Polarity	Common members	Pin order (TO-220, front view)
78xx	**Positive**	7805 (+5 V), 7809, 7812, 7815	1 = Input, 2 = Ground, 3 = Output
79xx	**Negative**	7905 (−5 V), 7912, 7915	1 = **Ground**, 2 = Input, 3 = Output (note the different order!)

- "xx" = output voltage. Typical output current up to 1 A (with heat sink); 78Lxx = 100 mA versions.
- **Dropout voltage ≈ 2 V**: input must exceed output by ≥ ~2 V (e.g. 7805 needs V_{in} ≥ ~7 V). LDO (low-dropout) regulators work with ~0.1–0.6 V headroom.
- Built-in **thermal shutdown, current limiting and SOA protection**.
- 0.33 µF input and 0.1 µF output capacitors recommended for stability.
- To make 78xx adjustable/boosted: add a resistor divider or zener in the ground leg — V_0 = V_{xx} + V_{ground-leg}.

4.5.3 IC 723 — general-purpose adjustable regulator

- 14-pin IC containing **temperature-compensated reference (≈ 7.15 V), error amplifier, series pass transistor (150 mA) and current-limit transistor**.
- Output adjustable **2 V – 37 V**; both **low-voltage (V_0 < 7.15 V, via divider on the reference)** and **high-voltage (V_0 > 7.15 V, via divider in feedback)** connections; external pass transistor extends current to amps; supports **foldback current limiting**.

4.5.4 LM317 — adjustable positive regulator ★

Three terminals: **Input, Output, Adjust**. It maintains **1.25 V (V_{ref}) between Output and Adjust**; a constant ≈ 50–100 µA flows from ADJ (usually neglected).

$V_0 = 1.25\,(1 + R_2/R_1)$ (+ I_{ADJ}R_2, usually neglected)

R_1 (Output→Adjust) is typically 240 Ω. Range 1.25–37 V, up to 1.5 A. Negative counterpart: **LM337**.

WE-8 (LM317). R_1 = 240 Ω, R_2 = 2.4 kΩ:

$V_0 = 1.25(1 + 2400/240) = 1.25 \times 11 =$ **13.75 V**.

For V_0 = 5 V with R_1 = 240 Ω: $R_2 = R_1(V_0/1.25 - 1) = 240(4-1) =$ **720 Ω**.

4.5.5 Linear vs switching (SMPS) regulators

Feature	Linear (series)	SMPS
Pass element operation	Active (rheostat) region — continuous	Switch (cut-off/saturation) at 20 kHz–1 MHz
Efficiency	30–60% (drops V_{in} − V_0 across pass device as heat)	**70–95%**
Noise/ripple	Very low (clean)	Switching noise/EMI present
Size/weight	Heavy (mains transformer, heat sink)	Small (HF transformer/inductor)
Output vs input	Step-down only (V_0 < V_{in})	Buck (down), **boost (up)**, buck-boost (invert/either)
Use	Audio, precision analog	Computers, chargers, TVs

Basic SMPS topologies: **buck** ($V_0 = D \cdot V_{in}$), **boost** ($V_0 = V_{in}/(1-D)$), **buck-boost** ($V_0 = -D \cdot V_{in}/(1-D)$); D = duty cycle. Control by **PWM** of the switching transistor.

4.6 IC 555 Timer — in depth ★

8-pin monolithic timer; supply 4.5–16 V (up to 18 V); output can sink/source 200 mA; name from the **three 5 kΩ resistors** of the internal divider.

Pins: 1 GND, 2 Trigger, 3 Output, 4 Reset (active-low), 5 Control voltage, 6 Threshold, 7 Discharge, 8 $+V_{CC}$.

4.6.1 Internal block diagram ★

- **Voltage divider:** three equal 5 kΩ resistors set two references: **$(2/3)V_{CC}$** and **$(1/3)V_{CC}$**.
- **Comparator 1 (upper):** (+) = Threshold pin 6, (−) = 2/3 V_{CC}. When threshold > 2/3 V_{CC} → **R** input of flip-flop → output LOW.
- **Comparator 2 (lower):** (−) = Trigger pin 2, (+) = 1/3 V_{CC}. When trigger < 1/3 V_{CC} → **S** input → output HIGH.
- **SR flip-flop** drives the **output buffer (pin 3)** and the **discharge transistor** (open-collector NPN, pin 7) — transistor ON (capacitor discharges) when output is LOW.
- **Reset (pin 4):** overrides everything, forces output LOW when pulled < ~0.7 V; tie to V_{CC} when unused.
- **Control (pin 5):** direct access to the 2/3 V_{CC} node — external voltage here changes both thresholds ⇒ **voltage-controlled pulse width / VCO**; bypass with 0.01 µF when unused.

4.6.2 Monostable (one-shot) mode ★

R from V_{CC} to pins 6+7, C from there to ground; negative trigger pulse (< 1/3 V_{CC}) on pin 2.

Action: trigger → output HIGH, discharge transistor OFF → C charges through R toward V_{CC} → when v_C reaches $(2/3)V_{CC}$, comparator 1 resets FF → output LOW, C discharges. One clean pulse per trigger.

Derivation of T: $v_C(t) = V_{CC}(1 - e^{(-t/RC)})$. Set $v_C = (2/3)V_{CC}$:


$2/3 = 1 - e^{(-T/RC)} \Rightarrow e^{(-T/RC)} = 1/3 \Rightarrow$ **$T = RC \cdot \ln 3 = 1.0986\,RC \approx 1.1\,RC$**

WE-9 (Monostable). Design a 1.1 ms one-shot with C = 0.1 µF:

$R = T/(1.1C) = 1.1\times10^{-3}/(1.1\times10^{-7}) =$ **10 kΩ**. (Check: $T = 1.1 \times 10^4 \times 10^{-7} = 1.1$ ms ✓)

Applications: timing delay, pulse-width stretching, missing-pulse detector, frequency divider, debouncing, PWM (with control-pin modulation).

4.6.3 Astable (free-running) mode ★

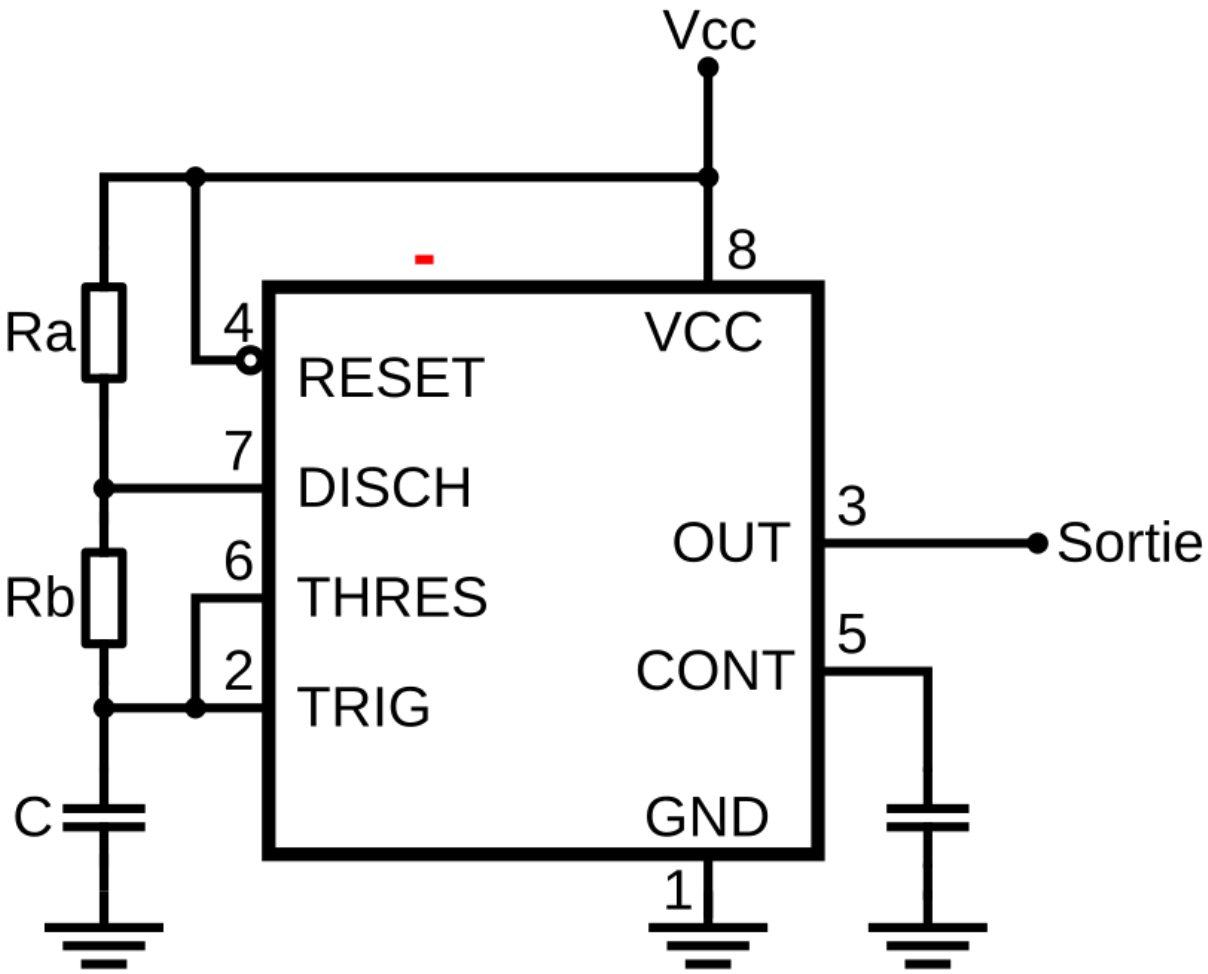

555 timer in astable mode.

R_A from V_{CC} to pin 7, R_B from pin 7 to pins 6+2, C from there to ground. No stable state: C charges through **R_A+R_B** from 1/3 to 2/3 V_{CC} (output HIGH), discharges through **R_B** alone via pin 7 from 2/3 to 1/3 V_{CC} (output LOW).

t_{HIGH} = 0.693 (R_A+R_B) C t_{LOW} = 0.693 R_B C

T = 0.693 (R_A+2R_B) C f = 1.44 / ((R_A+2R_B) C)

Duty cycle D = t_{HIGH}/T = (R_A+R_B)/(R_A+2R_B) — always **> 50%**; D → 50% when R_B ≫ R_A; exact 50% (and < 50%) needs a diode across R_B (charging bypasses R_B: then t_H = 0.693R_AC, t_L = 0.693R_BC).

(The 0.693 factor is ln 2 — charging between fixed fractions 1/3→2/3 of V_{CC} always takes τ·ln 2.)

WE-10 (Astable). R_A = 2.2 kΩ, R_B = 4.7 kΩ, C = 0.1 µF.

t_{HIGH} = 0.693(6.9k)(0.1µ) = 0.478 ms; t_{LOW} = 0.693(4.7k)(0.1µ) = 0.326 ms.


T = 0.804 ms ⇒ **f ≈ 1.24 kHz**; D = 6.9/11.6 = **59.5%**.

(Formula check: f = 1.44/((2.2k+9.4k)×0.1µ) = 1.44/(1.16×10^{-3}) ≈ 1.24 kHz ✓)

Applications: clock generation, LED/lamp flasher, tone generation, FSK modulator, voltage-controlled oscillator via pin 5, ramp generation.

556 = dual 555; **7555** = CMOS 555 (µA-level supply current, up to 2 MHz).

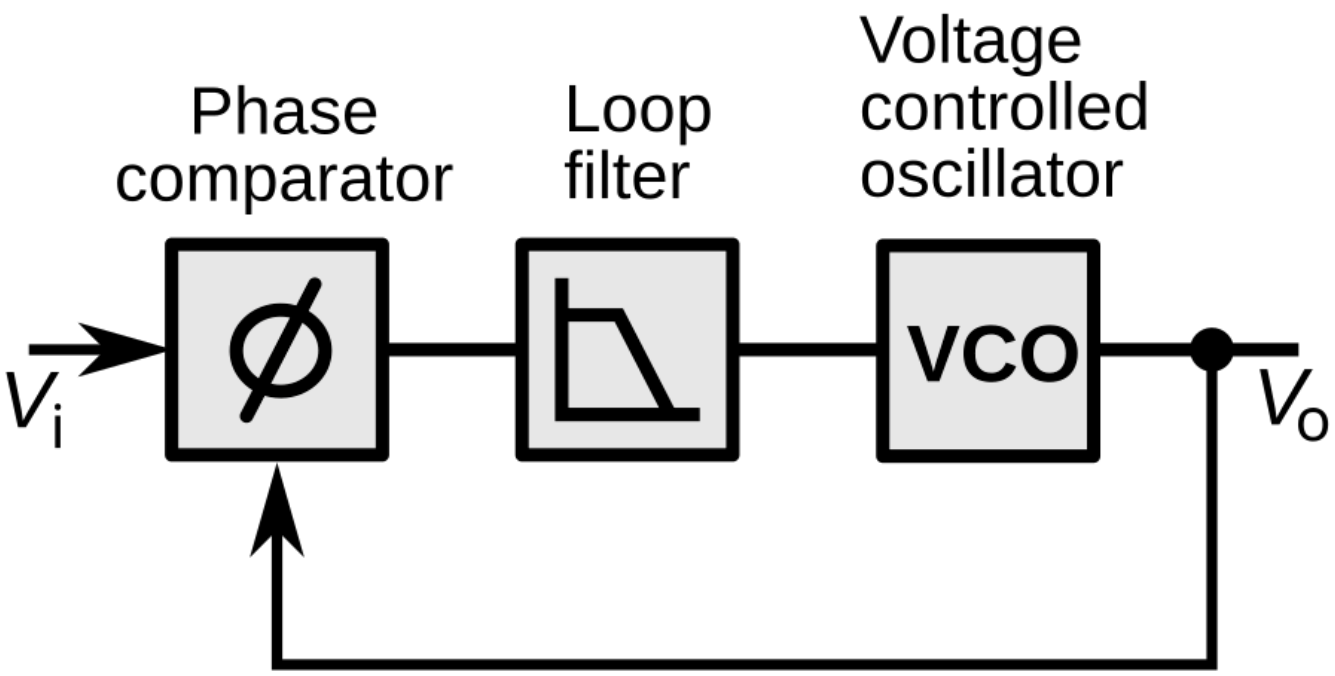4.7 Phase-Locked Loop (PLL) — in depth ★ (also feeds Communication unit)



Phase-locked loop (PLL) block diagram.

A PLL is a **negative-feedback frequency/phase control system** that locks an internal oscillator's frequency *and phase* to an incoming signal.

4.7.1 Block diagram ★

```
f_in ──►[ Phase Detector / Comparator ]──►[ Low-Pass Filter ]──►[ Error Amplifier ]──┬──► V_c (control voltage)
                  ▲                                                                  │
                  └──────────────────[ VCO ]◄────────────────────────────────────────┘
                                     f_out (fed back)
```

Block	Function
Phase detector (PD)	Multiplies/compares f_{in} with VCO output; produces error voltage ∝ **phase difference** (plus sum-frequency terms)
Low-pass filter (LPF)	Removes high-frequency components of the PD output, leaves DC error; **its bandwidth sets the capture range** and loop dynamics
Error amplifier	Amplifies the DC error voltage
VCO	Free-runs at f_0 (centre frequency); output frequency shifts in proportion to control voltage V_c: f = f_0 + K_VV_c

Operation states: free-running (no input; VCO at f_0) → **capture** (loop pulling VCO toward f_{in}) → **locked/tracking** (f_{VCO} = f_{in} exactly; only a small static phase difference — ideally 90° for an analog multiplier PD — remains, generating the needed V_c).

4.7.2 Lock range vs capture range ★

	Lock (tracking) range Δf_L	Capture (acquisition) range Δf_C
Meaning	Band over which PLL, **once locked**, can *stay* locked as f_{in} drifts	Band over which an **unlocked** PLL can *acquire* lock
Determined by	PD gain, amplifier gain, VCO gain (loop DC gain)	Mainly **LPF bandwidth** (+ loop gain)
Relation	**Δf_C ≤ Δf_L** — capture range is always the smaller, both centred on f_0	

For the IC 565: lock range **$f_L = \pm 8 f_0 / V$** (V = total supply $V^+ - V^-$); capture range **$f_C = \pm\sqrt{f_L / (2\pi \cdot (3.6 \times 10^3) \cdot C)}$**, C = LPF capacitor. Pull-in time decreases with wider LPF.

4.7.3 Applications ★★ (asked under Communication in 2025)

1. **FM demodulation (most-asked):** locked PLL forces the VCO to track the FM input's instantaneous frequency; the **VCO control voltage V_c is therefore a replica of the original modulating signal — V_c itself is the demodulated output**. Linear, needs no tuned circuits — the standard IC FM detector.
2. **AM detection (synchronous/coherent):** PLL locks to the AM carrier and regenerates it; the regenerated carrier (phase-shifted 90° back to 0°) multiplies the AM signal in a separate mixer; the LPF output is the envelope. Superior noise performance vs diode envelope detector.
3. **Frequency synthesis / multiplication:** insert a **÷N counter** in the feedback path between VCO and PD ⇒ lock forces f_{VCO}/N = f_{in} ⇒ **f_{out} = N·f_{in}**. A programmable N gives many crystal-stable channels from one reference — used in every synthesised receiver/transmitter. (Divide the *input* instead ⇒ frequency division; harmonic locking also multiplies.)
4. **FSK demodulation:** FSK's two frequencies produce two distinct DC levels at the PLL error output; a comparator restores the binary data (e.g. 1070/1270 Hz modem tones).
5. **Others:** carrier recovery, clock recovery from data, bit synchronisation, tone decoding (IC 567), motor speed control, frequency translation.

4.7.4 IC 565 basics

- Monolithic PLL, 14-pin; usable to **~500 kHz**; supply ±6 V to ±12 V.

- Contains PD (analog multiplier type), error amplifier, and a highly linear VCO; the **LPF is external** (internal 3.6 kΩ resistor + external capacitor C to supply).
- **Free-running frequency: $f_0 = 1.2/(4R_1C_1) = 0.3/(R_1C_1)$** ($R_1$, C_1 = external timing components; 2 kΩ ≤ R_1 ≤ 20 kΩ recommended).
- VCO output (pin 4) is externally connected to PD input (pin 5) — the break lets you insert a ÷N counter for synthesis.
- Related ICs: **NE566** = VCO only; **NE567** = PLL tone decoder.

WE-11 (565 free-running frequency). R_1 = 10 kΩ, C_1 = 0.01 µF:

$f_0 = 0.3/(10^4 \times 10^{-8}) = 0.3/10^{-4}$ = **3 kHz**. With V_{total} = 12 V, lock range f_L = ±8(3000)/12 = **±2 kHz** (i.e. 1 kHz–5 kHz).

WE-12 (Schmitt trigger trip points). Inverting Schmitt: R_1 = 10 kΩ (to ground), R_2 = 90 kΩ (to output), V_{sat} = ±13 V.

β = 10/(10+90) = 0.1 ⇒ UTP = +1.3 V, LTP = −1.3 V, hysteresis = **2.6 V**. A noisy sine of 0.5 V ripple riding on the signal cannot false-trigger (0.5 V < 2.6 V).

4.8 PYQ Corner — actual 22-04-2025 CBT-2 questions, fully solved

PYQ 1 (2025). *In the internal block diagram of IC 741 op-amp, the second stage is:*

(a) Input differential amplifier (b) **Intermediate (gain) stage** (c) Complementary push-pull output stage (d) Class-B amplifier stage

Solution. 741 stage order: **input differential stage → intermediate/gain stage → level shifter → push-pull output**. The second stage is the **intermediate gain stage** — a dual-input *unbalanced*-output differential amplifier providing most additional gain (some texts merge it with the level shifter and call it the "level-shift and gain" stage). **Answer: (b).**

PYQ 2 (2025). *The output of an op-amp integrator is:*

(a) Proportional to the derivative of the input (b) Equal to the input (c) **Proportional to the integral of the input** (d) Proportional to the logarithm of the input

Solution. With C in feedback and R at the inverting input, the virtual ground gives $I = V_{in}/R = -C\,dV_0/dt \Rightarrow$ **$V_0 = -(1/RC)\int V_{in}\,dt$**. Output ∝ (negative) integral of input; a square-wave input yields a triangular output. **Answer: (c).**

PYQ 3 (2025, asked under Communication — PLL-framed). *In a PLL used as an FM demodulator, the demodulated output is taken from:*

(a) VCO output (b) Phase-detector direct output (c) **Error/control voltage applied to the VCO (after the LPF)** (d) The feedback divider

Solution. In lock, the VCO exactly tracks the FM signal's instantaneous frequency; the control voltage that steers the VCO must therefore vary exactly as the modulating signal did ⇒ **V_c (LPF/error-amp output) = demodulated audio**. **Answer: (c).**

PYQ 4 (2025, Communication-framed). *The capture range of a PLL is:*

(a) Always greater than the lock range (b) **Always less than or equal to the lock range and decided mainly by the LPF bandwidth** (c) Independent of the LPF (d) Equal to the VCO free-running frequency

Solution. An unlocked loop must pass the beat (difference) frequency through the LPF to develop a pull-in voltage — so a narrower LPF ⇒ smaller capture range. Once locked, the PD output is near-DC and passes regardless, so tracking (lock) extends further: **$\Delta f_C \le \Delta f_L$**, both centred on f_0. **Answer: (b).**

4.9 Practice MCQs (20)

1. In a monolithic IC, all components are fabricated on:

(a) separate substrates (b) a single silicon chip (c) a ceramic film (d) a PCB

2. The first (input) stage of IC 741 is a:

(a) push-pull amplifier (b) level shifter (c) dual-input balanced-output differential amplifier (d) class-C amplifier

3. The purpose of the level-shifting stage in 741 is to:

(a) increase gain (b) shift the DC level so the output swings about 0 V (c) increase bandwidth (d) reduce noise

4. An ideal op-amp has:

(a) zero input resistance (b) infinite output resistance (c) infinite CMRR (d) finite bandwidth

5. The slew rate of IC 741 is approximately:

(a) 0.5 V/µs (b) 5 V/µs (c) 50 V/µs (d) 0.5 V/ms

6. In an inverting amplifier, the inverting input terminal is at virtual ground because:

(a) it is wired to ground (b) A is very large with negative feedback so $V_- \approx V_+ = 0$ (c) input resistance is zero (d) output is zero

7. For R_1 = 1 kΩ, R_f = 10 kΩ, the non-inverting amplifier gain is:

(a) −10 (b) 10 (c) 11 (d) −11

8. A voltage follower is chiefly used for:

(a) high voltage gain (b) impedance matching / buffering (c) phase inversion (d) rectification

9. A square wave applied to an op-amp integrator produces:

(a) spikes (b) a sine wave (c) a triangular wave (d) a square wave

10. A triangular wave applied to an op-amp differentiator produces:

(a) a square wave (b) a triangular wave (c) a ramp (d) a sine wave

11. In a practical integrator, a resistor R_f is connected across C to:

(a) increase gain at all frequencies (b) limit the DC gain and prevent output saturation (c) make it a differentiator (d) improve slew rate

12. A zero-crossing detector converts a sine input into:

(a) a triangular wave (b) a square wave (c) a DC level (d) spikes

13. In an op-amp Schmitt trigger with V_{sat} = ±12 V, R_1 = 1 kΩ (to ground), R_2 = 5 kΩ (to output), the hysteresis is:

(a) 2 V (b) 4 V (c) 12 V (d) 1 V

14. A precision rectifier can rectify signals smaller than 0.7 V because:

(a) it uses Schottky diodes (b) the diode is inside the feedback loop, dividing its drop by the open-loop gain (c) it uses a transformer (d) the op-amp saturates

15. In a Wien-bridge oscillator using an op-amp, the minimum amplifier gain and R_f/R_1 ratio are:

(a) 3 and 2 (b) 2 and 3 (c) 29 and 28 (d) 1 and 0

16. The dropout voltage of a 7805 regulator is about:

(a) 0.2 V (b) 2 V (c) 5 V (d) 7 V

17. For an LM317 with R_1 = 240 Ω and R_2 = 1.2 kΩ, the output voltage is:

(a) 1.25 V (b) 6.25 V (c) 7.5 V (d) 5 V

18. In a 555 astable circuit, the capacitor discharges through:

(a) R_A only (b) R_A + R_B (c) R_B only (via the discharge pin) (d) the output pin

19. A 555 monostable with R = 100 kΩ and C = 10 µF gives a pulse width of about:

(a) 0.11 s (b) 1.1 s (c) 11 s (d) 1.44 s

20. In a PLL frequency synthesiser, a ÷N counter placed between the VCO and the phase detector makes the output frequency:

(a) f_{in}/N (b) N·f_{in} (c) f_{in} (d) f_0/N

Answer key with brief explanations

Q	Ans	Why
1	b	Monolithic = "single stone": everything diffused into one silicon chip
2	c	Input stage = dual-input, balanced-output diff amp (high Z_{in}, high CMRR)
3	b	Direct coupling builds up DC; the level translator restores 0 V quiescent output
4	c	Ideal: $A = \infty$, $R_{in} = \infty$, $R_{out} = 0$, BW = ∞, CMRR = ∞
5	a	741 SR ≈ 0.5 V/μs — its main speed limitation
6	b	Virtual short with (+) grounded ⇒ $V_- \approx 0$ without a physical ground
7	c	$A = 1 + R_f/R_1 = 1 + 10 = 11$
8	b	Unity gain, Z_{in} huge, $Z_{out} \approx 0$ ⇒ buffer
9	c	Integral of a constant = ramp; alternating ramps = triangle
10	a	Derivative of the triangle's constant slopes = alternating constants = square
11	b	R_f makes DC gain finite ($-R_f/R$) so offset can't integrate to saturation
12	b	Output flips between $\pm V_{sat}$ at each zero crossing
13	b	$V_H = 2V_{sat}R_1/(R_1+R_2) = 2\times12\times1/6 = 4$ V
14	b	Effective diode drop ≈ 0.7/A ≈ microvolts
15	a	Wien network feeds back 1/3 at f_0 ⇒ gain 3 ⇒ $R_f = 2R_1$
16	b	78xx needs ≈ 2 V input–output headroom
17	c	$V_0 = 1.25(1 + 1200/240) = 1.25\times6 = 7.5$ V
18	c	Discharge path: C → R_B → pin 7 transistor → ground
19	b	$T = 1.1RC = 1.1\times10^{5}\times10^{-5} = 1.1$ s
20	b	Lock forces $f_{VCO}/N = f_{in}$ ⇒ $f_{out} = N \cdot f_{in}$

4.10 Rapid-Revision Formula Sheet

Op-amp basics

- $V_0 = A(V_+ - V_-)$; 741: $A \approx 2\times10^5$, $R_{in} \approx 2$ MΩ, $R_{out} \approx 75$ Ω, SR ≈ 0.5 V/µs, GBW ≈ 1 MHz, CMRR ≈ 90 dB
- 741 stages: **Input diff amp → Intermediate gain → Level shifter → Push-pull output ★**
- CMRR (dB) = $20 \log(A_d/A_{cm}) \cdot f_{max} = SR/(2\pi V_m) \cdot BW_{CL} = GBW/A_{CL}$
- Golden rules (with −ve feedback): $V_+ = V_-$ (virtual short); input currents = 0

Linear circuits

Circuit	Output
Inverting amp	$V_0 = -(R_f/R_1)V_{in}$
Non-inverting amp	$V_0 = (1 + R_f/R_1)V_{in}$
Follower	$V_0 = V_{in}$ (buffer)
Inverting summer	$V_0 = -R_f(V_1/R_1 + V_2/R_2 + \ldots)$
Difference amp	$V_0 = (R_2/R_1)(V_2 - V_1)$
Instrumentation amp	$V_0 = (1 + 2R/R_G)(V_2 - V_1)$
Integrator ★	$V_0 = -(1/RC)\int V_{in}dt$ (square → triangle)
Differentiator	$V_0 = -RC \cdot dV_{in}/dt$ (triangle → square)
I→V converter	$V_0 = -I_{in}R_f$
V→I converter	$I_L = V_{in}/R_1$ (load-independent)

Non-linear / filters / oscillators

- Schmitt: $UTP/LTP = \pm V_{sat}R_1/(R_1+R_2)$; hysteresis $= 2V_{sat}R_1/(R_1+R_2)$
- Op-amp astable: $T = 2RC \ln((1+\beta)/(1-\beta))$; $\beta = 0.5 \Rightarrow T \approx 2.2RC$
- Wien bridge: $f_0 = 1/(2\pi RC)$; gain = 3 ($R_f = 2R_1$) · Phase-shift: $f_0 = 1/(2\pi RC\sqrt{6})$, gain 29
- Filters: $f_c = 1/(2\pi RC)$; 1st order 20 dB/dec, 2nd order 40 dB/dec; Butterworth = maximally flat (2nd-order S-K gain 1.586); $f_0(BP) = \sqrt{(f_L f_H)}$, $Q = f_0/BW$

Regulators

- 78xx = +ve fixed, 79xx = −ve fixed; dropout ≈ 2 V; pins 78xx: In-Gnd-Out; 79xx: Gnd-In-Out
- LM317: **$V_0 = 1.25(1 + R_2/R_1)$** ★; range 1.25–37 V; LM337 = negative twin
- 723: reference 7.15 V, 2–37 V adjustable, foldback limiting
- SMPS: buck $V_0 = DV_{in}$; boost $V_0 = V_{in}/(1-D)$; efficiency 70–95% vs linear 30–60%

555 timer ★

- Thresholds: trigger < $(1/3)V_{CC}$ → HIGH; threshold > $(2/3)V_{CC}$ → LOW; three 5 kΩ divider resistors
- Monostable: **$T = 1.1\ RC$**
- Astable: $t_H = 0.693(R_A + R_B)C$; $t_L = 0.693R_BC$; **$f = 1.44/((R_A+2R_B)C)$**; $D = (R_A+R_B)/(R_A+2R_B) > 50\%$

PLL ★

- Blocks: **Phase detector → LPF → Error amp → VCO** (feedback to PD)
- Capture range ≤ lock range; capture set by LPF bandwidth; both centred on f_0
- FM demodulation: **output = VCO control voltage** ★
- ÷N in feedback ⇒ f_{out} = N·f_{in} (synthesis) · FSK: two frequencies → two DC levels → comparator
- IC 565: $f_0 = 0.3/(R_1C_1) = 1.2/(4R_1C_1)$; f_L = $\pm 8f_0/V$; NE566 = VCO, NE567 = tone decoder

---

End of Chapter 4. Next: Chapter 5 — Microprocessor & Microcontroller (8085/8051).

Chapter 5 — Microprocessor and Microcontroller

RRB JE CBT-2 · Electronics & Allied Engineering (CEN 05/2025, Annexure-VII C) · Syllabus Unit 5

> **Unit coverage:** Introduction to microprocessor · 8085 microprocessor working · Assembly Language programming · Peripherals & other microprocessors · Microcontrollers.

📊 Weightage & Trend Box

Parameter	Detail
Approx. weight	**~8% of technical marks (≈ 4 out of 50 questions)** in the 22-04-2025 CBT-2 paper
Difficulty	Easy–Moderate; mostly single-concept, formula/fact recall + one small program trace
Best scoring areas	8085 program tracing, interrupt facts, 8051 basic architecture, DMA handshake

Questions actually observed in the 22-04-2025 CBT-2 paper (solved fully in the PYQ Corner):

1. **8085 program trace:** `MVI B, 06H` → `MVI A, F2H` → `ADD B` — what is the accumulator content? *(Answer: F2H + 06H = **F8H**)*
2. **8051 register banks:** How many register banks does the 8051 have? *(Answer: **four**, each with R0–R7)*
3. **8085 interrupts:** Which interrupt is **positive-edge-triggered**? *(Answer: **RST 7.5**)*
4. **DMA:** When is the **DACK** (DMA acknowledge) signal issued in a DMA transfer? *(Answer: after the CPU grants the bus via HLDA and the DMA controller places the address — DACK tells the peripheral the transfer cycle is starting.)*

Trend takeaways

- Every recent paper has **one small 8085 program-tracing question** (usually MVI/ADD/SUB with flag or accumulator result). Practise hex arithmetic until it is automatic.
- Interrupt facts (edge vs level trigger, vector addresses, TRAP highest priority) and 8051 basics (128 B RAM, 4 register banks, 5 interrupts, 12 clocks per machine cycle) are recycled almost verbatim.
- Peripheral chips are tested at the "one-line function" level: 8255 = PPI, 8257 = DMA, 8259 = PIC, 8279 = keyboard/display — plus one deeper question (control word or handshake) occasionally.

5.1 Introduction to Microprocessors

5.1.1 What is a microprocessor?

A **microprocessor (µP)** is a programmable, clock-driven, register-based electronic device fabricated on a single chip (VLSI) that:

1. reads binary **instructions** from memory,
2. **decodes** them, and
3. **executes** them — performing arithmetic/logic operations on data and producing results/control actions.

A microprocessor by itself is only a CPU. To make a working computer it needs **memory** (ROM + RAM), **I/O devices**, and interconnecting **buses**. The combination is a **microcomputer**:

```
Microcomputer = Microprocessor (CPU) + Memory + I/O + Buses
```

5.1.2 Basic terms you must know

Term	Meaning	8085 value
Word length	Number of bits the µP processes at a time (data bus width)	8 bits → "8-bit µP"
Address bus	Unidirectional bus carrying memory/I-O addresses	16 lines → 2^{16} = **64 KB** address space
Data bus	Bidirectional bus carrying data	8 lines
Control bus	Individual lines carrying timing/control signals (RD, WR, ALE …)	—
Clock	Fixed-frequency square wave synchronising all operations	Crystal 6.144 MHz; internal clock = crystal/2 = **3.072 MHz** (max rated internal clock of 8085A = 3 MHz class)
T-state	One period of the internal clock; smallest unit of processor timing	1/3.072 MHz ≈ 325.5 ns (with 6.144 MHz crystal)
Machine cycle	Time to complete one memory/I-O access (3–6 T-states)	e.g. opcode fetch = 4T
Instruction cycle	Time to fetch + execute one full instruction (1–5 machine cycles)	e.g. `MOV A,B` = 4T; `LDA addr` = 13T
Bit / Nibble / Byte / Word	1 bit / 4 bits / 8 bits / word-length group	—

Addressing capacity rule: an *n*-line address bus addresses **2^n** locations.


16 lines → 64 KB (8085); 20 lines → 1 MB (8086); 24 lines → 16 MB (80286).

5.1.3 Evolution snapshot (exam one-liners)

Processor	Year	Bits	Address bus	Note
Intel 4004	1971	4	12-bit	**First microprocessor**
Intel 8008	1972	8	14-bit	First 8-bit µP
Intel 8080	1974	8	16-bit	Needed +12 V, −5 V, +5 V
Intel 8085	1976	8	16-bit	Single **+5 V** supply, on-chip clock, serial I/O
Intel 8086	1978	16	20-bit	First x86; segmentation, pipelining
Intel 8088	1979	16 (8-bit ext. data bus)	20-bit	Used in IBM PC
80286 / 386 / 486 / Pentium	1982→	16/32	24/32-bit	Protected mode, cache, superscalar


RISC vs CISC (quick): CISC (8085, 8086, x86) — many complex variable-length instructions, microprogrammed control. RISC (ARM, AVR, PIC newer cores) — few fixed-length instructions, load–store architecture, hardwired control, one instruction ≈ one cycle.

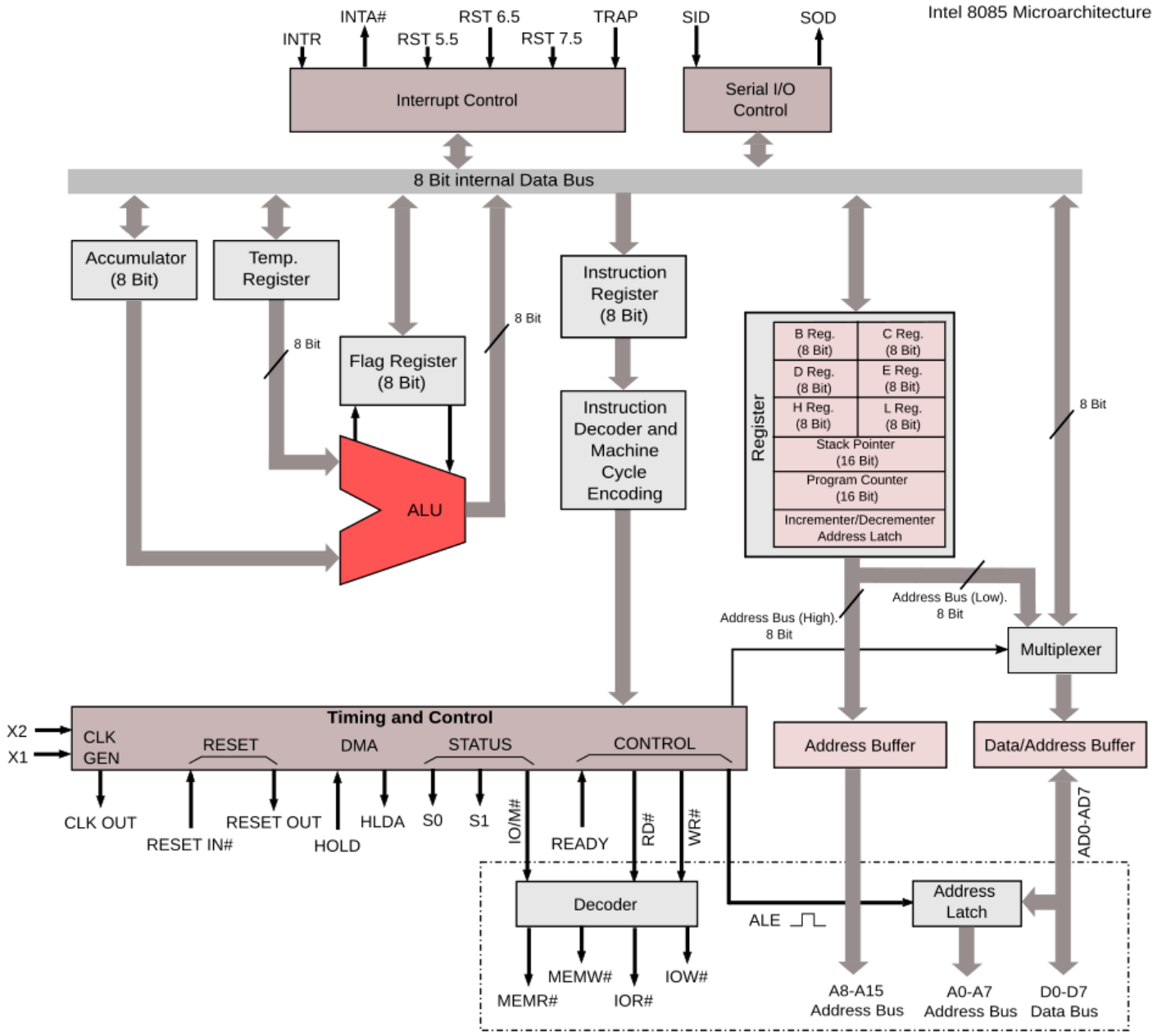5.2 Intel 8085 — Architecture (Block Diagram)



Intel 8085 internal architecture.

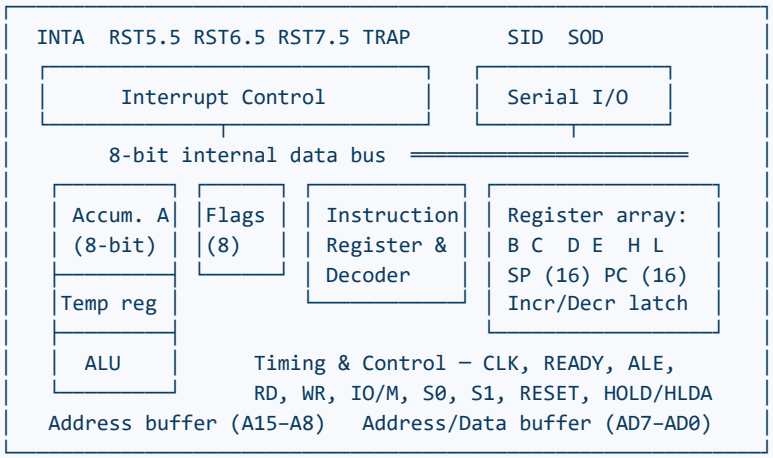The 8085 is an **8-bit, 40-pin DIP, NMOS** microprocessor running on a **single +5 V** supply. Its functional blocks:



5.2.1 ALU

Performs 8-bit **arithmetic** (add, subtract, increment, decrement, decimal adjust) and **logic** (AND, OR, XOR, complement, compare, rotate). Inputs: **Accumulator** and **Temporary register**; result normally goes back to the accumulator; **flags** are updated.

5.2.2 Register set

Register	Size	Role
A (Accumulator)	8-bit	One operand and destination of most ALU operations; used for I/O (`IN` / `OUT`)
B, C, D, E, H, L	8-bit each	General-purpose; usable in pairs **BC, DE, HL** as 16-bit registers
HL	16-bit pair	Default **memory pointer** — the operand "M" means the byte at address (HL)
PC (Program Counter)	16-bit	Holds address of the **next instruction byte** to be fetched
SP (Stack Pointer)	16-bit	Holds address of the **top of stack**; stack grows **downward** (toward lower addresses)
Instruction Register	8-bit	Holds the opcode currently being decoded (not programmer-accessible)
Temp / W / Z	8-bit	Internal scratch registers (not programmer-accessible)

5.2.3 Flag register (PSW low byte)

```
Bit:   D7   D6   D5   D4   D3   D2   D1   D0
Flag:  S    Z    x    AC   x    P    x    CY
```

Only **5 flags** are defined (D5, D3, D1 unused):

Flag	Name	Set (=1) when…
S	Sign	Bit D7 of the result is 1 (result negative in 2's-complement sense)
Z	Zero	Result is exactly 00H
AC	Auxiliary Carry	A carry propagates from bit D3 to bit D4 (used by `DAA` for BCD)
P	Parity	Result has an **even number of 1s** (even parity → P = 1)
CY	Carry	An arithmetic **carry out of D7** (add) or a **borrow** (subtract) occurs; also affected by rotate-through-carry instructions

> **Exam rules:** `INR` / `DCR` affect **all flags except CY**. Logical `ANA` sets CY = 0 and **AC = 1**; `ORA` / `XRA` set CY = 0 and AC = 0. `CMP` / `SUB` set CY = 1 when A < operand (borrow). Data-transfer instructions (`MOV` , `MVI` , `LXI` , `LDA` …) affect **no flags**.

5.2.4 Multiplexed bus and demultiplexing with ALE

To fit in 40 pins, the **low-order address byte A7–A0 shares pins with the data bus D7–D0**, called **AD7–AD0**.

- During **T1** of every machine cycle the pins carry the address low byte and **ALE (Address Latch Enable)** goes **high**.
- The falling edge of ALE clocks an external latch (**74LS373/8212**) that captures A7–A0.
- From T2 onward the same pins carry **data**.

A15–A8 are on dedicated pins throughout the cycle.

5.2.5 Control & status signals

Signal	Type	Meaning
ALE	Out	High pulse in T1; latch low address
RD̄	Out, active low	Read strobe — data valid on bus while low
WR̄	Out, active low	Write strobe
IO/M̄	Out	**1 = I/O operation, 0 = memory operation**
S1, S0	Out	Machine-cycle status (see table)
READY	In	Low ⇒ 8085 inserts **wait states** (slow memory/peripheral)
HOLD / HLDA	In / Out	DMA bus request / bus grant acknowledgement
RESET IN̄ / RESET OUT	In / Out	Reset: PC ← 0000H, buses tristated / reset for peripherals
CLK OUT	Out	System clock (crystal/2) for peripherals
X1, X2	In	Crystal connections

Status combinations:

IO/M̄	S1	S0	Machine cycle
0	1	1	**Opcode fetch**
0	1	0	Memory read
0	0	1	Memory write
1	1	0	I/O read
1	0	1	I/O write
1	1	1	Interrupt acknowledge
—	0	0	Halt

5.2.6 8085 pin summary (40-pin DIP)

- **Address:** A15–A8 (pins 21–28), AD7–AD0 (pins 12–19)
- **Control:** ALE(30), RD̄(32), WR̄(31), IO/M̄(34), S0(29), S1(33), READY(35)
- **Interrupts:** TRAP(6), RST 7.5(7), RST 6.5(8), RST 5.5(9), INTR(10), INTĀ(11)
- **Serial:** SID(5), SOD(4)
- **DMA:** HOLD(39), HLDA(38)
- **Clock/Reset:** X1(1), X2(2), CLK OUT(37), RESET IN̄(36), RESET OUT(3)
- **Power:** Vcc +5 V(40), Vss(20)

5.3 Instruction Cycle, Machine Cycles & T-States

Instruction cycle = Fetch + Decode + Execute. Each instruction takes **1 to 5 machine cycles**; each machine cycle takes **3 to 6 T-states**.

Machine cycle	T-states	Notes
Opcode fetch (OF)	**4T** (6T for `CALL`-class first cycle)	Only cycle with 4T minimum: T4 used for decoding
Memory read (MR)	3T	Fetch operand/address bytes
Memory write (MW)	3T	Store to memory
I/O read (IOR)	3T	`IN port`
I/O write (IOW)	3T	`OUT port`
Interrupt acknowledge (INA)	6T	For INTR response
Bus idle (BI)	2–3T	e.g. internal cycles of `DAD`

Timings of common instructions (memorise):

Instruction	Bytes	Machine cycles	T-states
`MOV r, r`	1	1 (OF)	**4T**
`MOV r, M` / `MOV M, r`	1	2 (OF + MR/MW)	**7T**
`MVI r, data`	2	2 (OF + MR)	**7T**
`MVI M, data`	2	3	10T
`LXI rp, data16`	3	3 (OF + 2 MR)	**10T**
`LDA addr`	3	4 (OF + 2 MR + MR)	**13T**
`STA addr`	3	4 (OF + 2 MR + MW)	**13T**
`ADD r`	1	1	4T
`ADD M`	1	2	7T
`INX rp` / `DCX rp`	1	1 (6T OF)	**6T**
`DAD rp`	1	3 (OF + 2 BI)	**10T**
`JMP addr`	3	3	**10T**
Conditional jump	3	2/3	**7T (false) / 10T (true)**
`CALL addr`	3	5	**18T**
`RET`	1	3	**10T**
`PUSH rp`	1	3	**12T**
`POP rp`	1	3	**10T**
`RST n`	1	3	12T
`XCHG`	1	1	4T
`NOP`	1	1	4T
`HLT`	1	1+	5T

Opcode-fetch timing (4T):

T1 — ALE high, AD bus = A7–A0, A15–A8 out, IO/$\bar{M}$=0 S1=1 S0=1.

T2 — $\bar{RD}$ low, memory places opcode on bus.

T3 — opcode latched into IR, $\bar{RD}$ high.

T4 — opcode decoded internally (bus idle).

5.4 Addressing Modes of the 8085

Mode	Operand location	Examples
Immediate	Inside the instruction itself	`MVI A, 32H` ; `ADI 47H` ; `LXI H, 2500H`
Register	In a CPU register	`MOV A, B` ; `ADD C` ; `XCHG`
Direct	16-bit address given in the instruction	`LDA 2050H` ; `STA 3000H` ; `IN 01H`
Register indirect	Address held in a register pair (usually HL)	`MOV A, M` ; `LDAX B` ; `STAX D`
Implied / Implicit	Operand implied by the opcode (usually A)	`CMA` ; `RLC` ; `DAA` ; `EI` ; `NOP`

> **Note:** The 8085 has **no indexed or relative addressing** (those appear in 8086/8051).

5.5 8085 Instruction Set — Group by Group

Total **246 opcodes / 74 instruction types**. Instruction lengths: 1-byte, 2-byte (opcode + data/port), 3-byte (opcode + 16-bit address/data).

5.5.1 Data transfer group (no flags affected)

Instruction	Action
`MOV rd, rs`	rd ← rs
`MOV r, M` / `MOV M, r`	register ↔ memory (HL)
`MVI r, d8` / `MVI M, d8`	Load immediate byte
`LXI rp, d16`	Load register pair immediate (BC/DE/HL/SP)
`LDA a16` / `STA a16`	A ↔ memory[direct address]
`LHLD a16` / `SHLD a16`	HL ↔ two memory bytes (L from a16, H from a16+1)
`LDAX B/D` / `STAX B/D`	A ↔ memory[(BC) or (DE)]
`XCHG`	HL ↔ DE
`IN p8` / `OUT p8`	A ↔ I/O port

5.5.2 Arithmetic group

Instruction	Action	Flags
`ADD r/M`	A ← A + operand	all
`ADI d8`	A ← A + immediate	all
`ADC r/M` / `ACI d8`	A ← A + operand + CY	all
`SUB r/M` / `SUI d8`	A ← A − operand	all (CY = borrow)
`SBB r/M` / `SBI d8`	A ← A − operand − CY	all
`INR r/M`	operand + 1	**all except CY**
`DCR r/M`	operand − 1	**all except CY**
`INX rp` / `DCX rp`	16-bit ±1	**no flags**
`DAD rp`	HL ← HL + rp	**only CY**
`DAA`	Decimal-adjust A after BCD addition	all

DAA rule: if lower nibble > 9 or AC = 1 → add 06H; if upper nibble > 9 or CY = 1 → add 60H.

5.5.3 Logical group

Instruction	Action	CY, AC after
`ANA r/M`, `ANI d8`	A ← A AND op	CY = 0, **AC = 1**
`ORA r/M`, `ORI d8`	A ← A OR op	CY = 0, AC = 0
`XRA r/M`, `XRI d8`	A ← A XOR op	CY = 0, AC = 0
`CMA`	A ← $\bar{A}$ (complement)	**no flags**
`CMC` / `STC`	CY ← $\bar{CY}$ / CY ← 1	only CY
`CMP r/M`, `CPI d8`	A − op (result discarded)	A < op ⇒ CY=1; A = op ⇒ Z=1; A > op ⇒ CY=0, Z=0
`RLC`	Rotate A left; D7 → D0 **and** → CY	only CY
`RRC`	Rotate A right; D0 → D7 and → CY	only CY
`RAL`	Rotate A left **through carry** (CY → D0, D7 → CY)	only CY
`RAR`	Rotate A right through carry	only CY

> `XRA A` is the standard trick to **clear the accumulator and CY** in one byte (also sets Z = 1, P = 1).

5.5.4 Branch group

Instruction	Condition
`JMP a16`	Unconditional
`JC` / `JNC`	CY = 1 / CY = 0
`JZ` / `JNZ`	Z = 1 / Z = 0
`JP` / `JM`	S = 0 (plus) / S = 1 (minus)
`JPE` / `JPO`	P = 1 (even) / P = 0 (odd)
`CALL a16` (+ conditional CC, CNC, CZ, CNZ, CP, CM, CPE, CPO)	Push PC on stack, jump
`RET` (+ conditional RC, RNC, RZ, RNZ, RP, RM, RPE, RPO)	Pop PC from stack
`PCHL`	PC ← HL (computed jump)
`RST 0…7`	1-byte call to vector **n × 8** (RST 5 → 0028H, RST 7 → 0038H)

5.5.5 Stack & machine-control group

Instruction	Action
`PUSH B/D/H/PSW`	(SP−1) ← high byte, (SP−2) ← low byte, SP ← SP − 2
`POP B/D/H/PSW`	low ← (SP), high ← (SP+1), SP ← SP + 2
`XTHL`	Exchange HL with top of stack
`SPHL`	SP ← HL
`EI` / `DI`	Enable / disable interrupts (set/clear INTE flip-flop)
`SIM`	**Set Interrupt Mask** + send serial output bit (uses A)
`RIM`	**Read Interrupt Mask** + read serial input bit (into A)
`HLT`	Halt CPU until interrupt or reset
`NOP`	No operation (4T delay / patching)

PSW = A (high byte) + Flags (low byte) when pushed/popped.

5.6 Assembly Language Programming — Worked Programs

Program 1 — 8-bit addition of two memory bytes

```
; Add bytes at 2050H and 2051H, store sum at 2052H, carry at 2053H
        LXI H, 2050H    ; HL points to first number
        MOV A, M        ; A <- (2050H)
        INX H           ; HL = 2051H
        MOV B, M        ; B <- (2051H)
        MVI C, 00H      ; carry counter = 0
        ADD B           ; A <- A + B
        JNC SKIP        ; no carry? skip
        INR C           ; record carry
SKIP:   INX H           ; HL = 2052H
        MOV M, A        ; store sum
        INX H
        MOV M, C        ; store carry
        HLT
```

Program 2 — 8-bit subtraction (with borrow indication)

```
; (2050H) - (2051H) -> 2052H ; CY = 1 indicates a borrow
        LDA 2050H       ; A <- minuend
        MOV B, A        ; save minuend in B
        LDA 2051H       ; A <- subtrahend
        MOV C, A        ; save subtrahend in C
        MOV A, B        ; A <- minuend
        SUB C           ; A <- minuend - subtrahend ; CY=1 if borrow
        STA 2052H       ; store difference
        HLT
```

Program 3 — Largest number in an array

```
; Array of N bytes starting at 2501H, count N at 2500H; result to 2600H
        LXI H, 2500H
        MOV C, M        ; C = count
        INX H
        MOV A, M        ; A = first element (current max)
        DCR C
LOOP:   INX H
        CMP M           ; compare A with next element
        JNC NEXT        ; A >= M ? keep A
        MOV A, M        ; else new max
NEXT:   DCR C
        JNZ LOOP
        STA 2600H
        HLT
```

Program 4 — Block transfer of 10 bytes (2001H → 3001H)

```
        MVI C, 0AH      ; counter = 10
        LXI H, 2001H    ; source pointer
        LXI D, 3001H    ; destination pointer
LOOP:   MOV A, M        ; read source byte
        STAX D          ; write to (DE)
        INX H
        INX D
        DCR C
        JNZ LOOP
        HLT
```

Program 5 — Count number of 1s in a byte

```
; Byte at 2050H; count of set bits -> 2051H
        LDA 2050H
        MVI B, 00H      ; ones counter
        MVI C, 08H      ; 8 bits to test
AGAIN:  RLC             ; rotate left, D7 -> CY
        JNC ZERO
        INR B
ZERO:   DCR C
        JNZ AGAIN
        MOV A, B
        STA 2051H
        HLT
```

Program 6 — Software delay loop (see Worked Example 5 for the calculation)

```
DELAY:  MVI C, FFH      ; 7T
LOOP:   DCR C           ; 4T
        JNZ LOOP        ; 10T taken / 7T last pass
        RET             ; 10T
```

Program 7 — 16-bit addition using DAD

```
; (2050H,2051H) + (2052H,2053H) -> (2054H,2055H)   [low byte first]
        LHLD 2050H      ; HL <- first 16-bit number
        XCHG            ; DE <- first number
        LHLD 2052H      ; HL <- second number
        DAD D           ; HL <- HL + DE, CY set on overflow
        SHLD 2054H
        HLT
```

5.7 8085 Interrupts

An **interrupt** is a hardware/software signal that suspends the main program and transfers control to a service routine (ISR).

5.7.1 The five hardware interrupts (priority order)

Interrupt	Priority	Trigger	Vector address	Maskable?
TRAP (RST 4.5)	1 (highest)	**Edge AND level** (rising edge, then held high)	**0024H**	**Non-maskable** (only disabled by reset/HLT states)
RST 7.5	2	**Positive (rising) edge-triggered**; latched by internal flip-flop	**003CH**	Maskable (SIM M7.5)
RST 6.5	3	**Level (high)** triggered	**0034H**	Maskable (SIM M6.5)
RST 5.5	4	**Level (high)** triggered	**002CH**	Maskable (SIM M5.5)
INTR	5 (lowest)	Level triggered	**No fixed vector** — external device supplies an instruction (usually `RST n` or `CALL`) during INTĀ cycle	Maskable by `DI`

Vector formula for software RST n: vector = **n × 0008H**. For the "half" interrupts: RST 5.5 → 5.5 × 8 = 44 = **002CH**, RST 6.5 → 52 = **0034H**, RST 7.5 → 60 = **003CH**, TRAP (4.5) → 36 = **0024H**.

> **PYQ fact:** RST 7.5 is the **only purely positive-edge-triggered** interrupt of the 8085. Because it is latched internally, a momentary pulse is remembered until served or reset (via SIM bit R7.5 or RESET).

5.7.2 SIM instruction format (contents of A before `SIM`)

```
D7    D6    D5    D4    D3    D2    D1    D0
SOD   SDE   x     R7.5  MSE   M7.5  M6.5  M5.5
```

- **M7.5/M6.5/M5.5 = 1 masks (disables)** that interrupt; effective only if **MSE = 1**.
- **R7.5 = 1** resets the RST 7.5 latch.
- **SDE = 1** enables serial output; **SOD** bit is then sent out on the SOD pin.

Example: enable only RST 6.5 → mask 7.5 & 5.5 → A = 0000 1101_2 = **0DH**, then `SIM` (after `EI`).

5.7.3 RIM instruction format (contents of A after `RIM`)

```
D7    D6    D5    D4    D3    D2    D1    D0
SID   I7.5  I6.5  I5.5  IE    M7.5  M6.5  M5.5
```

- I-bits = pending interrupts; IE = interrupt-enable flip-flop state; M-bits = current masks; SID = serial input pin level.

5.7.4 Serial I/O — SID and SOD

The 8085 has **software-driven single-line serial I/O**:

- **SID** (Serial Input Data, pin 5) read into bit D7 of A by `RIM`.
- **SOD** (Serial Output Data, pin 4) written from bit D7 of A by `SIM` (with SDE = 1).

Bit-banged serial transfer (framing, baud timing) is done entirely in software delay loops.

5.8 Memory Interfacing & Address Decoding

5.8.1 Steps

1. **Demultiplex** AD7–AD0 with ALE + 74LS373 → full 16-bit address A15–A0.
2. Generate **MEM$\bar{R}$ / MEM$\bar{W}$** from R$\bar{D}$, W$\bar{R}$ and IO/$\bar{M}$ (e.g., MEM$\bar{R}$ = R$\bar{D}$ OR IO/M).
3. **Address decoding:** low address lines go to the chip's address pins; the remaining high lines drive a decoder (74LS138) or logic gates to produce **chip select (C$\bar{S}$)**.

Lines needed by a chip: a 2^k-byte chip uses **k** address lines.

1 KB → 10 lines (A9–A0); 2 KB → 11; 4 KB → 12 (A11–A0); 8 KB → 13.

5.8.2 Worked memory map

Interface a 4 KB EPROM at 0000H and a 2 KB RAM at 3000H (see Worked Examples 6–7 for the decoding maths):

Device	Size	Address lines used	Decoded lines	Range
EPROM	4 KB	A11–A0	A15 A14 A13 A12 = 0 0 0 0	**0000H–0FFFH**
RAM	2 KB	A10–A0	A15...A11 = 0 0 1 1 0	**3000H–37FFH**

Range check: 4 KB = 1000H bytes → 0000H + 0FFFH ✓; 2 KB = 0800H bytes → 3000H + 07FFH = 37FFH ✓.

Absolute vs partial decoding: absolute decoding uses **all** unused high lines (unique map, more hardware); partial decoding ignores some lines → the device responds at **multiple (fold-back/shadow) ranges** — cheaper, used in small systems.

5.8.3 I/O interfacing: two schemes

Feature	I/O-mapped I/O (peripheral-mapped)	Memory-mapped I/O
Instructions	Only `IN p8`, `OUT p8`	All memory instructions (`MOV M`, `LDA`, `ADD M` ...)
Address size	8-bit → **256 input + 256 output ports**	16-bit (ports occupy memory space)
IO/$\bar{M}$ during access	1	0
Decoding hardware	Simpler (8 lines)	Full 16-line decode
Data transfer	Only via accumulator	Between memory-port and any register; ALU ops possible
Memory space	Fully preserved (64 KB)	Reduced by ports

5.9 Peripheral (Support) Chips

5.8.1 Intel 8255 — Programmable Peripheral Interface (PPI)

- 40-pin chip providing **24 programmable I/O lines**: **Port A**, **Port B**, **Port C** (C-upper CU + C-lower CL, 4 bits each).
- Two internal groups: **Group A** = PA + CU; **Group B** = PB + CL.
- Selected via A1 A0: 00 = Port A, 01 = Port B, 10 = Port C, 11 = **Control register**.

Operating modes

Mode	Description
Mode 0	Simple/basic I/O — no handshake; all 3 ports as plain input or output
Mode 1	**Strobed (handshake) I/O** — Ports A & B with Port C lines as handshake (STB̄, IBF, INTR / OBF̄, ACK̄)
Mode 2	**Bidirectional bus** on Port A only (with 5 Port C handshake lines); Port B may be Mode 0/1
BSR mode	Bit Set/Reset of individual **Port C** bits (control word D7 = 0)

I/O-mode control word (D7 = 1):

```
D7  D6 D5   D4   D3    D2   D1   D0
1   MA1,MA0 PA   PCU   MB   PB   PCL
|   Group A mode |     Group B mode  |
(port bit = 1 -> input, 0 -> output; MA 00=mode0 01=mode1 1x=mode2; MB 0=mode0 1=mode1)
```

Worked example: Mode 0, **PA = output, PB = input, PCU = input, PCL = output**:

D7=1, D6 D5=00, D4(PA)=0, D3(PCU)=1, D2(MB)=0, D1(PB)=1, D0(PCL)=0 → 1000 1010_2 = **8AH**.

BSR example: set bit PC3 → 0000 0111_2 = **07H** (D7=0, bits D3–D1 = 011 select PC3, D0 = 1 = set).

5.9.2 Intel 8253/8254 — Programmable Interval Timer

- **Three independent 16-bit down-counters** (Counter 0, 1, 2), each with CLK, GATE, OUT pins; max clock 8254 ≈ 8–10 MHz (8253 ≈ 2.6 MHz).
- **Six modes:** 0 = interrupt on terminal count; 1 = programmable one-shot; 2 = **rate generator (divide-by-N)**; 3 = **square-wave generator**; 4 = software-triggered strobe; 5 = hardware-triggered strobe.
- Control word selects counter, read/load format (LSB/MSB), mode, and binary/BCD counting.
- *Frequency rule:* OUT frequency = CLK frequency ÷ N (mode 2/3).

5.9.3 Intel 8257 — DMA Controller (also study 8237 conceptually)

DMA (Direct Memory Access) = high-speed data transfer between peripheral (disk, ADC) and memory **without CPU involvement in each byte**.

Handshake sequence (exam favourite):

1. Peripheral raises **DRQ (DMA request)** to the 8257 channel.
2. 8257 asserts **HRQ → HOLD** input of the 8085.
3. 8085 finishes the **current machine cycle**, tristates its buses, and replies **HLDA** (Hold Acknowledge).
4. The 8257 becomes **bus master**: it drives the address bus (its channel address register contents are placed on the bus, upper byte via an external latch) and control lines, and issues **DACK̄ (DMA acknowledge) to the requesting peripheral** — DACK works as the peripheral's chip-select, telling it the bus is granted and the memory read/write cycle is beginning.
5. Bytes transfer directly memory ↔ peripheral; the channel's 14-bit terminal counter decrements; on terminal count **TC** goes high.
6. DRQ removed → 8257 drops HRQ → 8085 regains the bus.

> **PYQ timing point: DACK is issued only after HLDA is received and the DMA controller has taken over and placed the address on the bus** — i.e., at the start of each DMA transfer cycle for that channel, not at the instant of DRQ.

- 8257: **4 channels** (CH0–CH3), each with 16-bit address register + 14-bit counter → up to **16 KB per programmed block**.
- **Transfer modes: Cycle stealing** — one byte per DMA cycle, bus returned to CPU between bytes (CPU slowed slightly); **Burst/Block mode** — whole block moved while CPU is held (fastest); (8237 also offers demand mode).

5.9.4 Intel 8259 — Programmable Interrupt Controller (PIC)

- Expands 8085/8086 interrupt capability: **8 vectored priority interrupt inputs (IR0–IR7)**; cascadable (1 master + 8 slaves) to **64 levels**.
- Contains IRR (request register), ISR (in-service), IMR (mask), priority resolver.
- Programmed with ICWs (initialisation) and OCWs (operation); supports fully-nested, rotating, and specific-mask priority schemes.
- Works with INTR/INTĀ: on INTĀ it supplies a `CALL` opcode + vector address (8085 mode) or vector type (8086 mode).

5.9.5 Intel 8279 — Programmable Keyboard/Display Interface

- Scans up to a **64-key matrix (8 × 8)** with 2-key lockout / N-key rollover; debouncing built in; 8-character **FIFO** for key codes (interrupts CPU via IRQ).
- Drives a multiplexed display of up to **16 digits** (7-segment) from internal 16 × 8 display RAM — relieves the CPU of refresh duty.

5.9.6 Other classic peripherals (one-liners)

- **8251 USART** — programmable serial communication (sync/async).
- **8155/8156** — 256-byte RAM + 22 I/O lines + 14-bit timer (companion to 8085 multiplexed bus).
- **8212/74LS373** — 8-bit latch for address demultiplexing.
- **8284 / 8288** — clock generator / bus controller for 8086.

5.10 Other Microprocessors — the 8086 in One Page

Intel 8086 (1978): first **16-bit** x86 processor.

Feature	Detail
Data bus	16-bit
Address bus	**20-bit → 1 MB** physical memory
Clock	5/8/10 MHz versions
Architecture	Split into **BIU** (Bus Interface Unit: segment registers, IP, 6-byte instruction **queue** → pipelining) and **EU** (Execution Unit: ALU, general registers, flags)
Registers	AX BX CX DX (each splittable AH/AL…), SP BP SI DI, segment CS DS SS ES, IP, 16-bit FLAGS (9 flags: CF PF AF ZF SF TF IF DF OF)
I/O space	64 K ports (16-bit port address)
Modes	Minimum (single processor) / Maximum (co-processor 8087, 8288 bus controller)

Memory segmentation: memory is accessed through 64 KB **segments**. Physical address (20-bit) is formed as:

```
Physical address = Segment register × 10H + Offset
Example: CS = 2000H, IP = 1234H  →  20000H + 1234H = 21234H
```

Segmentation allows relocatable code and separates code/data/stack.

8085 vs 8086 key differences

Point	8085	8086
Word length	8-bit	16-bit
Address bus / memory	16-bit / 64 KB	20-bit / 1 MB
Pipelining	None	6-byte prefetch queue
Multiply/Divide instructions	**No** (software only)	**Yes (MUL, DIV)**
Segmentation	No	Yes
Flags	5	9
Clock (typ.)	3 MHz	5–10 MHz
Duplicated in 8088	—	Same core, 8-bit external bus

5.11 Microprocessor vs Microcontroller

Feature	Microprocessor (8085/8086)	Microcontroller (8051)
Definition	CPU only on chip	**Computer-on-a-chip**: CPU + ROM + RAM + I/O + timers + serial port
External parts	Needs external memory & I/O chips	Mostly self-contained
Application	General-purpose computing	Embedded/dedicated control (washing machines, meters, automotive)
Instruction focus	Data processing	**Bit-manipulation** (Boolean processor) & I/O intensive
Power / cost / size	Higher	Low power, low cost, compact
Bus access	Address/data buses brought out	Buses mostly internal (P0/P2 can extend)
Registers	Few, operations register-based	More on-chip RAM; register banks
Examples	8085, 8086, Pentium, Core	8051, PIC16F, AVR ATmega, ARM Cortex-M MCUs

5.12 The 8051 Microcontroller

The Intel **8051 (MCS-51 family, 1980)** is the world's most exam-quoted 8-bit microcontroller.

5.12.1 Headline specifications (memorise)

Feature	Value
CPU	8-bit
On-chip **ROM**	**4 KB** (8031 = 0 KB, 8751 = 4 KB EPROM, 8052 = 8 KB)
On-chip **RAM**	**128 bytes** (8052 = 256 B)
Register banks	**Four banks** (Bank 0–3), each with **R0–R7**
I/O ports	**Four 8-bit ports P0–P3 = 32 I/O lines**
Timers	**Two 16-bit** timers/counters T0, T1 (8052 adds T2)
Interrupt sources	**Five** (2 external + 2 timer + 1 serial)
Serial port	Full-duplex UART (SBUF, 4 modes)
External memory	Up to 64 KB program + 64 KB data (16-bit address via P0/P2 + ALE)
Machine cycle	**12 clock periods** (e.g., 12 MHz crystal → 1 µs machine cycle)
Pins / package	40-pin DIP
Special pins	ALE, PSEN̄ (program store enable — external code fetch), EĀ (external access: 0 = ignore internal ROM), RST (active **high**, ≥ 2 machine cycles)

5.12.2 Internal RAM map (128 bytes: 00H–7FH)

Address	Contents
00H–1FH	**Four register banks × 8 bytes** (Bank0: 00–07, Bank1: 08–0F, Bank2: 10–17, Bank3: 18–1F)
20H–2FH	**Bit-addressable area** — 16 bytes = **128 individually addressable bits** (bit addresses 00H–7FH)
30H–7FH	General-purpose scratchpad / stack area (stack grows **upward**; SP reset value = **07H**)
80H–FFH (direct)	**SFR space** (ports, control registers)

Bank selection — PSW bits RS1, RS0 (PYQ fact):

RS1	RS0	Active bank	Addresses
0	0	Bank 0 (default after reset)	00H–07H
0	1	Bank 1	08H–0FH
1	0	Bank 2	10H–17H
1	1	Bank 3	18H–1FH

PSW format: `CY AC F0 RS1 RS0 OV – P` (P = parity of accumulator, updated every cycle; OV = overflow for signed arithmetic).

5.12.3 Important SFRs

A (E0H), B (F0H), PSW (D0H), SP (81H), DPTR = DPH:DPL (83H:82H), P0 (80H), P1 (90H), P2 (A0H), P3 (B0H), TMOD (89H), TCON (88H), TH0/TL0 (8CH/8AH), TH1/TL1 (8DH/8BH), SCON (98H), SBUF (99H), IE (A8H), IP (B8H), PCON (87H). SFRs whose address ends in 0H or 8H are **bit-addressable**.

5.12.4 Ports P0–P3

Port	Alternate function
P0	Multiplexed **AD7–AD0** for external memory; **open-drain** — needs external pull-ups for plain I/O
P1	Plain I/O only (8052: P1.0 = T2, P1.1 = T2EX)
P2	High address byte **A15–A8** for external memory
P3	P3.0 RXD, P3.1 TXD, P3.2 $\overline{\text{INT0}}$, P3.3 $\overline{\text{INT1}}$, P3.4 T0, P3.5 T1, P3.6 $\overline{\text{WR}}$, P3.7 $\overline{\text{RD}}$

To use a port pin as **input**, first write **1** to it (quasi-bidirectional ports).

5.12.5 Timers T0 & T1 — TMOD and TCON

TMOD (89H): upper nibble = Timer 1, lower = Timer 0. Each nibble = `GATE C/T M1 M0`.

- **C/$\overline{\text{T}}$ = 0** → timer (counts machine cycles = XTAL/12); **= 1** → counter (counts pulses on T0/T1 pin).
- **GATE = 1** → run only while INT$\overline{\text{x}}$ pin is high (hardware gating).

M1 M0	Mode	Description
0 0	**Mode 0**	13-bit timer (8192 counts) — legacy
0 1	**Mode 1**	**16-bit timer** (65536 counts) — most used
1 0	**Mode 2**	**8-bit auto-reload** (TH reloads TL) — baud-rate generation
1 1	Mode 3	Split timer (T0 as two 8-bit timers)

TCON (88H, bit-addressable): `TF1 TR1 TF0 TR0 IE1 IT1 IE0 IT0` — TRx starts the timer, TFx = overflow flag; ITx = 1 selects **edge**-trigger for INT$\overline{\text{x}}$.

Count/overflow rule (mode 1): delay = (65536 − initial count) × machine-cycle time. See Worked Example 9.

5.12.6 Interrupts — five sources

Source	Flag	Vector	Default priority
External $\overline{\text{INT0}}$	IE0	**0003H**	1 (highest)
Timer 0 overflow	TF0	**000BH**	2
External $\overline{\text{INT1}}$	IE1	**0013H**	3
Timer 1 overflow	TF1	**001BH**	4
Serial (RI or TI)	RI/TI	**0023H**	5 (lowest)

(Reset vector = 0000H; vectors are 8 bytes apart.)

IE register: `EA – ET2 ES ET1 EX1 ET0 EX0` — EA must be 1 to enable anything. **IP register** raises chosen sources to high priority.

5.12.7 Serial port (SCON modes)

Mode	SM0 SM1	Description	Baud
0	00	Shift register (synchronous)	XTAL/12
1	01	**8-bit UART** (most used)	Variable — Timer 1 mode 2
2	10	9-bit UART	XTAL/32 or /64
3	11	9-bit UART	Variable

Baud (mode 1, SMOD=0) = XTAL / (12 × 32 × (256 − TH1)). With 11.0592 MHz and TH1 = FDH (−3): 11 059 200/(384 × 3) = **9600 baud**.

5.12.8 8051 assembly flavour — quick examples

```
; Toggle all bits of Port 1 forever
BACK:  MOV  A, #55H     ; 0101 0101
       MOV  P1, A
       ACALL DELAY
       CPL  A           ; complement -> AAH
       MOV  P1, A
       ACALL DELAY
       SJMP BACK
```

```
; Timer 0, mode 1: create one 50 ms tick @ 12 MHz (count = 15536 = 3CB0H)
       MOV  TMOD, #01H  ; T0 mode 1
       MOV  TH0, #3CH
       MOV  TL0, #0B0H
       SETB TR0         ; start
WAIT:  JNB  TF0, WAIT   ; poll overflow
       CLR  TR0
       CLR  TF0
```

Addressing modes of 8051: immediate (`#`), register (Rn), direct (RAM/SFR address), register-indirect (`@R0/@R1` , `@DPTR` via MOVX), indexed (`MOVC A,@A+DPTR` — table lookup), plus rich **bit addressing** (`SETB` , `CLR` , `JB` , `JNB`).

5.12.9 Modern microcontrollers (one-liners)

- **AVR (Atmel/Microchip ATmega328 — Arduino Uno):** 8-bit **RISC**, Harvard architecture, most instructions in 1 clock, flash program memory.
- **PIC (Microchip PIC16/18):** 8-bit RISC Harvard, banked RAM, very popular in low-cost control.
- **ARM Cortex-M (STM32, LPC, nRF): 32-bit RISC** licensed core, Thumb-2 instruction set, NVIC interrupt controller — dominant modern embedded platform.
- **MSP430 (TI):** 16-bit ultra-low-power RISC MCU.
- **Harvard vs Von Neumann:** Harvard = separate program & data memory/buses (8051, AVR, PIC); Von Neumann = shared memory/bus (8085, 8086).

5.13 Worked Examples (10)

WE-1 (Hex addition + all flags). `MVI A, 9CH` → `MVI B, 64H` → `ADD B` . Find A and flags.

9CH + 64H: C+4 = 10H → nibble 0, AC = 1. 9+6+1 = 10H → result high nibble 0, carry out = 1.

A = 00H; CY = 1, AC = 1, Z = 1, S = 0, P = 1 (zero has even number of 1s). ✓ (9C = 156, 64H = 100, 156+100 = 256 = 100H.)

WE-2 (Subtraction/borrow). A = 45H, `SUI 62H`.

45H − 62H = 45 + (2's comp of 62 = 9EH) = E3H with no carry out → **CY = 1 (borrow)**. A = **E3H**, S = 1, Z = 0, P: E3 = 1110 0011 → six 1s → **P = 1**. (Check decimal: 69 − 98 = −29; E3H = 227 = 256 − 29 ✓.)

WE-3 (Logic + rotate). A = C5H. After `ANI 0FH` → A = 05H (CY=0, AC=1). Then `RLC` → 0000 1010 = **0AH**, CY = 0. Then `RRC` twice on 0AH: 0AH → 05H (CY=0) → 82H (CY=1, since D0 of 05H = 1 rotates into D7). Final **A = 82H, CY = 1**.

WE-4 (Program trace).

```
MVI A, 07H
RLC
MOV B, A
RLC
RLC
ADD B
```

07H → RLC → 0EH; B = 0EH; RLC → 1CH; RLC → 38H; 38H + 0EH = **46H**. (This computes 7 × 10: 7×2 + 7×8 = 70 = 46H ✓.)

WE-5 (Delay calculation). Crystal 6.144 MHz → clock 3.072 MHz → T = 325.5 ns. Loop:

```
MVI C, FFH   ; 7T (once)
LOOP: DCR C  ; 4T
JNZ LOOP     ; 10T (254 times) / 7T (last)
```

T-states = 7 + 255 × 4 + 254 × 10 + 7 = 7 + 1020 + 2540 + 7 = **3574T** → 3574 × 0.3255 µs ≈ **1.163 ms**. General inner-loop formula: ≈ 14 × N T-states (+ overhead), N = count.

WE-6 (Address decoding). A 74LS138 decoder driven by A15 A14 A13 (E-inputs tied active). Output Y5 selects an 8 KB RAM. Range?

Y5 → A15 A14 A13 = 1 0 1; chip uses A12–A0 (13 lines). Range = 1010 0000 0000 0000 to 1011 1111 1111 1111 = **A000H–BFFFH** (size BFFF−A000+1 = 2000H = 8 KB ✓).

WE-7 (Chip-select logic). A 1 KB EPROM must sit at 0800H–0BFFH. 1 KB → A9–A0 to the chip. Fixed high bits: 0800H = 0000 10xx …; so **A15 A14 A13 A12 A11 A10 = 0 0 0 0 1 0**. $\overline{CS}$ = NAND of ($\bar{A}15 \cdot \bar{A}14 \cdot \bar{A}13 \cdot \bar{A}12 \cdot A11 \cdot \bar{A}10$) — e.g., a 6-input gate arrangement. Verify top: 0000 1011 1111 1111 = 0BFFH ✓.

WE-8 (Interrupt vector). A device pulls RST 6.5 high while IE = 1 and M6.5 = 0. Where does the 8085 go? Vector = 6.5 × 8 = 52 = **0034H**. (The CPU internally executes a restart: pushes PC, jumps to 0034H.)

WE-9 (8051 timer count). Generate a **2 ms** delay with Timer 1, mode 1, XTAL = 12 MHz.

Machine cycle = 12/12 MHz = 1 µs → need 2000 counts. Initial value = 65536 − 2000 = 63536 = **F830H** → `MOV TH1,#0F8H`, `MOV TL1,#30H`. (Check: F830H = 63536; 65536 − 63536 = 2000 ✓.)

WE-10 (8051 max timer delay & 8255 word). (a) Max mode-1 delay @ 12 MHz = 65536 µs ≈ **65.54 ms** (TH=TL=00H). (b) 8255 control word for **all three ports output, mode 0**: 1000 0000 = **80H**; for **all input**: 1001 1011 = **9BH**.

5.14 PYQ Corner — 22-04-2025 CBT-2 (solved)

Q1. After executing the program below, the content of the accumulator is:

```
MVI B, 06H
MVI A, F2H
ADD B
```

(a) F6H (b) F8H (c) 08H (d) F2H

Solution. `MVI B,06H` loads B = 06H (no flags). `MVI A,F2H` loads A = F2H. `ADD B`: F2H + 06H → 2+6 = 8 (no aux carry), F+0 = F → **A = F8H**; CY = 0, Z = 0, S = 1 (D7=1), P: F8 = 1111 1000 has five 1s → P = 0. **Answer: (b) F8H.**

Q2. The number of register banks available in the 8051 microcontroller is:

(a) Two (b) Three (c) Four (d) Eight

Solution. Internal RAM 00H–1FH holds **four register banks** (Bank 0–3), each containing registers **R0–R7** (8 bytes per bank = 32 bytes total). The active bank is chosen by bits **RS1, RS0 of the PSW**; Bank 0 is default after reset. **Answer: (c) Four.**

Q3. Which 8085 interrupt is positive-edge-triggered?

(a) TRAP (b) RST 7.5 (c) RST 6.5 (d) INTR

Solution. RST 7.5 is triggered by a **rising (positive) edge** and is internally **latched** — the request is remembered even if the pin returns low, until serviced or cleared by SIM bit R7.5/reset. RST 6.5, RST 5.5 and INTR are level-triggered; TRAP needs **both** an edge and sustained level. **Answer: (b) RST 7.5.**

Q4. In a DMA transfer using the 8257, the DACK̄ signal is sent to the peripheral:

(a) immediately when the peripheral raises DRQ

(b) after the CPU acknowledges HOLD with HLDA and the DMA controller, as bus master, begins the transfer cycle for that channel

(c) only after the entire block is transferred

(d) simultaneously with the HOLD request

Solution. Sequence: DRQ → 8257 raises HRQ/HOLD → CPU completes its current machine cycle, floats the buses and returns **HLDA** → 8257 takes bus mastership, **places the memory address on the bus, and only then asserts DACK̄** to the requesting peripheral, which uses it as a chip-select for the actual read/write cycle. DACK therefore marks the **grant of the bus and the start of the DMA cycle**, not the request. **Answer: (b).**

5.15 Practice MCQs (25)

1. The number of address lines in the 8085 is:

(a) 8 (b) 16 (c) 20 (d) 40

2. The 8085 flag register does **not** contain:

(a) Sign (b) Overflow (c) Parity (d) Auxiliary carry

3. The instruction `MOV A, M` uses which addressing mode?

(a) Direct (b) Immediate (c) Register indirect (d) Implied

4. An opcode fetch machine cycle of the 8085 requires a minimum of:

(a) 3 T-states (b) 4 T-states (c) 5 T-states (d) 6 T-states

5. After `XRA A`, the flags are:

(a) Z=1, CY=1 (b) Z=1, CY=0, P=1 (c) Z=0, CY=0 (d) Z=1, P=0

6. ALE of the 8085 is used to:

(a) enable interrupts (b) latch the low-order address (c) strobe data writes (d) select I/O

7. The vector address of RST 5.5 is:

(a) 002CH (b) 0034H (c) 003CH (d) 0024H

8. Which interrupt of the 8085 is non-maskable?

(a) RST 7.5 (b) INTR (c) TRAP (d) RST 5.5

9. `PUSH B` changes the stack pointer by:

(a) +1 (b) +2 (c) −1 (d) −2

10. If A = 3FH, after `INR A` the flags AC and Z are:

(a) AC=1, Z=0 (b) AC=0, Z=0 (c) AC=1, Z=1 (d) AC=0, Z=1

11. The number of I/O ports addressable with 8085 `IN` / `OUT` instructions:

(a) 256 in + 256 out (b) 64 K (c) 128 (d) 65536 combined

12. In memory-mapped I/O:

(a) only IN/OUT can access ports (b) arithmetic can be done directly on port data (c) IO/$\bar{M}$ = 1 during access (d) 256 ports maximum

13. The 8255 control word 90H (mode 0) configures:

(a) PA in, PB out, PC out (b) PA out, PB in (c) all ports input (d) all ports output

14. The mode of the 8253/54 used as a square-wave generator is:

(a) Mode 0 (b) Mode 1 (c) Mode 3 (d) Mode 5

15. During DMA, the 8085 responds to HOLD with:

(a) INT$\bar{A}$ (b) HLDA (c) READY (d) ALE

16. Cycle-stealing DMA means:

(a) the CPU is halted for the full block (b) one byte is transferred per bus grant, interleaved with CPU cycles (c) transfer without DACK (d) transfer via the accumulator

17. The 8259 PIC, fully cascaded, supports:

(a) 8 interrupts (b) 16 (c) 64 (d) 256

18. Physical address for CS = 1000H, IP = 2000H in the 8086:

(a) 3000H (b) 12000H (c) 102000H (d) 21000H

19. The 8086 instruction queue in the BIU is:

(a) 4 bytes (b) 6 bytes (c) 8 bytes (d) 16 bytes

20. On-chip data RAM of the standard 8051 is:

(a) 64 B (b) 128 B (c) 256 B (d) 4 KB

21. With a 12 MHz crystal, one 8051 machine cycle takes:

(a) 83 ns (b) 0.5 µs (c) 1 µs (d) 12 µs

22. Which 8051 port is open-drain and needs external pull-ups for I/O use?

(a) P0 (b) P1 (c) P2 (d) P3

23. Timer mode 2 of the 8051 is:

(a) 13-bit (b) 16-bit (c) 8-bit auto-reload (d) split timer

24. The 8051 interrupt with the highest default priority is:

(a) Timer 0 (b) Serial (c) External INT0 (d) Timer 1

25. Register banks in the 8051 are selected by:

(a) bits in TCON (b) RS1, RS0 in PSW (c) bits in IE (d) the SP value

Answer Key with brief explanations

Q	Ans	Why
1	b	A15–A0 → 64 KB
2	b	8085 has S, Z, AC, P, CY only; overflow flag appears in 8086/8051 (OV)
3	c	Operand address in HL pair
4	b	4T (T4 = decode); some opcodes take a 6T fetch
5	b	A XOR A = 00H → Z=1, CY=0, AC=0, S=0, P=1 (even)
6	b	ALE clocks the external 74LS373 in T1
7	a	5.5 × 8 = 44 = 002CH
8	c	TRAP (RST 4.5) is non-maskable, vector 0024H
9	d	Two bytes pushed → SP ← SP − 2
10	a	3FH+1 = 40H: carry from D3→D4 ⇒ AC=1; result ≠ 0 ⇒ Z=0 (CY unchanged by INR)
11	a	8-bit port address, separate read/write spaces
12	b	Ports behave as memory bytes; any memory instruction works
13	a	1001 0000: D4=1 → PA input; D1=0 → PB output; D3=D0=0 → PC output
14	c	Mode 3 = square wave; Mode 2 = rate generator
15	b	HLDA acknowledges bus release
16	b	Byte-at-a-time interleave; burst mode holds the bus for the block
17	c	1 master + 8 slaves × 8 = 64 levels
18	b	1000H × 10H + 2000H = 10000H + 2000H = 12000H
19	b	6-byte prefetch queue (8088 has 4)
20	b	128 bytes (00–7FH); 8052 has 256 B
21	c	12 clocks per machine cycle → 12/12 MHz = 1 µs
22	a	P0 doubles as AD7–AD0; open-drain outputs
23	c	TH auto-reloads TL on overflow — used for baud rates
24	c	Order: INT0 > TF0 > INT1 > TF1 > Serial
25	b	RS1 RS0 = 00/01/10/11 → Bank 0/1/2/3

5.16 Rapid-Revision Sheet

8085 interrupt vector table

Interrupt	Trigger	Vector	Maskable
TRAP	edge + level	0024H	No
RST 7.5	**+ve edge (latched)**	003CH	Yes (SIM)
RST 6.5	level	0034H	Yes
RST 5.5	level	002CH	Yes
INTR	level	external (RST n/CALL)	Yes (DI)
RST n (software)	—	n × 8	—

Flag rules in one breath

- **CY**: carry out of D7 / borrow; unaffected by INR, DCR, INX, DCX; cleared by ANA/ORA/XRA; only flag touched by DAD, STC, CMC, rotates.
- **AC**: carry D3 → D4; ANA forces AC = 1.
- **Z**: result = 00H. **S**: copy of D7. **P**: 1 for even count of 1s.
- CMP/CPI: A < op → CY=1; A = op → Z=1; A > op → CY=0 & Z=0.

T-state quick table

Item	T
Opcode fetch	4 (or 6)
Memory/I-O read or write cycle	3
MOV r,r / ADD r / NOP	4
MVI r / MOV r,M / ADD M	7
LXI / JMP / DAD / RET / POP	10
PUSH / RST	12
LDA / STA	13
CALL	18
Conditional jump	7 fail / 10 pass

8085 vs 8086 vs 8051 comparison

Feature	8085	8086	8051
Type	8-bit µP	16-bit µP	8-bit µC
Address bus / memory	16-bit / 64 KB	20-bit / 1 MB	64 KB code + 64 KB data (ext.)
On-chip memory	None	None	4 KB ROM + 128 B RAM
Architecture	Von Neumann	Von Neumann (BIU+EU pipeline)	**Harvard**
Flags	5	9	PSW (CY AC F0 RS1 RS0 OV P)
Interrupt inputs	5 hardware	INTR + NMI (256 types)	5 sources, 2 priority levels
Timers on chip	None	None	Two 16-bit (T0, T1)
Multiply/Divide instr.	No	Yes	Yes (MUL AB, DIV AB)
Machine cycle	3–6 T-states	4 T-states basic bus cycle	**12 clock periods**
Register banks	No	No	**4 banks (R0–R7), RS1 RS0**
Serial port	SID/SOD (software)	External 8251	Built-in full-duplex UART
Typical use	Learning/legacy systems	PCs (x86 origin)	Embedded control

Peripheral chips in one line each

Chip	Role
8255	PPI — 24 I/O lines, modes 0/1/2 + BSR
8253/54	3 × 16-bit programmable timers, 6 modes
8257	4-channel DMA controller (DRQ/DACK, HRQ/HLDA)
8259	Priority interrupt controller, 8→64 levels
8279	Keyboard scan (64 keys) + display refresh (16 digits)
8251	USART serial communication
8155	RAM + I/O + timer companion for 8085

Last-minute one-liners

- First microprocessor = **Intel 4004** (1971, 4-bit).
- 8085: 40-pin, +5 V, 246 opcodes, 74 instructions, 6.144 MHz crystal → 3.072 MHz clock.
- ALE latches A7–A0; IO/$\bar{M}$ = 1 for I/O, 0 for memory.
- `XRA A` clears A and CY together.
- Stack grows downward in 8085 (upward in 8051; 8051 SP reset = 07H).
- 8051 vectors: 0003, 000B, 0013, 001B, 0023H (8 bytes apart).
- 9600-baud magic crystal for 8051 = **11.0592 MHz** with TH1 = FDH.
- DAC$\bar{K}$ = peripheral's chip-select during a DMA cycle, issued after HLDA/bus grant.

End of Chapter 5. Next: Chapter 6 as per syllabus sequence.

Chapter 6 — Electronic Measurements

RRB JE CBT-2 · Electronics & Allied Engineering (CEN 05/2025, Annexure-VII C) · Syllabus Unit 6

> **Syllabus scope:** Measuring systems; Basic principles of measurement; Range Extension methods; Cathode Ray Oscilloscope, LCD, LED panel; Transducers.

📊 Weightage & Trend Box

Item	Detail
Approximate weight	~4% → **2 questions out of 50** in the actual CBT-2 paper of 22-04-2025
Observed 2025 Q1	Why is the oscilloscope probe cable **shielded (coaxial)**? → To reduce pickup of **external electrical interference/noise (EMI)** on the small signal being carried to the CRO.
Observed 2025 Q2	On what does the length (delay) of an **electrical delay line** in a CRO depend? → On the **signal propagation speed**, which is fixed by the **L and C parameters** of the lumped LC line (delay per section = √(LC)).
Trend	Questions are **conceptual, one-liner, CRO-centric** so far — but the unit officially covers instruments, range extension, bridges, displays and transducers, all of which are standard JE-level question banks. Expect shunt/multiplier numericals, LVDT/thermocouple facts, and Lissajous figures in future papers.
Strategy	Master (i) CRO block diagram + probes, (ii) Rsh and Rs formulas, (iii) transducer one-liners (LVDT, gauge factor, Seebeck, PT100, NTC), (iv) the four AC bridges and what each measures.

6.1 Measuring Systems — The Generalized Measurement System

A **measurement** is the process of comparing an unknown quantity (the *measurand*) with a predefined, accepted **standard**. Every practical instrument — from a simple ammeter to a DSO — can be decomposed into the same chain of **functional elements**:

```
Measurand → [Primary Sensing Element] → [Variable Conversion Element]
          → [Signal Conditioning Element] → [Data Transmission]
          → [Data Presentation Element] → Observer
```

Functional element	Job	Example
Primary sensing element	First element to receive energy from the measurand; produces an output that depends on the measurand	Bourdon tube (pressure), thermocouple junction, strain gauge grid
Variable conversion element	Converts the sensed variable into a more convenient form (often electrical) without changing the information	Displacement → inductance change (LVDT core), resistance → voltage (bridge)
Signal conditioning element	Amplifies, filters, attenuates, modulates, integrates or otherwise manipulates the signal to suit the next stage	Instrumentation amplifier, low-pass filter, A/D converter
Data transmission element	Carries the conditioned signal to the display/recording point	Shielded cable, 4–20 mA current loop, telemetry link
Data presentation element	Presents the result to the observer in readable/usable form	Pointer & scale, seven-segment LED, LCD, chart recorder, CRO screen

Exam nuggets

- The **primary sensing element** is also called the **detector**; it is the *transducer* in most electronic systems.
- The order **sensing → conversion → conditioning → presentation** is a favourite one-mark sequencing question.
- Data may also pass through **data processing** (computation, linearization) before presentation in modern digital instruments.

6.2 Basic Principles of Measurement

6.2.1 Accuracy, Precision, Resolution, Sensitivity

Term	Meaning	Key point
Accuracy	Closeness of the measured value to the **true value**	Expressed as % of full-scale deflection (FSD) or % of reading
Precision	Closeness of **repeated measurements to each other** (repeatability/reproducibility)	An instrument can be precise but inaccurate (consistent offset)
Resolution	**Smallest change** in input that the instrument can detect/display	For a 3½-digit DVM on 2 V range: resolution = 1 mV
Sensitivity	Ratio of **change in output** to **change in input**: S = Δoutput/Δinput	Slope of the static calibration curve; for a voltmeter, sensitivity = 1/I_fsd in **Ω/V**
Threshold	Minimum input below which no output change is seen (starting from zero)	—
Dead zone / dead band	Largest change of input to which the instrument does not respond	Caused by friction, backlash, hysteresis
Drift	Gradual shift of output with time at constant input	Zero drift, span drift
Hysteresis	Different output for the same input depending on whether input is increasing or decreasing	Magnetic/mechanical causes
Linearity	Closeness of the calibration curve to a straight line	Non-linearity quoted as % of FSD

> ☆ **Accuracy vs precision picture:** darts clustered tightly away from bullseye = *precise, not accurate*; darts scattered around the bullseye = *accurate on average, not precise*.

6.2.2 Errors in Measurement

Classification (very frequent MCQ):

1. **Gross errors** — human mistakes: misreading the scale, parallax, wrong recording, wrong instrument choice. *Remedy:* care, multiple readings by different observers. They **cannot be treated mathematically**.
2. **Systematic errors** — consistent, repeatable, of definite sign:

- **Instrumental errors** — inherent shortcomings (weak spring, friction, worn parts), misuse (not zeroing), and **loading effect** (instrument alters the quantity it measures — e.g., a low-sensitivity voltmeter across a high resistance).
- **Environmental errors** — temperature, humidity, pressure, external magnetic/electrostatic fields. *Remedy:* shielding, temperature compensation, controlled conditions.
- **Observational errors** — parallax (remedy: mirror-backed scales), estimation habits.

1. **Random (residual) errors** — remain after gross and systematic errors are removed; caused by many small unpredictable effects. They follow the **Gaussian (normal) distribution** and are treated statistically (mean, standard deviation, probable error = 0.6745 σ).

Error definitions

- **Absolute error:** $\delta A = A_m - A_t$ (measured − true)
- **Relative / percentage error:** $\varepsilon = \delta A / A_t \times 100\ \%$
- **Static correction:** $\delta C = A_t - A_m = -\delta A$
- **Limiting (guarantee) error:** manufacturer guarantees error within ± x % of **full scale**. Hence, the *percentage error of a reading is worst at low readings* — always use an instrument in the **upper third of its scale**.

> **Worked Example 6.1 (limiting error).**

> A 0–150 V voltmeter has a guaranteed accuracy of ±1 % of full scale. It reads 75 V. Find the limiting error in the reading.

> Absolute limiting error = 1 % × 150 = ±1.5 V.

> % limiting error at 75 V = 1.5/75 × 100 = **±2 %**.

> (If it read 15 V, the error would be 1.5/15 = ±10 % — this is why we avoid the low end of the scale.)

> **Worked Example 6.2 (absolute & % error).**

> True value of a resistor is 100.0 Ω; a bridge measures 100.4 Ω.

> Absolute error δA = 100.4 − 100.0 = **+0.4 Ω**; % error = 0.4/100 × 100 = **+0.4 %**; correction = **−0.4 Ω**.

Combination of errors (quantities in a product/quotient): if $X = A \cdot B / C$, then

% error in X ≈ (%err A) + (%err B) + (%err C) (worst-case limiting errors add).

6.2.3 Standards and Calibration

Standard	Description
International standards	Defined by international agreement (SI); maintained at BIPM, Sèvres; not available for ordinary use
Primary standards	Maintained by national labs (NPL New Delhi, NIST); used to calibrate secondary standards
Secondary standards	Reference standards in industrial labs; periodically sent to national labs for certification
Working standards	Day-to-day lab/shop-floor calibration tools

Calibration = comparing the instrument against a standard of known accuracy and adjusting/recording the deviations. Calibration removes/quantifies **systematic** errors; it cannot remove random errors.

6.2.4 Static vs Dynamic Characteristics

- **Static characteristics** — apply when the measurand is constant or slowly varying: accuracy, precision, sensitivity, resolution, drift, linearity, hysteresis, dead zone.
- **Dynamic characteristics** — apply to rapidly varying inputs:
- **Speed of response** — rapidity with which the instrument responds.
- **Fidelity** — faithfulness of output waveform to input changes.
- **Lag** — delay in response (retardation lag, time-delay lag).
- **Dynamic error** — difference between true time-varying value and indicated value (with static error removed).
- Standard test inputs: **step, ramp, sinusoidal**; first-order instruments characterized by **time constant τ**, second-order by **natural frequency ω_n and damping ratio ξ**.

6.3 Classification of Instruments

Basis	Types
Nature of standard	**Absolute instruments** — give the value in terms of physical constants and dimensions (tangent galvanometer, Rayleigh current balance); no calibration needed. **Secondary instruments** — must be calibrated against absolute/standard instruments; all practical meters (ammeter, voltmeter, wattmeter).
Function	**Indicating** (pointer & scale — ammeter, voltmeter), **Recording** (continuous trace vs time — strip-chart recorder, X-Y recorder), **Integrating** (totalize over time — **energy meter**, ampere-hour meter).
Signal handling	**Analog** — output varies continuously (PMMC meter); **Digital** — output in discrete steps/digits (DMM, DVM, frequency counter).
Power source	**Deflection type** (deflection ∝ measurand) vs **null type** (balance is restored; e.g., potentiometer, bridge — more accurate because at balance no current is drawn).

6.4 Operating Principles — The Three Torques

Every analog indicating instrument needs three torques:

1. Deflecting torque (T_d)

Produced by the effect being exploited (magnetic, electrodynamic, electrostatic, thermal, induction, hall). It moves the pointer up-scale.

2. Controlling torque (T_c)

Opposes T_d and brings the pointer to rest where **T_c = T_d**; also returns the pointer to zero when the measurand is removed.

Method	Torque law	Notes
Spring control	T_c = K·θ (∝ deflection)	Two phosphor-bronze spiral springs wound in opposite directions (also serve as current leads in PMMC); instrument can be used in **any position**; scale can be uniform if T_d ∝ I
Gravity control	T_c = W·l·sin θ	Small adjustable weight on the spindle; **must be used vertical/levelled**; cheaper; gives **cramped (non-uniform) scale** at low end since T_c ∝ sin θ

3. Damping torque

Acts only while the pointer **moves**; brings it to rest quickly without oscillation. The instrument should be **just under-damped / critically damped** ("dead-beat").

Method	Mechanism	Used in
Air-friction damping	Light piston in an air chamber, or vane in a sector box	Moving-iron, hot-wire instruments
Fluid-friction damping	Vane submerged in oil	Rare; used where instrument is upright; adds buoyancy support
Eddy-current damping	Aluminium former/disc moving in a permanent-magnet field; induced eddy currents oppose motion (Lenz's law)	**PMMC** (aluminium former), **induction energy meter** (brake magnet on disc). **Most efficient** method; *cannot* be used where the operating field would be disturbed (e.g., moving-iron)
Electromagnetic damping	Circuit closed through low resistance so induced current damps motion	Galvanometers

> ☆ If damping is too strong → **over-damped**, sluggish; too weak → **under-damped**, oscillatory. "Dead-beat" ≈ critically damped.

6.5 PMMC (Permanent Magnet Moving Coil) Instruments

Construction: a light rectangular coil of fine wire wound on an **aluminium former**, pivoted in the uniform radial field of a permanent magnet (with soft-iron core), spring-controlled, eddy-current damped (the former itself provides damping).

Torque equation:

T_d = N·B·I·l·b = N·B·A·I = **G·I** where G = NBA (galvanometer constant)

At balance: $G \cdot I = K \cdot \theta \Longrightarrow \boldsymbol{\theta = (G/K) \cdot I \Longrightarrow \theta \propto I}$ → **uniform (linear) scale**.

Property	PMMC
Works on	**DC only** (with AC, torque reverses each half-cycle → mean torque = 0; pointer just vibrates)
Scale	Uniform
Damping	Eddy-current (Al former)
Control	Spring (springs also lead current in/out)
Sensitivity	Very high (20 kΩ/V typical); low power consumption (25–200 μW)
Errors	Ageing of magnet & springs, temperature (coil Cu resistance +0.4 %/°C — compensated with swamping resistance of manganin), friction
Applications	DC ammeters & voltmeters (with shunt/multiplier), galvanometer, ohmmeter, and — with a rectifier — AC measurement; basis of most analog multimeters

Why DC only? The direction of $T_d = NBAI$ depends on current direction. On AC (50 Hz) the inertia of the movement cannot follow the reversals; average deflecting torque is zero.

6.6 Moving-Iron (MI) Instruments

Two types:

1. **Attraction type** — an eccentrically pivoted soft-iron vane is attracted **into** the field of a fixed coil carrying the current.
2. **Repulsion type** — two soft-iron vanes (one fixed, one movable) inside the coil are **similarly magnetized** by the coil current and repel each other. (Radial-vane and coaxial-vane variants.)

Torque: $T_d = \tfrac{1}{2} I^2 \left(dL/d\theta\right) \Longrightarrow \boldsymbol{\theta \propto I^2}$ (approximately)

Property	Moving iron
Works on	**Both AC and DC** (deflection $\propto I^2$, independent of current direction); on AC it reads **RMS**
Scale	**Non-uniform** — cramped at the lower end (square-law); made more uniform by shaping vanes
Control	Spring or gravity
Damping	**Air friction** (eddy-current damping would need a magnet that distorts the operating field)
Errors	Hysteresis (reads higher on descending DC), stray magnetic fields, frequency error (coil inductance) on AC, temperature
Merits	Cheap, robust, AC/DC, withstands overloads
Uses	Switchboard AC ammeters/voltmeters (most common industrial AC meter)

6.7 Electrodynamometer (Dynamometer) Instruments & Wattmeter

Replace the permanent magnet of PMMC with **fixed current coils**; a movable **pressure (potential) coil** rotates in their field.

- Torque: $T_d \propto i_1 \cdot i_2 \cdot (dM/d\theta)$ where M = mutual inductance between coils.
- As ammeter/voltmeter: both coils carry the same current → $\theta \propto I^2$ → **square-law scale**, reads RMS, works on AC and DC — used as **transfer instruments** (calibrated on DC, used on AC).
- **As a wattmeter (chief use):**
- **Fixed coils = current coils (CC)** in series with load (carry load current, few turns, thick wire).
- **Moving coil = pressure coil (PC)** across the load through a high series resistance (current ∝ voltage, in phase with V).
- Average torque $\propto V \cdot I \cdot \cos\varphi$ = **true power**; **scale is uniform** ($\theta \propto P$).
- Air-friction damping; spring control.
- **Errors:** pressure-coil inductance (reads high at lagging PF), connection error (whether PC is on supply side or load side — compensated wattmeter uses a compensating winding), eddy currents, stray fields.
- **Low power factor wattmeter (LPF):** special design (low PC resistance, compensating coil) for measuring power where cos φ is small (e.g., no-load test of transformer).

6.8 Single-Phase Induction Energy Meter (Integrating Instrument)

Principle: two alternating fluxes — from a **shunt (pressure) magnet** (flux ∝ V, made to lag V by ~90° using a copper shading band) and a **series (current) magnet** (flux ∝ I) — induce eddy currents in a rotating **aluminium disc**. Interaction of each flux with the eddy current of the other produces a driving torque $\propto V \cdot I \cdot \cos\varphi$ = power.

- **Braking:** a permanent **brake magnet** near the disc edge produces braking torque ∝ speed. At steady state: speed **N ∝ power**, so total revolutions ∝ **energy** (kWh). Registered by a geared counting mechanism.
- **Meter constant** = revolutions per kWh.

Errors & adjustments

Error	Cause	Adjustment
Phase (lag) error	Pressure flux not exactly 90° behind V	Lag adjustment: shading band/loop on shunt magnet
Creep	Disc rotates slowly with **only voltage applied, no load** (due to supply overvoltage/vibration/pressure-coil asymmetry)	**Two diametrically opposite holes drilled in the disc** — disc rests when a hole comes under the shunt pole
Speed error	Wrong braking	Move brake magnet radially (in = faster, out = slower)
Friction	Bearing/counter friction, worst at light load	Friction-compensating shading loop gives small constant torque
Overload/temperature/frequency errors	—	Design compensation

> **Worked Example 6.3 (energy meter).**
>
> Meter constant = 1200 rev/kWh. On a 230 V, 10 A, UPF load the disc makes 46 revolutions in 60 s. Is the meter accurate?
>
> Energy actually consumed = 230 × 10 × 1 × (60/3600) = 38.33 Wh = 0.03833 kWh.
>
> Revolutions expected = 1200 × 0.03833 = 46.0. **Meter is reading correctly (0 % error).**

6.9 Rectifier and Thermal Instruments

Rectifier instruments: a PMMC movement fed through a bridge (or half-wave) rectifier measures AC. The PMMC responds to the **average** of the rectified wave but the scale is marked in **RMS assuming a sine wave** (form factor 1.11). Hence, on non-sinusoidal waveforms rectifier meters show **waveform error**. High sensitivity and wide frequency range (up to ~kHz–MHz) — used in analog multimeters for AC ranges.

Thermal instruments (one paragraph): Hot-wire and **thermocouple** instruments use the heating effect I^2R. In the thermocouple type, the current heats a heater wire whose temperature is sensed by a thermocouple driving a PMMC meter. Deflection $\propto I^2$ → they read **true RMS regardless of waveform**, work on AC and DC, and are useful at **radio frequencies** (up to tens of MHz) because there is no coil inductance error. Drawbacks: fragile heater, sluggish, poor overload capacity, cramped square-law scale.

Electrostatic instruments (bonus): force between charged plates, $\theta \propto V^2$; used only as **voltmeters** (especially high voltage); draw negligible current; AC (RMS) and DC.

6.10 Range Extension Methods (High-Yield ★★★)

6.10.1 Ammeter Shunt

A PMMC movement of resistance R_m and full-scale current I_m can measure a larger current I by bypassing the excess through a low resistance **shunt R_sh in parallel**.

Derivation. The shunt and meter are in parallel, so they share the same voltage:

I_sh·R_sh = I_m·R_m, and I_sh = I − I_m.

Define **multiplying power m = I / I_m**. Then

(I − I_m) R_sh = I_m R_m ⟹ R_sh = I_m R_m / (I − I_m)

R_sh = R_m / (m − 1) and **m = 1 + R_m/R_sh**

- Shunts are made of **manganin** (DC) / constantan — very low temperature coefficient, and are 4-terminal (separate current and potential terminals) to avoid contact-resistance error.
- A **swamping resistance** (manganin, ~3×R_m) in series with the coil reduces temperature error.
- **Ayrton (universal) shunt** gives multiple ranges without ever leaving the meter unshunted.

> **Worked Example 6.4 (shunt design).**
>
> A meter has R_m = 50 Ω, I_m = 1 mA. Design a shunt for 1 A full scale.
>
> m = 1 A / 1 mA = 1000. R_sh = 50/(1000 − 1) = **0.05005 Ω ≈ 50.05 mΩ**.

> **Worked Example 6.5.**
>
> The same 1 mA, 50 Ω movement must read 100 mA. m = 100 ⟹ R_sh = 50/99 = **0.505 Ω**. Voltage across the parallel combination at FSD = 1 mA × 50 Ω = 50 mV (all shunted meters are really 50 mV millivoltmeters!).

6.10.2 Voltmeter Multiplier

To measure voltage V with a movement of FSD voltage V_m = I_m R_m, connect a high **series (multiplier) resistance R_s**:

V = I_m (R_m + R_s), with **m = V/V_m**:

$R_s = R_m (m - 1)$ $\Leftrightarrow$ $m = 1 + R_s/R_m$

> **Worked Example 6.6 (multiplier design).**

> Movement: I_m = 1 mA, R_m = 100 Ω (so V_m = 0.1 V). Required range 10 V.

> $m = 10/0.1 = 100 \Longrightarrow R_s = 100 \times (100 - 1) =$ **9900 Ω = 9.9 kΩ**.

6.10.3 Voltmeter Sensitivity (Ω/V) and Loading Effect

Sensitivity S = 1/I_{fsd} (Ω per volt). Total voltmeter resistance on a range = S × (range).

E.g., a 20 kΩ/V meter on the 10 V range presents 200 kΩ.

A voltmeter of finite resistance **loads** the circuit: it lowers the very voltage it is measuring. Loading error is serious in **high-resistance circuits** with **low-sensitivity meters**. DMMs (10 MΩ input) load far less than analog VOMs.

> **Worked Example 6.7 (loading effect).**

> Two 100 kΩ resistors in series across 100 V; true voltage across the lower one = 50 V. A 1000 Ω/V voltmeter on its 50 V range (R_v = 50 kΩ) is connected across the lower resistor.

> Effective lower resistance = 100k ∥ 50k = 33.33 kΩ.

> Reading = 100 × 33.33/(100 + 33.33) = **25 V**.

> % error = (25 − 50)/50 × 100 = **−50 %** (!)

> With a 20 kΩ/V meter (R_v = 1 MΩ): 100k ∥ 1M = 90.9 kΩ; reading = 100 × 90.9/190.9 = 47.6 V; error = −4.8 %. **Higher Ω/V ⇒ less loading.**

6.10.4 Instrument Transformers — CT and PT

For heavy AC currents and high AC voltages, shunts/multipliers become impractical (loss, insulation, safety). **Instrument transformers** step down the quantity and also **isolate** the meter from the high-voltage line.

	Current Transformer (CT)	Potential Transformer (PT/VT)
Connection	**Primary in series** with the line (often 1 turn/bar primary)	**Primary across** the line
Steps	Current down (e.g., 100/5 A, 1000/5 A)	Voltage down (e.g., 11 kV/110 V)
Secondary standard	**5 A (or 1 A)**	**110 V**
Ratio	**Transformation ratio R = I_p/I_s**; nominal ratio = rated I_p/rated I_s; turns ratio n = N_s/N_p	R = V_p/V_s
Errors	**Ratio error** = (nominal ratio − actual ratio)/actual ratio ×100 %; **phase-angle error** (secondary current not exactly 180° from primary) — both caused by magnetizing & core-loss components of excitation current	Ratio and phase-angle errors (usually smaller)
Burden	The load (VA) on the secondary — meters/relays + leads. Quoted in **VA at rated secondary current**. Exceeding rated burden increases errors.	Same concept

> ☆ **Why must a CT secondary NEVER be open-circuited while the primary is energized?**

> The primary current is fixed by the load (CT primary is in series with the line), *not* by the CT. Normally the secondary MMF opposes the primary MMF, keeping core flux small. If the secondary is opened, the **opposing MMF vanishes**, the entire primary MMF magnetizes the core → flux rises enormously → (i) **dangerously high voltage** (kV) induced across the open secondary — lethal to personnel and insulation; (ii) **core saturates and overheats** (huge iron loss); (iii) the core may be left permanently magnetized, ruining accuracy. Therefore CT secondaries are **short-circuited (via a shorting switch) before removing the burden**.

Range extension of wattmeter & energy meter: connect the wattmeter current coil via a **CT** and pressure coil via a **PT**;

Actual power = wattmeter reading × CT ratio × PT ratio (with correction factors for CT/PT phase errors in precision work). Energy meters on HV feeders are similarly operated through CT/PT, and the meter constant is scaled by the same product.

6.11 Measurement of Resistance

Resistances are classed as **low (< 1 Ω)**, **medium (1 Ω – 100 kΩ)**, **high (> 100 kΩ)**.


6.11.1 Voltmeter–Ammeter Method (medium R)

R ≈ V/I. Two connections:

- Ammeter near the unknown (voltmeter across both A and R): measured R = R + R_a → good for **high R**.
- Voltmeter directly across R (ammeter reads I_R + I_v): measured R = R ∥ R_v → good for **low R**.

Simple but accuracy limited (~1 %) by meter errors and connection error.

6.11.2 Wheatstone Bridge (medium R) ☆

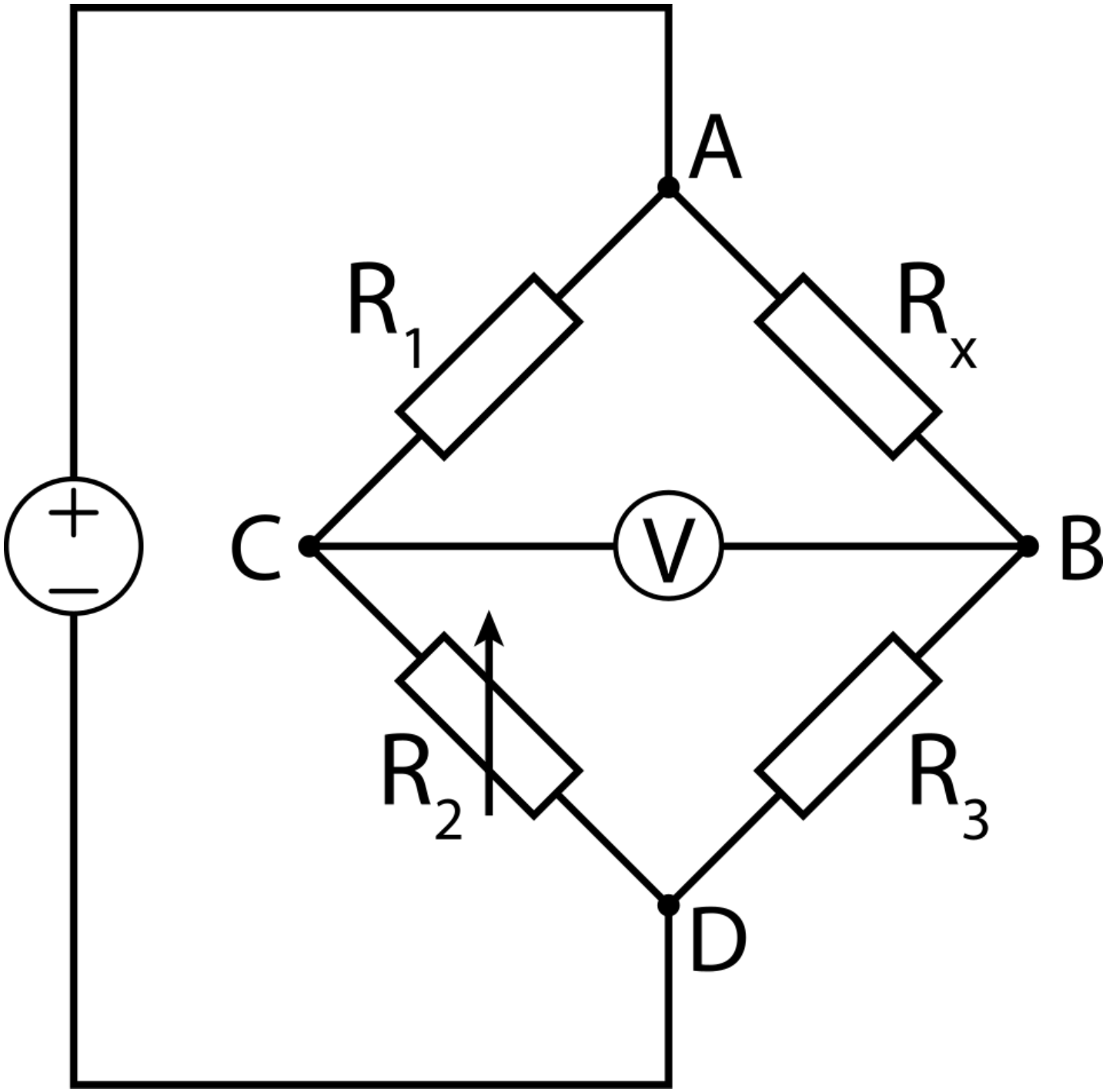

Wheatstone bridge for resistance measurement.

Four arms P, Q (ratio arms), S (standard variable), R (unknown); galvanometer across the detector diagonal; battery across the other.

Balance condition (no galvanometer current):

Potential at both galvanometer terminals equal ⟹ **P/Q = R/S ⟹ R = (P/Q)·S**

- Null method → high accuracy (0.1 % or better); independent of supply voltage.
- Sensitivity greatest when all four arms are of the same order.
- **Limitations:** for very low R, lead & contact resistances swamp the unknown; for very high R, insulation leakage and low sensitivity spoil it.

6.11.3 Kelvin Double Bridge (low R, 0.1 μΩ – 1 Ω) ☆

A modified Wheatstone with a **second set of ratio arms (p, q)** that eliminates the effect of the **link (yoke) resistance** and connecting-lead resistance. With p/q = P/Q, the balance gives simply

R = (P/Q)·S

and the lead/contact resistances cancel. Unknown and standard are **four-terminal** resistances. Used for shunts, armature/contact resistance, cable strips.

6.11.4 High Resistance / Insulation — Megger ☆

- High R measured by **loss-of-charge method**, **megohm bridge**, or the field instrument: the **megohmmeter (Megger)**.
- **Megger** = a hand-cranked (or battery/electronic) **DC generator (250 V/500 V/1 kV/2.5 kV)** + a **ratiometer (ohmmeter) movement with two coils** (current coil and pressure coil) on one spindle with **no control spring** — the pointer floats when idle and the deflection depends on the *ratio* V/I, i.e., directly on resistance, independent of crank speed.
- **Guard terminal** bypasses surface leakage so only volume insulation resistance is read.
- Used for **insulation resistance of cables, machines, transformers** (readings in MΩ).

6.12 AC Bridges — Overview

General four-arm bridge with impedances $Z_1Z_2Z_3Z_4$, AC source (usually 1 kHz oscillator), detector (headphones/tuned amplifier). Balance:

$Z_1 Z_4 = Z_2 Z_3$ — must be satisfied in **both magnitude and phase**, so two independent adjustments are needed.

Bridge	Measures	Balance equations	Remarks
Maxwell's inductance–capacitance bridge	**Medium-Q inductance (1 < Q < 10)** in terms of a standard capacitor	**$L_1 = R_2R_3C_4$**, $R_1 = R_2R_3/R_4$	Balance independent of frequency; standard capacitor (loss-free) preferred over standard inductor; unsuitable for high Q (R_4 becomes impractically large)
Hay's bridge	**High-Q inductance (Q > 10)**	**$L_1 = R_2R_3C_4 / (1 + \omega^2C_4^2R_4^2)$**; for Q > 10, $L_1 \approx R_2R_3C_4$	C_4 in **series** with R_4 (Maxwell has them in parallel); balance is **frequency-dependent**
Schering bridge	**Capacitance and dissipation factor (loss angle δ) of capacitors/insulation**, incl. HV testing	**$C_1 = C_2\cdot(R_4/R_3)$**, $R_1 = R_3\cdot(C_4/C_2)$; **$D = \tan\delta = \omega C_4R_4$**	The standard HV bridge for insulation/bushings/cables
Wien bridge	**Frequency** (also audio capacitance)	**$f = 1 / (2\pi\sqrt{(R_1R_2C_1C_2)})$**; with $R_1=R_2=R$, $C_1=C_2=C$: **$f = 1/(2\pi RC)$** and $R_4/R_3 = 2$	Basis of the **Wien-bridge oscillator**; frequency-sensitive
(Also asked) **Anderson bridge**	Inductance in terms of fixed capacitor (modification of Maxwell)	—	Very accurate over wide L range
(Also asked) **De Sauty bridge**	Capacitance (loss-free) comparison	$C_1/C_2 = R_4/R_3$	Simple, only for perfect capacitors

Wagner earthing device: removes errors due to stray capacitances to earth at the detector terminals.

6.13 Multimeters, DVMs and DMMs

Analog multimeter (VOM): one PMMC movement + switched shunts (DC A), multipliers (DC V), rectifier + multipliers (AC V), internal battery + series/shunt network (ohms — scale reads **right-to-left, non-linear**, zero-ohm adjust needed). Typical sensitivity 20 kΩ/V DC.

Digital Multimeter (DMM): signal conditioner (attenuator/amplifier, AC-DC converter, I→V shunt, ohms current source) + **A/D converter** + counter + display. Advantages: no parallax, high input impedance (≈10 MΩ constant on all ranges), auto-ranging, auto-polarity, better accuracy (±0.5 % to ±0.005 %), resolution specified in **digits (3½, 4½)** — a 3½-digit meter displays up to **1999** (max leading digit 1); **overranging** = the extra ½ digit.


Digital voltmeter (DVM) types — one line each:

- **Ramp-type DVM:** measures the time a linear ramp takes to go from 0 to V_in; counts clock pulses in that gate time.
- **Staircase-ramp DVM:** DAC output steps up until it equals V_in; count = reading.
- **Integrating (voltage-to-frequency) DVM:** converts V to a proportional pulse rate; counts pulses — averages out noise.
- **Dual-slope integrating DVM:** integrates V_in for a fixed time, then de-integrates with a reference; reading independent of R, C and clock drift; **excellent 50 Hz noise rejection** — the standard DMM technique.
- **Successive-approximation DVM:** binary search using a DAC + comparator; **fastest** for given resolution.

6.14 Cathode Ray Oscilloscope (CRO) — In Depth ★★★

The CRO displays **voltage vs time** (or X vs Y) in real time; input impedance typically **1 MΩ ‖ 10–30 pF**.

6.14.1 Block Diagram

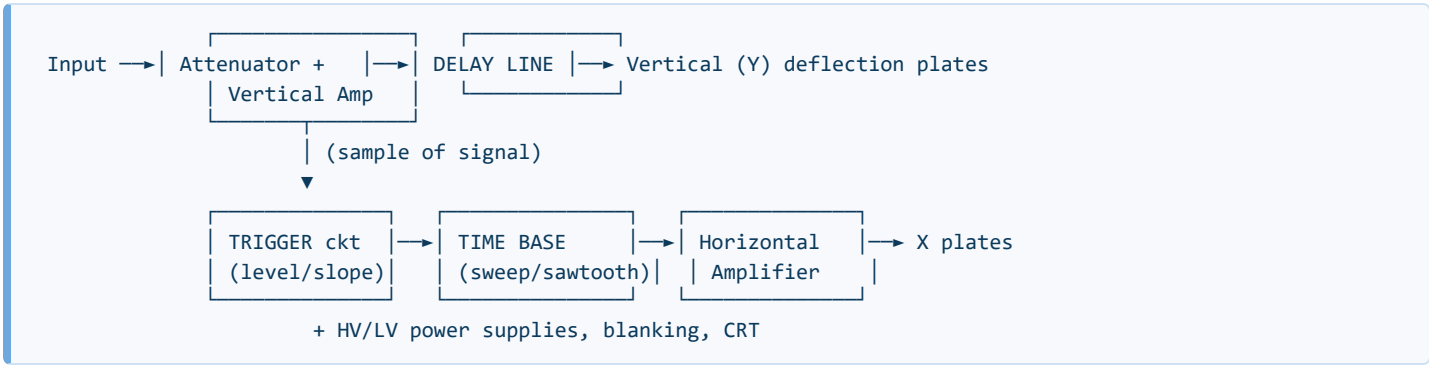

- **Vertical (Y) system:** input attenuator (V/div switch, compensated RC dividers) → wideband **vertical amplifier** (sets sensitivity & bandwidth) → delay line → Y-plates.
- **Trigger circuit:** picks a sample of the vertical signal (or EXT/LINE source), compares with the set **level** on the chosen **slope (+/−)**, and fires the time base at the same waveform point every sweep → **stable, stationary display**.
- **Time base (horizontal system):** generates a linear **sawtooth**: slow linear **sweep** (spot moves left→right at uniform speed = TIME/div) followed by rapid **retrace/flyback** (blanked). Modes: auto, normal, single. In X-Y mode the sawtooth is replaced by an external X signal.
- **Blanking:** negative gate to the control grid extinguishes the beam during retrace.

6.14.2 The Delay Line ★ (asked in 22-04-2025)

Why needed: The trigger + time-base circuits need **~80–200 ns** to start the sweep after the triggering edge arrives. Without compensation, the **leading edge of the very signal that caused the trigger would already be past** before the sweep starts, so the start of the waveform would never be seen. The **delay line, placed in the vertical channel after the point where the trigger signal**

is tapped, delays the signal to the Y-plates by slightly **more** than the trigger+sweep initiation time, so the sweep is already running when the signal edge reaches the plates → **the entire leading edge is displayed**.


Two constructions:

1. **Lumped-parameter (electrical) delay line:** a cascade of n identical symmetrical **LC sections** (low-pass filter chain).

- Delay per section: **$t_s = \sqrt{(L \cdot C)}$**; total delay **$t_d = n \cdot \sqrt{(LC)}$**.
- Characteristic impedance **$Z_0 = \sqrt{(L/C)}$** — the line must be terminated in Z_0 to avoid reflections/ringing.
- Hence the **delay (effective electrical "length") is determined by the propagation speed of the signal along the line, which is fixed by the L and C values per section and the number of sections.** ⭐ *This is exactly the 2025 PYQ.*

1. **Distributed-parameter delay line:** a special helical-inner-conductor **coaxial cable**; delay ≈ 180 ns/m typical (vs ~5 ns/m for ordinary coax); used in high-bandwidth scopes.

6.14.3 CRT Construction

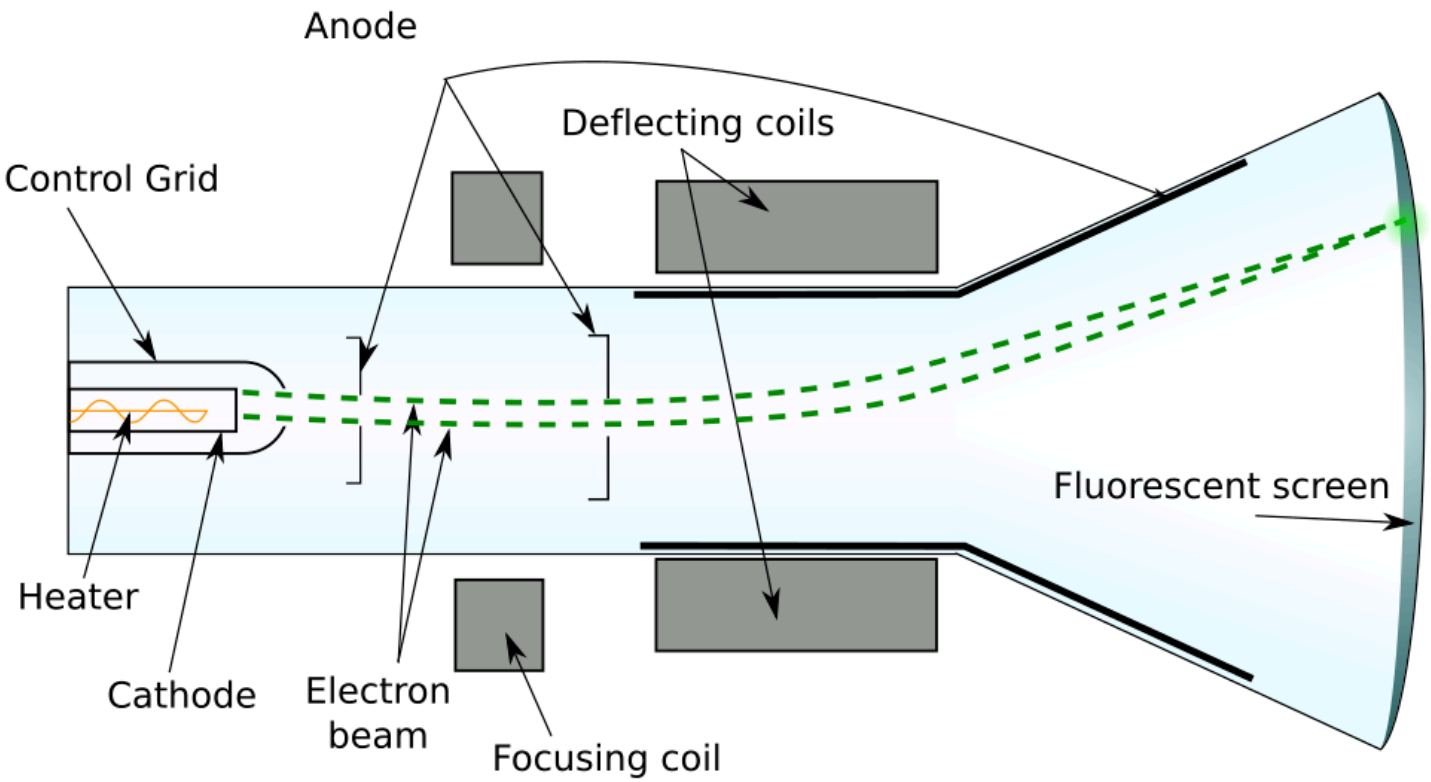

Cathode-ray tube of a CRO.

Evacuated funnel-shaped glass tube containing:

1. **Electron gun:** indirectly heated **cathode** (barium/strontium oxide coated) emits electrons → **control grid** (negative w.r.t. cathode; sets beam current ⇒ **intensity/brightness** control) → **pre-accelerating & accelerating anodes** (high +ve) → **focusing anode** (electrostatic lens; **focus** control). "Astigmatism" control shapes the spot round.
2. **Deflection system:** two pairs of **electrostatic deflection plates** — vertical (Y) plates deflect vertically, horizontal (X) plates deflect horizontally. (Electrostatic deflection is used in CROs because it responds to high frequencies; TVs used magnetic deflection.)

- **Deflection on screen:** $D = (l \cdot L \cdot V_d) / (2 \cdot d \cdot V_a)$

where l = plate length, L = plate-centre-to-screen distance, d = plate separation, V_d = deflecting voltage, V_a = accelerating voltage.

- **Deflection sensitivity S = D/V_d = lL/(2dV_a)** (mm/V) — **inversely proportional to accelerating voltage**; **deflection factor = 1/S (V/mm)**.
- **Post-deflection acceleration (PDA)** electrodes brighten the trace without hurting sensitivity.

1. **Screen:** inside face coated with **phosphor** (e.g., P31 for general use — green, medium persistence; P11 short persistence for photography; long-persistence types for slow phenomena). Light emission on impact = **fluorescence**; continued glow after = **phosphorescence**; **persistence** = time the glow lasts.
2. **Aquadag coating:** conductive **graphite coating** on the inner funnel; it (i) is held at accelerating potential to accelerate/collect **secondary-emission electrons** from the screen, completing the beam return path, and (ii) shields the beam.

6.14.4 Probes ☆ (asked in 22-04-2025)

Probe	Description
1:1 (direct) probe	Shielded coaxial lead, no attenuation; loads the circuit with full cable + input capacitance (~100 pF); only for low-frequency, strong signals
10:1 attenuating (passive) probe	9 MΩ resistor **with adjustable parallel capacitor** in the tip, working against the scope's 1 MΩ ‖ C_in → attenuation 10×, input resistance raised to **10 MΩ**, capacitive loading cut ~10×
Probe compensation	The tip capacitor is trimmed so $\mathbf{R_1C_1 = R_2C_2}$ (a *compensated attenuator* — division ratio then independent of frequency). Checked on the scope's ~1 kHz **CAL square wave**: flat top = compensated; rounded = under-compensated; overshoot/spiked = over-compensated
Active (FET) probe	FET buffer at the tip: very low capacitance, no attenuation, for high frequency
Current probe	Clamp-on Hall/transformer sensor — measures current without breaking circuit

Why is the probe cable shielded (coaxial)? ☆ The signal conductor is surrounded by a **grounded braided shield**. The shield intercepts external electric fields and diverts induced currents to ground, so **stray pickup of external electrical interference — mains hum, RF, switching noise (EMI) — is prevented from corrupting the small measured signal**. It also defines a controlled impedance and keeps the probe from radiating. *This is exactly the 2025 PYQ.*

6.14.5 Measurements with a CRO

- **Amplitude:** V = (vertical divisions) × (VOLTS/div) × probe factor. Peak-to-peak read directly; V_rms = V_pp/(2√2) for a sine.
- **Time period:** T = (horizontal divisions for one cycle) × (TIME/div).
- **Frequency:** f = 1/T.
- **Phase difference (dual trace):** φ = (Δt / T) × 360°.
- **Phase by ellipse (X-Y):** sin φ = (Y-intercept)/(Y-max) = B/A.
- **Frequency by Lissajous figures (X-Y mode):**

f_Y / f_X = (number of horizontal tangencies) / (number of vertical tangencies)

(= points of tangency to a horizontal line / to a vertical line)

Ratio f_y : f_x	Pattern (equal amplitudes)
1 : 1, φ = 0°	Straight line at 45°
1 : 1, φ = 90°	Circle
1 : 1, 0<φ<90°	Ellipse
1 : 1, φ = 180°	Straight line at 135°
2 : 1	Figure-of-eight (∞ rotated) — 2 tangencies top, 1 on side
3 : 1	Three-lobed pattern
3 : 2	Complex loop — 3 horizontal tangencies, 2 vertical

6.14.6 Dual-Trace vs Dual-Beam; DSO

- **Dual-trace CRO: one** electron beam, electronically switched between two Y channels — **ALTERNATE mode** (a full sweep of each channel alternately; good for fast signals) and **CHOP mode** (switches between channels at ~100–500 kHz during each sweep; good for slow signals). Cannot truly capture two one-shot events simultaneously.
- **Dual-beam CRO: two** independent beams (two guns or split beam) with separate vertical systems — genuinely simultaneous display; costlier.
- **Digital Storage Oscilloscope (DSO):** input → attenuator/amp → **sample-and-hold → ADC → acquisition memory → microprocessor → display** (raster LCD).

Advantages: stores waveforms indefinitely; captures **single-shot/transient** events; **pre-trigger viewing** (see what happened *before* the trigger); automatic measurements, cursors, FFT, averaging (noise reduction), storage/USB/printing; no CRT drift.

Key specs: **sampling rate (Sa/s ≥ 2× bandwidth by Nyquist, practically ≥10×)**, record length, resolution (8-bit typical). Modes: real-time sampling (single shot) and equivalent-time sampling (repetitive signals). *Aliasing* occurs if sampling is too slow.

6.15 Display Panels — LED and LCD

6.15.1 LED Displays

- **LED** = forward-biased **p–n junction** in a direct-band-gap material (GaAs — IR; GaAsP — red/orange/yellow; GaP, GaN/InGaN — green/blue). Emits light by **injection electroluminescence — radiative recombination** of electrons and holes; photon energy ≈ E_g, so **λ = 1240/E_g(eV) nm**.
- Typical drop 1.8–3.3 V; always used with a **current-limiting resistor**; fast (ns), long life, rugged, wide temperature range.
- **Seven-segment display:** segments **a–g (+ dp)**.
- **Common-anode (CA):** all anodes tied to +V; a segment lights when its cathode is pulled **LOW** (driver sinks current, e.g., 7447 decoder).
- **Common-cathode (CC):** all cathodes grounded; segment lights on **HIGH** (e.g., 7448/4511 decoder).
- **Multiplexing:** in a multi-digit display all like segments are bussed together and digits are enabled **one at a time in rapid rotation (> ~50–100 Hz refresh)**; persistence of vision shows all digits lit. Saves driver pins and power.
- Dot-matrix (5×7) LED displays show alphanumerics.

6.15.2 LCD Displays

- **Principle:** liquid crystals (nematic phase) do not emit light — they **modulate external light**. The dominant type is the **Twisted Nematic (TN) field-effect** cell: LC fluid between two glass plates with transparent **ITO electrodes** and crossed **polarizers**; the molecular director twists 90° across the cell.
- **No field:** the twist rotates the polarization 90° → light passes the second polarizer → segment **clear/bright**.

- **Field applied (few volts AC):** molecules align with the field, twist destroyed, no rotation → light blocked → segment appears **dark**.
- **Driven by AC (30–100 Hz square wave), never DC** — DC causes electrochemical degradation of the electrodes.
- **Dynamic-scattering** LCDs (older) become milky-white under field.
- Reflective (uses ambient light + rear mirror) or **backlit/transmissive**.

6.15.3 LED vs LCD Comparison ☆

Feature	LED display	LCD display
Light	**Emits** its own light (active)	**Modulates** ambient/backlight (passive)
Power	mA per segment (10–20 mA) — relatively high	**µW per segment** — extremely low (ideal for watches, DMMs, calculators)
Drive	DC, current-driven	**Low-voltage AC**, voltage-driven
Visibility	Excellent in dark; washes out in sunlight	Excellent in bright light; needs backlight in dark
Viewing angle	Wide	Limited (TN)
Speed	ns — very fast	**ms — slow**; sluggish at low temperature
Temperature range	Wide (−40 to +85 °C)	Narrow (LC freezes/clears outside range)
Life/ruggedness	Very long, rugged	Long but fluid-based, fragile glass

6.15.4 OLED (brief)

Organic LED: thin films of organic semiconductor emit light on current injection — **self-emissive** (no backlight), so true blacks, very high contrast, wide viewing angle, thin/flexible panels, fast response; drawbacks: differential ageing of blue emitters and burn-in. Each pixel is its own light source — conceptually "an LED display with LCD-class resolution."

6.16 Transducers — In Depth ☆☆☆

A **transducer** converts one form of energy/physical quantity into another — in instrumentation, usually a non-electrical measurand into an **electrical** signal. (Sensor = sensing element; transducer = sensor + conversion.)

6.16.1 Classification

Basis	Types	Examples
Power source	**Active (self-generating)** — generate their own electrical output, need **no external supply**	Thermocouple, piezoelectric, photovoltaic cell, electromagnetic (tachogenerator)
	Passive — need external excitation; measurand changes a passive parameter (R, L, C)	Strain gauge, RTD, thermistor, LVDT, capacitive, LDR
Conversion stage	**Primary** — first element sensing the measurand (may give mechanical output)	Bourdon tube, diaphragm, bimetal
	Secondary — converts the primary's output to electrical	LVDT sensing Bourdon-tube tip motion
Output nature	**Analog** (continuous)	LVDT, thermocouple, strain gauge
	Digital (discrete/pulse)	Shaft encoder, turbine flowmeter pulses
Principle	Resistive, inductive, capacitive, piezoelectric, thermoelectric, photoelectric, Hall-effect	see below

Selection criteria: range & span, required accuracy/linearity/sensitivity, operating environment (temperature, corrosion, vibration), loading effect on the measurand, frequency response/speed, output impedance & signal level, ruggedness, size, cost, availability of excitation.

6.16.2 Resistive Transducers

(a) Potentiometer (POT): resistance wire/film with sliding wiper; **linear or rotary displacement → resistance/voltage ratio**. Simple, cheap, high output; but friction, wear, limited resolution (wire-wound), loading error if output is loaded.

(b) Strain gauge ⭐: a metal foil/wire grid bonded to the specimen; strain changes its resistance.

Gauge factor:

$G_f = (\Delta R/R) / (\Delta l/l) = (\Delta R/R)/\varepsilon = 1 + 2\nu + (\Delta\rho/\rho)/\varepsilon$

(1 from length, 2ν from area/Poisson effect ν ≈ 0.3, last term = piezoresistive effect.)

- Metal gauges: $G_f \approx$ **2** (constantan/advance, nichrome); semiconductor gauges: $G_f \approx$ **100–200** (large piezoresistive term) but temperature-sensitive and non-linear.
- Used in a **Wheatstone bridge** (quarter/half/full) — full bridge with 4 active gauges gives 4× output and temperature compensation; **dummy gauge** compensates temperature in quarter-bridge.

> **Worked Example 6.8 (strain gauge).**
>
> A 120 Ω strain gauge, $G_f = 2.0$, is bonded to a steel member under stress $\sigma = 100$ MN/m² ($E = 200$ GN/m²). Find ΔR.
>
> Strain $\varepsilon = \sigma/E = 100\times10^{6} / 200\times10^{9} = 5\times10^{-4}$ (= 500 microstrain).
>
> $\Delta R = G_f \cdot \varepsilon \cdot R = 2 \times 5\times10^{-4} \times 120 =$ **0.12 Ω** ($\Delta R/R = 0.1$ %).

(c) RTD (Resistance Temperature Detector): pure metal (usually **platinum**) whose resistance rises almost linearly with temperature — **positive temperature coefficient**.

$R_t = R_0(1 + \alpha\Delta T)$, $\alpha_{Pt} \approx 0.00385$ /°C.


PT100 = platinum RTD with R = 100 Ω at 0 °C (≈ 138.5 Ω at 100 °C). Range ≈ −200 to +850 °C; excellent accuracy & stability; 3-wire/4-wire connection cancels lead resistance; needs excitation current (self-heating error must be limited).

(d) Thermistor: sintered metal-oxide semiconductor bead; **NTC** — resistance **falls exponentially** with temperature:

$R_T = R_0 \cdot \exp[\beta(1/T - 1/T_0)]$, β ≈ 3000–4500 K.

Very high sensitivity (−4 %/°C, ~10× RTD), small, fast, cheap; but **highly non-linear**, narrow range (−50 to +300 °C), interchangeability issues. (PTC thermistors exist — used as resettable fuses/protection, not measurement.)

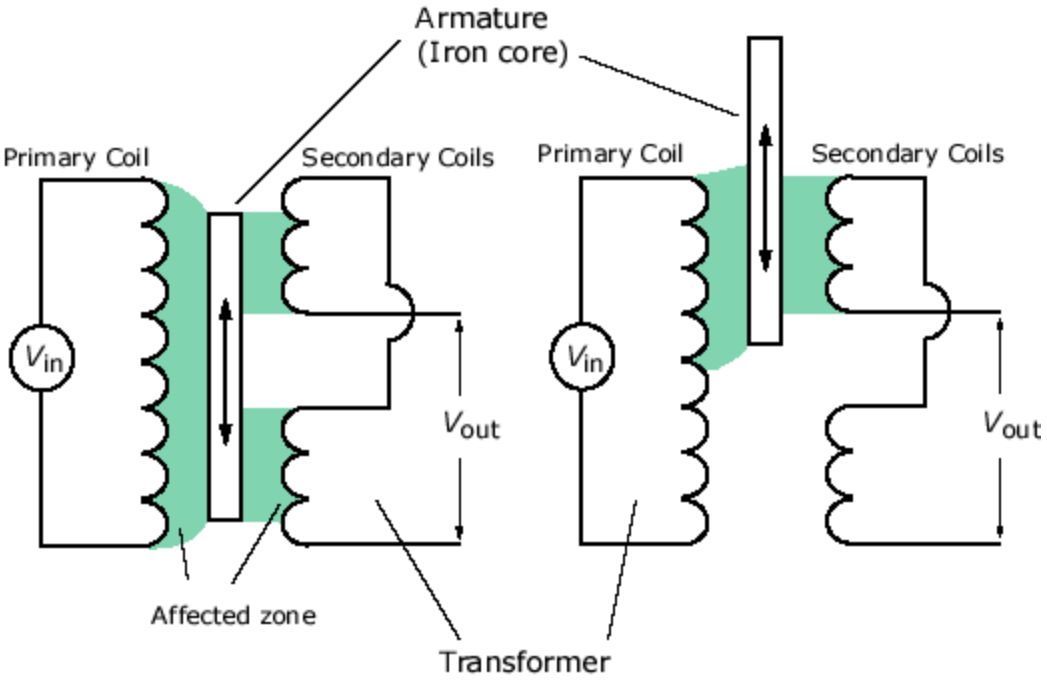6.16.3 Inductive — LVDT ☆☆ (exam favourite)



LVDT displacement transducer.

Linear Variable Differential Transformer — passive, inductive **displacement** transducer.

Construction: one **primary** winding centred between **two identical secondaries wound in series opposition**, on a hollow former; a **soft-iron (Ni-Fe) core** attached to the moving member slides inside without touching.

Working: primary excited by AC (50 Hz–20 kHz).

- Core central (**null position**): equal coupling → V_s1 = V_s2 → net output **$V_0 = V_{s1} - V_{s2} = 0$**.
- Core moves toward secondary 1: V_s1 > V_s2 → output rises **in phase** with a reference.
- Core moves the other way: output rises with **180° phase reversal**.

Thus $|V_0|$ ∝ displacement (linear over the rated range) and **phase gives direction** (phase-sensitive detector converts to signed DC).

Residual (null) voltage: the small output (< 1 % of FS) that remains at the null position — caused by harmonics in excitation, stray capacitance and winding asymmetry. It limits resolution; minimized by good construction and phase-sensitive demodulation.

Advantages: frictionless & wear-free (no contact between core and coils) → essentially **infinite resolution** and very long life; excellent **linearity** (~0.5 %); high sensitivity/output; rugged; overload-safe; DC-out versions available.

Limitations: sensitive to stray AC fields (needs shielding), core mass limits fast dynamics, temperature effects, needs AC excitation + demodulation.

Applications: displacement 1 μm – 25 cm; secondary transducer for pressure (with Bourdon/diaphragm), load, thickness, machine-tool gauging. (**RVDT** = rotary version for angles ±40°.)

6.16.4 Capacitive Transducers

$C = \varepsilon_0 \varepsilon_r A/d$. Vary any of the three:

- **Δd (gap change):** most sensitive, non-linear ($C \propto 1/d$) — pressure microphones, diaphragm pressure sensors; differential (push-pull) arrangement linearizes.
- **ΔA (area overlap):** linear — angular/linear displacement.
- **Δε_r (dielectric change):** liquid **level** gauging, moisture/humidity sensors.

High impedance output → needs shielded leads and AC bridge/oscillator circuits; very sensitive, tiny forces needed, good frequency response; affected by stray capacitance.

6.16.5 Piezoelectric Transducers

Active transducer: mechanical stress on an asymmetric crystal displaces its internal charge centres → **charge appears on the faces** (piezoelectric effect); converse effect used in ultrasonic generators.

- Materials: **quartz** (stable, natural), Rochelle salt (most sensitive, fragile), synthetic ceramics **barium titanate, PZT** (lead-zirconate-titanate).
- Charge output **Q = d·F** (d = charge sensitivity, C/N; for quartz d ≈ 2.3 pC/N); voltage V = Q/C = g·t·P.
- Very high output impedance → **charge amplifier** needed; **cannot measure true static (DC) quantities** — charge leaks away; superb for **dynamic** measurements: vibration **accelerometers**, force/pressure transients, ultrasonics, spark igniters.

6.16.6 Thermocouple ☆

Seebeck effect: in a circuit of **two dissimilar metals** with junctions at different temperatures, an EMF proportional (approx.) to the junction temperature difference is generated: **$E \approx \alpha(T_{hot} - T_{cold})$**. Active transducer.

(Related: **Peltier effect** — heat absorbed/liberated at a junction carrying current; **Thomson effect** — EMF along a single conductor with a temperature gradient.)

Type	Materials (+/−)	Range (approx.)	Sensitivity	Notes
J	Iron / Constantan	−40 to 750 °C	~55 μV/°C	Cheap; iron rusts, not for oxidizing high temp
K	Chromel / Alumel	−200 to 1260 °C	~41 μV/°C	**General-purpose workhorse**, most common
T	Copper / Constantan	−200 to 350 °C	~43 μV/°C	Best for low/cryogenic temperatures
E	Chromel / Constantan	−200 to 900 °C	~68 μV/°C	**Highest sensitivity**
R	Pt–13 %Rh / Pt	0 to 1600 °C	~10 μV/°C	High temperature, precious metal
S	Pt–10 %Rh / Pt	0 to 1600 °C	~10 μV/°C	Standard instrument thermocouple (old IPTS standard)
B	Pt-30%Rh / Pt-6%Rh	up to 1800 °C	very low	Highest range

Cold-junction compensation (CJC): thermocouple EMF depends on **both** junction temperatures; tables assume the reference junction at **0 °C**. In practice the reference sits at ambient, so either keep it in an ice bath, or (modern way) **measure the terminal-**

block temperature with an RTD/thermistor/IC sensor and add the corresponding EMF electronically. **Law of intermediate metals** allows the meter's copper terminals in the loop without error if both connections are at the same temperature; **compensating/extension cables** must match the thermocouple alloys.

6.16.7 Photoelectric Transducers

- **Photodiode:** reverse-biased p-n/PIN junction; light generates carriers → reverse (photo)current ∝ **illumination**; very fast (ns) — optical communication, encoders, light meters. (Phototransistor = photodiode + gain, slower.)
- **LDR (photoconductive cell, CdS/CdSe):** resistance **falls** (MΩ → hundreds of Ω) with illumination; cheap, sensitive, but slow (ms–s) — light-operated relays, street-light controls.
- **Photovoltaic (solar) cell: active** — illuminated junction generates EMF (~0.5 V Si) with no bias; power source + lux meters.
- (Photoemissive tubes/photomultipliers: electron emission from a photocathode; PMT for extremely low light.)

6.16.8 Hall-Effect Sensor

Current-carrying semiconductor slab in a **perpendicular magnetic field B** develops a transverse voltage:

$V_H = (B \cdot I)/(n \cdot q \cdot t) = R_H \cdot B \cdot I/t$ (t = thickness, R_H = Hall coefficient, large in semiconductors).

Measures **magnetic field**, and hence anything convertible to B: **contactless current sensing (clamp meters), position/proximity, brushless-DC rotor position, keyboards, speed sensing**. Output exists even for **DC fields** (unlike inductive pickups); polarity of V_H identifies carrier type (n or p).

6.16.9 Load Cell

Elastic member (column, ring, cantilever or shear beam) + **four bonded strain gauges in a full Wheatstone bridge** → output mV/V proportional to applied **force/weight**; temperature-compensated, linear to 0.02 %; the heart of electronic weighing machines, tank weighing, and material-testing machines. (Hydraulic/pneumatic load cells exist for special environments; piezoelectric washers for dynamic force.)

6.16.10 Digital Encoders (one paragraph)

A **shaft encoder** converts angular (or, as a linear scale, translational) position directly into digital form. **Incremental encoders** output pulse trains from an optical disc (LED–photodiode reading slots); position = pulse count, speed = pulse rate, and two channels in **quadrature (90°)** give direction; an index pulse marks zero — but position is lost at power-down. **Absolute encoders** carry a multi-track coded disc that outputs a unique word per position; **Gray code** is used instead of straight binary so that **only one bit changes between adjacent positions**, preventing gross misreads at track boundaries. Resolution = $360°/2^n$ for n tracks; encoders are noise-immune, wear-free (optical) and interface directly to digital systems.

6.17 Worked Numericals (Consolidated Set)

(Examples 6.1–6.8 above are part of the count; three more below complete the mandated set.)

> **Worked Example 6.9 (CRO time-base reading).**

> A CRO displays 2.5 complete cycles across 10 horizontal divisions with TIME/div = 20 µs. The waveform is 6 divisions peak-to-peak with VOLTS/div = 0.5 V via a 10:1 probe. Find f and V_{rms} (sine).

> One cycle occupies 10/2.5 = 4 div ⟹ T = 4 × 20 µs = 80 µs ⟹ **f = 12.5 kHz**.

> V_{pp} = 6 × 0.5 × 10 = 30 V ⟹ V_m = 15 V ⟹ **$V_{rms} = 15/\sqrt{2} = 10.6$ V**.

Worked Example 6.10 (Lissajous frequency ratio).

An unknown frequency f_y drives the Y-input and a 2 kHz standard drives X. The stationary pattern touches a horizontal tangent line at **3** points and a vertical tangent line at **2** points. Find f_y.

f_y/f_x = horizontal tangencies / vertical tangencies = 3/2 $\Longrightarrow$ f_y = (3/2)(2 kHz) = **3 kHz**.

Worked Example 6.11 (delay line).

A CRO lumped delay line has 30 identical sections with L = 60 μH and C = 1.5 pF per section. Find the delay per section, total delay and characteristic impedance.

$t_s = \sqrt{(LC)} = \sqrt{(60\times10^{-6} \times 1.5\times10^{-12})} = \sqrt{(9\times10^{-17})} = 9.49$ ns? → $\sqrt{(9.0\times10^{-17})} = 9.49\times10^{-9}$ s ≈ **9.5 ns/section**? Recheck: $60\times10^{-6} \times 1.5\times10^{-12} = 90\times10^{-18} = 9.0\times10^{-17} \Longrightarrow \sqrt{} = 9.49\times10^{-9}$ s ✓.

Hmm — that is large per section; realistic lines use smaller L. Taking the given values: t_s ≈ **9.5 ns**, total t_d = 30 × 9.5 ns ≈ **285 ns**; $Z_0 = \sqrt{(L/C)} = \sqrt{(60\times10^{-6}/1.5\times10^{-12})} = \sqrt{(4\times10^{7})}$ = **6.32 kΩ** — the line must be terminated in ~6.3 kΩ to prevent reflections.

Takeaway: delay is set purely by **n√(LC)** — the 2025 PYQ point.

Worked Example 6.12 (deflection sensitivity).

In a CRT, plate length l = 2 cm, plate separation d = 0.5 cm, plate-centre-to-screen distance L = 20 cm, accelerating voltage V_a = 2000 V. Find deflection sensitivity.

$S = lL/(2dV_a) = (0.02 \times 0.20)/(2 \times 0.005 \times 2000) = 0.004/20 = 2\times10^{-4}$ m/V = **0.2 mm/V**. Deflection factor = 1/S = **5 V/mm**.

(Count of worked numericals in this chapter: 6.1 limiting error, 6.2 % error, 6.3 energy meter, 6.4 & 6.5 shunt, 6.6 multiplier, 6.7 loading, 6.8 strain gauge, 6.9 CRO reading, 6.10 Lissajous, 6.11 delay line, 6.12 deflection — 12 total.)

6.18 PYQ Corner — Fully Solved

PYQ 1 (RRB JE CBT-2, 22-04-2025)

Q. Why is the cable of an oscilloscope probe shielded?

(a) To increase its mechanical strength (b) To reduce pickup of external electrical interference/noise (c) To increase the probe's attenuation ratio (d) To provide the delay required by the time base

Solution. The probe carries a small, high-impedance signal from the circuit to the CRO. An unshielded lead acts as an antenna, picking up mains hum, RF and switching noise through capacitive and electromagnetic coupling. The **grounded coaxial shield** surrounds the inner signal conductor, intercepts external fields and returns induced currents to ground, so the displayed signal is not corrupted. **Answer: (b).** (Note: shielding does not set attenuation — the tip RC divider does — and delay is the job of the delay line inside the scope.)

PYQ 2 (RRB JE CBT-2, 22-04-2025)

Q. The length (delay) of the electrical delay line in a CRO is determined by:

(a) The brightness of the trace (b) The speed at which the signal propagates along it, fixed by its L and C parameters (c) The phosphor persistence (d) The vertical amplifier gain

Solution. The electrical delay line is a lumped low-pass chain of identical LC sections. A signal travels along it at a finite speed set by L and C; delay per section = **$\sqrt{LC}$** and total delay = **$n\sqrt{LC}$**, with $Z_0 = \sqrt{L/C}$. The physical/electrical "length" needed is therefore governed by the **propagation speed of the signal on the line** — i.e., by its LC parameters — so that the vertical signal reaches the plates ~100–200 ns after the trigger has started the sweep. **Answer: (b).**

PYQ-style 3

Q. A 1 mA, 100 Ω movement is to be converted into a 0–10 A ammeter. The required shunt is:

(a) 0.01 Ω (b) 0.1 Ω (c) 0.010001 Ω (d) 1 Ω

Solution. m = 10/0.001 = 10 000. $R_{sh} = R_m/(m-1) = 100/9999$ = **0.010001 Ω ≈ 0.01 Ω**. Strictly **(c)** (≈ (a) to 2 s.f.); in exam options the exact value 100/9999 Ω is the correct pick. **Answer: (c).**

PYQ-style 4

Q. In an LVDT, when the core is exactly at the centre, the output voltage is ideally zero, but a small voltage is still observed. This is called:

(a) Offset voltage (b) Residual/null voltage (c) Ripple voltage (d) Quadrature drive

Solution. With the two secondaries in series opposition, perfect symmetry would give zero at centre; in practice harmonics, stray capacitance and winding mismatch leave a small **residual (null) voltage**, typically < 1 % of full-scale output. **Answer: (b).**

PYQ-style 5

Q. A Wheatstone bridge has P = 1000 Ω, Q = 100 Ω, and balances with the standard arm S = 46.3 Ω. The unknown resistance is:

(a) 4.63 Ω (b) 46.3 Ω (c) 463 Ω (d) 4630 Ω

Solution. At balance $R = (P/Q)\cdot S = (1000/100) \times 46.3$ = **463 Ω**. **Answer: (c).**

6.19 Practice MCQs (25) with Answer Key

1. The first element of a generalized measurement system that receives energy from the measurand is the:

(a) signal conditioner (b) primary sensing element (c) data presentation element (d) transmission channel

2. An instrument gives readings 50.1, 50.0, 50.2, 50.1 V when the true value is 49.0 V. The instrument is:

(a) accurate and precise (b) accurate but not precise (c) precise but not accurate (d) neither

3. Parallax error is a:

(a) random error (b) gross/observational error (c) instrumental systematic error (d) environmental error

4. A 0–100 V voltmeter guaranteed to ±2 % of FSD reads 40 V. The possible % error in the reading is:

(a) ±2 % (b) ±0.8 % (c) ±5 % (d) ±8 %

5. Gravity control gives a scale that is:

(a) uniform (b) cramped at the lower end (c) cramped at the upper end (d) logarithmic

6. Eddy-current damping cannot be used in moving-iron instruments because:

(a) it is too weak (b) the required permanent magnet would distort the operating field (c) MI instruments need no damping (d) the vane is non-conducting

7. A PMMC meter connected to 50 Hz AC will:

(a) read RMS (b) read average (c) read peak (d) show zero/vibrate about zero

8. In a PMMC instrument, the deflecting torque is:

(a) $\propto I^2$ (b) $\propto I$ (c) $\propto \sqrt{I}$ (d) $\propto 1/I$

9. An energy meter with only the potential coil energized rotates slowly. This is prevented by:

(a) a lag coil (b) two holes drilled in the disc (c) moving the brake magnet inward (d) shading the series magnet

10. A dynamometer wattmeter deflection is proportional to:

(a) $V \cdot I$ (b) $V \cdot I \cdot \cos\varphi$ (c) $V \cdot I \cdot \sin\varphi$ (d) I^2

11. A 50 μA, 2 kΩ movement is used as a voltmeter. Its sensitivity is:

(a) 2 kΩ/V (b) 10 kΩ/V (c) 20 kΩ/V (d) 40 kΩ/V

12. For the meter of Q.11 to read 0–100 V, the multiplier resistance is:

(a) 2 MΩ (b) 1.998 MΩ (c) 2.002 MΩ (d) 200 kΩ

13. The secondary of a current transformer should never be open-circuited because:

(a) the primary fuse blows (b) dangerously high voltage is induced and the core saturates/overheats (c) the secondary current becomes excessive (d) the burden rises to infinity

14. Kelvin double bridge is preferred for low resistances because it eliminates the effect of:

(a) supply variations (b) contact and lead resistances (c) temperature (d) galvanometer resistance

15. Insulation resistance of a cable is measured with:

(a) Kelvin bridge (b) Wheatstone bridge (c) Megger (d) potentiometer

16. The bridge best suited for measuring an inductor with $Q > 10$ is:

(a) Maxwell (b) Hay (c) Schering (d) De Sauty

17. The Schering bridge is chiefly used to measure:

(a) frequency (b) low resistance (c) capacitance and loss angle of insulation (d) mutual inductance

18. A Wien bridge with $R_1 = R_2 = 10$ kΩ and $C_1 = C_2 = 0.01$ μF balances at a frequency of about:

(a) 15.9 Hz (b) 159 Hz (c) 1.59 kHz (d) 15.9 kHz

19. A 3½-digit DVM on its 20 V range has a resolution of:

(a) 1 mV (b) 10 mV (c) 100 mV (d) 1 V

20. In a CRO, the delay line is placed:

(a) before the attenuator (b) in the trigger circuit (c) in the vertical channel between amplifier and Y-plates (d) after the time base

21. The aquadag coating in a CRT serves to:

(a) focus the beam (b) collect secondary-emission electrons and complete the return path (c) generate the sweep (d) blank the retrace

22. A 10:1 probe is "compensated" when:

(a) its resistance equals the scope input resistance (b) $R_1C_1 = R_2C_2$ so division is frequency-independent (c) the cable is exactly 1 m (d) the shield is left floating

23. A Lissajous pattern shows 4 tangencies to a horizontal line and 1 to a vertical line. If f_x = 500 Hz, f_y is:

(a) 125 Hz (b) 500 Hz (c) 1 kHz (d) 2 kHz

24. Which transducer is active (self-generating)?

(a) strain gauge (b) LVDT (c) thermocouple (d) thermistor

25. PT100 denotes:

(a) a thermistor of 100 Ω at 25 °C (b) a platinum RTD of 100 Ω at 0 °C (c) a thermocouple with 100 µV/°C (d) a potentiometer of 100 Ω

Answer Key with Brief Explanations

Q	Ans	Why
1	b	Primary sensing element (detector) contacts the measurand first
2	c	Tight cluster (precise) but offset ~1.1 V from truth (inaccurate)
3	b	Human/observational mistake; mirror scales reduce it
4	c	±2 V absolute; 2/40 × 100 = ±5 %
5	b	$T_c = WI \sin\theta \rightarrow$ small controlling torque at small θ → crowded low end
6	b	A damping magnet would superpose on the operating flux of the MI coil
7	d	Mean torque zero on AC; pointer merely vibrates
8	b	$T_d = NBAI = GI \rightarrow$ linear scale
9	b	Creep; holes rest under the shunt-magnet pole
10	b	Average torque ∝ VI cos φ = true power
11	c	$S = 1/I_{fsd} = 1/50\ \mu A = 20\,000\ \Omega/V$
12	b	$R_{total} = 20\ k\Omega/V \times 100\ V = 2\ M\Omega$; $R_s = 2\ M\Omega - 2\ k\Omega = 1.998\ M\Omega$
13	b	No opposing MMF → flux soars → high secondary EMF + core heating
14	b	Second ratio-arm pair cancels yoke/lead resistance
15	c	Megger: hand-driven DC generator + ratiometer ohmmeter
16	b	Hay (series R-C arm) suits high-Q; Maxwell suits 1<Q<10
17	c	Standard bridge for capacitor/insulation tan δ, incl. HV
18	c	$f = 1/(2\pi RC) = 1/(2\pi \times 10^4 \times 10^{-8}) = 1591$ Hz
19	b	3½ digits → 2000 counts; 20 V/2000 = 10 mV
20	c	Delays signal so the sweep (already triggered) shows the leading edge
21	b	Graphite layer at anode potential collects secondaries, shields beam
22	b	Compensated attenuator condition; check on CAL square wave
23	d	$f_y/f_x = 4/1 \rightarrow f_y = 4 \times 500 = 2000$ Hz

Q	Ans	Why
24	c	Seebeck EMF is self-generated; others need excitation
25	b	Platinum, 100 Ω at 0 °C, α ≈ 0.00385/°C

6.20 Rapid-Revision Sheet

Torque & Instrument Formulas

Item	Formula / fact				
PMMC torque	$T_d = NBAI = GI$; $\theta \propto I$ (uniform scale, DC only, eddy-current damping)				
Moving iron	$T_d = \frac{1}{2} I^2 dL/d\theta$; $\theta \propto I^2$, AC+DC (RMS), air-friction damping				
Dynamometer	$T \propto i_1 i_2 dM/d\theta$; wattmeter reads $VI \cos\varphi$, uniform scale				
Energy meter	$N \propto$ power; revolutions $\propto$ energy; creep → 2 holes in disc; brake magnet in → faster				
Spring control	$T_c = K\theta$	Gravity control	$T_c = WI \sin\theta$ (vertical use, cramped scale)		
Shunt	**$R_{sh} = R_m/(m-1)$**, $m = I/I_m$				
Multiplier	**$R_s = R_m(m-1)$**, $m = V/V_m$				
Sensitivity	$S = 1/I_{fsd}$ (Ω/V); $R_v = S \times$ range				
CT/PT	CT primary in series (sec. 5 A/1 A); PT across line (sec. 110 V); **never open a live CT secondary**; burden in VA				
Wheatstone	$R = (P/Q)S$	Kelvin double	low R, cancels lead/contact R	Megger	insulation MΩ
CRT sensitivity	$S = lL/(2dV_a)$ — ↓ as V_a ↑				
Delay line	$t_d = n\sqrt{(LC)}$; $Z_0 = \sqrt{(L/C)}$; shielded probe → noise immunity				
Lissajous	f_y/f_x = horizontal tangencies / vertical tangencies				
Limiting error	worst at low scale → use upper third				

AC Bridge Table

Bridge	Measures	Key relation
Maxwell	L (1 < Q < 10)	$L = R_2R_3C_4$ (freq-independent)
Hay	L (Q > 10)	$L \approx R_2R_3C_4$ (freq-dependent)
Schering	C & tan δ (insulation, HV)	$C_1 = C_2R_4/R_3$; $D = \omega C_4R_4$
Wien	Frequency	$f = 1/(2\pi RC)$, $R_4/R_3 = 2$
Kelvin (DC)	Low R	$R = (P/Q)S$
De Sauty	Loss-free C	$C_1/C_2 = R_4/R_3$

Transducer Classification Table

Class	Members	Memory hook
Active (no excitation)	Thermocouple, piezoelectric, photovoltaic, tachogenerator	"They **generate**"
Passive (R, L, C change)	Strain gauge, RTD, thermistor, POT (R); LVDT (L); capacitive (C); LDR	"They **modulate**"
Resistive facts	G_f = 1+2ν+piezoresistive ≈ **2** (metal), 100–200 (semiconductor); **PT100** = Pt, 100 Ω @ 0 °C, **+TC**; thermistor **NTC**, exponential	
LVDT	Two secondaries in series opposition; null output at centre; phase reverses through null; **residual voltage** at null; frictionless, infinite resolution	
Piezoelectric	Active; quartz/PZT; Q = dF; **dynamic only** (no static DC)	
Hall	V_H = BI/(nqt); contactless current & position sensing	
Load cell	4 strain gauges, full bridge	
Encoders	Incremental (quadrature, count) vs absolute (**Gray code**, unique word)	

Thermocouple Types

Type	Pair	Range	Note
J	Fe/Constantan	to 750 °C	cheap
K	Chromel/Alumel	to 1260 °C	**most common**
T	Cu/Constantan	to 350 °C	cryogenic
E	Chromel/Constantan	to 900 °C	highest μV/°C
R/S	Pt-Rh/Pt	to 1600 °C	precision, high T
B	PtRh30/PtRh6	to 1800 °C	highest range
CJC	Reference junction at 0 °C assumed; compensate electronically (RTD/IC at terminals)		

Display One-Liners

- **LED:** emits (electroluminescence), λ = 1240/E_g nm, CA segment lights on LOW, CC on HIGH; multiplex digits > 50 Hz.
- **LCD:** modulates light, twisted-nematic 90°, **AC drive only**, μW power, slow (ms), poor in dark without backlight.
- **OLED:** self-emissive organic pixels — true black, thin, flexible; ageing/burn-in.

CRO One-Liners

- Trigger = same point every sweep → stable trace; sweep = linear sawtooth; retrace blanked.
- **Delay line delays vertical signal ≈ 100–200 ns so the triggering edge itself is displayed; delay = n√(LC).**
- **Probe cable is shielded coax to stop external EMI/noise pickup**; 10:1 probe → 10 MΩ, compensate on CAL square wave.
- Dual-trace = one beam switched (ALT/CHOP); dual-beam = two beams; DSO = S/H + ADC + memory → single-shot & pre-trigger capture; beware aliasing.

End of Chapter 6. Next: Chapter 7 as per book plan.

Chapter 7 — Communication Engineering

RRB JE CBT-2 · Electronics & Allied Engineering (CEN 05/2025, Annexure-VII C) · Syllabus Unit 7

📊 Weightage & Trend Box

Parameter	Detail
Approx. weightage	~16% of technical marks — one of the two heaviest units
Questions in 22-04-2025 CBT-2 paper	**8 out of 50** technical questions
Difficulty profile	Mostly conceptual one-liners + 1–2 direct formula numericals
Hottest sub-topics	PLL applications (FM & AM detection), pulse modulation family (PWM/PDM/PPM), digital modulation (QPSK), pulse shaping, AM power relations, Fourier symmetry

Actual questions observed in the 22-04-2025 paper (all solved in the PYQ Corner):

1. FM detection (demodulation) using a **PLL** — identifying the correct statement/output point.
2. Alternate name of **PWM** — Pulse **Duration** Modulation (PDM), a member of the Pulse **Time** Modulation (PTM) family.
3. **QPSK** — the four carrier phase shifts **0°, 90°, 180°, 270°**.
4. **Pulse-shaping filters** — identify the *non*-pulse-shaping filter among raised-cosine, sinc, Gaussian, and a distractor.
5. **AM sideband power**: 100% modulation, carrier 100 W ⇒ power in **LSB = 25 W**.
6. **Fourier transform of a real and even** function ⇒ result is **real and even**.
7. **AM detection using a PLL** — correct/incorrect statements (coherent detection, multiplier + LPF).
8. **PPM demodulation** — components used (ramp/pulse generator + **flip-flop** + LPF, or conversion to PWM first).

Preparation strategy: master (i) every block diagram (transmitter, superheterodyne receiver, PLL, PCM chain, PPM demodulator), (ii) the AM/FM power–bandwidth formula set, (iii) the pulse & digital modulation "family trees", and (iv) one-line facts on OFC, radar, cellular and satellite. That combination alone secures 6–8 marks.

7.1 Introduction to Communication

7.1.1 Elements of a Communication System

Every communication system, from a PA system in a railway station to a satellite link, has the same skeleton:

```
Information → Input      → Transmitter → Channel → Receiver → Output     → Destination
Source        Transducer                (+noise)              Transducer
```

Block	Function	Example
Information source	Produces the message (speech, music, picture, data)	Human voice
Input transducer	Converts message into an electrical signal (baseband signal)	Microphone, camera
Transmitter	Processes the baseband signal for efficient transmission — amplification, **modulation**, filtering	AM/FM broadcast transmitter
Channel	Physical medium carrying the signal; introduces attenuation, distortion and **noise**	Free space, coaxial cable, twisted pair, optical fibre
Receiver	Extracts (demodulates) the message from the received signal, amplifies it	Superheterodyne radio
Output transducer	Converts electrical signal back to the original message form	Loudspeaker, display


Baseband signal: the original band of frequencies produced by the source (speech ≈ 300 Hz–3.4 kHz; audio ≈ 20 Hz–20 kHz; video ≈ 0–4.2 MHz).

7.1.2 Why Modulate? (Need for Modulation)

Modulation = varying some parameter (amplitude, frequency, or phase) of a high-frequency **carrier** in accordance with the baseband (modulating) signal.

1. **Practical antenna length** — efficient radiation needs antenna ≈ λ/4. For 10 kHz audio, λ/4 = 7.5 km (impossible); for a 1 MHz carrier, λ/4 = 75 m (practical).
2. **Multiplexing** — many stations can share the channel by using different carrier frequencies (frequency translation avoids mutual interference).
3. **Reduced noise & interference** — FM particularly; also allows bandwidth–SNR trade-off.
4. **Range increase** — high-frequency signals propagate farther for a given power.
5. **Narrowbanding** — the ratio f_max/f_min of the transmitted band becomes ≈ 1, easing equipment design (antennas, amplifiers work over a narrow fractional bandwidth).

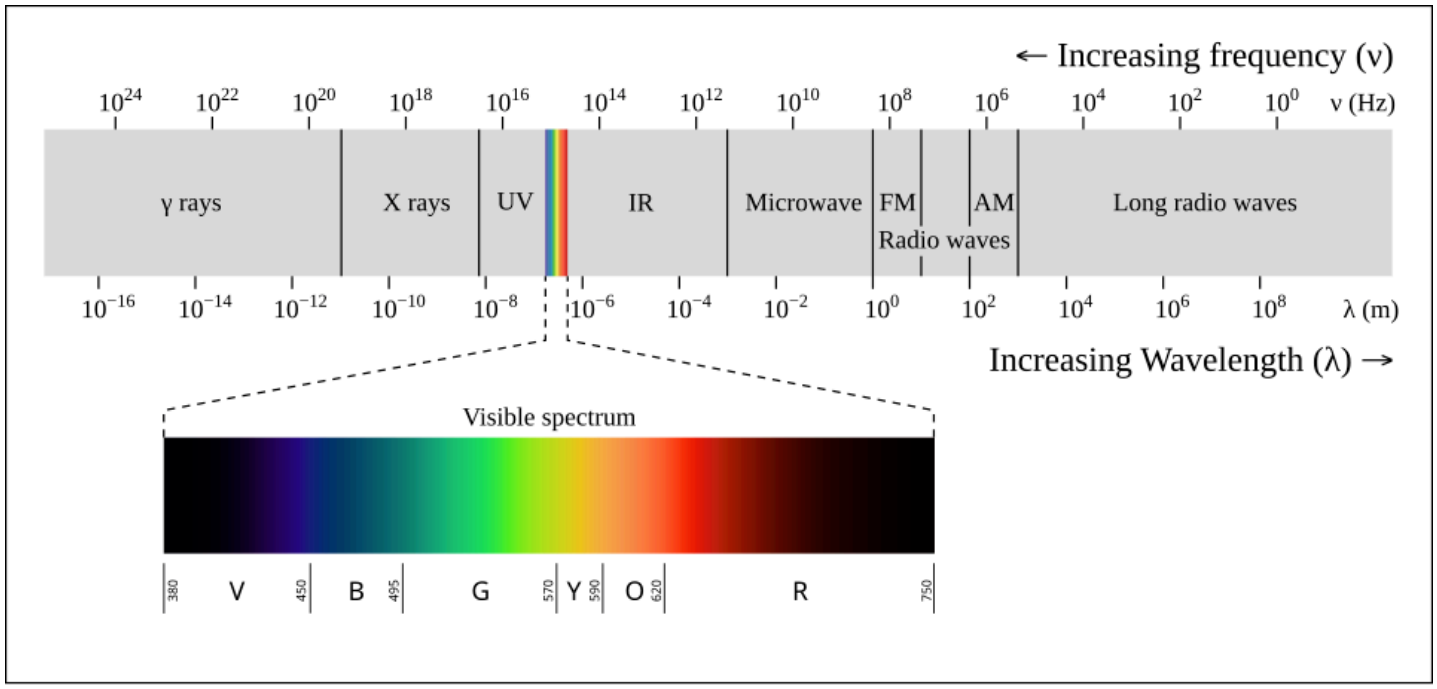7.1.3 Frequency Bands (memorise — direct questions)



Electromagnetic spectrum.

Band	Frequency range	Typical use / propagation
VLF	3–30 kHz	Navigation, submarine comm (ground wave)
LF	30–300 kHz	Radio beacons (ground wave)
MF	300 kHz–3 MHz	**AM broadcast (535–1605 kHz)** — ground wave day, sky wave night
HF	3–30 MHz	Short-wave radio — **sky wave (ionosphere)**
VHF	30–300 MHz	**FM broadcast (88–108 MHz)**, TV — space wave (LOS)
UHF	300 MHz–3 GHz	TV, **cellular mobile**, GPS — LOS
SHF	3–30 GHz	**Satellite (C, Ku), radar, microwave links** — LOS
EHF	30–300 GHz	mm-wave, 5G high band, radio astronomy

7.1.4 Noise

Noise = unwanted random signal that corrupts the message.

External noise (enters from outside the receiver):

- **Atmospheric (static)** — lightning discharges; dominant below ~30 MHz.
- **Extraterrestrial** — solar noise, cosmic (galactic) noise (~8 MHz–1.4 GHz window).
- **Industrial (man-made)** — motors, ignition, arc welding; dominant in urban areas, 1–600 MHz.

Internal noise (generated inside equipment):

Type	Cause	Key facts
Thermal (Johnson) noise	Random motion of electrons in a resistor	$P_n = kTB$ (available power); $V_{n(rms)} = \sqrt{(4kTRB)}$. **White** noise — flat PSD.
Shot noise	Discrete arrival of charge carriers across a junction	$i_{n(rms)} = \sqrt{(2qI_{DC}B)}$
Partition noise	Random division of current between electrodes (BJT, mixer tubes)	Mixers noisier than amplifiers
Flicker (1/f) noise	Surface/contact imperfections	Dominant below ~1 kHz; PSD ∝ 1/f (pink noise)
Transit-time noise	Carrier transit time comparable to signal period	Significant at very high (microwave) frequencies

$k = 1.38 \times 10^{-23}$ J/K, T in kelvin, B = bandwidth in Hz.

Signal-to-noise ratio: SNR = S/N; in dB, $SNR(dB) = 10 \log_{10}(S/N)$.

Noise figure (F) — how much a device degrades SNR:

F = (SNR at input)/(SNR at output) ($F \geq 1$; ideal noiseless device $F = 1 \Rightarrow 0$ dB)

Noise figure in dB: $NF = 10 \log_{10} F$.

Equivalent noise temperature: $T_e = (F - 1)T_0$, with $T_0 = 290$ K.

Friis formula for cascaded stages (noise figure of a chain):

$F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/(G_1G_2) + \ldots$

⇒ the **first stage** (LNA) dominates overall noise figure — put the low-noise, high-gain amplifier first.

7.2 Signals & Fourier Basics

7.2.1 Signal Classification

- **Analog vs digital**, **continuous-time vs discrete-time**.
- **Periodic**: $x(t) = x(t + T_0)$ — expandable in a **Fourier series** (discrete spectrum at nf_0).
- **Aperiodic / energy signals** — described by the **Fourier transform** (continuous spectrum).
- **Deterministic vs random** (noise is random — described statistically by PSD).

7.2.2 Fourier Transform

$X(f) = \int_{-\infty}^{\infty} x(t)\, e^{(-j2\pi ft)}\, dt$ $x(t) = \int_{-\infty}^{\infty} X(f)\, e^{(+j2\pi ft)}\, df$

Standard pairs:

x(t)	X(f)
$\delta(t)$	1
1 (DC)	$\delta(f)$
$\cos 2\pi f_0 t$	$\frac{1}{2}[\delta(f-f_0) + \delta(f+f_0)]$
$\sin 2\pi f_0 t$	$(1/2j)[\delta(f-f_0) - \delta(f+f_0)]$
rect(t/T) (pulse of width T)	T·sinc(fT)
sinc(2Wt)	(1/2W)·rect(f/2W)
e^(−at)u(t), a>0	1/(a + j2πf)
Gaussian $e^{(-\pi t^2)}$	Gaussian $e^{(-\pi f^2)}$ (self-transform)

Key properties:

Property	Time domain	Frequency domain				
Linearity	$a\,x_1(t) + b\,x_2(t)$	$a\,X_1(f) + b\,X_2(f)$				
Time shift	$x(t - t_0)$	$X(f)\,e^{(-j2\pi f t_0)}$				
Frequency shift (modulation)	$x(t)\,e^{(j2\pi f_0 t)}$	$X(f - f_0)$				
Scaling	x(at)	(1/|	a|	) X(f/a)		
Duality	X(t)	x(−f)				
Convolution	$x_1(t) * x_2(t)$	$X_1(f)\cdot X_2(f)$				
Multiplication	$x_1(t)\cdot x_2(t)$	$X_1(f) * X_2(f)$				
Differentiation	dx/dt	$j2\pi f\,X(f)$				
Parseval	∫|	x(t)|	^{2}dt	= ∫|	X(f)|	^{2}df

7.2.3 Symmetry Properties — ⭐ Exam Favourite (asked 22-04-2025)


For x(t) real: X(−f) = X*(f) (**conjugate/Hermitian symmetry**) ⇒ |X(f)| is even, phase is odd.

If x(t) is …	Then X(f) is …
Real and even	**Real and even** ✅ (2025 PYQ)
Real and odd	**Imaginary and odd**
Imaginary and even	Imaginary and even
Imaginary and odd	Real and odd
Real (general)	Conjugate-symmetric: X(−f) = X*(f)

Memory hook: "*even keeps the character (real↔real), odd flips it (real↔imaginary).*"

7.3 Amplitude Modulation (AM)

7.3.1 Expression & Modulation Index

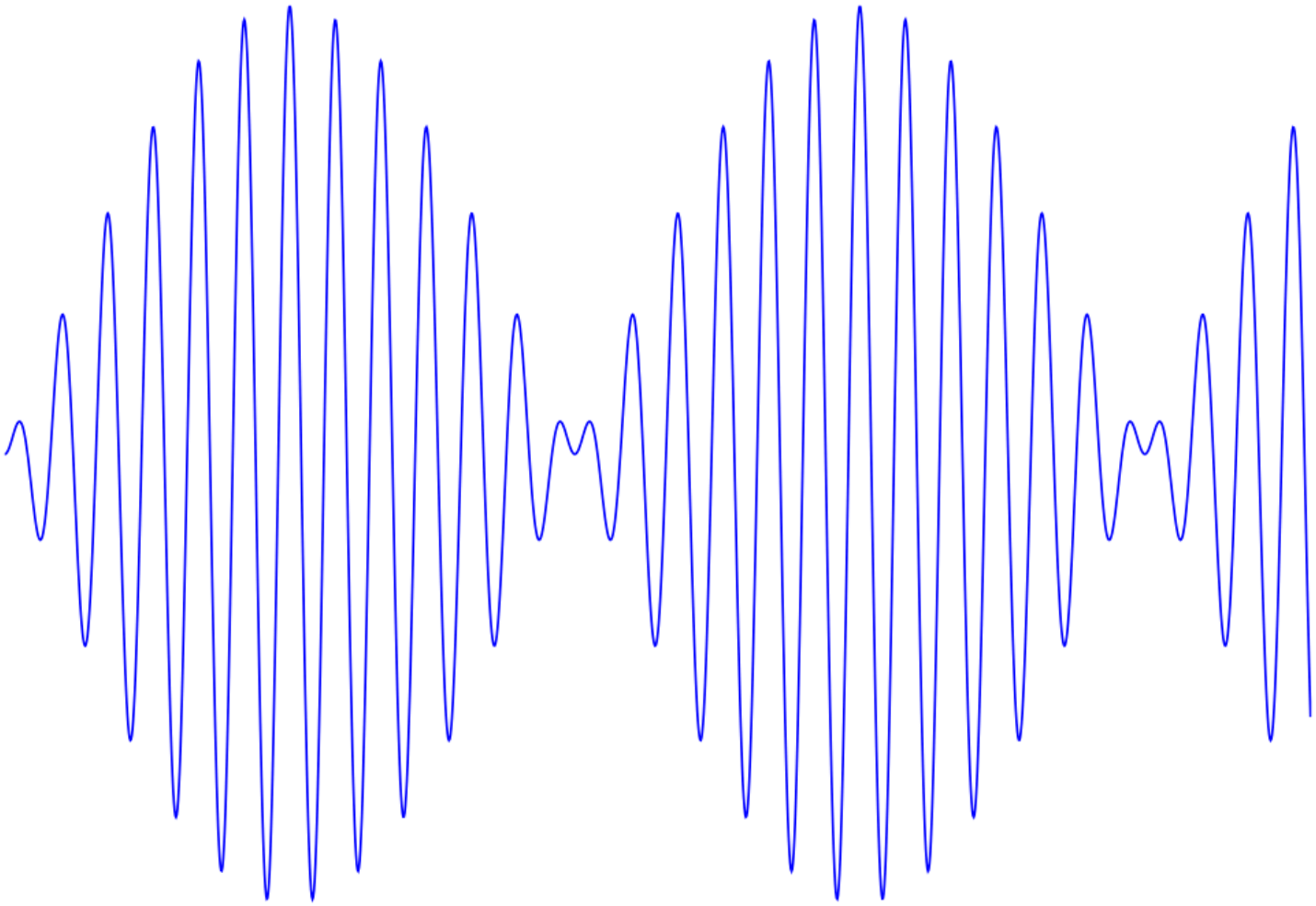

Amplitude modulation: message, carrier, AM wave.

Carrier: $c(t) = A_c \cos \omega_c t$. Message: $m(t) = A_m \cos \omega_m t$.

Standard AM (DSB-Full Carrier):

$s(t) = A_c[1 + m \cdot \cos \omega_m t] \cos \omega_c t$

Modulation index (depth):

$m = A_m/A_c = (V_{max} - V_{min})/(V_{max} + V_{min})$

where V_{max}, V_{min} are envelope maximum and minimum. Also $A_m = (V_{max} - V_{min})/2$, $A_c = (V_{max} + V_{min})/2$.

- $m < 1$: under-modulation; $m = 1$: 100% (critical) modulation; **$m > 1$: over-modulation** → envelope crosses zero → **envelope distortion & sideband splatter**; envelope detection fails.
- Percent modulation = $m \times 100\%$.
- **Multiple tones**: $m_t = \sqrt{(m_1^2 + m_2^2 + m_3^2 + \ldots)}$

7.3.2 Spectrum & Bandwidth

Expanding:

$s(t) = A_c \cos \omega_c t + (mA_c/2) \cos(\omega_c + \omega_m)t + (mA_c/2) \cos(\omega_c - \omega_m)t$

Three components: **carrier at f_c**, **USB at $f_c + f_m$**, **LSB at $f_c - f_m$**.

Bandwidth of AM: $B = 2f_m$ (twice the highest modulating frequency).

7.3.3 Power Relations — ☆ direct 2025 numerical

With carrier power $P_c = A_c^2/2R$:

$P_{total} = P_c(1 + m^2/2)$

Power per sideband: $P_{USB} = P_{LSB} = m^2P_c/4$ Total sideband power = $m^2P_c/2$.

Transmission efficiency: $\eta = P_{sidebands}/P_{total} = m^2/(2 + m^2)$.

- At $m = 1$: $\eta = 1/3 \approx$ **33.3%** (maximum for standard AM) — carrier wastes ≥ 2/3 of the power.

Current relation: $I_t = I_c\sqrt{(1 + m^2/2)}$ (antenna current).

> **2025 PYQ flash:** $P_c = 100$ W, $m = 1 \Rightarrow$ each sideband = $m^2P_c/4 = 100/4 =$ **25 W**; total = 150 W.

7.3.4 AM Variants — DSB-SC, SSB, VSB

Scheme	What is transmitted	Bandwidth	Power saving vs AM (m=1)	Detection	Uses
DSB-FC (standard AM)	Carrier + both sidebands	$2f_m$	—	Simple envelope detector	Broadcast radio
DSB-SC	Both sidebands, carrier suppressed	$2f_m$	66.7% (carrier removed)	Coherent (synchronous) only	Analog TV colour subcarrier, stereo pilot systems
SSB-SC	One sideband only	**f_m** (half)	83.3%	Coherent; needs precise carrier reinsertion	Point-to-point HF, marine, amateur radio
VSB	One full SB + vestige of other	$f_m < B < 2f_m$	intermediate	Envelope (with carrier)	**Analog TV video** (video has strong low frequencies; SSB filter impractical)

- DSB-SC generation: **balanced modulator / ring modulator** (multiplier).
- SSB generation: **filter method** (sharp BPF after balanced modulator), **phase-shift method** (two balanced modulators + 90° Hilbert phase shifters), **Weaver (third) method**.
- Coherent detection needs a locally generated carrier synchronised in **frequency and phase**; phase error θ scales output by $\cos \theta$ (quadrature null effect at $\theta = 90°$).

7.3.5 AM Generation

- **Low-level modulation**: modulate at low power then amplify with **linear** amplifiers.
- **High-level modulation**: modulate at the final high-power stage (collector/plate modulation) — allows efficient class-C carrier amplifiers.

- **Square-law modulator**: nonlinear device $i = a\,v + b\,v^2$; the v^2 term produces the product $m(t)\cdot c(t)$; a BPF at f_c selects the AM band. Works for small signals.
- **Switching modulator**: diode driven hard by the large carrier acts as a switch; output = $[c(t)+m(t)]\cdot g_p(t)$; BPF extracts AM.
- **Balanced modulator**: two matched square-law/switching modulators in push-pull cancel the carrier → DSB-SC.

7.3.6 AM Detection (Demodulation)

(a) Square-law detector — small-signal nonlinear device; output contains a term $\propto m(t)$ plus distortion (m^2 term); used only for very small signals.

(b) Envelope detector (the workhorse) — diode + parallel RC.

- Diode charges C on positive peaks; C discharges through R between peaks, tracking the envelope.
- **Design condition:** $1/f_c \ll RC \ll 1/f_m$ (more precisely $RC \le \sqrt{(1-m^2)}/(2\pi f_m \cdot m)$).
- **Diagonal (clipping) distortion**: RC too large → discharge slower than envelope fall → output follows a diagonal line instead of the envelope. Occurs when the envelope's negative slope exceeds the RC discharge slope; worst at high m and high f_m.
- **Negative-peak clipping**: caused by different DC/AC load impedances after the detector.

(c) Synchronous (coherent) detector — multiply received signal by a local carrier $\cos \omega_c t$, then low-pass filter:

$s(t)\cdot\cos \omega_c t \rightarrow \tfrac{1}{2}A_c[1+m\cdot\cos \omega_m t] +$ (terms at $2f_c$, removed by LPF)

Required for DSB-SC/SSB; also works for standard AM.

(d) PLL-based AM detection — ☆ 2025 PYQ.


A PLL locks to the incoming AM carrier. Because the PLL's VCO output tracks the carrier **frequency and phase** but has **constant amplitude**, it serves as the clean, coherent local carrier. This VCO output (shifted 90° as needed so it is in phase with the incoming carrier) is fed to a **multiplier (product detector)** along with the AM input; the multiplier output through a **low-pass filter** yields the message m(t).

Correct statements to recognise:

- PLL regenerates a **coherent carrier** from the AM wave itself.
- Detection is **synchronous/coherent**, hence superior noise performance vs envelope detection and immune to selective carrier fading.
- The demodulated output is taken from the **multiplier + LPF**, *not* from the loop error voltage (contrast with FM, where the error/control voltage *is* the output).

7.4 Angle Modulation — FM & PM

7.4.1 Expressions

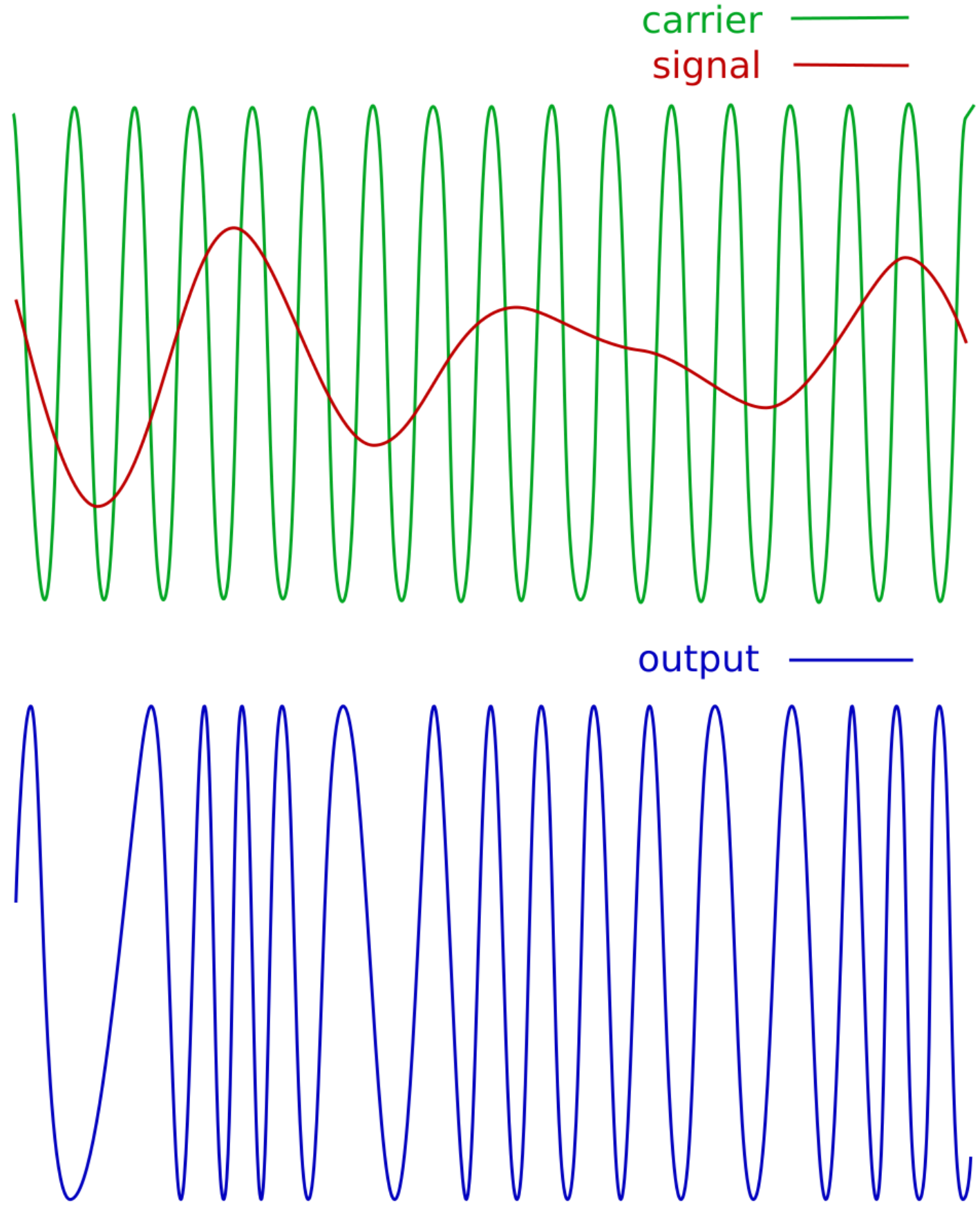

Frequency modulation waveform.

General angle-modulated wave: $s(t) = A_c \cos \theta(t)$, instantaneous frequency $f_i = (1/2\pi)\cdot d\theta/dt$.

Phase modulation (PM): $\theta(t) = \omega_c t + k_p m(t)$

$s(t) = A_c \cos[\omega_c t + k_p m(t)]$

Frequency modulation (FM): $f_i = f_c + k_f m(t)$

$s(t) = A_c \cos[\omega_c t + 2\pi k_f \int m(t)dt]$

For single-tone $m(t) = A_m \cos \omega_m t$:

$s_{FM}(t) = A_c \cos(\omega_c t + \beta \sin \omega_m t)$

Frequency deviation: $\Delta f = k_f A_m$ (maximum shift of instantaneous frequency from f_c).

FM modulation index: $\beta = \Delta f / f_m$ (dimensionless; can exceed 1 — unlike AM).

PM modulation index: $\beta_p = k_p A_m = \Delta\theta$ (peak phase deviation, independent of f_m).

FM–PM duality: PM of $\int m(t)dt$ ≡ FM of $m(t)$; FM of dm/dt ≡ PM of $m(t)$. (Integrator before a phase modulator ⇒ FM — Armstrong's idea.)

Deviation ratio (broadcast FM): $D = \Delta f_{max}/f_{m(max)} = 75\text{ kHz}/15\text{ kHz} = 5$.

7.4.2 Spectrum & Bandwidth

Single-tone FM expands in **Bessel functions**: $s(t) = A_c \Sigma J_n(\beta) \cos(\omega_c + n\omega_m)t$ — theoretically **infinite sidebands** at $f_c \pm nf_m$; amplitudes $J_n(\beta)$. Carrier amplitude $\propto J_0(\beta)$ and **vanishes** at $\beta \approx 2.405, 5.52, \ldots$ (used for deviation calibration).

Carson's rule (practical bandwidth ≈ 98% power):

$B = 2(\Delta f + f_m) = 2f_m(\beta + 1)$

- **NBFM**: $\beta \ll 1$ ($\beta < 0.3$): only first pair of sidebands significant; $B \approx 2f_m$ (like AM). Used in mobile/2-way radio.
- **WBFM**: $\beta \gg 1$: $B \approx 2\Delta f$. Commercial FM: $\Delta f = 75$ kHz, $f_m = 15$ kHz ⇒ $B = 2(75+15) =$ **180 kHz** (channel spacing 200 kHz).

7.4.3 FM Power

Amplitude is constant ⇒ **total power $= A_c^2/2R$ = carrier's unmodulated power, independent of β**. Modulation only redistributes power among sidebands. (Contrast AM: power grows with m.)

7.4.4 Noise in FM; Pre-emphasis & De-emphasis

- FM output noise PSD rises **parabolically with frequency** ($\propto f^2$) — high audio frequencies suffer more noise.
- **Pre-emphasis** (at transmitter): boost high frequencies before modulation — an RC high-pass/lead network, standard time constant **75 µs** (India/US; 50 µs Europe), corner ≈ 2.1 kHz.
- **De-emphasis** (at receiver): matching RC low-pass restores flat response while cutting the amplified high-frequency noise ⇒ net SNR improvement.
- FM also exhibits the **capture effect** (stronger signal suppresses the weaker co-channel one) and **threshold effect** (SNR advantage collapses below a carrier-to-noise threshold ≈ 10 dB).

7.4.5 FM Generation

Direct methods (vary oscillator frequency directly):

- **Varactor (voltage-variable capacitor) modulator** — message changes tank capacitance of an LC/VCO oscillator.
- **Reactance modulator** — FET/BJT circuit simulating a voltage-dependent reactance across the tank.

- Advantage: large deviation directly. Drawback: carrier (LC oscillator) has poor frequency stability — needs AFC against a crystal reference.

Indirect (Armstrong) method:


1. Crystal oscillator (stable carrier) → 90° phase shift.
2. Message → **integrator** → balanced modulator with the shifted carrier → adding back the carrier gives **NBFM** (small β).
3. **Frequency multipliers** (×n nonlinear stages) multiply both f_c and Δf; a mixer (heterodyne) repositions f_c without changing Δf.

⇒ Wideband FM with crystal stability. (Multiplier scales deviation; mixer does not.)

7.4.6 FM Detection

Detector	Principle	Notes
Slope detector	Off-tuned LC circuit converts Δf → amplitude variation, then envelope detector	Simple, nonlinear, poor
Balanced slope (Travis)	Two slope detectors tuned above/below f_c, outputs subtracted	Better linearity, hard to align (3 tuned circuits)
Foster–Seeley (phase) discriminator	Phase shift of a tuned coupled circuit varies with frequency; two diodes rectify vector sums	Very linear; **responds to amplitude variations too ⇒ needs a preceding limiter**
Ratio detector	Modified Foster–Seeley: one diode reversed + large stabilising capacitor holds sum voltage constant	**Built-in amplitude limiting** (≈ no separate limiter needed); output = half of discriminator
Quadrature detector	90° phase-shift network + phase comparator (IC receivers)	Common in TV sound ICs
PLL demodulator ☆	See below	Best linearity & threshold performance; no tuned circuits

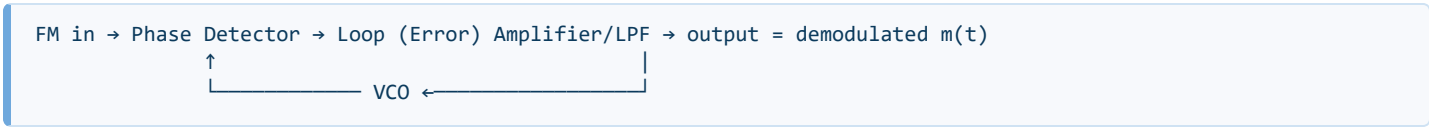PLL FM demodulator — ☆ 2025 PYQ (know this cold):




- The **phase detector** compares the incoming FM signal with the VCO output.
- The loop filter/**error amplifier** output (control voltage) drives the **VCO** so that VCO frequency tracks the instantaneous input frequency.
- In lock, VCO frequency $f_{VCO} = f_i(t) = f_c + k_f m(t)$. Since VCO frequency is proportional to its control voltage, the **control (error) voltage is directly proportional to m(t)** — *the loop-filter/error-amplifier output IS the demodulated signal.*
- Advantages: high linearity (set by VCO), inductor-less/IC-friendly, extends threshold, self-tuning.
- Contrast with PLL-AM detection: FM output = **loop error voltage**; AM output = **separate multiplier + LPF** using the VCO as coherent carrier.

7.4.7 AM vs FM (quick table)

Aspect	AM	FM
Parameter varied	Amplitude	Frequency
Bandwidth	2f_m (small)	2(Δf+f_m) (large)
Power	Varies with m	Constant
Noise immunity	Poor	Excellent (constant envelope + limiter)
Circuits	Simple	Complex
Coverage	Large (sky/ground wave, MF/HF)	Line-of-sight (VHF)
Broadcast band	535–1605 kHz	88–108 MHz

7.5 Radio Receivers

7.5.1 TRF vs Superheterodyne

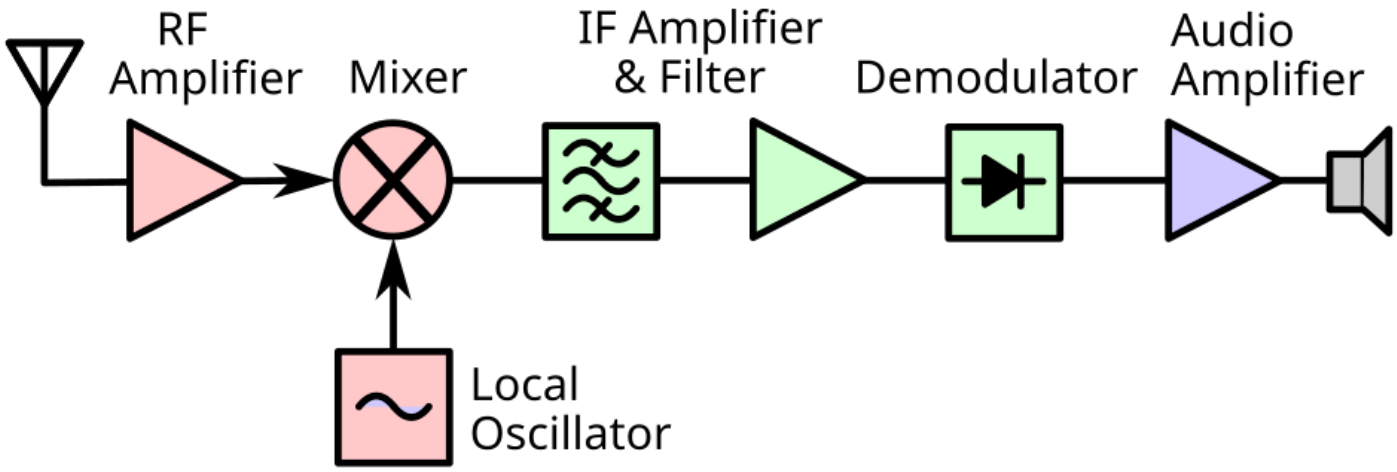

Superheterodyne receiver block diagram.

TRF (Tuned Radio Frequency): several cascaded RF amplifiers all tuned to the station frequency → gain/selectivity vary across the band, tracking of multiple tuned stages is hard, unstable at high gain. Obsolete.

Superheterodyne (all modern receivers): convert every incoming station to a fixed **intermediate frequency (IF)** where most gain & selectivity are provided.

```
Antenna → RF amplifier → Mixer → IF amplifier(s) → Detector → AF amplifier → Speaker
                          ↑            (455 kHz AM / 10.7 MHz FM)
                  Local Oscillator (ganged tuning: f_LO = f_s + f_IF)
```

- **Standard IF: 455 kHz (AM broadcast), 10.7 MHz (FM), 38.9 MHz vision IF (TV, India)**.
- Local oscillator usually **above** the signal: f_LO = f_s + f_IF (smaller capacitor tuning ratio).
- **AGC** (automatic gain control): DC from detector controls IF/RF gain to keep output constant.

7.5.2 Image Frequency — classic numerical source

The mixer also converts f_image = **f_s + 2f_IF** (LO above) to the same IF — an unwanted "image" station.

- Image must be rejected **before** the mixer (RF stage selectivity); after mixing it is inseparable.
- **Image Frequency Rejection Ratio**: IFRR = $\sqrt{(1 + Q^2\rho^2)}$, where $\rho = f_{im}/f_s - f_s/f_{im}$ and Q = loaded Q of the RF tuned circuit. Cascaded stages: multiply IFRRs.
- Higher f_{IF} ⇒ image farther away ⇒ easier rejection (but harder selectivity); hence double-conversion receivers.

7.5.3 Receiver Characteristics

- **Sensitivity** — minimum input signal for a standard output (μV); set by gain & noise figure.
- **Selectivity** — ability to reject adjacent channels; mostly from IF filters.
- **Fidelity** — faithful reproduction of the whole baseband (needs adequate bandwidth — conflicts with selectivity).
- **Double spotting** — one station received at two dial points due to poor image rejection.

7.6 Pulse Modulation

7.6.1 Sampling Theorem — the gateway

Nyquist/Shannon sampling theorem: a band-limited signal with highest frequency f_m is completely recoverable from its samples if the sampling rate

$f_s \geq 2f_m$ (Nyquist rate = $2f_m$; Nyquist interval = $1/2f_m$)

- $f_s < 2f_m$ ⇒ **aliasing** (spectral overlap; irreversible distortion). Anti-aliasing LPF precedes the sampler.
- Types of sampling: **ideal (impulse)**, **natural** (pulse tops follow signal), **flat-top** (sample-and-hold; introduces **aperture effect**, corrected by a $(\sin x/x)^{-1}$ equaliser).
- Telephony: f_m = 3.4 kHz → standard **f_s = 8 kHz**.

7.6.2 Analog Pulse Modulation Family

Scheme	Parameter varied	Class	Bandwidth	Noise immunity
PAM	Pulse **amplitude**	—	Lowest of the three	Poor (amplitude carries info)
PWM = PDM = PLM	Pulse **width/duration/length**	**PTM**	Higher	Good
PPM	Pulse **position** (timing)	**PTM**	Highest	Best; also most power-efficient (constant-width, constant-amplitude narrow pulses)

☆ **2025 PYQ:** PWM is also called **Pulse Duration Modulation (PDM)** (and Pulse Length Modulation, PLM). PWM and PPM together form the **Pulse Time Modulation (PTM)** family because the information rides on pulse *timing*, not amplitude.

Generation:

- **PAM**: sample-and-hold / multiplying the message with a pulse train.
- **PWM**: compare message with a **ramp/sawtooth** in a comparator — the crossing instant sets the trailing edge ⇒ width ∝ message. (Also: monostable multivibrator with message-controlled timing.)
- **PPM from PWM**: differentiate PWM, keep the trailing-edge trigger, fire a **monostable** ⇒ constant-width pulse whose *position* ∝ message.

Detection:

- **PAM**: low-pass filter (plus equaliser for flat-top).
- **PWM**: simple **low-pass filter** (average value of PWM ∝ width ∝ message) — after regeneration/limiting.
- **PPM demodulation — ⭐ 2025 PYQ:** first convert PPM back to PWM, then LPF. Standard circuit: a **reference (synchronising) pulse generator + flip-flop (bistable)**: the reference clock pulse **sets** the flip-flop; the received PPM pulse **resets** it. The flip-flop output is a PWM wave whose width equals the position delay; a **low-pass filter** then recovers m(t). (Alternative: ramp generator started by the reference pulse and stopped by the PPM pulse — ramp height ∝ position.)

Components to tick in the MCQ: **pulse/ramp generator, flip-flop (bistable multivibrator), low-pass filter**.

7.6.3 PCM — Pulse Code Modulation (digital)

```
m(t) → LPF (anti-alias) → Sampler → Quantiser → Encoder → line coder → channel
Receiver: regenerator → decoder → reconstruction LPF
```

- **Quantisation**: rounding samples to L = 2^n discrete levels (n bits/sample). Step size Δ = (V_pp)/L.
- **Quantisation noise power** = $\Delta^2/12$ (uniform quantiser).
- **SQNR for full-scale sinusoid:**

SQNR = $1.5 \cdot L^2$ ⇒ SQNR(dB) = 6.02 n + 1.76 ≈ (6 dB per bit)

Each extra bit ⇒ **+6 dB** SNR but ×(n+1)/n bandwidth.

- **Bit rate**: R_b = n·f_s. **Minimum channel bandwidth** ≈ R_b/2 = n·f_s/2.
- **Companding** — non-uniform quantisation for speech: **μ-law (μ = 255, N. America/Japan)**, **A-law (A = 87.6, India/Europe)** — compress at Tx, expand at Rx to keep SNR uniform across amplitudes.
- Telephony PCM: 8 kHz × 8 bits = **64 kbps per voice channel** (DS0).
- Advantages: regeneration (noise does not accumulate), TDM-friendly, encryption/coding possible. Cost: bandwidth.

7.6.4 DPCM, DM, ADM

- **DPCM (Differential PCM)**: transmit the quantised **difference** between the sample and its predicted value — exploits correlation, fewer bits for the same quality.
- **Delta modulation (DM)**: 1-bit DPCM — staircase approximation, step ±Δ per clock.
- **Slope overload distortion** when Δ/T_s < |dm/dt|_max (signal rises faster than the staircase). Avoid: Δ f_s ≥ 2π f_m A_m for a tone.
- **Granular (idle) noise** when Δ too large for a slowly varying/flat signal.
- **ADM (Adaptive DM / CVSD)**: step size grows during overload, shrinks in granular regions — resolves the Δ conflict.

7.7 Digital (Carrier) Modulation

7.7.1 Binary Keying

Scheme	Carrier parameter keyed	Signal for bit 1 / 0	Bandwidth (≈, bit rate R_b)	Detection	Notes
ASK (OOK)	Amplitude	$A \cos \omega_c t$ / 0	$2R_b$	Envelope or coherent	Worst noise performance; simplest
FSK	Frequency	f_1 / f_2	$2(\Delta f + R_b)$ (Carson-like)	Non-coherent (discriminator) or coherent	Used in modems, RTTY; MSK = CPFSK with h=0.5
BPSK	Phase	0° / 180°	$2R_b$ (main lobe)	Coherent (Costas loop)	Best binary error performance
DPSK	Phase difference	data in phase *changes*	$2R_b$	Differentially coherent (no carrier recovery)	~1 dB worse than BPSK

Error-rate ranking (best → worst at same E_b/N_0): **BPSK/QPSK > DPSK > coherent FSK > non-coherent FSK > ASK**.

7.7.2 QPSK — ☆ 2025 PYQ

- 2 bits per symbol ⇒ 4 symbols ⇒ 4 carrier phases.
- **Conventional QPSK phases: 0°, 90°, 180°, 270°** (equivalently π/4, 3π/4, 5π/4, 7π/4 for offset constellation — but when the exam lists 0/90/180/270 vs other sets, tick **0°, 90°, 180°, 270°**).
- Symbol rate = $R_b/2$ ⇒ **bandwidth is half of BPSK** for the same bit rate, with the same error performance per bit.
- Implementation: serial-to-parallel splitter → I and Q BPSK modulators on $\cos \omega_c t$ and $\sin \omega_c t$ → adder. Variants: OQPSK (Q delayed T_b — avoids 180° transitions), π/4-QPSK.

Gray coding on constellations: adjacent symbols differ in one bit — minimises bit errors.

7.7.3 M-ary & QAM

- **M-PSK**: $\log_2 M$ bits/symbol on one amplitude circle; error rate worsens as points crowd.
- **QAM**: both **amplitude and phase** carry data (square constellations 16-QAM, 64-QAM, 256-QAM …). Best bandwidth efficiency; needs high SNR & linear amplifiers. Used in Wi-Fi, LTE/5G, cable modems, microwave links.
- Bandwidth efficiency $\eta = R_b/B$ (bits/s/Hz) increases with $\log_2 M$; power efficiency decreases.

7.7.4 Pulse Shaping & ISI — ☆ 2025 PYQ

Rectangular data pulses have sinc-shaped spectra with huge sidelobes; band-limiting them smears pulses into neighbours → **Inter-Symbol Interference (ISI)**.

Nyquist criterion for zero ISI: the overall pulse $p(t)$ must satisfy $p(kT_s) = 0$ for all integers $k \neq 0$ (zero crossings at all other sampling instants). Minimum bandwidth solution = **ideal sinc pulse** (brick-wall filter, $B = R_s/2$) — unrealisable and timing-sensitive.

Practical pulse-shaping filters:

Filter	Key property
Sinc (ideal Nyquist)	Minimum bandwidth $R_s/2$; unrealisable; slow $1/t$ tail decay
Raised-cosine (RC)	Roll-off factor α (0…1); $B = (1+\alpha)R_s/2$; zero-ISI zero crossings preserved; tails decay $\propto 1/t^3$
Root-raised-cosine (RRC)	RC split equally between Tx and Rx (matched filtering); cascade = RC
Gaussian	Used in **GMSK/GSM**; very compact spectrum, small controlled ISI; no zero-ISI property but excellent spectral containment

Exam trap (2025): raised-cosine, sinc (ideal Nyquist) and Gaussian **are** pulse-shaping filters; options like a plain **Butterworth/Chebyshev/high-pass/notch** filter are **not** pulse-shaping filters — that is the odd one out.

Eye diagram: oscilloscope overlay of symbol periods; eye opening ⇒ ISI margin & timing jitter tolerance.

7.8 Multiplexing Techniques

Multiplexing = combining several message signals for transmission over one channel.

Technique	Resource divided	Guard element	Typical use
FDM	Frequency slots (each signal SSB-translated to its own subcarrier)	**Guard bands**	Analog telephony groups, radio/TV broadcast, ADSL
TDM	Time slots (samples interleaved)	**Guard times**; needs frame **synchronisation**	Digital telephony (E1/T1), SONET/SDH
WDM/DWDM	Optical wavelengths on one fibre (FDM at light frequencies)	Channel spacing (e.g., 0.8 nm/100 GHz)	Fibre backbones
CDM/CDMA	Orthogonal/PN spreading codes — all users share full band & time	Code cross-correlation	3G (IS-95/WCDMA), GPS
SDM	Space (separate beams/antennas/MIMO)	Spatial isolation	Cellular sectoring, MIMO

FDM telephone hierarchy (classic): Group = 12 channels (48 kHz), Supergroup = 5 groups = 60 ch, Mastergroup = 5 supergroups = 300 ch.

TDM digital hierarchy — memorise the two primary rates:

Standard	Channels	Frame	Bit rate
T1 (DS1, N. America/Japan)	24 × 64 kbps + 8 kbps framing (193 bits/frame × 8000)	125 µs	**1.544 Mbps**
E1 (Europe/India)	32 slots × 64 kbps (30 voice + TS0 sync + TS16 signalling)	125 µs	**2.048 Mbps**

Higher orders: E2 = 8.448, E3 = 34.368, E4 = 139.264 Mbps; T2 = 6.312, T3 = 44.736 Mbps.

- **Synchronous vs statistical TDM**: fixed slots vs on-demand slots (better efficiency for bursty data).
- **OFDM** (used in 4G/5G/Wi-Fi/DVB): data split over many **orthogonal** closely-spaced subcarriers via IFFT; cyclic prefix combats multipath ISI.

7.9 Wave Propagation

7.9.1 Modes

Mode	Frequency range	Mechanism	Range
Ground (surface) wave	Up to ~2 MHz (VLF–MF)	Vertically polarised wave glides along earth; attenuation grows with f	Few hundred km; AM daytime
Sky wave (ionospheric)	**3–30 MHz (HF)**	Refraction (bending) by ionised layers	Thousands of km with hops; short-wave broadcast
Space wave (tropospheric/LOS)	> 30 MHz (VHF and above)	Direct + ground-reflected rays, line of sight	Tens of km; FM, TV, mobile, radar

Others: **tropospheric scatter** (100 MHz–10 GHz, beyond-horizon links), **duct propagation** (super-refraction layers).

7.9.2 Ionospheric Layers

Layer	Height (approx.)	Behaviour
D	50–90 km	Exists only in daytime; **absorbs** MF/HF (does not reflect usable HF); disappears at night → distant AM reception at night
E	90–140 km	Daytime reflection up to ~20 MHz; sporadic-E patches
F_1	140–250 km	Daytime only; merges into F at night
F_2	250–400 km	**Main reflecting layer**, day & night; highest electron density

7.9.3 Key Formulas

- **Critical frequency** (highest frequency returned at vertical incidence):

$f_c = 9\sqrt{N_{max}}$ (Hz, N_{max} = max electron density per m^3).

- **Maximum Usable Frequency** (oblique incidence at angle θ from vertical):

$MUF = f_c \cdot \sec\theta = f_c/\cos\theta$ (secant law). Optimum working frequency ≈ 0.85 MUF.

- **Skip distance**: minimum ground distance at which a sky wave of given frequency returns; between ground-wave limit and skip distance lies the **skip (silent) zone**.
- **Virtual height**: apparent reflection height assuming straight-line travel.
- **LOS (radio horizon) range** for antenna heights h_t, h_r (metres), with 4/3-earth correction:

$d\ (km) \approx 4.12(\sqrt{h_t} + \sqrt{h_r})$ (optical horizon: $3.57(\sqrt{h_t} + \sqrt{h_r})$)

- Ionospheric refraction: refractive index $n = \sqrt{(1 - 81N/f^2)}$.

7.10 Transmission Lines

7.10.1 Primary & Secondary Constants

Primary constants (per unit length): R (Ω/m), L (H/m), G (S/m), C (F/m).

Secondary constants:

- **Characteristic impedance:** $Z_0 = \sqrt{[(R + j\omega L)/(G + j\omega C)]}$
- **Lossless / high-frequency line: $Z_0 = \sqrt{(L/C)}$** (purely resistive) — the exam default.
- Common values: 50 Ω (RF/coax), 75 Ω (TV/CATV), 300 Ω (twin-lead), 600 Ω (open-wire telephone).
- **Propagation constant:** $\gamma = \alpha + j\beta = \sqrt{[(R+j\omega L)(G+j\omega C)]}$; α = attenuation (Np/m), β = phase constant = $2\pi/\lambda = \omega/v_p$.
- **Velocity:** $v_p = \omega/\beta = 1/\sqrt{(LC)}$ (lossless); velocity factor VF = v_p/c (≈ 0.66 for solid-PE coax).
- **Distortionless line (Heaviside condition): R/L = G/C** ⇒ α frequency-independent, v_p constant — achieved historically by **loading coils** (increasing L).

7.10.2 Reflection, VSWR & Impedance Transformation

- **Voltage reflection coefficient at the load:**

$\Gamma = (Z_L - Z_0)/(Z_L + Z_0)$, $|\Gamma| \le 1$.

Matched ($Z_L = Z_0$): $\Gamma = 0$. Open circuit: $\Gamma = +1$. Short circuit: $\Gamma = -1$.

- **VSWR:**

$S = (1 + |\Gamma|)/(1 - |\Gamma|) = V_{max}/V_{min}$, $1 \le S \le \infty$. Also $|\Gamma| = (S-1)/(S+1)$.

For purely resistive loads: $S = Z_L/Z_0$ or Z_0/Z_L (whichever ≥ 1).

- **Reflected power fraction** = $|\Gamma|^2$; transmitted fraction = $1 - |\Gamma|^2$. **Return loss** = $-20 \log|\Gamma|$ dB.
- **Input impedance of a lossless line of length l:**

$Z_{in} = Z_0 \cdot (Z_L + jZ_0 \tan \beta l)/(Z_0 + jZ_L \tan \beta l)$

Special cases (memorise):


Line section	Z_in behaviour
λ/4 with load Z_L	**$Z_{in} = Z_0^2/Z_L$** (impedance inverter — quarter-wave transformer)
λ/2	$Z_{in} = Z_L$ (repeats every λ/2)
Shorted stub, l < λ/4	Inductive ($jZ_0 \tan \beta l$)
Open stub, l < λ/4	Capacitive ($-jZ_0 \cot \beta l$)
Shorted λ/4	Open circuit (parallel-resonant, "metallic insulator")
Open λ/4	Short circuit

7.10.3 Impedance Matching

- **Quarter-wave transformer**: to match real Z_L to Z_0, insert a λ/4 section of impedance **$Z_0' = \sqrt{(Z_0 \cdot Z_L)}$**. Narrow-band (length is λ/4 at one frequency).
- **Single-stub matching**: a short-circuited (preferred) or open stub in parallel at a computed distance from the load cancels the susceptance — done graphically on the **Smith chart**.
- **Double-stub**: two fixed-position stubs with adjustable lengths.

- **Smith chart**: polar plot of Γ; constant-r and constant-x circles; one full revolution = λ/2 along the line; centre = matched point.

7.11 Optical Fibre Communication (OFC)

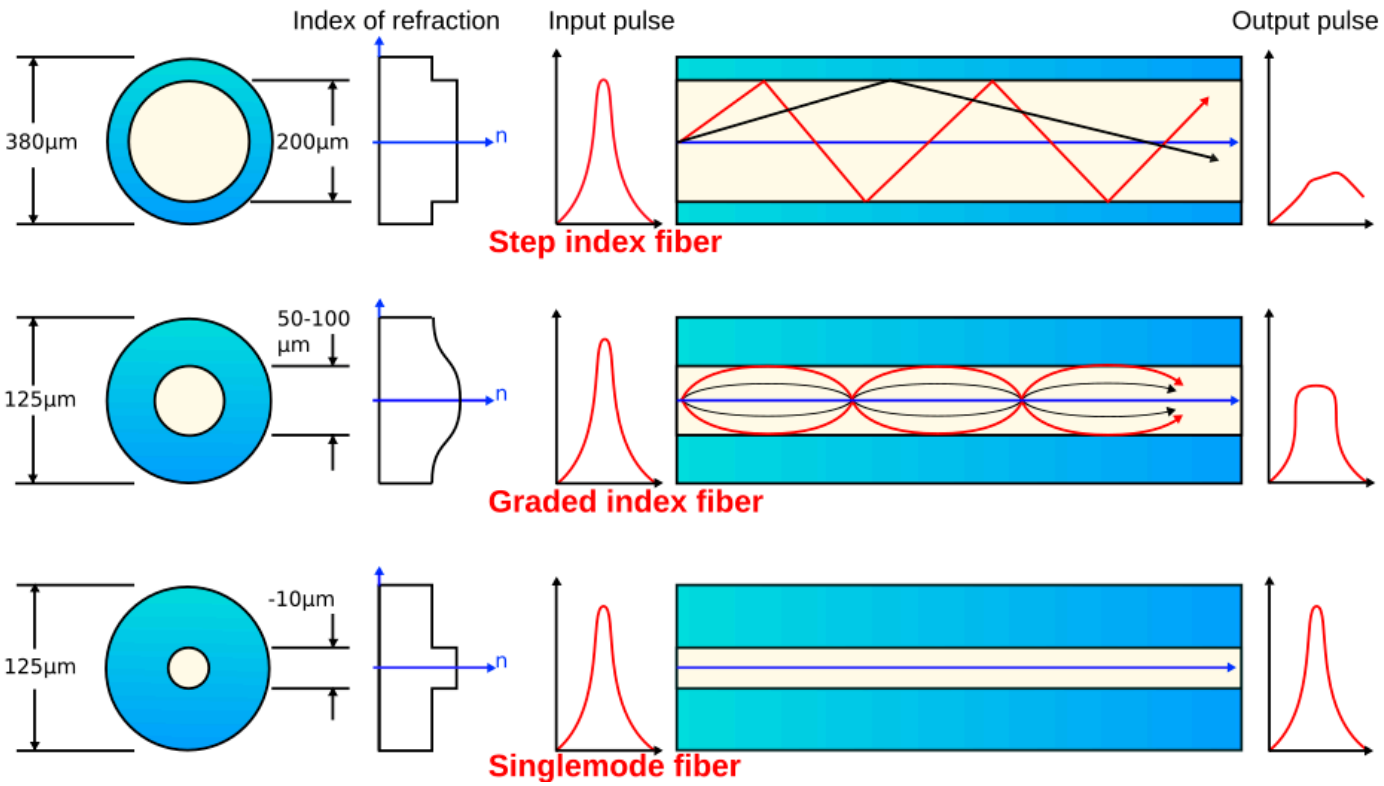

Step-index vs graded-index optical fibre.

7.11.1 Structure & Guidance

Concentric layers: **core** (n_1, highest index) → **cladding** ($n_2 < n_1$) → buffer coating → strength members (Kevlar) → outer jacket. Light is guided by **total internal reflection (TIR)** at the core–cladding boundary (θ_incidence > critical angle θ_c = $\sin^{-1}(n_2/n_1)$).

7.11.2 Numerical Aperture & Acceptance Angle — numericals guaranteed

- **Numerical aperture: NA = $\sqrt{(n_1^2 - n_2^2)} = n_1\sqrt{(2\Delta)}$**, where **$\Delta = (n_1 - n_2)/n_1$** (fractional index difference; typically 0.01–0.03).
- **Acceptance angle** (half-angle of the entry cone, launch from air $n_0 = 1$):

$\theta_a = \sin^{-1}(NA)$; acceptance cone solid angle; rays inside the cone are guided.

- **Number of modes** (step-index): V number **$V = (2\pi a/\lambda)\cdot NA$**; modes ≈ $V^2/2$. **Single-mode condition: V < 2.405.**

7.11.3 Fibre Types

Type	Core dia.	Index profile	Dispersion	Use
Multimode step-index	50–200 µm	Abrupt $n_1 \rightarrow n_2$	Large **intermodal** dispersion	Short links, illumination
Multimode graded-index	50/62.5 µm	Parabolic (n max at axis)	Intermodal dispersion largely equalised (outer rays travel faster)	LANs, campus links
Single-mode step-index	**8–10 µm**	Abrupt, tiny core	No intermodal dispersion; only chromatic	**Long-haul, highest bandwidth**

7.11.4 Losses & Dispersion

- **Attenuation mechanisms**: material **absorption** (OH^- water peaks; intrinsic IR/UV), **Rayleigh scattering** ($\propto 1/\lambda^4$ — dominant at short λ), bending losses (macro/micro), splice/connector losses.
- **Low-loss windows**: **850 nm (~2–3 dB/km), 1310 nm (~0.35 dB/km, zero-dispersion), 1550 nm (~0.2 dB/km, minimum loss — long-haul/DWDM band)**.
- Loss in dB: $\alpha(dB) = 10 \log_{10}(P_{in}/P_{out})$; per-km figure = α/L.
- **Dispersion** (pulse spreading limits bit rate): intermodal (multimode), **chromatic** (material + waveguide; zero near 1310 nm in standard SMF), polarisation-mode dispersion (PMD).

7.11.5 Sources & Detectors

Parameter	LED	LASER diode
Emission	Spontaneous, incoherent	Stimulated, coherent
Spectral width	Broad (30–60 nm)	Narrow (< 1–2 nm)
Coupled power / speed	Low, ≤ ~200 Mbps	High, multi-Gbps
Linearity, cost, drive	Simple, cheap, rugged	Threshold current, temperature control, costly
Fibre pairing	Multimode, short links	Single-mode, long-haul

Detectors: **PIN photodiode** (simple, no gain) and **APD — avalanche photodiode** (internal gain via avalanche multiplication, better sensitivity, higher bias & noise).

7.11.6 Advantages of OFC (list the exam loves)

Enormous bandwidth; lowest loss (≈ 0.2 dB/km) ⇒ long repeater spacing; complete **immunity to EMI** & crosstalk; no ground loops, sparkless (safe in hazardous areas); light weight, small size; high security (no radiation, hard to tap); raw material (silica) abundant. Limitations: splicing/termination skill, bend sensitivity, opto-electronic conversion cost.

7.12 Public Address (PA) Systems

A PA system = **microphones → mixer/pre-amplifier → (tone/graph EQ) → power amplifier → loudspeakers**, reinforcing sound over a large area (railway platforms, auditoria).

7.12.1 Microphones

Type	Principle	Impedance	Notes
Carbon	Resistance of carbon granules varies with pressure	Low	Old telephones; needs DC; noisy
Moving-coil (dynamic)	Coil in magnetic field — electromagnetic induction	Low (~200–600 Ω)	Rugged, no external power — the PA workhorse
Ribbon (velocity)	Thin metal ribbon in field	Very low	Bidirectional (figure-8), delicate
Condenser (capacitor)	Capacitance varies with diaphragm motion	Very high (needs FET buffer + phantom 48 V)	Best fidelity; studio
Electret	Permanently charged condenser	High	Cheap, small (phones, lapel mics)
Crystal (piezoelectric)	Piezoelectric voltage	Very high	High output, poor fidelity

Directional patterns: omnidirectional, cardioid (uni-), bidirectional. **Feedback (howling)** is controlled by cardioid mics, speaker placement, and equalisers.

7.12.2 Amplifiers & Loudspeakers

- Chain: pre-amplifier (raises mV mic signal, mixing, tone control) → driver → **power amplifier** (class B/AB push-pull or class D for efficiency).
- **Loudspeaker**: moving-coil cone driver; voice-coil impedance typically **4, 8 or 16 Ω**; woofer/mid/tweeter split by **crossover networks**; horn (compression) drivers for high-efficiency outdoor PA.
- **Impedance matching** — maximum power transfer from amplifier to speakers; mismatch causes power loss or amplifier damage.

7.12.3 Constant-Voltage (70 V / 100 V) Line — ☆ PA speciality

For **many speakers over long cable runs** (platforms, factories), low-impedance (8 Ω) distribution would need impractically thick cable. Instead:

- A **step-up transformer** at the amplifier raises the output to a standard line voltage — **70.7 V (US) or 100 V (India/Europe)** at full rated power.
- Each speaker has its own **step-down matching transformer** with power taps (e.g., 10 W, 5 W, 2.5 W); speakers connect in **parallel** across the line.
- High voltage ⇒ low current ⇒ **small I^2R cable loss**, easy addition/removal of speakers; total tapped power must not exceed amplifier rating.
- Effective load impedance seen by amplifier: $Z = V_{line}^2/P$ (e.g., 100 V line, 100 W ⇒ 100 Ω).

7.13 Telephony & Electronic Exchange

7.13.1 Basics

- Telephone set: microphone + receiver + **hybrid (2-wire↔4-wire)** + dialler + ringer; local loop = twisted pair to the exchange; exchange supplies **−48 V DC** battery.
- Signalling: **pulse (rotary) dialling** vs **DTMF** (dual-tone multi-frequency — each digit = one low-group + one high-group tone).
- Call progress tones: dial tone, ring-back, busy.
- **Erlang**: unit of telephone traffic (1 Erlang = one circuit occupied continuously); grade of service = blocking probability.

7.13.2 Switching Evolution → Electronic Exchange

Generation	Technology
Manual	Operator + plugboard
Strowger (step-by-step)	Electromechanical, direct pulse-driven selectors
Crossbar	Electromechanical matrix + common control
SPC electronic exchange	**Stored Program Control** — a computer (software) controls switching; e.g., E-10B, EWSD, OCB-283, Indian **C-DOT** exchanges
Digital SPC	**PCM voice + time-division switching**

SPC advantages: flexible services (call waiting, forwarding, conference), easy tariff/number changes by software, self-diagnostics, faster call set-up, detailed billing.

Digital switching fabrics: **Space switch (S)** — crosspoint matrix connects physical lines; **Time switch (T)** — Time-Slot Interchanger (TSI) writes PCM slots into memory and reads them in a different order; large exchanges combine them: **T-S-T** or S-T-S architectures.

7.13.3 PSTN Hierarchy

Subscriber → **Local exchange (end office)** → **Tandem/junction exchange** (intra-city) → **Trunk (toll) exchange** (inter-city, STD) → **International gateway (ISD)**. Modern networks flatten this with digital trunks and IP (NGN/VoIP), but the hierarchy remains the exam answer.

7.14 Radar

RADAR = RAdio Detection And Ranging. Transmit EM pulses; receive echoes from targets; measure delay (range), direction (antenna bearing) and Doppler shift (velocity).

7.14.1 Range Measurement

$R = c\cdot\Delta t/2$ — factor 2 because the pulse travels out **and** back ($c = 3 \times 10^8$ m/s). Handy: 1 µs delay ⇔ 150 m range.

- **Maximum unambiguous range**: $R_{unamb} = c/(2\cdot PRF)$ — echo must return before the next pulse (PRF = pulse repetition frequency).
- **Range resolution**: $\Delta R = c\tau/2$ (τ = pulse width) — shorter pulses resolve closer targets.
- **Duty cycle** = $\tau\cdot PRF$; average power = peak power × duty cycle.

7.14.2 Radar Range Equation

Received echo power:

$$P_r = (P_t\cdot G^2\cdot\lambda^2\cdot\sigma)/((4\pi)^3\cdot R^4)$$

⇒ maximum range:

$$R_{max} = [\ P_t\cdot G^2\cdot\lambda^2\cdot\sigma\ /\ ((4\pi)^3\cdot S_{min})\ ]^{(1/4)}$$

- σ = radar cross-section (m^2), S_{min} = minimum detectable signal, G = antenna gain (same antenna Tx/Rx via **duplexer** — TR/ATR switch).
- **$R_{max} \propto P_t^{(1/4)}$**: to double range, transmit power must rise **16×**.

7.14.3 Radar Types

Type	Principle	Use
Pulse radar	Timed pulses → range & bearing	Air surveillance, ATC
CW radar	Continuous wave; measures only **Doppler shift** $f_d = 2v_r/\lambda$ (no range)	Speed guns
FM-CW radar	Frequency-swept CW; beat frequency gives range **and** velocity	Radio altimeters, automotive radar
MTI / pulse-Doppler	Doppler filtering rejects stationary clutter	Weather, military
Secondary radar (SSR)	Interrogator + transponder replies	ATC identification (IFF)

Displays: **PPI (Plan Position Indicator)** — polar map; A-scope — amplitude vs range. Radar bands: L (1–2 GHz), S (2–4), C (4–8), **X (8–12, most common)**, Ku, Ka.

Doppler shift: $f_d = 2v_r/\lambda = 2v_r f/c$ (approaching ⇒ $+f_d$).

Applications: air-traffic control, weather monitoring, speed enforcement, navigation (ship/air), altimetry, remote sensing, defence.

7.15 Cellular Communication

7.15.1 Cell Concept & Frequency Reuse

- Service area divided into **hexagonal cells**, each served by a low-power base station — the same frequencies are **reused** in sufficiently separated cells ⇒ enormous capacity from limited spectrum.
- **Cluster**: group of N cells using the whole allocated spectrum once; valid $N = i^2 + ij + j^2$ = 1, 3, 4, **7**, 12, 19 … (N = 7 classic).
- **Frequency reuse factor = 1/N**; channels per cell = total/N.
- **Co-channel reuse ratio**: $D/R = \sqrt{(3N)}$ (D = distance between co-channel cells, R = cell radius). Larger N ⇒ less co-channel interference but lower capacity.
- Capacity expansion: **cell splitting** (smaller cells), **sectoring** (120°/60° directional antennas), microcells/femtocells.

7.15.2 Handoff (Handover) & Roaming

- **Handoff**: transferring an ongoing call to a new base station as the mobile crosses cell boundaries — decided on received signal strength with hysteresis margin.
- **Hard handoff** ("break-before-make", FDMA/TDMA-GSM) vs **soft handoff** ("make-before-break", CDMA — mobile connected to ≥ 2 base stations simultaneously).
- **Roaming**: obtaining service outside the home network. Core entities (GSM): BTS → BSC → MSC, with HLR (home register), VLR (visitor register), AuC, EIR; SIM holds IMSI.
- GSM 900: uplink 890–915 MHz, downlink 935–960 MHz, 200 kHz carriers, 8 TDMA slots; GMSK modulation.

7.15.3 Generations — one-line evolution (memorise)

Gen	Era	Technology	Signature
1G	1980s	Analog FM, FDMA (AMPS/NMT)	Voice only
2G	1990s	Digital — **GSM (TDMA)** / IS-95 (CDMA)	Voice + **SMS**; 2.5G GPRS/EDGE data
3G	2000s	**WCDMA/UMTS, CDMA2000**	Mobile data ~Mbps, video calls
4G	2010s	**LTE — OFDMA + MIMO, all-IP**	Mobile broadband 100 Mbps–1 Gbps
5G	2020s	**NR — massive MIMO, mm-wave, network slicing**	eMBB, URLLC (~1 ms), mMTC/IoT

7.16 Satellite Communication

7.16.1 Orbits & the Geostationary Satellite

- **Geostationary orbit (GEO)**: circular, **equatorial**, eastward, period = 23 h 56 min 4 s (sidereal day) ⇒ satellite appears fixed. **Height ≈ 35,786 km** above the equator (orbital radius ≈ 42,164 km); velocity ≈ 3.07 km/s.
- **Three GEO satellites** spaced 120° cover almost the whole earth (Clarke, 1945) — polar regions excluded.
- **Propagation delay**: one hop up+down ≈ 2 × 36,000 km/c ≈ **240–280 ms** — noticeable in voice.
- Other orbits: **LEO** (500–2000 km — Iridium, Starlink; low delay, many satellites), **MEO** (~20,200 km — **GPS**), **Molniya** (highly elliptical, high-latitude coverage). India: INSAT/GSAT (GEO), NavIC/IRNSS (GEO+GSO navigation).

7.16.2 Space Segment: Transponder

Transponder = the satellite's receive–amplify–retransmit chain:

Receive antenna → LNA → **frequency down-converter (uplink→downlink)** → channel filter → high-power amplifier (**TWTA**/SSPA) → transmit antenna.

- Typical C-band transponder bandwidth **36 MHz**; a satellite carries 24+ transponders.
- **Uplink frequency > downlink frequency** (uplink power is easier to raise on the ground; lower downlink frequency suffers less path loss/rain for the power-limited satellite).

Band	Uplink/Downlink (GHz)	Notes
C band	**6 / 4** (5.925–6.425 up, 3.7–4.2 down)	Rain-resistant; large dishes
Ku band	**14 / 12** (14–14.5 up, 11.7–12.2 down)	DTH TV, VSAT; rain fade significant
Ka band	30 / 20	High-throughput satellites; worst rain fade
X band	8 / 7	Military

- Bus subsystems: power (solar array + batteries), attitude & orbit control (station-keeping within ±0.05°), TT&C (telemetry, tracking & command), thermal.
- Earth station: large dish + feed, LNA/LNB, up/down converters, HPA; **EIRP = $P_t \cdot G_t$**; link budget uses free-space path loss FSPL(dB) = 92.4 + 20 log f(GHz) + 20 log d(km). G/T = figure of merit of receive station.

7.16.3 VSAT & Applications

- **VSAT (Very Small Aperture Terminal)**: small earth station (dish **0.75–2.4 m**), Ku/C band, usually a **star network through a central hub** (or mesh); access by TDMA/SCPC/DAMA.
- Applications: banking/ATMs, reservations (railways!), rural telephony & internet, DTH broadcast, disaster-recovery links, SCADA telemetry.
- Satellite services: FSS (fixed), BSS (broadcast/DTH), MSS (mobile — INMARSAT), navigation (GPS/NavIC), remote sensing, weather (INSAT-3DR).

7.17 Worked Numericals (12)

N1. AM power (the 2025 style). A 100 W carrier is amplitude-modulated to 100% by a sine tone. Find total power, power per sideband and efficiency.

$P_t = P_c(1 + m^2/2) = 100(1 + 0.5) =$ **150 W**.

Each sideband $= m^2P_c/4 = 100/4 =$ **25 W** (so both sidebands = 50 W).

$\eta = m^2/(2+m^2) = 1/3 \approx$ **33.3%**.

N2. Modulation index from antenna current. Unmodulated antenna current 10 A rises to 11.2 A with sinusoidal modulation. Find m.

$I_t = I_c\sqrt{(1+m^2/2)} \Rightarrow (11.2/10)^2 = 1 + m^2/2 \Rightarrow 1.2544 - 1 = m^2/2 \Rightarrow m^2 = 0.5088 \Rightarrow$ **$m \approx 0.713$ (71.3%)**.

N3. Multi-tone AM. P_c = 400 W modulated simultaneously by tones with $m_1 = 0.3$ and $m_2 = 0.4$. Total power?

$m_t = \sqrt{(0.09+0.16)} = 0.5$. $P_t = 400(1 + 0.25/2) = 400 \times 1.125 =$ **450 W**.

N4. Envelope readings. An AM display shows V_{max} = 20 V, V_{min} = 4 V. Find m, A_c, A_m.

$m = (20-4)/(20+4) = 16/24 =$ **0.667**; $A_c = (20+4)/2 =$ **12 V**; $A_m = (20-4)/2 =$ **8 V**.

N5. Carson's rule. An FM signal has deviation 50 kHz with a 10 kHz tone. Bandwidth and β?

$\beta = 50/10 =$ **5**. $B = 2(\Delta f + f_m) = 2(50+10) =$ **120 kHz**.

N6. FM deviation scaling. In FM, k_f gives Δf = 20 kHz for A_m = 2 V at f_m = 4 kHz. If amplitude doubles and frequency halves, find new β.

$\Delta f \propto A_m \Rightarrow \Delta f' = 40$ kHz; $f_m' = 2$ kHz $\Rightarrow \beta' = 40/2 =$ **20** (old β was 5 — β quadruples).

N7. Image frequency. An AM receiver (IF = 455 kHz, LO above signal) is tuned to 1000 kHz. Find LO and image frequencies.

$f_{LO} = 1000 + 455 =$ **1455 kHz**; $f_{image} = f_s + 2f_{IF} = 1000 + 910 =$ **1910 kHz**.

N8. Sampling & PCM bit rate. A 4 kHz voice signal is sampled at 25% above Nyquist and encoded with 8 bits/sample. Find f_s, bit rate and minimum bandwidth.

Nyquist = 8 kHz; $f_s = 1.25 \times 8$ k = **10 kHz**. $R_b = 10$ k $\times 8 =$ **80 kbps**. $B_{min} = R_b/2 =$ **40 kHz**.

N9. PCM SNR. How many bits per sample guarantee SQNR ≥ 40 dB, and what SQNR results?

$6.02n + 1.76 \geq 40 \Rightarrow n \geq 6.35 \Rightarrow$ **n = 7 bits**, giving $6.02\times7 + 1.76 \approx$ **43.9 dB**.

N10. Radar range. A radar echo returns 200 μs after transmission. Target range? Also the maximum unambiguous range for PRF = 1 kHz.

$R = c\Delta t/2 = (3\times10^8 \times 200\times10^{-6})/2 =$ **30 km**.

$R_{unamb} = c/(2 \cdot PRF) = 3\times10^8/(2\times1000) =$ **150 km**.

N11. Numerical aperture. A fibre has $n_1 = 1.50$ (core), $n_2 = 1.47$ (cladding). Find NA and the acceptance angle in air.

$NA = \sqrt{(1.50^2 - 1.47^2)} = \sqrt{(2.25 - 2.1609)} = \sqrt{0.0891} \approx$ **0.298**.

$\theta_a = \sin^{-1}(0.298) \approx$ **17.4°** (acceptance cone ≈ 34.7° full angle).

(Also $\Delta = (1.50-1.47)/1.50 = 0.02$; check: $NA = n_1\sqrt{(2\Delta)} = 1.5\sqrt{0.04} = 0.3$ ✓)

N12. VSWR & reflection. A 50 Ω line is terminated in 75 Ω. Find Γ, VSWR and % power reflected.

$\Gamma = (75-50)/(75+50) = 25/125 =$ **0.2**.

$S = (1+0.2)/(1-0.2) =$ **1.5** (= 75/50 ✓).

Reflected power $= |\Gamma|^2 = 0.04 \Rightarrow$ **4%** reflected, 96% delivered.

Bonus N13. Quarter-wave match. Match a 100 Ω antenna to a 50 Ω line with a λ/4 transformer.

$Z_0' = \sqrt{(50\times100)} = \sqrt{5000} \approx$ **70.7 Ω** (hence 70–75 Ω sections are common).

Bonus N14. Delta modulation slope overload. DM with $f_s = 64$ kHz, step $\Delta = 0.1$ V on a tone $A \sin(2\pi\times1000t)$. Max A without slope overload?

Need $\Delta \cdot f_s \geq 2\pi f_m \cdot A \Rightarrow A \leq (0.1 \times 64000)/(2\pi\times1000) = 6400/6283 \approx$ **1.02 V**.

7.18 PYQ Corner — 22-04-2025 CBT-2 (fully solved)

Q1. In the detection (demodulation) of an FM signal using a PLL, the demodulated output is obtained from —

(a) the VSO free-running port (b) the phase-detector RF port directly (c) **the error amplifier / loop-filter output (VCO control voltage)** (d) a separate envelope detector

Answer: (c). In lock the VCO tracks the instantaneous input frequency $f_c + k_f m(t)$. Because VCO frequency is proportional to its control voltage, that control (error) voltage is a replica of m(t). The PLL FM demodulator therefore delivers the message at the loop-filter/error-amplifier output — no tuned circuits, excellent linearity.

Q2. Pulse Width Modulation (PWM) is also known as —

(a) Pulse Amplitude Modulation (b) **Pulse Duration Modulation (PDM)** (c) Pulse Code Modulation (d) Delta Modulation

Answer: (b). PWM ≡ **PDM** ≡ Pulse Length Modulation (PLM). Together with PPM it belongs to the **Pulse Time Modulation (PTM)** family, since the information is carried by pulse timing (width/position), not amplitude.

Q3. In QPSK, the phase of the carrier takes which set of values?

(a) 0°, 45°, 90°, 135° (b) **0°, 90°, 180°, 270°** (c) 0° and 180° only (d) 0°, 120°, 240°, 360°

Answer: (b). QPSK maps 2 bits/symbol onto 4 equally spaced carrier phases separated by 90°: **0°, 90°, 180°, 270°** (the offset constellation 45°/135°/225°/315° is the equivalent rotated version, but against these options the standard answer is 0/90/180/270). Symbol rate = $R_b/2$, so QPSK needs half the bandwidth of BPSK at the same bit rate.

Q4. Which of the following is NOT a pulse-shaping filter?

(a) Raised-cosine filter (b) Sinc (ideal Nyquist) filter (c) Gaussian filter (d) **Notch/Butterworth band-stop type filter (the non-Nyquist distractor)**

Answer: (d). Pulse-shaping filters are designed to limit bandwidth while controlling ISI: the **sinc** (ideal Nyquist, minimum bandwidth), the **raised-cosine / root-raised-cosine** (practical zero-ISI family with roll-off α) and the **Gaussian** (GMSK/GSM — compact spectrum). A generic frequency-selective filter (notch, plain Butterworth band-stop, high-pass etc.) is not a pulse-shaping filter.

Q5. A 100 W carrier is amplitude-modulated to a depth of 100%. The power in the lower sideband is —

(a) 50 W (b) **25 W** (c) 100 W (d) 12.5 W

Answer: (b). $P_{LSB} = m^2 P_c/4 = (1)^2(100)/4 =$ **25 W**. (USB also 25 W; total transmitted power = 100(1 + ½) = 150 W; sidebands together carry 50 W = 33.3%.)

Q6. If x(t) is a real and even function of time, its Fourier transform X(f) is —

(a) imaginary and odd (b) **real and even** (c) complex with odd magnitude (d) imaginary and even

Answer: (b). For real x(t), $X(-f) = X^*(f)$. Adding even symmetry forces the imaginary (sine-transform) part to vanish: $X(f) = 2\int_0^{\infty} x(t) \cos 2\pi ft \, dt$ — a **real and even** function of f. (Real-odd ⇒ imaginary-odd; the "even preserves, odd swaps real↔imaginary" rule.)

Q7. Which statement about AM detection using a PLL is correct?

(a) The demodulated AM output is the PLL error voltage itself

(b) **The PLL regenerates a coherent carrier (VCO output locked to the incoming carrier); this carrier multiplies the AM signal and a low-pass filter recovers the message — i.e., synchronous detection**

(c) A PLL cannot be used for AM because AM has no frequency information

(d) The VCO amplitude follows the AM envelope

Answer: (b). The PLL locks to the AM carrier and its constant-amplitude VCO output acts as the clean local carrier (phase-aligned via a 90° shifter). Feeding this and the AM wave to a **product detector (multiplier) + LPF** performs coherent detection — better than envelope detection under noise and carrier fading. Note the contrast with FM: in FM the error voltage is the output; in AM the multiplier+LPF output is.

Q8. The demodulation of PPM typically employs —

(a) only an envelope detector

(b) **a reference pulse generator with a flip-flop (converting PPM to PWM) followed by a low-pass filter**

(c) a frequency discriminator

(d) a Schmitt trigger alone

Answer: (b). Standard PPM demodulator: a synchronised **reference pulse sets a flip-flop**; the arriving **PPM pulse resets it**. The flip-flop output is a PWM signal whose width equals the transmitted position shift; averaging it in a **low-pass filter** recovers m(t). (Equivalent ramp-generator version: ramp started by the reference pulse, sampled/stopped by the PPM pulse — height ∝ position.)

7.19 Practice MCQs (30)

1. The main reason for modulation is —

(a) to reduce noise (b) reduction of antenna height to practical size (c) increase message power (d) reduce bandwidth

2. Thermal noise power available from a resistor is —

(a) kT/B (b) kTB (c) kT^2B (d) independent of bandwidth

3. In a cascade of amplifiers, the overall noise figure is dominated by —

(a) last stage (b) first stage (c) middle stage (d) all equally

4. An AM wave has V_max = 12 V and V_min = 4 V. The modulation index is —

(a) 0.33 (b) 0.5 (c) 0.66 (d) 0.75

5. The maximum transmission efficiency of standard AM is —

(a) 25% (b) 33.3% (c) 50% (d) 100%

6. The bandwidth of a standard AM signal modulated by 5 kHz audio is —

(a) 5 kHz (b) 10 kHz (c) 2.5 kHz (d) 15 kHz

7. Analog TV video is transmitted using —

(a) SSB (b) DSB-SC (c) VSB (d) FM

8. Diagonal clipping in an envelope detector occurs when —

(a) RC too small (b) RC too large (c) m = 0 (d) carrier absent

9. A carrier is frequency-modulated by a 2 kHz tone producing 10 kHz deviation. The modulation index is —

(a) 0.2 (b) 2 (c) 5 (d) 20

10. For commercial FM (Δf = 75 kHz, f_m = 15 kHz), Carson bandwidth is —

(a) 90 kHz (b) 150 kHz (c) 180 kHz (d) 200 kHz

11. Total power of an FM wave when modulation index doubles —

(a) doubles (b) quadruples (c) halves (d) remains unchanged

12. Pre-emphasis in FM broadcasting boosts —

(a) low frequencies at Tx (b) high frequencies at Tx (c) high frequencies at Rx (d) carrier amplitude

13. The FM detector with built-in amplitude limiting is the —

(a) slope detector (b) Foster–Seeley discriminator (c) ratio detector (d) square-law detector

14. The Armstrong method generates FM using —

(a) varactor diode (b) reactance FET (c) phase modulation of an integrated message with a crystal carrier (d) PLL

15. A superheterodyne AM receiver tuned to 700 kHz (IF = 455 kHz, LO high) has image frequency —

(a) 245 kHz (b) 1155 kHz (c) 1610 kHz (d) 910 kHz

16. Standard IF of an FM broadcast receiver is —

(a) 455 kHz (b) 1.6 MHz (c) 10.7 MHz (d) 38.9 MHz

17. A signal band-limited to 6 kHz must be sampled at least at —

(a) 6 kHz (b) 3 kHz (c) 12 kHz (d) 24 kHz

18. In PPM, the message information is carried by the pulse —

(a) amplitude (b) width (c) position (d) shape

19. Adding one bit per sample to a PCM system improves SQNR by about —

(a) 3 dB (b) 6 dB (c) 1.76 dB (d) 12 dB

20. Slope-overload distortion in delta modulation is reduced by —

(a) decreasing step size (b) increasing step size or sampling rate (c) reducing sampling rate (d) removing the integrator

21. For the same bit rate, the bandwidth of QPSK compared with BPSK is —

(a) same (b) double (c) half (d) quadruple

22. GMSK, used in GSM, employs which pulse-shaping filter?

(a) raised cosine (b) sinc (c) Gaussian (d) Chebyshev

23. The E1 PCM primary multiplex rate is —

(a) 1.544 Mbps (b) 2.048 Mbps (c) 8.448 Mbps (d) 64 kbps

24. Long-distance HF (short-wave) communication uses —

(a) ground wave (b) sky wave (c) space wave (d) duct propagation

25. If maximum ionospheric electron density is 1.21×10^{12} per m^3, the critical frequency is about —

(a) 4.95 MHz (b) 9.9 MHz (c) 11 MHz (d) 1.21 MHz

26. A lossless line has L = 0.5 µH/m and C = 200 pF/m. Its characteristic impedance is —

(a) 25 Ω (b) 50 Ω (c) 75 Ω (d) 100 Ω

27. A quarter-wave lossless line shorted at the far end appears at its input as —

(a) short circuit (b) open circuit (c) pure inductance (d) matched load

28. A fibre with NA = 0.242 launched from air has acceptance angle —

(a) 7° (b) 14° (c) 24.2° (d) 28°

29. The height of a geostationary satellite above the earth's surface is approximately —

(a) 6,378 km (b) 20,200 km (c) 35,786 km (d) 42,164 km

30. In a cellular system with cluster size N = 7, the co-channel reuse ratio D/R is —

(a) 3 (b) $\sqrt{21} \approx 4.58$ (c) 7 (d) 21

Answer Key & Brief Explanations

#	Ans	Explanation
1	b	Antenna ≈ λ/4; only practical at high (carrier) frequency.
2	b	$P_n = kTB$ — proportional to bandwidth.
3	b	Friis: later stages divided by preceding gains — first stage (LNA) dominates.
4	b	$m = (12-4)/(12+4) = 8/16 = 0.5$.
5	b	$\eta_{max} = m^2/(2+m^2)$ at $m = 1 \Rightarrow 1/3 = 33.3\%$.
6	b	$B_{AM} = 2f_m = 10$ kHz.
7	c	Vestigial sideband — saves bandwidth yet keeps low-frequency video content.
8	b	Large RC cannot discharge fast enough to follow the falling envelope.
9	c	$\beta = \Delta f/f_m = 10/2 = 5$.
10	c	$B = 2(75+15) = 180$ kHz.
11	d	FM amplitude constant ⇒ power independent of β.
12	b	Boost highs before modulation; de-emphasis at Rx cuts them with the noise.
13	c	Ratio detector's large capacitor stabilises the sum voltage — inherent limiting.
14	c	Integrator + balanced (phase) modulator on a crystal carrier → NBFM → multipliers.
15	c	$f_{im} = f_s + 2f_{IF} = 700 + 910 = 1610$ kHz.
16	c	AM: 455 kHz; FM: 10.7 MHz; TV vision: 38.9 MHz.
17	c	Nyquist rate = 2 × 6 = 12 kHz.
18	c	Position (timing) — PPM is a PTM scheme.
19	b	SQNR = 6.02n + 1.76 dB ⇒ ~6 dB/bit.
20	b	Overload when $\Delta \cdot f_s <$ slope; raise Δ or f_s (or use ADM).
21	c	2 bits/symbol ⇒ half the symbol rate ⇒ half the bandwidth.
22	c	Gaussian filter → Gaussian MSK; compact spectrum.
23	b	E1 = 32 × 64 kbps = 2.048 Mbps (T1 = 1.544 Mbps).
24	b	HF refracts off F-layers — multi-hop worldwide coverage.
25	b	$f_c = 9\sqrt{N} = 9 \times 1.1 \times 10^6 = 9.9$ MHz.

#	Ans	Explanation
26	b	$Z_0 = \sqrt{(L/C)} = \sqrt{(0.5\times10^{-6}/200\times10^{-12})} = \sqrt{2500} = 50\ \Omega$.
27	b	Shorted λ/4 inverts to an open (parallel-resonant "metallic insulator").
28	b	$\theta_a = \sin^{-1} 0.242 \approx 14°$.
29	c	35,786 km altitude (radius 42,164 km from earth's centre).
30	b	$D/R = \sqrt{(3N)} = \sqrt{21} \approx 4.58$.

7.20 Rapid-Revision Formula Sheet

Noise

- $P_n = kTB$; $V_n = \sqrt{(4kTRB)}$; $F = SNR_{in}/SNR_{out}$; $T_e = (F-1)\cdot290$
- Friis: $F = F_1 + (F_2-1)/G_1 + (F_3-1)/(G_1G_2)$

Fourier symmetry

- real-even → real-even · real-odd → imaginary-odd · real → $X(-f)=X^*(f)$

AM

- $m = A_m/A_c = (V_{max}-V_{min})/(V_{max}+V_{min})$; $m_t = \sqrt{\Sigma m_i^2}$
- $B = 2f_m$; $P_t = P_c(1+m^2/2)$; **each sideband = $m^2P_c/4$**; $I_t = I_c\sqrt{(1+m^2/2)}$
- $\eta = m^2/(2+m^2)$ → 33.3% max; SSB bandwidth = f_m

FM/PM

- $\beta = \Delta f/f_m$ (FM); $\Delta f = k_f A_m$; Carson: **$B = 2(\Delta f+f_m)$**
- FM power constant = $A_c^2/2R$; broadcast: Δf = 75 kHz, B_{ch} = 200 kHz; pre-emphasis τ = 75 µs
- PLL-FM: output = error/loop-filter voltage; PLL-AM: VCO = coherent carrier → multiplier + LPF

Receiver

- $f_{LO} = f_s + f_{IF}$; **$f_{image} = f_s + 2f_{IF}$**; IFRR = $\sqrt{(1+Q^2\rho^2)}$; IF: 455 kHz (AM), 10.7 MHz (FM)

Pulse & PCM

- $f_s \geq 2f_m$; PWM = PDM = PLM ∈ PTM; PPM demod = ref-pulse + flip-flop → PWM → LPF
- $L = 2^n$; $\Delta = V_{pp}/L$; $N_q = \Delta^2/12$; **SQNR = 6.02n + 1.76 dB**; $R_b = n\cdot f_s$; $B_{min} = R_b/2$
- Voice: 8 kHz × 8 bit = 64 kbps; DM overload: $\Delta f_s \geq 2\pi f_m A_m$

Digital modulation

- QPSK phases **0/90/180/270°**; QPSK BW = ½ BPSK BW; pulse-shaping: sinc, raised-cosine ($B = (1+\alpha)R_s/2$), RRC, Gaussian (GMSK)

Multiplexing

- T1 = 1.544 Mbps (24 ch); **E1 = 2.048 Mbps (30+2)**; FDM group = 12 ch

Propagation

- f_c = 9√N_max; MUF = f_c sec θ; d_LOS(km) = 4.12(√h_t+√h_r)

Transmission lines

- $Z_0 = \sqrt{(L/C)}$; $\Gamma = (Z_L - Z_0)/(Z_L + Z_0)$; $S = (1+|\Gamma|)/(1-|\Gamma|)$
- λ/4: $Z_{in} = Z_0^2/Z_L$ (match section $Z_0' = \sqrt{(Z_0 Z_L)}$); λ/2: $Z_{in} = Z_L$
- Reflected power = $|\Gamma|^2$; distortionless: R/L = G/C

OFC

- **$NA = \sqrt{(n_1^2 - n_2^2)} = n_1\sqrt{(2\Delta)}$**; $\theta_a = \sin^{-1}NA$; $V = (2\pi a/\lambda)NA$; single-mode V < 2.405
- Windows: 850/1310/1550 nm; loss ≈ 0.2 dB/km @1550; Rayleigh ∝ $1/\lambda^4$

PA systems

- Constant-voltage line 70.7 V / **100 V**; speaker transformers in parallel; $Z = V^2/P$

Radar

- **$R = c\Delta t/2$** (1 μs ↔ 150 m); $R_{unamb} = c/2PRF$; $\Delta R = c\tau/2$
- R_max = [P_tG²λ²σ/((4π)³S_min)]^¼ ⇒ R ∝ P_t^¼; $f_d = 2v_r/\lambda$

Cellular

- Cluster $N = i^2 + ij + j^2$; reuse 1/N; **$D/R = \sqrt{(3N)}$**; soft handoff = CDMA
- 1G analog → 2G GSM/SMS → 3G WCDMA → 4G LTE/OFDM → 5G NR/mm-wave

Satellite

- GEO height **35,786 km**, period = sidereal day, equatorial; delay ≈ 250 ms/hop
- Uplink > downlink: **C 6/4 GHz, Ku 14/12 GHz**; transponder BW 36 MHz; VSAT dish 0.75–2.4 m, star/hub

---

End of Chapter 7. Next: Chapter 8 — Measurement & Instrumentation (as per syllabus sequence).

Chapter 8 — Data Communication and Networks

Syllabus (CEN 05/2025, Annexure-VII C, Unit 8): Introduction to data communication; Hardware and interface; Introduction to Networks and Networking devices; Local Area Network and Wide Area Network; Internet working.

8.0 Weightage & Trend Box

Parameter	Detail
Weight in Technical section	**~8% → 4 questions of 50** (scaled: 8 of 100) in the 22-04-2025 CBT-2 paper
Difficulty level observed	Easy–moderate; purely conceptual, **no numericals** appeared, but Nyquist/Shannon and subnetting are standard JE-level askables
Negative marking	−1/3, so guess only when you can eliminate two options

Actual questions observed in the 22-04-2025 CBT-2 (Electronics & Allied) paper from this unit:

1. **Modem vs NIC** — which statement correctly distinguishes a modem from a Network Interface Card.
2. **UTP vs STP** — identify the **incorrect** statement (the trap: "UTP has higher EMI resistance than STP" — FALSE; the shield in STP gives it the higher EMI immunity).
3. **Topology failure behaviour** — how star / bus / ring / mesh topologies behave when a node or cable fails.
4. **SNMP** — the manager–agent model and which messages (GET/SET/TRAP) flow in which direction.

Preparation strategy: This chapter is fact-dense rather than derivation-heavy. Master the comparison tables (topologies, devices vs OSI layer, UTP/STP, TCP/UDP, port numbers) — RRB lifts questions almost verbatim from such tables. Do the 8 worked examples so that a Shannon-capacity or subnetting numerical, if it appears, is free marks.

8.1 Introduction to Data Communication

8.1.1 What is data communication?

Data communication is the exchange of data between two devices via some transmission medium (wire, cable, or air). For communication to occur, the devices must be part of a communication system made up of hardware (physical equipment) and software (programs and protocols).

The effectiveness of a data-communication system depends on four fundamental characteristics:

Characteristic	Meaning
Delivery	Data must reach the correct destination, and only the intended device/user
Accuracy	Data must be delivered without errors (altered bits are unusable)
Timeliness	Data must arrive in time to be useful (critical for audio/video — "real-time" delivery)
Jitter	Variation in packet arrival time; uneven delay ruins audio/video quality

8.1.2 Components of a data-communication system (five components)

```
Sender → [Message] → Transmission medium → Receiver
              ↑ governed by Protocol (both ends) ↑
```

#	Component	Role	Example
1	**Message**	The information to be communicated	Text, numbers, pictures, audio, video
2	**Sender**	Device that sends the message	Computer, phone, workstation, camera
3	**Receiver**	Device that receives the message	Computer, phone, TV
4	**Transmission medium**	Physical path from sender to receiver	Twisted pair, coax, fibre, radio waves
5	**Protocol**	Set of rules governing communication — an *agreement* between communicating devices	TCP/IP, HTTP, Ethernet

> Without a protocol, two connected devices may be linked but cannot *communicate* — like two people speaking different languages.

8.1.3 Data representation

Data type	Representation
Text	Bit patterns — coded character sets: **ASCII** (7-bit, 128 symbols), extended ASCII (8-bit), **Unicode** (32-bit, all world scripts; ASCII = first 127 Unicode characters)
Numbers	Binary directly (not character codes) for arithmetic
Images	Matrix of **pixels**; each pixel a bit pattern (RGB / YCM colour models)
Audio	Continuous signal sampled and digitised (PCM)
Video	Sequence of images (frames) + audio

8.1.4 Data flow (direction of transmission) — **frequent one-mark question**

Mode	Direction	Description	Example
Simplex	One way only	One device transmits, the other only receives; entire channel capacity in one direction	Keyboard → CPU, TV/radio broadcast
Half-duplex	Both ways, **one at a time**	Each station can both transmit and receive, but not simultaneously; entire capacity taken by whichever is sending	Walkie-talkie, CB radio
Full-duplex (duplex)	Both ways **simultaneously**	Either two physical paths, or channel capacity divided between the two directions	Telephone network, modern switched Ethernet

8.1.5 Serial vs parallel transmission

Feature	Parallel	Serial
Bits sent	n bits at a time over n wires	1 bit at a time over a single line
Speed (same clock)	n× faster	Slower per clock, but clocks can be much higher
Cost & distance	Expensive; crosstalk/skew limits to short distances (inside PC, old printer port)	Cheap; long distances (USB, RS-232, SATA, Ethernet, PCIe lanes)
Conversion	—	Needs parallel↔serial converters (UART/shift registers) at the interfaces

8.1.6 Synchronous vs asynchronous serial transmission

Feature	Asynchronous	Synchronous
Timing	No common clock; timing recovered per character	Common/embedded clock; continuous bit stream
Framing	Each byte framed by **1 start bit (0)** and **1–2 stop bits (1)**; gaps allowed between bytes	Data sent as long frames/blocks; no start–stop bits per byte
Overhead	High (≥ 2 extra bits per 8 data bits ≈ 20%+)	Low — higher efficiency
Speed	Lower	Higher
Example	RS-232 terminal, keyboard (UART)	HDLC, Ethernet frames, SONET

*(A third class, **isochronous**, guarantees data arrives at a fixed rate — used for real-time audio/video, e.g. USB isochronous transfers.)*

8.1.7 Bit rate vs baud rate — **classic trap**

- **Bit rate** = number of **bits** transmitted per second (bps).
- **Baud rate** = number of **signal units (symbols)** transmitted per second.
- If each signal element carries r bits: **Bit rate = Baud rate × r**, where r = $\log_2 L$ (L = number of signal levels).
- Baud rate ≤ bit rate always (equal when 1 bit/symbol). **Bandwidth required is proportional to baud rate, not bit rate** — that is why multi-level modulation (QAM) packs high bit rates into limited bandwidth.

Quick example: A 16-QAM signal (L = 16 → 4 bits/symbol) at 2400 baud carries 2400 × 4 = **9600 bps**.

8.1.8 Bandwidth, throughput, latency

Term	Meaning
Bandwidth (Hz)	Range of frequencies a channel passes (analog sense)
Bandwidth (bps)	Maximum data rate a link can carry (digital, loose usage)
Throughput	*Actual* measured rate of successful data delivery — always ≤ bandwidth
Latency (delay)	Time for a complete message to travel source → destination = propagation time + transmission time + queuing time + processing delay
Propagation time	Distance ÷ propagation speed (~2×10^8 m/s in cable/fibre)
Transmission time	Message size ÷ bandwidth
Bandwidth–delay product	Number of bits that can "fill the link" = bandwidth × round-trip delay

8.1.9 Channel capacity — Nyquist and Shannon (formulas + when to use which)

Nyquist bit rate (noiseless channel):

> **$C = 2 \times B \times \log_2 L$** bits/second

where B = bandwidth (Hz), L = number of discrete signal levels. Increasing L raises capacity but makes the receiver's job harder (levels closer together).

Shannon capacity (noisy channel) — theoretical upper limit:

> **$C = B \times \log_2 (1 + SNR)$** bits/second

where SNR is the **linear** (not dB) signal-to-noise ratio. Convert: SNR(linear) = 10^(SNR_dB/10). Handy identity: **$SNR_{dB} = 10 \log_{10} SNR$**.

- Shannon gives the *ceiling* no coding scheme can beat; Nyquist tells you *how many levels* you need to approach it.
- In practice: compute Shannon C for the limit, then choose a working rate below it and use Nyquist to find L.

(Worked Examples 1–3 in §8.10.)

8.2 Transmission Media

Transmission media sit **below the Physical layer** of the OSI model. Two broad classes:

```
Transmission media
├── Guided (wired): twisted pair, coaxial, optical fibre
└── Unguided (wireless): radio, microwave, infrared, satellite
```

8.2.1 Twisted-pair cable

Two insulated copper conductors twisted together. **Twisting cancels externally induced noise**: interference affects both wires nearly equally, so the *difference* signal (which carries the data) stays clean; more twists per unit length → better noise rejection.

UTP vs STP — 2025 PYQ area:

Feature	UTP (Unshielded Twisted Pair)	STP (Shielded Twisted Pair)
Construction	Twisted pairs in plastic jacket only	Each pair (or the bundle) wrapped in **metal foil/braid shield**
EMI / noise immunity	Lower — relies on twisting alone	**Higher — shield blocks electromagnetic interference**
Cost	Cheaper	Costlier
Installation	Easy, flexible, thin	Bulkier; shield must be **grounded** to work
Speed/attenuation	Comparable per category; STP performs better in electrically noisy environments	—
Usage	Overwhelmingly common in LANs, telephone	Industrial plants, near motors/heavy machinery

> ⚠ **PYQ trap (22-04-2025):** "UTP has higher resistance to EMI than STP" is **FALSE**. STP's grounded shield gives it superior EMI resistance. UTP's advantages are *cost, flexibility and ease of installation*, never EMI immunity.

UTP categories (EIA/TIA-568) — memorise Cat 5e/6/7:

Category	Max data rate	Bandwidth	Typical use
Cat 3	10 Mbps	16 MHz	Old telephone / 10Base-T
Cat 5	100 Mbps	100 MHz	Fast Ethernet
Cat 5e	**1 Gbps**	100 MHz	Gigabit Ethernet (most common legacy LAN cable)
Cat 6	1 Gbps (10 Gbps up to ~55 m)	250 MHz	Modern LAN standard
Cat 6a	10 Gbps (100 m)	500 MHz	10G LANs
Cat 7	10 Gbps	600 MHz	**Shielded (S/FTP) by design**; data centres
Cat 8	25/40 Gbps	2000 MHz	Short data-centre links (~30 m)

Standard UTP connector: **RJ-45** (8 pins). Max segment length for LAN Ethernet over UTP: **100 m**.

8.2.2 Coaxial cable

- Central copper core → insulating dielectric → braided outer conductor (acts as **shield + return path**) → plastic jacket.
- Carries higher-frequency signals than twisted pair; good noise immunity because of concentric shield; but higher attenuation → needs repeaters/amplifiers for long runs.
- Connector: **BNC** (also T-connector, terminator for old bus LANs).
- RG ratings: **RG-59** (75 Ω, cable TV), **RG-58** (50 Ω, thin Ethernet 10Base2), RG-11 (thick Ethernet 10Base5).
- Uses: cable TV networks, traditional Ethernet buses, CCTV.

8.2.3 Optical fibre

Transmits data as **light pulses** through a glass/plastic core using **total internal reflection** (core refractive index > cladding refractive index).

Item	Detail
Structure	Core (n_1) → cladding ($n_2 < n_1$) → buffer/jacket
Propagation modes	**Multimode step-index**, **multimode graded-index**, **single-mode**
Single-mode	Tiny core (~8–10 μm), laser source, longest distance, highest bandwidth, costliest
Multimode	Larger core (50/62.5 μm), LED source, shorter links (buildings/campus)
Sources / detectors	LED or laser diode / photodiode (PIN, APD)
Connectors	SC, ST, LC, MT-RJ

Advantages: enormous bandwidth (THz), very low attenuation (repeaters tens of km apart), **complete immunity to EMI** (light, not electricity), no crosstalk, light weight, hard to tap (secure), no spark hazard.

Disadvantages: costly installation and skilled splicing, unidirectional per fibre (pairs used), fragile to sharp bends.

Guided media comparison (exam table):

Feature	Twisted pair	Coaxial	Optical fibre
Bandwidth / data rate	Low–moderate	Moderate–high	**Highest**
EMI immunity	UTP low, STP moderate	Good	**Complete**
Attenuation	High	Moderate	**Lowest**
Cost	**Lowest**	Moderate	Highest
Distance per segment	~100 m	~500 m	km–tens of km
Installation	Easiest	Moderate	Hardest (splicing)

8.2.4 Unguided (wireless) media

Signals travel through free space; **antennas** radiate/receive. Propagation: ground wave (< 2 MHz), sky wave / ionospheric (2–30 MHz), line-of-sight (> 30 MHz).

Medium	Band (typical)	Character	Uses
Radio waves	3 kHz – 1 GHz	**Omnidirectional**, penetrate walls, prone to interference; licensed bands	AM/FM radio, TV, cordless phones, paging
Microwaves	1 – 300 GHz	**Unidirectional, line-of-sight**; parabolic dish/horn antennas; towers ~50 km apart (curvature); do not penetrate walls well; rain attenuation at high f	Terrestrial point-to-point links, cellular backhaul, satellite links, Wi-Fi (2.4/5 GHz ISM)
Infrared	300 GHz – 400 THz	Very short range, **cannot penetrate walls** (advantage: no inter-room interference; disadvantage: same-room only); unusable outdoors (sunlight)	TV remotes, IrDA device-to-device
Satellite	C (4/6 GHz), Ku (11/14), Ka bands	GEO satellite at **35,786 km** acts as repeater (transponder); one-hop covers ⅓ of Earth; **propagation delay ~270 ms** up+down	DTH TV, VSAT, GPS (MEO), remote-area links

8.3 Encoding, Modems and the NIC

8.3.1 Line coding one-liners (digital data → digital signal)

Scheme	Rule	Key point
Unipolar NRZ	1 = +V, 0 = 0 V	DC component; sync loss on long runs of same bit
Polar NRZ-L	1 = one level, 0 = the other	Level itself is the bit
NRZ-I	1 = **invert** at bit start, 0 = no change	Transition = 1 (differential; used in USB with stuffing)
RZ (Return-to-Zero)	Signal returns to 0 mid-bit	Self-syncing but needs **double bandwidth**
Manchester	**Transition in the middle of every bit** (low→high = 1, high→low = 0 per IEEE 802.3)	Self-clocking, no DC; used in **10 Mbps Ethernet**; needs 2× bandwidth
Differential Manchester	Mid-bit transition always (clock); transition **at start** = 0	Used in Token Ring
Bipolar AMI	0 = zero, 1 = alternating ±V	No DC; used in T1 lines

8.3.2 Modem — MOdulator/DEModulator

- Converts the computer's **digital** data into an **analog** signal suitable for an analog channel (telephone local loop) — *modulation* — and converts received analog back to digital — *demodulation*.
- Works with ASK/FSK/PSK/QAM constellations; V-series ITU standards (V.32 = 9600 bps, V.90/V.92 = 56 kbps down).
- Modem is a **DCE** (Data Circuit-terminating Equipment); computer/terminal is the **DTE**.
- Modern usage: DSL modem (digital data over telephone copper at higher frequencies), cable modem (DOCSIS over coax), optical modem/ONT.
- **56k asymmetric note:** V.90 gives 56 kbps downstream / 33.6 kbps upstream because the ISP side is digitally connected.

8.3.3 NIC (Network Interface Card) and MAC address

- The NIC (network adapter/LAN card) is the hardware that connects a host to the network medium. It frames data, computes the frame check sequence, performs media access (CSMA/CD for classic Ethernet), and does the parallel↔serial conversion onto the wire.
- Operates at the **Physical + Data Link layers (Layers 1–2)** of OSI.
- Every NIC has a globally unique **MAC address: 48 bits (6 bytes)**, written as 12 hex digits, e.g. `00:1A:2B:3C:4D:5E`. First 3 bytes = **OUI** (manufacturer ID assigned by IEEE); last 3 bytes = device serial. MAC address is **burned into ROM** (hence "physical/hardware/burned-in address"). Broadcast MAC = `FF:FF:FF:FF:FF:FF`.

8.3.4 Modem vs NIC — **2025 PYQ comparison table**

Point	Modem	NIC
Core job	**Signal conversion:** digital ↔ analog (modulation/demodulation) to use an analog channel (phone line/coax/RF)	**Network attachment:** physical + data-link interface of a host to a (digital) LAN
Typical use	Connects a computer/site to the **internet/WAN via the telephone or cable network**	Connects a computer to a **LAN (Ethernet/Wi-Fi)**
Conversion	Digital data → analog signal and back	Data → digital line-coded frames (no D/A of the modem type)
OSI position	Physical layer device (DCE)	Layers 1–2; owns the **MAC address**
Addressing	No host address of its own on the LAN	48-bit MAC address
Form	External/internal box between DTE and line	Card/chip on the motherboard

> **Exam answer:** "A modem converts digital signals to analog (and vice-versa) for transmission over telephone lines, whereas a NIC provides the physical interface between a computer and the network and has a unique MAC address." Both are needed in a home setup: NIC → router → modem → ISP.

8.4 Hardware and Interfaces

8.4.1 DTE and DCE

- **DTE (Data Terminal Equipment):** source/sink of digital data — computer, terminal, printer.
- **DCE (Data Circuit-terminating Equipment):** sits between DTE and the transmission line; converts/conditions signals — modem, NT1, CSU/DSU.
- Interface standards (RS-232 etc.) define the **DTE–DCE boundary**: mechanical (connector), electrical (voltage levels), functional (pin meanings) and procedural (handshake sequence) characteristics.

8.4.2 RS-232 (EIA-232) — the classic serial interface

Item	Detail
Type	**Asynchronous serial**, point-to-point, DTE↔DCE
Connector	DB-25 (original) / **DB-9** (common)
Logic levels	**Logic 1 (mark) = −3 to −15 V; Logic 0 (space) = +3 to +15 V** (negative logic — a favourite trick question)
Max cable length / speed	~15 m (50 ft) at 20 kbps nominal (practically 115.2 kbps short runs)
Mode	Full-duplex (separate TxD, RxD)
Key DB-9 pins	2 RxD, 3 TxD, 5 GND (signal ground), 7 RTS, 8 CTS, 4 DTR, 6 DSR, 1 DCD, 9 RI
Handshake	Hardware (RTS/CTS) or software (XON/XOFF)
Null modem	Cross-connected cable (TxD↔RxD) to link two DTEs directly

8.4.3 USB (Universal Serial Bus)

- Serial, hot-pluggable, plug-and-play; **tiered-star topology** with one host controller; up to **127 devices** per host; supplies power (5 V).
- Differential pair D+/D− (USB 2.0), NRZI encoding with bit stuffing.


Version	Speed	Marketing name
USB 1.1	1.5 Mbps (low) / 12 Mbps (full)	—
USB 2.0	**480 Mbps**	Hi-Speed
USB 3.0 / 3.1 Gen1	5 Gbps	SuperSpeed
USB 3.1 Gen2	10 Gbps	SuperSpeed+
USB4	20–40 Gbps	—

- Transfer types: control, bulk, interrupt, **isochronous** (guaranteed rate for audio/video).
- Connectors: Type-A, Type-B, Mini, Micro, reversible **Type-C**.

8.4.4 RJ-45 and Ethernet cabling basics

- **RJ-45**: 8-position 8-contact (8P8C) modular connector terminating 4 twisted pairs of UTP.
- Wiring standards **T568A** and **T568B** (differ only in swapping green and orange pairs).
- **Straight-through cable** (same standard both ends): PC → switch/hub (unlike devices).
- **Crossover cable** (T568A one end, T568B other): PC → PC, switch → switch (like devices) — largely obsolete because modern ports do **Auto-MDIX**.
- 10/100 Mbps Ethernet uses pins **1,2 (transmit)** and **3,6 (receive)**; Gigabit uses all 8 pins/4 pairs bidirectionally.
- RJ-11 (6P2C/6P4C) is the smaller **telephone** connector — don't confuse.

8.5 Networks: Types and Topologies

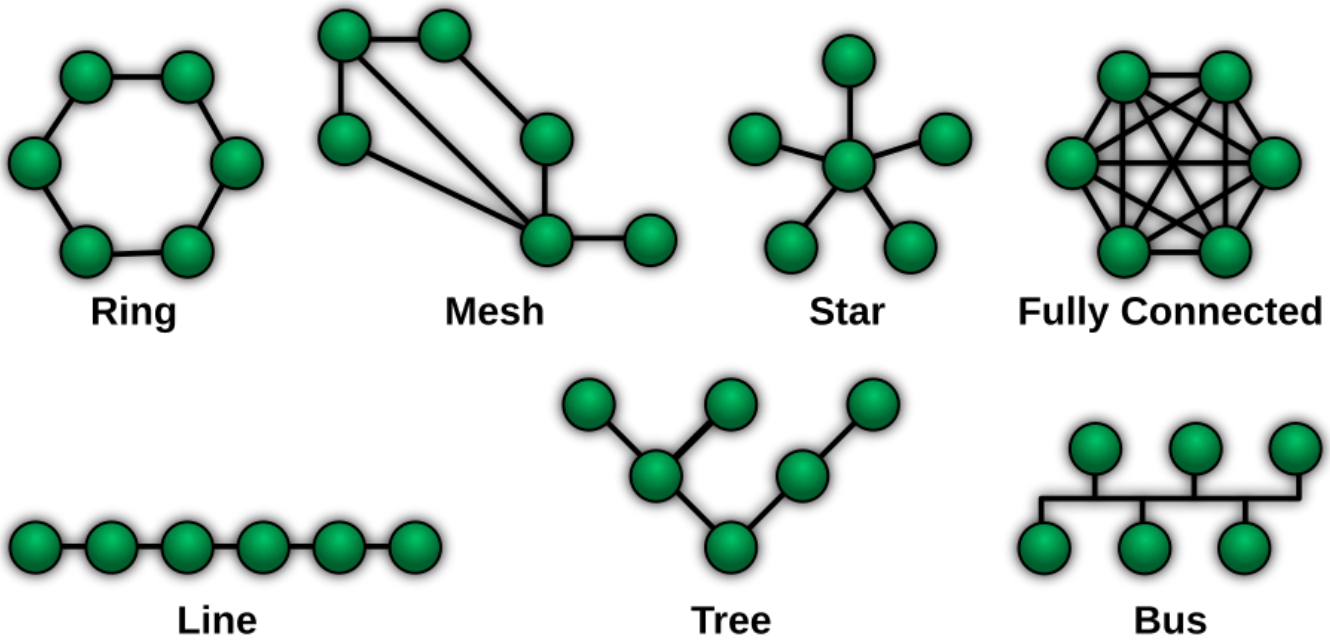

Bus, star, ring, mesh and tree topologies.

8.5.1 What is a network? Criteria

A **network** = a set of devices (nodes) connected by communication links to share resources (data, printers, internet). Key criteria: **performance** (throughput, delay), **reliability** (failure frequency, recovery time, robustness), **security**.

Connection types: point-to-point (dedicated link between two devices) vs **multipoint/broadcast** (link shared by many devices).

8.5.2 Network categories by geographic scale

Type	Full form	Span	Ownership	Examples
PAN	Personal Area Network	~10 m, around a person	Individual	Bluetooth, USB tether
LAN	Local Area Network	Room–building–campus (≤ a few km)	Single organisation (private)	Office Ethernet, home Wi-Fi
MAN	Metropolitan Area Network	A city (~5–50 km)	Single or multiple operators	Cable-TV network, city Wi-Fi/WiMAX
WAN	Wide Area Network	Country / world	Usually leased from carriers	Internet, bank branch network, leased lines

- LAN: **high speed (100 Mbps–10 Gbps), low error rate, cheap, privately owned**.
- WAN: lower speed per cost, higher delay, uses public/leased carrier infrastructure, connects LANs via **routers**.
- **Internetwork (internet, small i)** = two or more networks connected; **the Internet (capital I)** = the specific global internetwork.

8.5.3 Network topologies — **the biggest PYQ magnet in this unit**

Topology = the geometric layout of links and nodes.

Bus topology

- One **shared backbone cable**; every node taps on via drop lines; both ends terminated (terminators absorb signals to stop reflections).
- Cheapest cabling (least cable for small nets); used in legacy 10Base2/10Base5 Ethernet.
- **Node failure:** network keeps working (a dead station simply stops talking).
- **Backbone-cable failure/break: entire network goes down** (and reflections from the break disrupt both sides).
- Other cons: difficult fault isolation, collisions on the shared medium, hard to add nodes mid-run, degraded performance under heavy load.

Star topology

- Every node connects by a **dedicated point-to-point link to a central device** (hub/switch).
- Modern Ethernet LAN standard layout.
- **Node or single-cable failure: only that node is cut off — rest of network unaffected.** Easiest fault detection and isolation.
- **Central device (hub/switch) failure: whole network goes down — single point of failure.**
- More cable than bus (one run per node) but cheap installation & easy expansion.

Ring topology

- Each node connects to exactly **two neighbours**, forming a closed loop; data circulates (usually unidirectionally) node-to-node, each node **regenerating** the signal; access controlled by **token passing** → no collisions.
- **One node or one link failure breaks the ring — can disable the whole network** (unless a dual/counter-rotating ring, e.g. FDDI, provides wrap-around, or nodes are bypassed by relays).
- Adding/removing a node disturbs the whole ring. Predictable (deterministic) performance under load.

Mesh topology

- **Every node has a dedicated point-to-point link to every other node** (full mesh).
- Number of duplex links for n nodes: **$n(n-1)/2$**; each node needs **$n-1$ ports**.
- **Most robust/fault-tolerant: failure of any one link or node does NOT bring the network down — traffic reroutes** via alternative paths. Also most secure/private (dedicated links) and no traffic contention.
- **Most expensive** in cable and ports; installation/maintenance hardest. Used where reliability is paramount (backbones, military); *partial mesh* is the practical compromise.

Tree (hierarchical) topology

- **Star networks connected to a central bus/backbone** (star-bus hybrid); root hub → secondary hubs → nodes.
- Scalable, easy expansion & fault isolation per branch; **backbone failure splits the network**; root failure severs branches.

Hybrid topology

- Any combination (e.g. star-ring, star-bus) inheriting pros/cons of its parts; virtually all real large networks are hybrids.


Topology master comparison table ☆

Topology	Cable cost	Node failure effect	Cable/link failure effect	Central point of failure	Ease of expansion	Access method / notes
Bus	Lowest	Others unaffected	**Backbone break kills entire network**	Backbone itself	Poor	CSMA/CD; terminators needed
Star	Moderate	**Only that node lost**	Only that node lost	**Yes — hub/switch**	**Best**	Modern Ethernet; easiest troubleshooting
Ring	Moderate	**Can break whole ring**	**Breaks whole ring** (single ring)	No single centre, every node critical	Poor (disturbs ring)	Token passing; no collisions
Mesh	**Highest** — n(n−1)/2 links	**Network survives (reroutes)**	**Network survives**	**None**	Hard (n−1 new links per node)	Most reliable & secure
Tree	High	Branch above it affected	Backbone break partitions network	Root/backbone	Good	Hierarchical; DSL/cable-TV nets

> **2025 PYQ answer key:** star → one node failing does not affect others but hub failure kills all; bus → cable break kills all; ring → any single break kills all (single ring); mesh → survives individual failures.

8.6 Network Reference Models

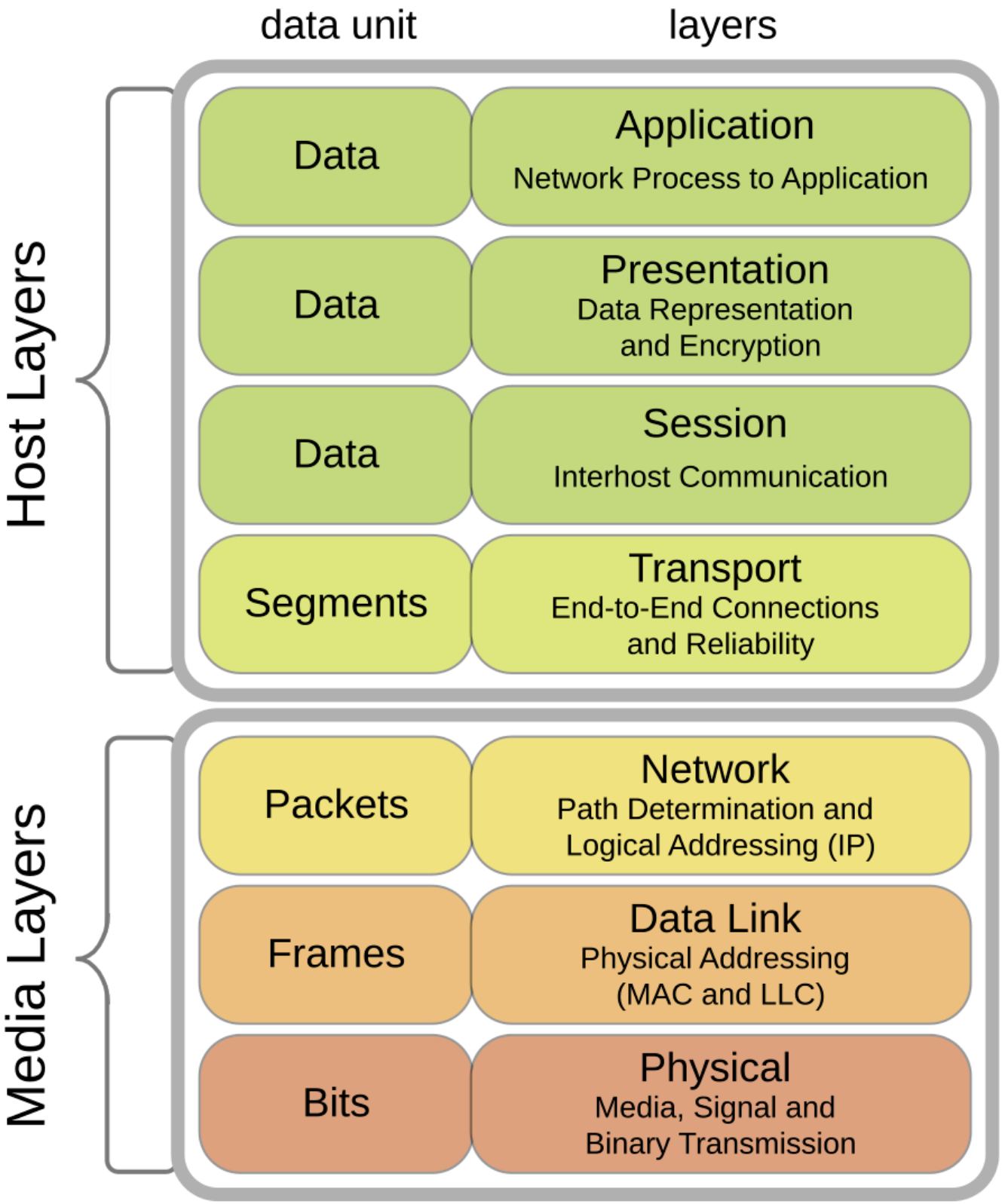8.6.1 OSI model (ISO — Open Systems Interconnection, 7 layers)



OSI seven-layer reference model.

Mnemonics: bottom-up "**P**lease **D**o **N**ot **T**hrow **S**ausage **P**izza **A**way"; top-down "**A**ll **P**eople **S**eem **T**o **N**eed **D**ata **P**rocessing".

#	Layer	Core functions	PDU name	Addressing	Typical devices/protocols
7	**Application**	Network services to user apps: file transfer, mail, remote login, directory	Data (message)	—	HTTP, FTP, SMTP, DNS, SNMP, Telnet
6	**Presentation**	Translation (syntax/EBCDIC↔ASCII), **encryption/decryption, compression**	Data	—	SSL/TLS (conceptually), JPEG, MPEG
5	**Session**	Dialog control (establish/maintain/terminate sessions), **synchronisation (checkpoints)**	Data	—	NetBIOS, RPC, sockets API
4	**Transport**	**Process-to-process (end-to-end) delivery**, segmentation & reassembly, connection control, end-to-end flow & error control	**Segment** (TCP) / Datagram (UDP)	**Port number**	TCP, UDP; (firewalls filter here)
3	**Network**	**Source-to-destination (host-to-host) delivery across networks: logical addressing & routing**	**Packet**	**IP address**	**Router**, L3 switch; IP, ICMP, ARP*, routing protocols
2	**Data Link**	**Node-to-node (hop-to-hop) delivery**: framing, physical (MAC) addressing, per-hop flow/error control (CRC), media access (MAC sublayer + LLC sublayer)	**Frame**	**MAC address**	**Switch, bridge, NIC**; Ethernet, HDLC, PPP
1	**Physical**	Transmit **raw bits**: media, connectors, voltages, bit rate, line encoding, topology, transmission mode	**Bit**	—	**Hub, repeater, cables, modem**

Key one-liners the exam loves:

- **Routing → Network layer. Framing & MAC address → Data Link. Port numbers & end-to-end reliability → Transport. Encryption/compression → Presentation. Dialog/synchronisation → Session.**

- Data Link = hop-to-hop; Network = host-to-host (source-to-destination); Transport = process-to-process.
- Encapsulation going down (each layer adds its header; Data Link also adds a trailer); decapsulation going up.

8.6.2 TCP/IP model and mapping

TCP/IP (4-layer, RFC view)	5-layer teaching model	Maps to OSI	Protocols
Application	Application	Application + Presentation + Session (5–7)	HTTP, FTP, SMTP, DNS, SNMP
Transport	Transport	Transport (4)	TCP, UDP, SCTP
Internet	Network	Network (3)	IP, ICMP, IGMP, ARP
Network Access (Host-to-Network / Link)	Data Link + Physical	Layers 1–2	Ethernet, Wi-Fi, PPP

OSI vs TCP/IP: OSI is a *prescriptive reference model* (protocol-independent, defined before its protocols); TCP/IP is a *descriptive, implemented* suite (protocols came first). OSI separates Presentation & Session; TCP/IP folds them into Application. The Internet runs on TCP/IP.

8.7 Networking Devices — which layer, which domain ⭐

Device	OSI layer	Function	Collision domains	Broadcast domains
Passive hub	— (below L1, just wiring)	Connection point only; **no regeneration**	one shared	one
Repeater	**1 – Physical**	**Regenerates** (not merely amplifies) the digital signal to extend segment length; 2 ports; cannot filter or connect different LAN types	Does **not** segment — one big collision domain	One
Active hub	**1 – Physical**	Multiport repeater; broadcasts every bit out of all ports; half-duplex	**One collision domain for all ports**	One
Bridge	**2 – Data Link**	Connects two LAN segments; **filters/forwards frames by MAC address** using a learned table; regenerates too	**Each port = separate collision domain**	One
Switch	**2 – Data Link** (L3 switches exist)	Multiport bridge; **MAC (CAM) table**; forwards a frame only to the destination port (unicast); full-duplex, dedicated bandwidth per port; methods: store-and-forward / cut-through	**Every port its own collision domain**	One (all ports, unless VLANs)
Router	**3 – Network**	Connects **different networks**; forwards **packets by IP address** using a routing table; chooses best path; **blocks broadcasts** by default; can join dissimilar link technologies	Each port separate	**Each port a separate broadcast domain**
Gateway	Up to **7 – Application** (protocol converter)	Connects networks using **entirely different protocol architectures**; translates protocols/data formats; "default gateway" in IP configs = the router to other networks	—	Separates
Access Point (AP)	2	Bridges wireless 802.11 stations to the wired LAN	Wireless is shared medium	One
Firewall	3–4 (packet filter) up to 7 (application/proxy)	Enforces security policy on traffic entering/leaving the network	—	—
Modem	1	Digital↔analog conversion for WAN	—	—

Device	OSI layer	Function	Collision domains	Broadcast domains
		access		
NIC	1–2	Host's network interface; MAC address	—	—

Hub vs Switch (asked repeatedly):

Point	Hub	Switch
Layer	Physical (1)	Data Link (2)
Forwarding	Broadcasts to **all** ports	Only to destination port (**MAC table**)
Collision domain	Single, shared	Per-port (collisions eliminated with full duplex)
Duplex / bandwidth	Half-duplex, shared bandwidth	Full-duplex, dedicated per port
Intelligence / security	None (dumb)	Learns addresses; better security & performance

Collision domain = set of devices whose simultaneous transmissions can collide (segmented by bridge/switch/router).

Broadcast domain = set of devices that receive each other's L2 broadcasts (segmented **only by a router** or VLANs).

8.8 LAN Technologies

8.8.1 Ethernet (IEEE 802.3)

Dominant LAN technology, invented at Xerox PARC (Metcalfe), standardised as **IEEE 802.3**.

Generation	Standard names	Speed	Media	Notes
Standard Ethernet	10Base5 (thick coax), 10Base2 (thin coax), **10Base-T** (UTP Cat3, star-hub), 10Base-F	**10 Mbps**	coax / UTP / fibre	Manchester encoding; CSMA/CD; half-duplex
Fast Ethernet (802.3u)	**100Base-TX** (2 pairs Cat5), 100Base-FX (fibre), 100Base-T4	**100 Mbps**	UTP/fibre	Auto-negotiation introduced
Gigabit Ethernet (802.3z/ab)	**1000Base-T** (4 pairs Cat5e), 1000Base-SX/LX (fibre)	**1 Gbps**	UTP/fibre	Full-duplex switching normal; CSMA/CD practically retired
10-Gigabit (802.3ae/an)	10GBase-T (Cat6a), -SR/-LR	10 Gbps	UTP/fibre	Full-duplex only — **no CSMA/CD at all**

Naming: `<speed>Base<medium>` — "Base" = baseband signalling; T = twisted pair, F/S/L = fibre; 5/2 = old coax max segment (500 m/185 m). Max UTP segment: **100 m**; max nodes per legacy segment rules ("5-4-3": 5 segments, 4 repeaters, 3 populated).

CSMA/CD (Carrier Sense Multiple Access with Collision Detection) — the access method of classic (half-duplex, shared) Ethernet:

1. **Carrier sense:** listen; transmit only if the medium is idle.
2. **Transmit and keep listening** while sending.
3. **Collision detected** (received ≠ sent / voltage anomaly): abort, send a **32-bit jam signal** so all stations notice.

4. **Back-off:** wait a random time chosen by **binary exponential back-off** (after nth collision pick a random slot from 0…2^n-1, cap n = 10, give up after 16 attempts), then retry.

- Constraint: minimum frame length must outlast twice the end-to-end propagation delay (**slot time**) so the sender is still transmitting when a far-end collision returns → Ethernet **minimum frame = 64 bytes**; frames shorter are padded; a fragment < 64 B is a collision "runt".
- Wireless uses **CSMA/CA (Collision Avoidance)** instead, because a radio cannot transmit and listen for its own collision simultaneously (and due to the hidden-station problem).

Ethernet (802.3) frame basics:

Field	Size
Preamble (7 B, 10101010…) + SFD (1 B, 10101011)	8 B (physical-layer added)
Destination MAC	6 B
Source MAC	6 B
Length/Type	2 B
Data + pad	**46 – 1500 B** (1500 = max payload, MTU)
FCS — CRC-32	4 B
Frame size (excl. preamble)	**64 – 1518 B**

8.8.2 Wi-Fi — IEEE 802.11 family ☆

Wireless LAN; access method **CSMA/CA**; infrastructure mode (via AP, forming a BSS/ESS) or ad-hoc (IBSS); network name = **SSID**; security: WEP (broken) → WPA → **WPA2 (AES-CCMP)** → WPA3.

Standard	Year	Band	Max PHY rate	Note
802.11a	1999	**5 GHz**	54 Mbps	OFDM
802.11b	1999	**2.4 GHz**	11 Mbps	DSSS; longest-lived legacy
802.11g	2003	2.4 GHz	54 Mbps	OFDM, b-compatible
802.11n (Wi-Fi 4)	2009	2.4 & 5 GHz	600 Mbps	**MIMO**, 40 MHz channels
802.11ac (Wi-Fi 5)	2013	5 GHz	~6.9 Gbps	MU-MIMO, 160 MHz, 256-QAM
802.11ax (Wi-Fi 6/6E)	2019	2.4/5 (+6 GHz for 6E)	~9.6 Gbps	OFDMA, 1024-QAM, high density

Related IEEE 802 standards: **802.3 Ethernet, 802.11 WLAN, 802.15 Bluetooth/WPAN, 802.16 WiMAX**, 802.1Q VLAN tagging, 802.1D spanning tree.

8.8.3 Token Ring (IEEE 802.5) — one paragraph

IBM's LAN standard (4/16 Mbps): stations form a logical ring (physically often a star through a MAU — Multistation Access Unit); a small frame called the **token** circulates, and only the station **holding the token may transmit**, so collisions are impossible and access is **deterministic** (bounded worst-case wait — good for real-time/industrial loads). The frame travels around the ring, is copied by the destination, and is removed by the sender, which then releases the token. Uses differential Manchester encoding. FDDI extended the idea to a 100 Mbps dual counter-rotating fibre ring (self-healing on a single break). Both are now obsolete, displaced by switched Ethernet, but token passing remains a favourite exam contrast to CSMA/CD.

8.9 WAN Technologies

8.9.1 Switching techniques

Circuit switching

- A **dedicated physical path** is established end-to-end **before** data flows (setup phase), held for the whole session, then released (teardown).
- Fixed bandwidth reserved whether used or not → inefficient for bursty data, but **no congestion once connected, constant delay, guaranteed rate** — ideal for voice.
- Example: **PSTN telephone network**. Three phases: setup → data transfer → teardown.

Packet switching

- Message broken into **packets**, each carrying addressing; links shared by many flows (**statistical multiplexing**); **store-and-forward** at each node.
- Efficient for bursty computer data; per-packet delays vary (queuing), congestion possible.
- Two flavours:

Feature	Datagram approach	Virtual circuit approach
Setup	None — each packet routed **independently**	Logical path (VC) set up first; all packets follow it
Header carries	**Full destination address**	Short **VC identifier (label)**
Ordering	Packets may arrive **out of order**, may take different routes	**In-order** delivery along fixed path
On node failure	Later packets route around	VC broken; must be re-established
Analogy / examples	Postal letters; **IP, UDP**	Phone-call-like; **X.25, Frame Relay, ATM, MPLS LSPs**

(Message switching = store-and-forward of whole messages — historical telegraph, high storage/delay.)

8.9.2 WAN access technologies — one-liners

Technology	One-liner
PSTN / dial-up	Public Switched Telephone Network; analog local loop + modem; ≤ 56 kbps; circuit-switched
ISDN	Integrated Services Digital Network — end-to-end **digital** telephony; **BRI = 2B + D** (2×64 kbps bearer + 16 kbps signalling = 144 kbps), **PRI = 30B + D** (E1, India/Europe) or 23B + D (T1)
Leased line	Dedicated point-to-point circuit rented from carrier, fixed bandwidth 24×7 (64 kbps…E1 = 2.048 Mbps, T1 = 1.544 Mbps…); secure, costly
DSL / ADSL	Digital data on existing telephone copper above the voice band; **A**symmetric = downstream ≫ upstream; splitter/filter separates voice
Frame Relay	Packet-switched virtual-circuit WAN service (successor of X.25, less error checking, faster); PVCs identified by DLCI
ATM	Asynchronous Transfer Mode — fixed **53-byte cells (48 data + 5 header)**, virtual circuits, QoS classes; once the B-ISDN backbone
MPLS	Multi-Protocol Label Switching — routers forward by short **labels** instead of IP lookup along Label-Switched Paths; "layer 2.5"; backbone of modern carrier VPNs & traffic engineering
SONET/SDH	Optical carrier TDM hierarchy for long-haul trunks (STM-1 = 155.52 Mbps)

8.10 Internetworking and the TCP/IP Suite

Internetworking = connecting multiple, possibly heterogeneous networks with **routers/gateways** so they function as one logical network. The glue is the **Internet Protocol (IP)**: every host gets a logical IP address, and routers forward packets between networks using routing tables (protocols: RIP — hop-count distance vector; OSPF — link state; BGP — inter-AS path vector).

8.10.1 IPv4 addressing

- **32-bit** logical address, written in **dotted decimal**: four octets 0–255, e.g. `192.168.10.5`.
- Total address space = 2^{32} ≈ 4.29 billion.
- Two parts: **Network ID + Host ID** (boundary set by class or by subnet mask/CIDR).

Classful addressing (identify class by the FIRST octet):

Class	First bits	First-octet range	Default mask	Net/Host octets	Networks × hosts	Use
A	0	**1 – 126**	255.0.0.0 (/8)	N.H.H.H	126 nets × 16,777,214 hosts	Very large orgs
B	10	**128 – 191**	255.255.0.0 (/16)	N.N.H.H	16,384 × 65,534	Large orgs
C	110	**192 – 223**	255.255.255.0 (/24)	N.N.N.H	2,097,152 × **254**	Small networks
D	1110	**224 – 239**	—	—	—	**Multicast**
E	1111	**240 – 255**	—	—	—	**Experimental/reserved**

Special addresses:

- **127.x.x.x — loopback** (`127.0.0.1` = localhost); that's why 127 is missing from Class A's usable range.
- Host bits all 0 = **network address**; host bits all 1 = **directed broadcast**; `255.255.255.255` = limited broadcast; `0.0.0.0` = "this host/any".
- Hosts per subnet = 2^(host bits) − 2 (network & broadcast reserved).

Private address ranges (RFC 1918) — not routable on the public Internet; used with NAT:

Class	Range	CIDR
A	10.0.0.0 – 10.255.255.255	10.0.0.0/8
B	172.16.0.0 – 172.31.255.255	172.16.0.0/12
C	192.168.0.0 – 192.168.255.255	192.168.0.0/16

(APIPA/link-local self-assigned range: 169.254.0.0/16 — appears when DHCP fails.)

8.10.2 Subnet mask, subnetting and CIDR

- **Subnet mask**: 32-bit pattern — 1s over the network+subnet part, 0s over the host part. `IP AND mask = network address`.
- **CIDR notation** `/n` = number of leading 1-bits: /24 ↔ 255.255.255.0, **/26 ↔ 255.255.255.192**, /30 ↔ 255.255.255.252.
- **Subnetting** borrows host bits to create subnets: borrowing s bits → **2^s subnets**, each with **2^(host bits remaining) − 2** hosts.
- **Block size trick:** block size = 256 − (mask's interesting octet); subnet boundaries step by the block size. E.g. mask .192 → block 64 → subnets start at 0, 64, 128, 192.
- CIDR (classless) also allows **supernetting/route aggregation** (e.g. combining four /24s into one /22).

(Worked Examples 4–7 below.)

8.10.3 IPv6 basics

Item	Detail
Address size	**128 bits** → $2^{128} \approx 3.4\times10^{38}$ addresses
Notation	Eight groups of 4 hex digits separated by colons: `2001:0db8:0000:0000:0000:ff00:0042:8329` ; leading zeros droppable; one run of zero groups → `::` (once only): `2001:db8::ff00:42:8329`
Loopback	`::1`
Header	Fixed **40 bytes**, simpler than IPv4's; extension headers chained
Removed from IPv4	Header checksum, router fragmentation, broadcast (replaced by multicast + **anycast**)
Built-in features	Auto-configuration (SLAAC), IPsec support, better QoS (flow label)
Transition	Dual stack, tunnelling (6to4), translation (NAT64)

8.10.4 TCP vs UDP ⭐

Feature	TCP (Transmission Control Protocol)	UDP (User Datagram Protocol)
Connection	**Connection-oriented** (3-way handshake before data)	**Connectionless** (just send)
Reliability	Reliable — ACKs, retransmission, checksums	Unreliable, best-effort (checksum optional-ish)
Ordering	In-order delivery (sequence numbers)	No ordering guarantee
Flow / congestion control	Yes (sliding window / AIMD)	None
Speed / overhead	Slower; header **20–60 B**	Faster; header **8 B** (src port, dst port, length, checksum)
Data unit	Segment (byte-stream service)	Datagram (message service)
Used by	HTTP/HTTPS, FTP, SMTP, Telnet, SSH	DNS queries, DHCP, SNMP, TFTP, VoIP/streaming

TCP three-way handshake (connection establishment):

1. Client → Server: **SYN** (seq = x)
2. Server → Client: **SYN + ACK** (seq = y, ack = x+1)
3. Client → Server: **ACK** (ack = y+1) — connection established; data may flow.

Termination uses FIN/ACK exchanges (four-way). TCP header flags to know: SYN, ACK, FIN, RST, PSH, URG.

8.10.5 Port numbers ⭐ (memorise cold — direct one-mark questions)

Port = 16-bit number (0–65535) identifying a **process/application** on a host. Ranges: **well-known 0–1023**, registered 1024–49151, dynamic/ephemeral 49152–65535. Socket = IP address + port.

Protocol	Port	Transport	Purpose
FTP data / control	**20 / 21**	TCP	File transfer
SSH	**22**	TCP	Secure remote login
Telnet	**23**	TCP	Remote login (plaintext)
SMTP	**25**	TCP	Sending e-mail
DNS	**53**	UDP (TCP for zone transfer)	Name resolution
DHCP	**67 (server) / 68 (client)**	UDP	Auto IP configuration
TFTP	69	UDP	Trivial file transfer
HTTP	**80**	TCP	Web
POP3	**110**	TCP	Mail retrieval (download-and-delete)
NTP	123	UDP	Time sync
IMAP	**143**	TCP	Mail retrieval (server-side folders/sync)
SNMP agent / manager (trap)	**161 / 162**	UDP	Network management
HTTPS	**443**	TCP	Secure web (TLS)
RDP	3389	TCP	Remote desktop

8.10.6 Support protocols of the TCP/IP suite

Protocol	Layer	Function
ARP (Address Resolution Protocol)	between L2/L3	**IP address → MAC address**: sender broadcasts "who has IP x?"; owner replies with its MAC; result cached in ARP table
RARP	"	**MAC → IP** for diskless stations (obsolete; replaced by BOOTP → **DHCP**)
ICMP (Internet Control Message Protocol)	3	Error reporting & diagnostics for IP: destination unreachable, time exceeded (TTL=0), redirect, **echo request/reply — used by** `ping` ; `traceroute` exploits TTL-expiry messages
IGMP	3	Hosts join/leave multicast groups
DHCP	Application (UDP 67/68)	Dynamically leases IP address, mask, gateway, DNS to clients; **DORA** sequence: **D**iscover → **O**ffer → **R**equest → **A**cknowledge
DNS	Application (53)	**Domain name → IP address** (and reverse); distributed hierarchical database: root → TLD (.com/.in) → authoritative servers; record types A (IPv4), AAAA (IPv6), MX (mail), CNAME (alias)

8.10.7 Application-layer protocols

Protocol	Port	One-liner
HTTP	80	HyperText Transfer Protocol — web request/response (GET, POST…); **stateless**
HTTPS	443	HTTP over **TLS/SSL** — encrypted + server authenticated (padlock)
FTP	21 control + 20 data	File transfer using **two separate TCP connections** (control & data); active/passive modes; secure variants SFTP (over SSH), FTPS
SMTP	25	Simple Mail Transfer Protocol — **sending/relaying** mail (client→server, server→server); a **push** protocol
POP3	110	Post Office Protocol v3 — **downloads** mail to one device, typically deletes from server; simple
IMAP	143	Internet Message Access Protocol — mail stays **on the server**, folders synchronised across devices; more capable than POP3
Telnet	23	Remote terminal login — **everything in plaintext** including passwords → insecure
SSH	22	Secure Shell — **encrypted** remote login, command execution, tunnelling, SFTP/SCP; replaces Telnet

8.10.8 SNMP — Simple Network Management Protocol ⭐ (2025 PYQ)

Framework for **managing and monitoring devices** (routers, switches, servers, printers) on an IP network. Application-layer protocol running over **UDP: agent listens on port 161, manager receives traps on port 162**.

Model — Manager / Agent / MIB:

Element	Role
Manager (NMS)	Central management station software; polls agents, receives alarms, presents network status
Agent	Software on each managed device; maintains local management data and answers the manager
MIB (Management Information Base)	The hierarchical **database of managed objects/variables** on the agent (interfaces, counters, uptime…), each identified by an **OID**; structure defined by SMI (uses ASN.1)

Message types (direction matters — the exam point):

Message	Direction	Purpose
GetRequest (GET)	**Manager → Agent**	Read the value of a MIB variable
GetNextRequest	Manager → Agent	Read the next variable (walk the MIB tree)
GetBulkRequest (v2+)	Manager → Agent	Read large blocks efficiently
SetRequest (SET)	**Manager → Agent**	**Write/modify** a variable — i.e. configure/control the device
GetResponse (Response)	**Agent → Manager**	Reply carrying requested values / confirmation
Trap	**Agent → Manager**	**Unsolicited alert** on an event (link down, reboot, threshold crossed) — agent-initiated, no polling
Inform (v2+)	Manager/agent → manager	Acknowledged trap

> **PYQ takeaway:** *The manager issues GET (read) and SET (write) requests to the agent; the agent answers with Response and can asynchronously send TRAPs to the manager.* Any option saying the *agent* sends GET/SET to the manager, or that the manager sends traps, is wrong.

Versions: SNMP**v1** (basic, community-string "security"), SNMP**v2c** (adds GetBulk/Inform, better error handling, still community strings), SNMP**v3** (adds real **security: authentication, encryption/privacy, and access control**).

8.10.9 Internet concepts

Term	Meaning
Internet	Global public network of interconnected networks running TCP/IP
WWW	World Wide Web — the system of interlinked hypertext documents *on* the Internet (invented by **Tim Berners-Lee, 1989, CERN**); Web ≠ Internet — the Web is one service on it
URL	Uniform Resource Locator — address of a resource: `protocol://host[:port]/path?query` e.g. `https://www.rrb.gov.in:443/results/list.html`; parts = scheme, domain (host), optional port, path
ISP	Internet Service Provider — organisation providing Internet access (BSNL, Jio, Airtel); tiers 1/2/3
Browser / web server	Client that renders pages (Chrome/Firefox) / program serving them (Apache, Nginx, IIS)
Intranet	An organisation's **private** internal network using Internet technologies (TCP/IP, web) — accessible to members only
Extranet	Controlled extension of an intranet to **selected outsiders** (partners, vendors, customers) — "partly private"
VPN	Virtual Private Network — a **secure encrypted tunnel** over the public Internet linking remote users/sites to the private network as if locally connected; protocols: IPsec, SSL/TLS VPN, L2TP, (old) PPTP; gives confidentiality + site-to-site or remote-access connectivity cheaply vs leased lines
NAT	Network Address Translation — router rewrites **private** source IPs (RFC 1918) to its one **public** IP on the way out and maps replies back (PAT/NAPT uses port numbers to multiplex many hosts on one public address); conserves IPv4 addresses and hides internal topology

---

8.11 Network Security (one page)

Goals — the CIA triad: Confidentiality (only authorised eyes), **I**ntegrity (no undetected alteration), **A**vailability (services up when needed); plus **authentication** (prove identity) and **non-repudiation** (sender can't deny sending — via digital signatures).

Firewalls — device/software enforcing an access policy between a trusted network and the outside:

Type	Works at	Idea
Packet-filtering	L3/L4	Permit/deny by source/dest IP, port, protocol — ACL rules; fast, stateless
Stateful inspection	L3/L4 + state	Tracks connections; allows only replies to legitimate outbound sessions
Application-level gateway (proxy)	L7	Understands the application protocol (HTTP, FTP); can filter content; terminates and re-originates connections
Circuit-level gateway	L5	Validates TCP handshakes/sessions (e.g. SOCKS)
DMZ	—	A buffer subnet between two firewalls hosting public-facing servers (web, mail)

Encryption:

- **Symmetric (secret-key):** the **same key** encrypts and decrypts — fast, suited to bulk data; problem = securely sharing the key. Algorithms: **DES (56-bit, broken), 3DES, AES (128/192/256 — current standard)**, RC4.
- **Asymmetric (public-key):** a mathematically linked **key pair** — encrypt with the receiver's **public** key, only the receiver's **private** key decrypts; also enables **digital signatures** (sign with private, verify with public). Algorithms: **RSA**, Diffie–Hellman (key exchange), ECC. Slower, so real systems (TLS/HTTPS) use asymmetric crypto to exchange a symmetric session key, then symmetric crypto for the data. **Hash functions** (MD5 — broken, SHA-256) provide integrity fingerprints.

Common threats (one-liners): Virus (attaches to files, needs host program), **worm** (self-replicates across the network on its own), **Trojan horse** (malicious code disguised as useful software), **spyware/keylogger**, **ransomware** (encrypts data for ransom), **phishing** (fraudulent mails/sites stealing credentials), **spoofing** (forged identity — IP/MAC/e-mail), **man-in-the-middle** (attacker secretly relays/alters traffic), **DoS/DDoS** (flooding a service to exhaust resources), **SQL injection** (malicious queries via input fields), **eavesdropping/sniffing** (packet capture on the medium). Defences: firewall + IDS/IPS, antivirus, patching, strong passwords/2-FA, encryption, backups.

8.12 Worked Examples (8)

Example 1 — Nyquist capacity.

A noiseless channel has a bandwidth of 3000 Hz and transmits a signal with 4 levels. Find the maximum bit rate. What if 8 levels are used?

$C = 2\,B \log_2 L = 2 \times 3000 \times \log_2 4 = 6000 \times 2 =$ **12,000 bps**.

With $L = 8$: $C = 2 \times 3000 \times 3 =$ **18,000 bps**. (Each extra bit per level adds $2B = 6000$ bps.)

Example 2 — Shannon capacity (telephone line).

A telephone channel has bandwidth 3000 Hz (300–3300 Hz) and SNR = 3162. Find the channel capacity. Also express the SNR in dB.

$C = B \log_2(1 + \text{SNR}) = 3000 \times \log_2(3163) \approx 3000 \times 11.63 \approx$ **34,880 bps** (~34.9 kbps — the theoretical basis of the ~33.6 kbps analog modem limit).

$\text{SNR}_{dB} = 10 \log_{10} 3162 \approx 10 \times 3.5 =$ **35 dB**.

Example 3 — Shannon then Nyquist (combined design).

A channel has B = 1 MHz and SNR = 63. (a) Find the upper limit on data rate. (b) If we operate at 4 Mbps, how many signal levels are needed?

(a) $C = 10^6 \times \log_2(1 + 63) = 10^6 \times \log_2 64 = 10^6 \times 6 =$ **6 Mbps**.

(b) Nyquist: $4\times10^6 = 2 \times 10^6 \times \log_2 L \rightarrow \log_2 L = 2 \rightarrow$ **L = 4 levels**. (4 Mbps < 6 Mbps, so achievable.)

Example 4 — Address class identification.

Identify the class of: (i) 10.34.2.1 (ii) 130.45.6.7 (iii) 200.11.5.9 (iv) 229.1.1.1 (v) 248.0.0.1.

Look at the first octet: (i) 10 ∈ 1–126 → **Class A (also a private address)**; (ii) 130 ∈ 128–191 → **Class B**; (iii) 200 ∈ 192–223 → **Class C**; (iv) 229 ∈ 224–239 → **Class D (multicast)**; (v) 248 ∈ 240–255 → **Class E (experimental)**.

Example 5 — Network address and host count.

A host has IP 192.168.10.77 with subnet mask 255.255.255.0. Find the network address, broadcast address, and number of usable hosts.

Mask /24 → network = first three octets: **192.168.10.0**. Broadcast = host bits all 1: **192.168.10.255**. Host bits = 8 → usable hosts = $2^8 - 2 =$ **254** (range 192.168.10.1 – .254).

Example 6 — Subnetting a Class C network.

Divide 192.168.1.0/24 into subnets that support at least 50 hosts each. Give the mask, number of subnets, and the subnet address of host 192.168.1.130.

Need ≥ 50 hosts → host bits h with $2^h - 2 \geq 50 \rightarrow h = 6$ (62 hosts). So mask = 32 − 6 = **/26 = 255.255.255.192**. Borrowed bits = 2 → **4 subnets**, block size 256 − 192 = 64: subnets **.0, .64, .128, .192**.

130 lies in 128–191 → host 192.168.1.130 is in subnet **192.168.1.128/26** (broadcast 192.168.1.191, usable .129–.190).

Example 7 — CIDR block reading.

For 172.16.40.20/12: state the mask in dotted decimal and the number of addresses in the block.

/12 → 12 ones: 255.240.0.0 (**255.11110000.0.0**). Host bits = 32 − 12 = 20 → addresses = $2^{20} =$ **1,048,576** (usable hosts $2^{20} - 2 =$ 1,048,574). Note 172.16.0.0/12 is exactly the RFC 1918 private Class-B block (172.16.0.0 – 172.31.255.255).

Example 8 — Bit rate vs baud rate.

A modem uses 8-PSK (8 phase states) and signals at 1600 baud. Find the bit rate. Conversely, what baud rate carries 72,000 bps using 64-QAM?

8-PSK → $\log_2 8 = 3$ bits/symbol → bit rate = 1600 × 3 = **4800 bps**.

64-QAM → 6 bits/symbol → baud = 72,000 / 6 = **12,000 baud**.

8.13 PYQ Corner — actual 22-04-2025 CBT-2 questions, solved

PYQ 1. Which of the following statements correctly differentiates a modem from a Network Interface Card (NIC)?

(a) A NIC converts digital signals to analog for transmission over telephone lines, while a modem connects a computer to the LAN

(b) **A modem converts digital signals to analog (and analog back to digital) for transmission over telephone lines, while a NIC provides the interface that connects a computer to a network and carries a unique MAC address**

(c) Both perform identical functions and are interchangeable

(d) A modem operates at the data-link layer while a NIC operates at the application layer

Answer: (b). The modem's defining job is signal conversion (MOdulation–DEModulation) so digital data can ride an analog channel; the NIC is the host's Layer-1/2 network attachment hardware with its burned-in 48-bit MAC address. (a) swaps the roles; (c) is plainly wrong; (d) misplaces both layers. *(See table §8.3.4.)*

PYQ 2. Which statement about twisted-pair cables is INCORRECT?

(a) STP contains a metal shield around the pairs that reduces electromagnetic interference

(b) UTP is cheaper and easier to install than STP

(c) **UTP offers higher resistance to electromagnetic interference than STP**

(d) Twisting of the wires helps cancel externally induced noise

Answer: (c) — this is the false statement. The grounded metallic shield of **STP** is precisely what gives it **better** EMI immunity; UTP relies on twisting alone, so its EMI resistance is *lower*. Statements (a), (b), (d) are all true. RRB framed this as "choose the incorrect statement," so the option praising UTP's EMI resistance is the answer. *(See §8.2.1.)*

PYQ 3. In which network topology does the failure of the central device bring down the entire network, while the failure of any single node leaves the rest of the network unaffected?

(a) Bus (b) Ring (c) Mesh (d) **Star**

Answer: (d) Star. In star topology each node has its own dedicated link to a central hub/switch: a node or its cable failing isolates only that node, but the central device is a single point of failure. Contrast: **bus** — backbone break kills all; **ring** — any single node/link break can stop the whole (single) ring; **mesh** — survives individual failures because traffic reroutes over alternative links. *(Master table §8.5.3.)*

PYQ 4. In the SNMP framework, which statement about manager–agent communication is CORRECT?

(a) The agent sends GET and SET requests to the manager to retrieve configuration data

(b) **The manager sends GET requests to read MIB variables from the agent and SET requests to modify them; the agent replies with responses and can send unsolicited TRAP messages to the manager**

(c) TRAP messages are sent by the manager to the agent to poll device status

(d) The MIB is maintained by the manager, and agents query it using GetNext

Answer: (b). SNMP direction rules: **GET/GetNext/GetBulk/SET flow manager → agent** (read/write of MIB objects); **Response and TRAP flow agent → manager** (Trap = asynchronous, event-driven alert, no request needed). The **MIB resides on the agent** (managed device), not the manager. Ports: agent 161, manager trap listener 162, over UDP. *(See §8.10.8.)*

8.14 Practice MCQs (25)

Q1. The transmission mode in which data flows in both directions but only one direction at a time is

(a) simplex (b) half-duplex (c) full-duplex (d) multiplex

Q2. In asynchronous serial transmission, each character is framed by

(a) a preamble and CRC (b) a start bit and stop bit(s) (c) sync bytes only (d) flag bytes 01111110

Q3. A signal uses 16 levels (16-QAM) at 3000 baud. The bit rate is

(a) 3000 bps (b) 6000 bps (c) 12,000 bps (d) 48,000 bps

Q4. The maximum data rate of a noiseless 4 kHz channel using binary (2-level) signalling is

(a) 4 kbps (b) 8 kbps (c) 16 kbps (d) 2 kbps

Q5. A channel of bandwidth 20 kHz has SNR = 1023. Its Shannon capacity is

(a) 100 kbps (b) 200 kbps (c) 20 kbps (d) 400 kbps

Q6. Which cable category supports 1 Gbps Ethernet over 100 m at 100 MHz bandwidth?

(a) Cat 3 (b) Cat 5e (c) Cat 7 only (d) RG-58

Q7. Optical fibre guides light by the principle of

(a) refraction through the cladding (b) total internal reflection (c) diffraction (d) polarisation

Q8. Which transmission medium is completely immune to electromagnetic interference?

(a) UTP (b) STP (c) coaxial cable (d) optical fibre

Q9. In Manchester encoding, the transition in the middle of each bit interval provides

(a) error correction (b) compression (c) self-clocking/synchronisation (d) encryption

Q10. The 48-bit MAC address of a NIC — the first three bytes represent

(a) the host serial number (b) the OUI (manufacturer ID) (c) the IP network (d) the port number

Q11. The RS-232 standard represents logic 1 by a voltage of

(a) +3 to +15 V (b) 0 V (c) −3 to −15 V (d) +5 V

Q12. A full mesh network of 10 nodes requires how many duplex links?

(a) 10 (b) 20 (c) 45 (d) 90

Q13. In which topology does a break anywhere in the single shared backbone cable stop all communication?

(a) star (b) bus (c) mesh (d) tree

Q14. Which OSI layer is responsible for routing and logical (IP) addressing?

(a) data link (b) transport (c) network (d) session

Q15. The PDU at the data-link layer is called a

(a) segment (b) packet (c) frame (d) bit

Q16. Encryption and data compression are functions of which OSI layer?

(a) session (b) presentation (c) application (d) transport

Q17. A switch differs from a hub mainly because a switch

(a) works at the physical layer (b) broadcasts every frame to all ports (c) forwards frames only to the destination port using a MAC table (d) converts digital signals to analog

Q18. Which device separates broadcast domains by default?

(a) repeater (b) switch (c) bridge (d) router

Q19. In CSMA/CD, after detecting a collision a station transmits a

(a) token (b) beacon (c) jam signal (d) preamble

Q20. The minimum Ethernet frame length (excluding preamble) is

(a) 46 bytes (b) 64 bytes (c) 128 bytes (d) 1518 bytes

Q21. IEEE 802.11n differs from 802.11g chiefly by introducing

(a) infrared links (b) MIMO and operation in both 2.4 and 5 GHz (c) token passing (d) 53-byte cells

Q22. The IP address 172.20.5.9 belongs to

(a) Class A public (b) Class B private range (c) Class C private range (d) Class D multicast

Q23. The subnet mask 255.255.255.240 in CIDR notation is /28. The number of usable hosts per subnet is

(a) 16 (b) 14 (c) 30 (d) 12

Q24. Which sequence is the correct TCP three-way handshake?

(a) ACK, SYN, SYN-ACK (b) SYN, SYN-ACK, ACK (c) SYN, ACK, FIN (d) FIN, ACK, SYN

Q25. Default port numbers of HTTPS, DNS and SMTP respectively are

(a) 80, 25, 53 (b) 443, 53, 25 (c) 443, 25, 110 (d) 22, 53, 25

Answer key with brief explanations

Q	Ans	Reason
1	b	Half-duplex = both directions, one at a time (walkie-talkie)
2	b	Async framing = start bit (0) + data + stop bit(s) (1)
3	c	16 levels → 4 bits/symbol; 3000 × 4 = 12,000 bps
4	b	Nyquist: $2 \times 4000 \times \log_2 2 = 8000$ bps
5	b	$C = 20k \times \log_2 1024 = 20k \times 10 = 200$ kbps
6	b	Cat 5e: 1 Gbps at 100 MHz (Cat 7 also does but 600 MHz/shielded — "only" makes c wrong)
7	b	Core n > cladding n → total internal reflection
8	d	Fibre carries light — no electrical pickup at all
9	c	Guaranteed mid-bit transition = embedded clock
10	b	First 3 bytes = IEEE-assigned OUI; last 3 = device serial
11	c	RS-232 is negative logic: mark (1) = −3…−15 V
12	c	$n(n-1)/2 = 10 \times 9/2 = 45$
13	b	Bus backbone is the single shared path; break kills the LAN
14	c	Network layer = logical addressing + routing
15	c	Bits→(L2) frames→(L3) packets→(L4) segments
16	b	Presentation = translation, encryption, compression
17	c	Switch learns MACs (CAM table) and unicasts frames
18	d	Bridges/switches split collision domains; only a router (or VLAN) splits broadcast domains
19	c	32-bit jam signal ensures every station sees the collision
20	b	64 B minimum (slot-time requirement); payload padded to ≥ 46 B
21	b	802.11n = Wi-Fi 4: MIMO, 40 MHz channels, dual-band, up to 600 Mbps
22	b	172.16.0.0–172.31.255.255 is the Class-B private (RFC 1918) block; 172.20 falls inside
23	b	/28 → 4 host bits → $2^4 - 2 = 14$ usable

Q	Ans	Reason
24	b	SYN → SYN+ACK → ACK
25	b	HTTPS 443, DNS 53, SMTP 25

8.15 Rapid-Revision Sheet

OSI at a glance

L	Layer	Keyword	PDU	Address	Device
7	Application	User services	Data	—	Gateway/firewall(L7)
6	Presentation	Translate, **encrypt, compress**	Data	—	—
5	Session	Dialog, **checkpoints**	Data	—	—
4	Transport	**Process-to-process**, TCP/UDP	Segment	**Port**	Firewall (L4)
3	Network	**Routing**, host-to-host	Packet	**IP**	**Router**
2	Data Link	Framing, hop-to-hop, CRC	Frame	**MAC**	**Switch, bridge, NIC**
1	Physical	Raw bits, media	Bit	—	**Hub, repeater, modem, cables**

Mnemonic (bottom-up): **P**lease **D**o **N**ot **T**hrow **S**ausage **P**izza **A**way.

Port numbers (cold-memory list)

FTP **20/21** · SSH **22** · Telnet **23** · SMTP **25** · DNS **53** · DHCP **67/68** · TFTP 69 · HTTP **80** · POP3 **110** · NTP 123 · IMAP **143** · **SNMP 161/162** · HTTPS **443** · RDP 3389.

Cable categories

Cat3 = 10 Mbps · **Cat5e = 1 Gbps/100 MHz** · **Cat6 = 1 G (10 G @55 m)/250 MHz** · Cat6a = 10 G/500 MHz · **Cat7 = 10 G/600 MHz, shielded** · UTP segment max **100 m** · connector **RJ-45** · **STP beats UTP on EMI; UTP wins on cost/ease**.

Device vs layer

Hub/repeater/modem → **L1** · NIC → L1–2 · bridge/switch/AP → **L2** · router → **L3** · gateway → up to **L7** · switch splits **collision** domains · router splits **broadcast** domains.

Topology snapshot

	Bus	Star	Ring	Mesh
Cable cost	least	medium	medium	most (n(n−1)/2)
Node fails	OK	**OK (only that node)**	ring breaks	OK (reroute)
Cable/backbone fails	**all down**	one node down	all down	OK (reroute)
Single point of failure	backbone	**hub/switch**	every node/link	none
Access	CSMA/CD	switched	token	routed

Numbers to remember

- Nyquist **$C = 2B \log_2 L$**; Shannon **$C = B \log_2(1+SNR)$**, SNR linear.
- Bit rate = baud × $\log_2$(levels).
- MAC = **48 bits**; IPv4 = **32 bits**; IPv6 = **128 bits**; port = 16 bits.
- Class ranges (1st octet): A 1–126, B 128–191, C 192–223, D 224–239 (multicast), E 240–255; loopback **127.0.0.1**.
- Private: **10/8, 172.16/12, 192.168/16**; APIPA 169.254/16.
- Hosts per subnet = 2^h − 2; subnets from s borrowed bits = 2^s; block size = 256 − mask octet.
- Ethernet frame **64–1518 B**; payload 46–1500 B; CRC-32; jam = 32 bits; min frame ↔ slot time.
- TCP header 20–60 B (reliable, ordered, 3-way SYN→SYN-ACK→ACK); UDP header **8 B** (fast, connectionless).
- DHCP = **DORA**; ARP: IP→MAC (broadcast request, unicast reply); ICMP → ping/traceroute; DNS: name→IP.
- SNMP: manager **GET/SET** → agent; agent **Response/TRAP** → manager; MIB lives **on the agent**; UDP **161/162**; v3 adds security.
- GEO satellite 35,786 km, ~270 ms hop delay; ISDN BRI = 2B+D = 144 kbps; ATM cell = **53 B (48+5)**.
- 802.11: a/g = 54 M, b = 11 M, n = 600 M (MIMO), ac = 5 GHz gigabit, ax = Wi-Fi 6.

End of Chapter 8. Next: Chapter 9 — Computer Programming (C/C++, Data Structures, DBMS).

Chapter 9 — Computer Programming

Syllabus (Unit 9, Annexure-VII C, CEN 05/2025): Programming concepts; Fundamentals of 'C' and C++; Operators in 'C' and C++; Control Statements; Functions, Array, String & Pointers, File Structure; Data Structure and DBMS.

9.0 Weightage & Trend Box

Parameter	Detail
Weight in Technical section	**~10% → 5 questions out of 50** (observed in 22-04-2025 CBT-2 Electronics paper)
Difficulty level	Easy to Moderate — dominated by **"predict the output"** and **one-line definition** questions
Negative marking	1/3 mark per wrong answer
Most tested areas	Operators (especially **bitwise** and **unary**), control-statement outputs (**infinite loops**), basics of `main()`, ternary operator syntax

Actual questions observed in the 22-04-2025 CBT-2 paper (solved fully in the PYQ Corner, Section 9.14):

1. Which operator performs **bitwise OR** in C? → `|`
2. If a C program contains only a **single function**, that function **must be** `main()`.
3. Identify the **unary operator** among given options → `--` (decrement).
4. Correct syntax of the **conditional (ternary) operator** → `expr1 ? expr2 : expr3`.
5. Output of `while(i<=10) printf("%d",i);` **without increment** → **infinite loop printing 1** repeatedly.

Preparation strategy: This unit gives the *best marks-per-hour ratio* in the paper. Every year the questions come from (a) operator classification/precedence, (b) tracing tiny programs, (c) one-liner definitions from Data Structures and DBMS. Master the 15 solved output programs (Section 9.13) and the rapid-revision sheet (Section 9.16) and these 5 marks are secured.

9.1 Programming Concepts

9.1.1 Algorithm

An **algorithm** is a finite, ordered sequence of unambiguous steps to solve a problem. Properties:

- **Finiteness** — must terminate after a finite number of steps.
- **Definiteness** — every step precisely defined.
- **Input** — zero or more inputs.
- **Output** — at least one output.
- **Effectiveness** — each step basic enough to be carried out exactly.

9.1.2 Flowchart Symbols (exam favourite)

Symbol shape	Name	Purpose
Oval / rounded rectangle	Terminal	Start / Stop
Parallelogram	Input/Output	Read or print data
Rectangle	Process	Computation / assignment
Diamond (rhombus)	Decision	Condition test (yes/no branch)
Circle	Connector	Join flow lines (on same page)
Pentagon (home plate)	Off-page connector	Continue on another page
Arrow	Flow line	Direction of control
Rectangle with double side bars	Predefined process	Subroutine / function call

9.1.3 Pseudocode

Pseudocode is an informal, English-like description of an algorithm using programming-style constructs (`IF...THEN...ELSE` , `WHILE` , `FOR`) without strict syntax. It is language-independent and easier to convert into any programming language.

9.1.4 Language Translators — Compiler vs Interpreter vs Assembler

Feature	Compiler	Interpreter	Assembler
Translates	Entire high-level program at once	High-level program line by line	Assembly language → machine code
Output	Object/machine code file	No object file; executes directly	Machine code
Speed of execution	Fast (after compilation)	Slow	Fast
Error reporting	All errors after full scan	Stops at first error, line by line	Line by line
Examples	C, C++	Python, BASIC (classic), JavaScript	MASM, TASM

- **Linker**: combines object files + library code into an executable.
- **Loader**: places the executable into memory for execution.
- **Preprocessor** (in C): processes `#` directives (`#include` , `#define`) before compilation.

9.1.5 Generations of Languages

1GL — Machine language (binary). 2GL — Assembly. 3GL — High-level procedural (C, Pascal). 4GL — Very high level / query oriented (SQL). 5GL — Constraint/AI based (Prolog).

9.1.6 Structured Programming vs Object-Oriented Programming

Structured (Procedural) — e.g. C	Object-Oriented — e.g. C++
Program divided into **functions**	Program divided into **objects** (instances of classes)
Top-down design	**Bottom-up** design
Data moves freely between functions (less secure)	Data hidden inside objects (**data hiding/encapsulation**)
No overloading	Function/operator **overloading** supported
Adding new data/functions is harder	Easy extension via **inheritance**
Focus on procedure/logic	Focus on data

9.2 Fundamentals of C

C was developed by **Dennis Ritchie** at **Bell Laboratories (AT&T) in 1972**. C++ was developed by **Bjarne Stroustrup** (1979–83, originally "C with Classes"). C is a **middle-level, procedural, compiled, case-sensitive** language.

9.2.1 Structure of a C Program

```
/* Documentation section  – comments              */
#include <stdio.h>       /* Link/preprocessor section */
#define PI 3.14159       /* Definition section        */
int g = 10;              /* Global declaration section */

int main(void)           /* main() – execution starts here */
{
    /* declaration part */
    int r = 2;
    /* executable part  */
    printf("Area = %f\n", PI * r * r);
    return 0;            /* status returned to OS */
}
/* user-defined functions (sub-program section) follow */
```

Key facts (repeated PYQ material):

- Execution of every C program **always begins at** `main()`.
- **If a C program contains only one function, that function must be** `main()` — a program without `main()` will compile-link fail. *(Asked verbatim in 2025.)*
- A C program can have **only one** `main()` but any number of other functions.
- Statements end with a **semicolon** `;`. C is **free-format** (whitespace insensitive).
- Comments: `/* ... */` (multi-line), `// ...` (single line, C99/C++).

9.2.2 Header Files

Header	Contains
`stdio.h`	`printf` , `scanf` , `fopen` , `fgetc` , `EOF`
`conio.h`	`clrscr()` , `getch()` (Turbo C, non-standard)
`string.h`	`strlen` , `strcpy` , `strcmp` , `strcat` , `strrev`
`math.h`	`sqrt` , `pow` , `abs(float→fabs)` , `sin`
`stdlib.h`	`malloc` , `calloc` , `free` , `exit` , `atoi` , `rand`
`ctype.h`	`isalpha` , `isdigit` , `toupper` , `tolower`

`#include <file>` searches standard directories; `#include "file"` searches the current directory first.

9.2.3 C Tokens

The smallest individual units of a program. Six types:

1. **Keywords** — reserved words; **C has 32 keywords** (ANSI C): `auto break case char const continue default do double else enum extern float for goto if int long register return short signed sizeof static struct switch typedef union unsigned void volatile while` . All keywords are in **lowercase**.
2. **Identifiers** — names of variables/functions/arrays. Rules: begin with a **letter or underscore**; subsequent characters letters/digits/underscore; **no spaces or special symbols**; cannot be a keyword; case-sensitive (`Sum` ≠ `sum`).
3. **Constants** — fixed values (integer, real, character `'A'` , string `"A"`).
4. **Strings** — sequence of characters in double quotes, terminated by `'\0'` .
5. **Operators** — see Section 9.3.
6. **Special symbols** — `[] {} () , ; # * &` etc.

9.2.4 Data Types and Typical Sizes

Type	Typical size (16-bit / 32-bit compiler)	Range (32-bit `int`)	Format specifier
`char`	1 byte / 1 byte	−128 to +127	`%c`
`unsigned char`	1 / 1	0 to 255	`%c`
`int`	2 / **4 bytes**	−2,147,483,648 to +2,147,483,647	`%d`
`unsigned int`	2 / 4	0 to 4,294,967,295	`%u`
`short int`	2 / 2	−32,768 to +32,767	`%hd`
`long int`	4 / 4 (or 8)	—	`%ld`
`float`	4 bytes	~6 significant digits	`%f`
`double`	8 bytes	~15 significant digits	`%lf`
`long double`	10/12/16 bytes	—	`%Lf`
`void`	— (no value)	—	—

Other specifiers: `%o` octal, `%x` hexadecimal, `%s` string, `%p` pointer address, `%e` exponential.

Type modifiers: `signed, unsigned, short, long`. **Escape sequences:** `\n` newline, `\t` tab, `\0` null, `\\` backslash, `\"` double quote, `\b` backspace, `\r` carriage return, `\a` alert(bell).

9.2.5 Constants

- **Literal constants**: `10`, `0x1A` (hex), `012` (octal), `3.14`, `'A'`, `"RRB"`.
- `const int x = 5;` — read-only variable.
- `#define MAX 100` — preprocessor macro (no memory, textual substitution, no semicolon).
- `enum color {RED, GREEN=5, BLUE};` — RED=0, GREEN=5, BLUE=6.

9.2.6 Storage Classes (very frequent MCQ)

Storage class	Storage	Default initial value	Scope	Lifetime
`auto`	Memory (stack)	**Garbage**	Local to block	Until block ends
`register`	**CPU register** (request)	Garbage	Local to block	Until block ends
`static`	Memory (data segment)	**Zero**	Local to block (but value **persists** between calls)	Entire program run
`extern`	Memory (data segment)	Zero	**Global** (declared elsewhere)	Entire program run

- Default storage class of a local variable = `auto`; of a global variable = `extern`-like (static duration).
- **Address of a `register` variable cannot be taken** (`&` not allowed).
- A `static` local variable is **initialised only once**.

9.2.7 Scope

- **Block scope** — variable visible only inside `{ }` where declared.
- **File (global) scope** — declared outside all functions; visible from declaration to end of file.
- **Function scope** — labels (used with `goto`).
- Local variable **shadows** a global of the same name inside its block.

9.3 Operators in C and C++ ★ (highest-yield section)

9.3.1 Classification by Number of Operands (asked in 2025)

Class	Operands	Examples			
Unary	1	`++ -- ! ~ sizeof & (address) * (dereference) unary + and - (type)cast`			
Binary	2	`+ - * / % < > == && \`	\	& \	^ << >> = +=`
Ternary	3	`? :` (the **only** ternary operator in C)			

> **2025 PYQ:** among `+ (binary), * (binary), && (binary), --`, the **unary operator is `--`**.

9.3.2 Arithmetic Operators

`+ - * / %`. Rules:

- `%` (modulus) works **only on integers** — `5.0 % 2` is a compile error (use `fmod`).
- **Integer division truncates**: `7/2 = 3`, but `7.0/2 = 3.5`.
- Sign of `a % b` follows the sign of `a` (C99): `-7 % 2 = -1`.

9.3.3 Relational Operators

`< <= > >= == !=` — result is **1 (true) or 0 (false)**, type `int`.

Classic trap: `=` (assignment) vs `==` (comparison). `if (x = 0)` assigns 0 → condition false.

9.3.4 Logical Operators

`&&` (AND), `||` (OR), `!` (NOT). Operate on truth values; any **non-zero value is true**.

Short-circuit evaluation: in `a && b`, if `a` is false, `b` is **not evaluated**; in `a || b`, if `a` is true, `b` is not evaluated. (Source of many output questions — see Program 6.)

9.3.5 Bitwise Operators ★ (2025 PYQ)

Operator	Name	Example (a=12=1100_2, b=10=1010_2)		
`&`	Bitwise AND	`a & b` = 1000_2 = **8**		
`\`	`` ` ``	**Bitwise OR**	`a \	b` = 1110_2 = **14**
`^`	Bitwise XOR	`a ^ b` = 0110_2 = **6**		
`~`	One's complement (unary)	`~a` = −(a+1) = **−13**		
`<<`	Left shift	`a << 2` = a × 2^2 = **48**		
`>>`	Right shift	`a >> 2` = a ÷ 2^2 = **3**		

> **2025 PYQ:** the operator that performs bitwise OR is `|` (not `||` which is *logical* OR, not `&` which is bitwise AND).

Shortcuts: `x << n` = $x \cdot 2^n$; `x >> n` = $x/2^n$ (integer); `x ^ x = 0`; `x ^ 0 = x`; swapping without temp uses XOR three times.

9.3.6 Assignment & Compound Assignment

`= += -= *= /= %= <<= >>= &= |= ^=`. `a += 5` ≡ `a = a + 5`. Assignment itself yields a value: `a = b = c = 10;` (right-to-left).

9.3.7 Increment/Decrement — Pre vs Post ★

Form	Meaning
`++a` (pre-increment)	Increment **first**, then use the value
`a++` (post-increment)	Use current value, **then** increment
`--a` / `a--`	Same logic with decrement

```
int a = 5, b;
b = a++;   /* b = 5, a = 6 */
b = ++a;   /* a = 7, b = 7 */
```

These operate only on **variables (lvalues)** — `5++` is illegal.

9.3.8 Conditional (Ternary) Operator ★ (2025 PYQ)

Syntax: `expression1 ? expression2 : expression3;`

If `expression1` is true (non-zero) → result is `expression2`, else `expression3`.

```
int max = (a > b) ? a : b;      /* max of two numbers */
printf("%d", (7 > 3) ? 10 : 20);  /* prints 10 */
```

It is the only operator in C taking **three operands**; it can replace a simple `if-else`. Nesting is allowed: `(a>b) ? ((a>c)?a:c) : ((b>c)?b:c)` gives max of three.

9.3.9 sizeof, Comma, and Other Operators

- `sizeof` — **compile-time unary operator**, returns size in **bytes**; `sizeof(int)` = 4 (32-bit), `sizeof('A')` = 4 in C (char literal is `int` in C; **1 in C++**).
- **Comma operator** `,` — evaluates left to right; value of the whole expression = **rightmost** operand: `x = (1, 2, 3);` → x = 3. Comma has the **lowest precedence** of all operators.
- `&` address-of, `*` dereference, `.` member access, `->` member via pointer, `[]` subscript, `()` function call, `(type)` cast.
- **C++ extras:** `::` scope resolution, `new`, `delete`, `>>` / `<<` overloaded as extraction/insertion for streams, `.*`, `->*`.

9.3.10 Precedence & Associativity Table (memorise top and bottom)

Rank (high→low)	Operators	Associativity
1	`() [] . -> postfix ++ --`	Left → Right
2	`prefix ++ -- unary + - ! ~ * & sizeof (cast)`	**Right → Left**
3	`* / %`	L → R
4	`+ -`	L → R
5	`<< >>`	L → R
6	`< <= > >=`	L → R
7	`== !=`	L → R
8	`&`	L → R
9	`^`	L → R
10	`|	L → R
11	`&&`	L → R
12	`||`	L → R
13	`? :`	**Right → Left**
14	`= += -= *= /= %= &= ^= |= <<= >>=`	**Right → Left**
15 (lowest)	`,`	L → R

Memory aid for 3–12: **A**rithmetic > **S**hift > **R**elational > **E**quality > **B**itwise (& ^ |) > **L**ogical (&& ||).

Worked example: `x = 2 + 3 * 4 > 10 && 5;` → `3*4=12` → `2+12=14` → `14>10=1` → `1&&5=1` → `x=1`.

9.4 Control Statements

9.4.1 Selection: if, if–else, nested if, else–if ladder

```
if (marks >= 90)      grade = 'A';
else if (marks >= 75) grade = 'B';
else                  grade = 'C';
```

- Condition non-zero ⇒ true. `if(1)` always executes; `if(0)` never.
- **Dangling else:** an `else` always pairs with the **nearest unmatched** `if`:

```
if (a > b)
    if (a > c) printf("A");
else printf("B");     /* this else belongs to if(a>c), NOT if(a>b) */
```

- **Semicolon trap:** `if (x > 5);` — the semicolon is an empty statement; the following block executes unconditionally.

9.4.2 switch–case and Fallthrough ★

```
switch (expression)   /* must be int or char type — NOT float or string */
{
    case 1: printf("One");   break;
    case 2: printf("Two");   break;
    default: printf("Other");
}
```

Rules:

- Case labels must be **integer/character constants** (constant expressions), all **distinct**; `float` and variables not allowed.
- **Without `break`, control falls through** into the next case — a classic output question:

```
int x = 2;
switch (x) {
    case 1: printf("A");
    case 2: printf("B");
    case 3: printf("C");
    default: printf("D");
}
/* Output: BCD  (fallthrough from case 2) */
```

- `default` is optional and may appear anywhere.

9.4.3 Loops

Loop	Type	Minimum executions
`while (cond) { }`	**Entry-controlled** (pre-test)	0
`do { } while (cond);`	**Exit-controlled** (post-test)	**1** (body runs at least once)
`for (init; cond; update)`	Entry-controlled	0

- `for(;;)` and `while(1)` are **infinite loops**.
- In `for`, all three expressions are optional; missing condition is treated as **true**.
- `do-while` ends with a **semicolon** after `while(cond)`.

9.4.4 break, continue, goto

- `break` — exits the **innermost** loop or switch immediately.
- `continue` — skips remaining body, jumps to the next iteration (in `for`, the update expression still executes).
- `goto label;` — unconditional jump to `label:` within the same function (discouraged; breaks structured flow).

9.4.5 Classic Trick Outputs (exam gold)

(a) Missing increment → infinite loop (2025 PYQ):

```
int i = 1;
while (i <= 10)
    printf("%d ", i);      /* i never changes */
/* Output: 1 1 1 1 ... printed infinitely (infinite loop) */
```

(b) Semicolon after loop:

```
int i;
for (i = 0; i < 5; i++);   /* empty body due to ; */
printf("%d", i);           /* Output: 5 */
```

(c) Post-decrement in while condition:

```
int i = 3;
while (i--)
    printf("%d ", i);      /* Output: 2 1 0 (condition uses old value) */
```

(d) do–while runs once even when false:

```
int i = 10;
do { printf("Hello"); } while (i < 5);   /* Output: Hello (printed once) */
```

9.5 Functions

9.5.1 Declaration, Definition, Call

```
int add(int, int);          /* declaration (prototype) — ends with ; */

int main(void) {
    int s = add(3, 4);      /* call — 3,4 are actual arguments */
    printf("%d", s);        /* 7 */
    return 0;
}

int add(int a, int b) {     /* definition — a,b are formal parameters */
    return a + b;
}
```

- A function can **return only one value** (via `return`); `void` = returns nothing.
- Default return type in old C = `int`; C99 onwards a declaration is required.
- Functions cannot be defined inside other functions in standard C (**no nesting of definitions**).
- **Library functions** (`printf`) vs **user-defined functions**.

9.5.2 Call by Value vs Call by Reference ★

Call by Value (default in C)	Call by Reference (via pointers in C; `&` reference in C++)
A **copy** of the argument is passed	The **address** of the argument is passed
Changes inside the function do **not** affect the caller's variable	Changes **do** affect the caller's variable
`swap(a, b)` with `void swap(int x, int y)` — no swap happens	`swap(&a, &b)` with `void swap(int *x, int *y)` — swap works

```
void swap(int *x, int *y) { int t = *x; *x = *y; *y = t; }
```

9.5.3 Recursion ★

A function calling itself. Needs a **base case** to terminate, otherwise **stack overflow**.

Factorial:

```
long fact(int n) {
    if (n <= 1) return 1;        /* base case */
    return n * fact(n - 1);      /* recursive case */
}
/* fact(5) = 5*4*3*2*1 = 120 */
```

Fibonacci (0 1 1 2 3 5 8 ...):

```
int fib(int n) {
    if (n <= 1) return n;
    return fib(n - 1) + fib(n - 2);
}
/* fib(6) = 8 */
```

Recursion uses the **stack** to store each call's local variables and return address. Iteration is generally more memory-efficient; recursion is more elegant for problems like Tower of Hanoi (moves = $2^n - 1$), tree traversals, quicksort/mergesort.

9.5.4 Storage of Local Variables

- `auto` locals → **stack** (created on entry, destroyed on exit; garbage default).
- `static` locals → **data segment** (persist across calls; zero default).
- Dynamically allocated memory (`malloc` / `new`) → **heap**.
- Code → text segment; globals/static → data segment (initialised) or BSS (uninitialised).

9.6 Arrays

9.6.1 1-D Arrays

```
int a[5] = {10, 20, 30, 40, 50};   /* indices 0..4 */
```

- Collection of elements of the **same type** in **contiguous memory**.
- Index starts at **0**; last index = size − 1. C does **no bounds checking**.
- `int a[5];` on 32-bit ⇒ occupies 5 × 4 = 20 bytes; `sizeof(a)` = 20; number of elements = `sizeof(a)/sizeof(a[0])` .
- Partial initialisation `int a[5] = {1, 2};` → remaining elements = **0**.
- **Array name = address of the first element** (`a ≡ &a[0]`).

Address arithmetic: if base address of `int a[5]` is 1000 (int = 4 bytes):

`Address of a[i] = Base + i × sizeof(type)` → `a[3]` is at 1000 + 3×4 = **1012**.

9.6.2 2-D Arrays

```
int m[2][3] = {{1,2,3},{4,5,6}};   /* 2 rows, 3 columns */
```

- Stored in **row-major order** in C: 1 2 3 4 5 6.
- `Address of m[i][j] = Base + (i × ncols + j) × size` (row-major).
- In declaration `int m[][3]` the row count may be omitted, the column count may **not**.

9.6.3 Strings

A string in C = **array of characters terminated by the null character** `'\0'`.

```
char s[] = "RRB";     /* stored as 'R','R','B','\0'  → sizeof(s)=4, strlen(s)=3 */
```

- `%s` in `printf` prints characters up to (not including) `'\0'`.
- `scanf("%s", s)` stops at whitespace; `gets` / `fgets` read a full line.

9.6.4 string.h Functions ★

Function	Purpose	Example
`strlen(s)`	Length **excluding** `'\0'`	`strlen("RRB JE")` = 6
`strcpy(d, s)`	Copy s into d	—
`strcat(d, s)`	Append s to end of d	`strcat("RRB","JE")` → "RRBJE"
`strcmp(a, b)`	Compare (ASCII): returns **0 if equal**, negative if a<b, positive if a>b	`strcmp("abc","abd")` < 0
`strrev(s)`	Reverse (non-standard/Turbo C)	—
`strlwr/strupr`	Case change (non-standard)	—
`strstr(a,b)`	Find substring b in a	—
`strchr(s,c)`	Find first occurrence of char c	—

Common output trap:

```
char s[] = "Hello\0World";
printf("%s", s);            /* Output: Hello  (stops at embedded \0) */
printf("%lu", strlen(s));   /* 5 */  /* but sizeof(s) = 12 */
```

9.7 Pointers ★

9.7.1 Basics

A pointer is a variable that **stores the address of another variable**.

```
int a = 10;
int *p = &a;      /* p holds address of a          */
printf("%d", *p); /* dereference: prints 10        */
*p = 20;          /* a becomes 20                  */
```

- `&` = address-of operator; `*` = dereference (value-at-address / indirection) operator.
- Size of any pointer on a given machine is the **same** regardless of type (4 bytes on 32-bit, 8 bytes on 64-bit).
- **NULL pointer** — points to nothing (`int *p = NULL;`); dereferencing it is undefined/crash.
- **Dangling pointer** — points to memory that has been **freed/deallocated** (e.g., after `free(p)` or returning address of a local variable).
- **Wild pointer** — uninitialised pointer.
- **void pointer** (`void *`) — generic pointer; can hold any address but must be cast before dereferencing; pointer arithmetic not allowed on it (standard C).

9.7.2 Pointer Arithmetic

`p + 1` advances by **sizeof(pointed-to type)** bytes, not by 1 byte.

```
int a[4] = {5, 10, 15, 20};
int *p = a;             /* p → a[0] */
p++;                    /* now p → a[1]; address increased by 4 */
printf("%d", *p);       /* 10 */
printf("%d", *(p + 2)); /* 20 */
```

Valid: `p+n`, `p−n`, `p2−p1` (number of elements between), comparisons. Invalid: `p1+p2`, `p*2`.

9.7.3 Pointers and Arrays

`a[i] ≡ *(a + i) ≡ *(i + a) ≡ i[a]` — all four are identical!

```
int a[3] = {1, 2, 3};
printf("%d", 1[a]);   /* prints 2 — legal though bizarre */
```

An array name is a **constant pointer**: `a++` is illegal, but `p = a; p++` is fine. Array of pointers: `int p[5];`. *Pointer to array:* `int ( p) [5];`.

9.7.4 Pointer to Pointer

```
int a = 5;
int *p = &a;
int **q = &p;
printf("%d", **q);   /* 5 */
```

9.7.5 Dynamic Memory (C)

Function	Action
`malloc(n)`	Allocates n bytes, returns `void*`, contents **garbage**
`calloc(k, size)`	Allocates k×size bytes, **initialised to 0**
`realloc(p, n)`	Resize earlier allocation
`free(p)`	Releases memory (else **memory leak**)

9.8 Structures and Unions

```
struct student {          union data {
    int  roll;                int  i;
    char name[20];            float f;
    float marks;              char c;
};                        };
```

Structure	Union
Each member gets **its own memory**	All members **share the same memory**
Size ≥ sum of member sizes (plus padding)	Size = size of the **largest** member
All members hold valid values simultaneously	Only **one** member valid at a time
Keyword `struct`	Keyword `union`

Example: members `int i; float f; char c;` (32-bit) → structure size ≈ 4+4+1(+padding)=12 bytes typically; **union size = 4 bytes**.

- Access: `s.roll` for variables, `p->roll` (≡ `(*p).roll`) for pointers.
- Structures can be **nested**, copied by assignment, passed to and returned from functions; arrays inside are copied too.
- `typedef struct {...} STUDENT;` creates an alias.
- **Self-referential structure** — contains a pointer to its own type; foundation of **linked lists**:

```
struct node { int data; struct node *next; };
```

- **Bit-fields**: `struct { unsigned flag : 1; }` — width in bits.

9.9 File Structure (File Handling in C)

Files provide **permanent storage** on disk; all functions in `stdio.h` operate through a `FILE *` **pointer**.

9.9.1 Opening and Closing

```
FILE *fp = fopen("data.txt", "r");
if (fp == NULL) { printf("Cannot open"); }
...
fclose(fp);
```

fopen modes ★

Mode	Meaning	If file doesn't exist	If file exists
`"r"`	Read	Returns **NULL** (error)	Reads from beginning
`"w"`	Write	Creates new	**Erases contents** (truncates)
`"a"`	Append	Creates new	Writes at **end**, old data safe
`"r+"`	Read + write	NULL	Both, from beginning
`"w+"`	Write + read	Creates	Truncates
`"a+"`	Append + read	Creates	Appends
`"rb" "wb" "ab"` ...	Same in **binary** mode	—	—

`fopen` returns **NULL on failure** — always check it.

9.9.2 I/O Functions

Character	String	Formatted	Block (binary)
`fgetc(fp)` / `fputc(c, fp)`	`fgets(s, n, fp)` / `fputs(s, fp)`	`fscanf(fp, ...)` / `fprintf(fp, ...)`	`fread` / `fwrite`

- **EOF** — special constant (usually **−1**) returned by `fgetc` at end of file. `feof(fp)` also tests end-of-file.

```
int c;
while ((c = fgetc(fp)) != EOF)
    putchar(c);                /* copy file to screen */
```

- **Random access:** `fseek(fp, offset, origin)` with origins `SEEK_SET` (0, beginning), `SEEK_CUR` (1), `SEEK_END` (2); `ftell(fp)` gives current position; `rewind(fp)` resets to start.

9.9.3 Text vs Binary Files

Text file	Binary file
Data stored as **ASCII characters**, human-readable	Data stored in **raw byte** (memory) form
Newline may be translated (`\r\n` ↔ `\n` on Windows)	No translation, exact bytes
Slightly larger, portable	Compact and faster, not human-readable
Modes `"r" "w" "a"`	Modes `"rb" "wb" "ab"`

9.10 C++ Additions (Object-Oriented Programming)

9.10.1 OOP Pillars

- **Class** — user-defined blueprint combining data + functions; **Object** — an instance of a class (memory is allocated when the object is created).
- **Encapsulation** — wrapping data and functions into one unit (class), with access control (`private` — default in class, `protected`, `public`).
- **Abstraction** — showing only essential features, hiding implementation.
- **Inheritance** — a class (derived) acquiring properties of another (base). **Types:** single, multiple (two or more base classes — allowed in C++, not in Java), multilevel (A→B→C), hierarchical (one base, many derived), hybrid (combination; can create the "diamond problem", solved with **virtual base classes**).
- **Polymorphism** — "one name, many forms."

Compile-time (static/early binding)	Run-time (dynamic/late binding)
Function overloading — same name, different parameter list, same class/scope	**Function overriding** — same signature redefined in derived class
Operator overloading (`+` redefined for objects)	Achieved via **virtual functions** and base-class pointers
Resolved by the compiler	Resolved at run time (vtable)

9.10.2 Constructors & Destructors

```
class Demo {
public:
    Demo()        { cout << "ctor";  }   // constructor
    Demo(int x)   { }                    // parameterised (overloadable)
    Demo(const Demo &d) { }              // copy constructor
    ~Demo()       { cout << "dtor";  }   // destructor
};
```

- Constructor: **same name as class, no return type (not even void)**, called automatically at object creation, can be overloaded, can take default arguments.
- Destructor: `~ClassName()`, **no parameters, no return type, cannot be overloaded** (only one), called automatically when the object is destroyed; runs in **reverse order** of construction.
- If none written, the compiler supplies a default constructor/destructor.

9.10.3 I/O, References, new/delete

```
#include <iostream>
using namespace std;
int main() {
    int n;
    cin  >> n;                 // extraction operator
    cout << "Value=" << n << endl;   // insertion operator
    int &r = n;                // reference — alias, must be initialised
    r = 50;                    // n becomes 50
    int *p = new int(7);       // heap allocation
    int *arr = new int[10];
    delete p;                  // release single object
    delete[] arr;              // release array
    return 0;
}
```

- `cin` / `cout` are stream **objects** in `iostream` (not functions). `endl` flushes and adds newline.
- A **reference** cannot be NULL, cannot be reseated, needs initialisation at declaration — unlike a pointer.
- `new` calls the constructor and returns a typed pointer (throws on failure); `malloc` does not call constructors and returns `void*`.
- Other C++ features: default arguments, `inline` functions, `friend` functions/classes (can access private members), `this` pointer, templates (generic programming), exception handling (`try/throw/catch`), `bool` type, `::` scope resolution operator.

9.11 Data Structures

A **data structure** is a way of organising data for efficient access and modification.

Linear (elements in sequence): array, linked list, stack, queue. **Non-linear:** tree, graph.

9.11.1 Arrays vs Linked Lists

Array	Linked List
Contiguous memory, fixed size (static)	Nodes anywhere in memory, dynamic size
Random access O(1) by index	**Sequential access O(n)**
Insertion/deletion costly O(n) (shifting)	Insertion/deletion O(1) once position known
Memory may be wasted/insufficient	Extra memory for pointer field

Linked list types:

- **Singly** — each node: `data + next`; traversal one direction; last node's next = NULL.
- **Doubly** — `prev + data + next`; traversal both directions; extra memory.
- **Circular** — last node points back to the **first** node (no NULL); can be singly or doubly circular.

9.11.2 Stack — LIFO ★

Last In, First Out. Insertion and deletion at one end only, called the **TOP**.

Operation	Meaning	Error condition
`push(x)`	Insert at top	**Overflow** (stack full)
`pop()`	Remove from top	**Underflow** (stack empty)
`peek()/top()`	Read top without removing	—

All stack operations are **O(1)**. Array implementation: `top` initialised to −1; push → `s[++top]=x`; pop → `return s[top--]`.

Applications: function-call management (recursion), **expression conversion & evaluation** (infix↔postfix/prefix), undo feature, parenthesis matching, backtracking, browser back button, reversing a string, DFS.

Notation forms of `A + B`:

Notation	Operator position	Example
Infix	Between operands	`A + B`
Prefix (Polish)	Before operands	`+ A B`
Postfix (Reverse Polish)	After operands	`A B +`

Worked example 1 — Infix → Postfix: convert `A + B * C - D`

Precedence: `*` > `+`, `-` (left-assoc).

`B * C` first → `BC`; *then* `A + BC` → `ABC+`; *then* `- D` → ***`ABC +D-`***

Worked example 2 — Infix → Postfix with brackets: `(A + B) * (C - D)`

→ `AB+` and `CD-` then multiply → **`AB+CD-*`**

Worked example 3 — Infix → Prefix: `(A + B) * C`

→ *applied to* `+AB` *and* `C` → **`+ABC`**

Worked example 4 — Evaluate postfix `5 6 2 + * 12 4 / -`:

Symbol	Action	Stack
5, 6, 2	push	5 6 2
`+`	6+2=8	5 8
`*`	5×8=40	40
12, 4	push	40 12 4
`/`	12/4=3	40 3
`-`	40−3=**37**	37

Answer: 37.

9.11.3 Queue — FIFO ★

First In, First Out. Insertion (**enqueue**) at the **REAR**, deletion (**dequeue**) at the **FRONT**. Both O(1).

- **Simple/linear queue** — array version wastes freed front space.
- **Circular queue** — rear wraps around: `rear = (rear + 1) % SIZE`; full when `(rear+1)%SIZE == front`; solves the wasted-space problem.
- **Deque** (double-ended queue) — insertion and deletion at **both** ends. Variants: input-restricted (insert one end only), output-restricted (delete one end only).
- **Priority queue** — element with highest priority served first (implemented efficiently by a **heap**).

Applications: CPU/printer job scheduling, buffering (keyboard, IO), BFS, call-centre systems.

9.11.4 Trees


A **tree** is a non-linear hierarchical structure: a **root**, and nodes connected by edges with **no cycles**. Node terms: parent, child, **leaf** (no children), siblings, **height/depth**, degree (number of children).

Binary tree: each node has **at most 2 children** (left, right). Maximum nodes at level l = 2^l (root level 0); maximum nodes in tree of height h = 2^(h+1) − 1. A **complete** binary tree fills levels left to right; a **full/strict** tree has 0 or 2 children per node.

Traversals ★ (L = left subtree, N = node, R = right subtree):

Traversal	Order
Inorder	L → N → R
Preorder	N → L → R
Postorder	L → R → N
Level order	Level by level (uses a **queue**)

Worked example. Tree:

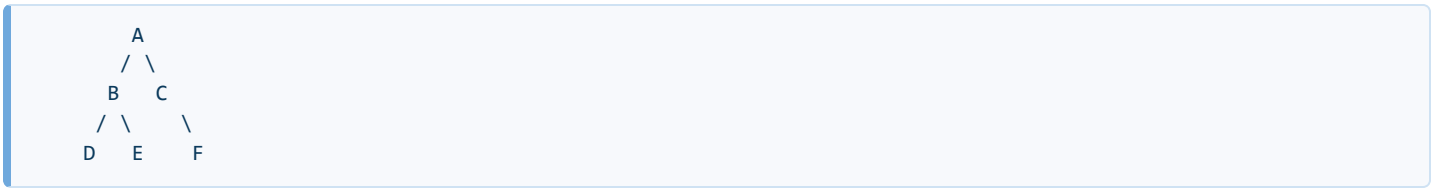

- **Inorder** (LNR): D B E A C F
- **Preorder** (NLR): A B D E C F
- **Postorder** (LRN): D E B F C A

Binary Search Tree (BST): left subtree keys < node key < right subtree keys. **Inorder traversal of a BST gives keys in sorted (ascending) order.** Search/insert/delete average O(log n), worst O(n) (skewed tree). Balanced variants: AVL, Red-Black.

Heap (one-liner): a complete binary tree where every parent ≥ children (**max-heap**) or ≤ children (**min-heap**); root holds max/min; used in **heapsort** and priority queues; array-based (children of index i at 2i+1, 2i+2).

9.11.5 Graphs (one-liners)

A graph G = (V, E) — set of **vertices** and **edges**; may be directed/undirected, weighted/unweighted, cyclic/acyclic. Representations: **adjacency matrix** ($O(V^2)$ space) and **adjacency list**.

- **BFS (Breadth-First Search)** — explores level by level; uses a **queue**; finds shortest path in unweighted graphs.
- **DFS (Depth-First Search)** — explores as deep as possible before backtracking; uses a **stack** (or recursion).
- A **tree is a connected acyclic graph** with exactly V−1 edges.

9.11.6 Searching

Algorithm	Requirement	Best	Average/Worst	Idea
Linear search	None (unsorted OK)	O(1)	**O(n)**	Check each element in turn
Binary search	**Sorted** data	O(1)	**O(log n)**	Compare middle, halve the range: `mid = (low+high)/2`

Maximum comparisons in binary search over n elements ≈ $\lceil \log_2(n+1) \rceil$ (e.g., 1024 elements → ~10 comparisons).

9.11.7 Sorting — Algorithms & Complexity Table ★

Algorithm	Best	Average	Worst	Space	Stable?	Method (one line)
Bubble sort	O(n)*	$O(n^2)$	$O(n^2)$	O(1)	Yes	Repeatedly swap adjacent out-of-order pairs; largest "bubbles" to the end each pass
Selection sort	$O(n^2)$	$O(n^2)$	$O(n^2)$	O(1)	No	Select the minimum of the unsorted part, swap into place; exactly n−1 swaps
Insertion sort	**O(n)**	$O(n^2)$	$O(n^2)$	O(1)	Yes	Insert each element into its correct place in the sorted left part; best for nearly-sorted data
Quick sort	O(n log n)	**O(n log n)**	**$O(n^2)$**	O(log n)	No	Partition around a **pivot**; divide & conquer; worst case on already-sorted input with bad pivot
Merge sort	O(n log n)	O(n log n)	**O(n log n)**	**O(n)**	Yes	Divide into halves, sort, **merge**; guaranteed n log n; good for linked lists/external sorting
Heap sort	O(n log n)	O(n log n)	O(n log n)	O(1)	No	Build max-heap; repeatedly extract root

*with early-exit swapped-flag optimisation.

Big-O growth order (slow-growing → fast): $O(1) < O(\log n) < O(n) < O(n \log n) < O(n^2) < O(n^3) < O(2^n) < O(n!)$.

Bubble sort passes on n elements = n−1; comparisons total = n(n−1)/2.

9.12 DBMS (Database Management System)

9.12.1 Data, Information, DBMS

- **Data** — raw, unorganised facts (e.g., 85, "Ravi").

- **Information** — processed, meaningful data (e.g., "Ravi scored 85%").
- **Database** — organised collection of related data.
- **DBMS** — software to create, store, retrieve, and manage databases (Oracle, MySQL, SQL Server, PostgreSQL, DB2).

Advantages over file systems: controlled **redundancy**, **consistency**, **data sharing**, **security** (access control), **integrity** constraints, **backup & recovery**, program–data **independence**, concurrent access. Disadvantages: cost, complexity, need for trained staff.

9.12.2 Three-Level (ANSI-SPARC) Architecture ★

Level	Also called	Describes
External level	View level	Individual user views (highest level)
Conceptual level	Logical level	What data is stored and relationships — whole-database schema
Internal level	Physical level	**How** data is physically stored (files, indexes — lowest level)

Data independence: *logical* (change conceptual schema without changing external views) and *physical* (change internal storage without changing conceptual schema).

9.12.3 Data Models

- **Hierarchical** — tree (parent–child), e.g., IBM IMS.
- **Network** — graph, records with multiple parents (CODASYL).
- **Relational** — data in **tables (relations)**; proposed by **E. F. Codd (1970)**; the dominant model.
- **Object-oriented**, **ER model** (design tool).

9.12.4 Relational Model Terms ★

Term	Meaning	Common name
Relation	Table	Table
Tuple	A **row** of the table	Record
Attribute	A **column**	Field
Domain	Set of permitted values for an attribute	—
Degree	Number of **attributes (columns)**	—
Cardinality	Number of **tuples (rows)**	—

9.12.5 Keys ★

Key	Definition
Super key	Any set of attributes that uniquely identifies a tuple
Candidate key	A **minimal** super key (no redundant attribute)
Primary key	The candidate key chosen by the designer; **unique + NOT NULL**; one per table
Alternate key	Candidate keys not chosen as primary
Foreign key	Attribute in one table referring to the **primary key of another** table — enforces **referential integrity**
Composite key	Key made of two or more attributes

9.12.6 SQL Basics ★

SQL (Structured Query Language) — standard language of relational databases; **not case-sensitive** for keywords.

Category	Full form	Commands
DDL	Data Definition Language	`CREATE, ALTER, DROP, TRUNCATE, RENAME`
DML	Data Manipulation Language	`SELECT, INSERT, UPDATE, DELETE`
DCL	Data Control Language	`GRANT, REVOKE`
TCL	Transaction Control Language	`COMMIT, ROLLBACK, SAVEPOINT`

- `DELETE` (DML) removes rows, can use WHERE, can be rolled back; `TRUNCATE` (DDL) removes **all** rows fast, no WHERE; `DROP` removes the **table itself** including structure.

SELECT syntax:

```
SELECT column1, column2          -- * = all columns
FROM   table_name
WHERE  condition                 -- row filter (=, <>, >, LIKE, IN, BETWEEN, AND/OR)
GROUP  BY column                 -- grouping for aggregates
HAVING group_condition           -- filter on groups (used with GROUP BY)
ORDER  BY column ASC|DESC;       -- sorting (ASC is default)
```

Examples:

```
SELECT name, marks FROM student WHERE marks > 80 ORDER BY marks DESC;
SELECT dept, COUNT(*) FROM emp GROUP BY dept HAVING COUNT(*) > 5;
INSERT INTO student VALUES (1, 'Ravi', 85);
UPDATE student SET marks = 90 WHERE roll = 1;
DELETE FROM student WHERE roll = 1;
```

Aggregate functions: `COUNT, SUM, AVG, MAX, MIN`. `WHERE` filters rows **before** grouping; `HAVING` filters **after**. `DISTINCT` removes duplicates. `LIKE 'A%'` — names starting with A (`%` = any string, `_` = one character).

9.12.7 Normalization ★

Normalization organises data to **minimise redundancy** and avoid insertion, update, and deletion **anomalies**, by decomposing tables.

- **1NF (First Normal Form):** every attribute contains only **atomic (indivisible) values** — no repeating groups or multi-valued cells. A table with a "phone numbers" cell holding two numbers violates 1NF; splitting into separate rows/tables fixes it.
- **2NF:** the table is in 1NF **and** every non-key attribute is **fully functionally dependent on the whole primary key** — no **partial dependency** on part of a composite key. E.g., in (StudentID, CourseID → CourseName), CourseName depends only on CourseID, violating 2NF; move it to a Course table.
- **3NF:** the table is in 2NF **and** has **no transitive dependency** — no non-key attribute depends on another non-key attribute. E.g., Student → DeptID → DeptName means DeptName transitively depends on Student; move DeptName into a Department table.
- **BCNF** (Boyce–Codd NF): stricter 3NF — every determinant must be a candidate key.

9.12.8 ER Model Basics

Proposed by **Peter Chen (1976)** as a design tool. Components and diagram symbols:

Concept	Symbol	Example
Entity (real-world object)	**Rectangle**	STUDENT
Attribute	**Ellipse/oval**	name, roll
Relationship	**Diamond**	ENROLLS
Key attribute	Ellipse with **underlined** text	roll
Multivalued attribute	**Double ellipse**	phone
Derived attribute	**Dashed ellipse**	age (from DOB)
Weak entity	**Double rectangle**	—

Relationship cardinalities: **1:1, 1:N, M:N**.

9.12.9 ACID Properties ★

Properties every **transaction** must satisfy:

Property	Meaning
A — Atomicity	All operations of a transaction happen, or **none** do ("all or nothing")
C — Consistency	Database moves from one valid state to another valid state
I — Isolation	Concurrent transactions do not interfere; intermediate results invisible to others
D — Durability	Once committed, changes are **permanent**, surviving crashes

---

9.13 Predict-the-Output: 15 Solved Programs ★★★

(Assume `#include <stdio.h>` and `int main()` wrapping each snippet; 32-bit int.)

Program 1 — Post vs pre increment

```
int a = 5;
printf("%d %d %d", a++, a, ++a);
```

Note: evaluation order of printf arguments is compiler-dependent (typically right-to-left in exams/Turbo C): `++a` →6, `a` →6, `a++` →6 (then 7). **Typical exam answer: 6 6 6.** Concept tested: side effects + unspecified order. Safe version:

```
int a = 5;
int b = a++ + ++a;   /* 5 + 7 = 12, a = 7 */
printf("%d %d", a, b);
```

Output: `7 12` — `a++` yields 5 (a→6), then `++a` makes a=7 and yields 7; 5+7=12.

Program 2 — Integer division & modulus

```
int x = 17, y = 4;
printf("%d %d %d", x / y, x % y, x / y * y + x % y);
```

Output: `4 1 17` — 17/4 truncates to 4; 17%4 = 1; 4×4+1 = 17 (identity a = (a/b)*b + a%b).

Program 3 — Bitwise operators

```
int a = 12, b = 10;
printf("%d %d %d %d", a & b, a | b, a ^ b, a << 1);
```

Output: `8 14 6 24` — 1100 & 1010 = 1000 (8); OR = 1110 (14); XOR = 0110 (6); 12<<1 = 24.

Program 4 — Ternary operator

```
int a = 10, b = 20, c;
c = (a > b) ? a * 2 : b / 2;
printf("%d", c);
```

Output: `10` — condition 10>20 false → c = 20/2 = 10.

Program 5 — switch fallthrough

```
int i = 1;
switch (i) {
    case 1: printf("One ");
    case 2: printf("Two ");  break;
    case 3: printf("Three ");
    default: printf("Def");
}
```

Output: `One Two` — matches case 1, falls into case 2 (no break after case 1), then `break` exits.

Program 6 — Short-circuit evaluation

```
int i = 0, j = 1;
if (i++ && j++)
    printf("Inside ");
printf("%d %d", i, j);
```

Output: `1 1` — `i++` yields 0 (false) so `&&` short-circuits: `j++` never runs; i became 1, j stays 1; "Inside" not printed.

Program 7 — while with post-decrement

```
int i = 5;
while (i--)
    printf("%d ", i);
```

Output: `4 3 2 1 0` — condition tests old value then decrements: tests 5 prints 4 … tests 1 prints 0, tests 0 → exit.

Program 8 — Semicolon after for

```
int i, s = 0;
for (i = 1; i <= 5; i++);
    s += i;
printf("%d %d", i, s);
```

Output: `6 6` — the `;` makes the loop body empty; loop ends with i=6; then s += i runs **once** → s=6.

Program 9 — static local variable

```
void fun(void) {
    static int c = 0;
    c++;
    printf("%d ", c);
}
int main(void) { fun(); fun(); fun(); return 0; }
```

Output: `1 2 3` — `static` c initialised once and persists across calls (an `auto` c would print `1 1 1`).

Program 10 — Recursion (factorial trace)

```
int f(int n) {
    if (n == 0) return 1;
    return n * f(n - 1);
}
/* in main: */ printf("%d", f(4));
```

Output: `24` — f(4)=4·f(3)=4·3·f(2)=4·3·2·f(1)=4·3·2·1·f(0)=24.

Program 11 — Array and pointer arithmetic

```
int a[5] = {2, 4, 6, 8, 10};
int *p = a;
printf("%d %d %d", *p + 1, *(p + 1), *(a + 4));
```

Output: `3 4 10` — `p+1` = *2+1 = 3 (dereference binds first);* `(p+1)` = a[1] = 4; `*(a+4)` = a[4] = 10.

Program 12 — String with strlen vs sizeof

```
char s[] = "RRB JE";
printf("%lu %lu", (unsigned long)strlen(s), (unsigned long)sizeof(s));
```

Output: `6 7` — strlen counts characters before `'\0'` (R,R,B,space,J,E = 6); sizeof includes the `'\0'` → 7. *(Needs `string.h`.)*

Program 13 — strcmp result

```
printf("%d", strcmp("abc", "abc") == 0 ? 1 : 0);
```

Output: `1` — strcmp returns 0 for equal strings, so the ternary yields 1.

Program 14 — Call by value vs reference

```
void byval(int x)  { x = 100; }
void byref(int *x) { *x = 100; }
int main(void) {
    int a = 5, b = 5;
    byval(a);
    byref(&b);
    printf("%d %d", a, b);
    return 0;
}
```

Output: `5 100` — byval changes only a copy; byref changes the caller's variable through its address.

Program 15 — Union memory sharing

```
union u { int i; char c; };
int main(void) {
    union u v;
    v.i = 65;
    printf("%c %d", v.c, (int)sizeof(v));
    return 0;
}
```

Output: `A 4` — members share memory; low byte of 65 is ASCII 'A' (little-endian); union size = largest member = sizeof(int) = 4.

Bonus Program 16 — Comma operator

```
int x;
x = (3, 4, 5);
printf("%d", x);
```

Output: `5` — the comma expression's value is the rightmost operand. (But `int x = 3, 4, 5;` would be a declaration error, and `x = 3, 4, 5;` without parentheses assigns 3 because `=` binds tighter than `,`.)

9.14 PYQ Corner — Actual CBT-2 Questions (22-04-2025, Electronics & Allied)

Q1. Which of the following operators is used to perform bitwise OR operation in C?

(a) `||` (b) `&` (c) `|` (d) `^`

Answer: (c) `|`.

Explanation: `|` compares operands bit by bit and sets a result bit to 1 if **either** bit is 1 (e.g., `12 | 10 = 14`). Distinguish carefully: `||` is **logical** OR (works on truth values, returns 0/1), `&` is bitwise AND, `^` is bitwise XOR.

Q2. If a C program contains only a single function, then that function must be _____.

(a) `printf()` (b) `scanf()` (c) any user-defined function (d) `main()`

Answer: (d) `main()`.

Explanation: Program execution always begins at `main()`; the linker searches for it as the entry point. A C program without `main()` cannot form an executable, so if only one function exists, it has to be `main()`. `printf` / `scanf` are library functions, not entry points.

Q3. Which of the following is a unary operator in C?

(a) `+` (addition) (b) `&&` (c) `--` (d) `<=`

Answer: (c) `--`.

Explanation: Unary operators need **one** operand: `++ -- ! ~ sizeof & *(dereference)` and unary `+/-`. Binary `+`, logical `&&`, and relational `<=` each need two operands. The only ternary operator in C is `?:`.

Q4. The correct syntax of the conditional (ternary) operator in C is:

(a) `expr1 : expr2 ? expr3` (b) `expr1 ? expr2 : expr3` (c) `expr1 ? expr2 ? expr3` (d) `expr1 : expr2 : expr3`

Answer: (b) `expr1 ? expr2 : expr3`.

Explanation: If `expr1` evaluates non-zero (true), the whole expression takes the value of `expr2`; otherwise `expr3`. Example: `max = (a > b) ? a : b;`. It is a shorthand for a simple if–else and takes three operands.

Q5. What is the output of the following code?

```
int i = 1;
while (i <= 10)
    printf("%d", i);
```

(a) 1 2 3 ... 10 (b) 10 (c) 1 printed once (d) 1 printed infinitely (infinite loop)

Answer: (d) infinite loop printing 1.

Explanation: The loop body never modifies `i`, so the condition `1 <= 10` remains true forever — the program prints `1` endlessly. The fix is to add `i++;` inside the body. This "missing increment/update" pattern is the single most repeated trick in RRB computer questions.

9.15 Practice MCQs (30 Questions)

Q1. C language was developed by:

(a) Bjarne Stroustrup (b) Dennis Ritchie (c) James Gosling (d) Ken Thompson

Q2. The number of keywords in ANSI C is:

(a) 30 (b) 32 (c) 48 (d) 64

Q3. Which of the following is an invalid identifier?

(a) `_sum` (b) `sum1` (c) `1sum` (d) `Sum_1`

Q4. The format specifier used to print a hexadecimal integer is:

(a) `%o` (b) `%h` (c) `%x` (d) `%d`

Q5. Default initial value of a `static` variable in C is:

(a) garbage (b) 0 (c) 1 (d) NULL

Q6. `printf("%d", 9/2 + 9%2);` prints:

(a) 4.5 (b) 5 (c) 4 (d) 6

Q7. Which operator has the **lowest** precedence in C?

(a) `=` (b) `,` (c) `||` (d) `?:`

Q8. `int a = 5; printf("%d", a++ + a++);` (typical exam evaluation) gives:

(a) 10 (b) 11 (c) 12 (d) 13

Q9. `printf("%d", 5 & 3);` prints:

(a) 1 (b) 7 (c) 0 (d) 8

Q10. `x << 3` is equivalent to:

(a) x × 3 (b) x × 8 (c) x ÷ 8 (d) x + 3

Q11. Which loop executes its body **at least once**?

(a) for (b) while (c) do–while (d) none

Q12. The `switch` expression in C can be of type:

(a) float (b) double (c) int/char (d) string

Q13. `continue` statement inside a loop:

(a) exits the loop (b) skips to the next iteration (c) exits the program (d) restarts the loop from the first iteration

Q14. Output of:

```
int i;
for (i = 0; i < 3; i++)
    if (i == 1) continue;
    else printf("%d", i);
```

(a) 012 (b) 02 (c) 12 (d) 0

Q15. In call by value:

(a) address is passed (b) a copy of the value is passed (c) reference is passed (d) nothing is passed

Q16. Value of `fact(0)` returned by a standard recursive factorial function is:

(a) 0 (b) 1 (c) undefined (d) −1

Q17. If base address of `int a[10]` is 2000 (int = 4 bytes), the address of `a[5]` is:

(a) 2005 (b) 2010 (c) 2020 (d) 2040

Q18. `strlen("RAILWAY")` returns:

(a) 7 (b) 8 (c) 6 (d) 9

Q19. `strcmp(s1, s2)` returns 0 when:

(a) s1 > s2 (b) s1 < s2 (c) s1 equals s2 (d) both strings are empty only

Q20. A pointer that points to a memory location that has been freed is called:

(a) NULL pointer (b) void pointer (c) dangling pointer (d) far pointer

Q21. `a[i]` is exactly equivalent to:

(a) `(a + i)` *(b)* `&a + i` *(c)* `a + i` (d) `a + *i`

Q22. Size of `union { int i; char c; double d; }` on a system with double = 8 bytes is:

(a) 13 (b) 8 (c) 4 (d) 1

Q23. Which fopen mode **erases** an existing file's contents?

(a) "r" (b) "a" (c) "w" (d) "r+"

Q24. `fgetc()` returns _____ at end of file:

(a) 0 (b) NULL (c) EOF (d) '\0'

Q25. Function overloading is an example of:

(a) run-time polymorphism (b) compile-time polymorphism (c) inheritance (d) encapsulation

Q26. A destructor in C++:

(a) can be overloaded (b) takes parameters (c) has no return type and no parameters (d) must be called explicitly always

Q27. Which data structure works on the LIFO principle?

(a) queue (b) stack (c) linked list (d) tree

Q28. The postfix form of `A * (B + C)` is:

(a) `ABC+` *(b)* `AB+C` (c) `ABC+` *(d)* `A+BC`

Q29. Inorder traversal of a Binary Search Tree yields keys in:

(a) random order (b) descending order (c) ascending order (d) level order

Q30. Which of the following is a DDL command in SQL?

(a) SELECT (b) INSERT (c) UPDATE (d) CREATE

Answer Key with Brief Explanations

Q	Ans	Explanation
1	b	Dennis Ritchie, Bell Labs, 1972 (Stroustrup → C++, Gosling → Java)
2	b	ANSI C has 32 reserved keywords
3	c	Identifier cannot **start with a digit**
4	c	`%x` = hex, `%o` = octal, `%d` = decimal
5	b	static/extern default to 0; auto/register hold garbage
6	b	9/2 = 4 (integer), 9%2 = 1; 4+1 = 5
7	b	Comma has lowest precedence; `=` is second-lowest
8	b	5 + 6 = 11 (first a++ yields 5 then a=6, second yields 6) — the standard exam convention
9	a	101 & 011 = 001 = 1
10	b	Left shift by n multiplies by 2^n → x×8
11	c	do–while is exit-controlled: body first, test after
12	c	switch works on integral types only (int/char/enum)
13	b	continue skips rest of body, moves to next iteration
14	b	prints 0 and 2; i=1 skipped by continue
15	b	A copy is passed; original unchanged
16	b	Base case: 0! = 1
17	c	2000 + 5×4 = 2020
18	a	R-A-I-L-W-A-Y = 7 characters (\0 not counted)
19	c	0 = equal; negative/positive indicate ASCII ordering
20	c	Dangling pointer → freed/deallocated memory
21	a	Array indexing is defined as `*(a+i)`
22	b	Union size = size of largest member = 8 (double)
23	c	"w" truncates existing file; "a" preserves and appends
24	c	EOF (typically −1) signals end of file
25	b	Overloading resolved at compile time (static binding); overriding via virtual functions is run-time

Q	Ans	Explanation
26	c	`~Class()` — no arguments, no return type, cannot be overloaded
27	b	Stack = Last In First Out; queue = FIFO
28	a	(B+C) → `BC+` ; then `A * BC+` → operands A and BC+ followed by * → `ABC+*`
29	c	BST property ⇒ inorder gives sorted ascending sequence
30	d	CREATE/ALTER/DROP/TRUNCATE = DDL; SELECT/INSERT/UPDATE/DELETE = DML

> **Note on Q28:** option (b) `AB+C` *would correspond to* `(A+B) C` — a common distractor. Trace bracket-first: `(B+C)` → `BC+` , then multiply by A → `ABC+*` .

9.16 Rapid-Revision Sheet (last-day flip)

A. Operator Precedence (top → bottom)

```
() []  ->  .  postfix++/--          (highest)
prefix++/--  !  ~  unary+/-  *  &  sizeof  (cast)   [R→L]
*  /  %
+  -
<<  >>
<  <=  >  >=
==  !=
&      ^      |         (AND before XOR before OR)
&&     ||
?:                       [R→L]
=  +=  -=  ...           [R→L]
,                        (lowest)
```

One-liners: only ternary = `?:` · only ones needing lvalue = `++ -- = &` · `sizeof` is an operator, not a function · logical ops give 0/1; bitwise work on bits.

B. Format Specifiers & Escape Sequences

`%d` int · `%u` unsigned · `%ld` long · `%f` float · `%lf` double · `%c` char · `%s` string · `%o` octal · `%x` hex · `%p` address · `%%` percent sign

`\n` newline · `\t` tab · `\0` null · `\\` backslash · `\a` bell · `\b` backspace · `\r` carriage return

C. Sizes (32-bit) & Storage Classes

char 1 · short 2 · int 4 · long 4 · float 4 · double 8 · any pointer 4

auto → stack, garbage · register → CPU register, no `&` · static → persists, 0 · extern → global, 0

D. Complexity Table

Structure/Algo	Access	Search	Insert	Delete
Array	O(1)	O(n)	O(n)	O(n)
Linked list	O(n)	O(n)	O(1)*	O(1)*
Stack/Queue op	—	—	O(1)	O(1)
BST (avg)	—	O(log n)	O(log n)	O(log n)

*at known position. Linear search O(n) · Binary search O(log n), needs **sorted** data.

Sorting: Bubble/Selection/Insertion **$O(n^2)$** · Quick avg **O(n log n)** worst $O(n^2)$ · Merge & Heap **O(n log n)** always · Merge needs O(n) extra space · Stable: bubble, insertion, merge.

E. Data-Structure Flip Summary

DS	Principle	Insert/Delete point	Uses
Stack	**LIFO**	Top only (push/pop)	Recursion, undo, infix→postfix, DFS, parenthesis matching
Queue	**FIFO**	Rear in / Front out	Scheduling, buffering, BFS
Circular queue	FIFO	rear = (rear+1)%SIZE	Reuses freed space
Deque	Both ends	Front & rear	Both stack + queue behaviour
Singly LL	Sequential	Anywhere via pointers	Dynamic memory lists
Circular LL	Last → first	—	Round-robin scheduling
Binary tree	Hierarchical	—	Traversals: In = LNR, Pre = NLR, Post = LRN
BST	left < root < right	O(log n) avg	**Inorder = sorted**
Heap	Complete tree, parent ≥/≤ child	Root extract	Heapsort, priority queue
Graph	V, E	—	BFS uses **queue**, DFS uses **stack**

F. SQL Command Classification

DDL: CREATE · ALTER · DROP · TRUNCATE · RENAME

DML: SELECT · INSERT · UPDATE · DELETE

DCL: GRANT · REVOKE **TCL:** COMMIT · ROLLBACK · SAVEPOINT

Keys: Primary = unique + NOT NULL · Foreign = refers to another table's primary key · Candidate = minimal super key

Row = tuple · Column = attribute · #columns = degree · #rows = cardinality

ACID = Atomicity · Consistency · Isolation · Durability

1NF atomic values → 2NF no partial dependency → 3NF no transitive dependency → BCNF determinant = candidate key

Three levels: External (view) — Conceptual (logical) — Internal (physical)

G. Ten Facts They Keep Asking

1. Bitwise OR = `|`; logical OR = `||`.

2. Single-function C program ⇒ that function is `main()`.
3. `--`, `++`, `!`, `~`, `sizeof` are **unary**; `?:` is the only **ternary**.
4. Ternary syntax: `expr1 ? expr2 : expr3`.
5. Loop without an update of the control variable = **infinite loop**.
6. `do-while` executes at least once; `while` / `for` may execute zero times.
7. Missing `break` in switch ⇒ **fallthrough**.
8. String ends in `'\0'`; `strlen` excludes it, `sizeof` includes it.
9. Stack = LIFO (push/pop at top); Queue = FIFO (rear-in, front-out).
10. Inorder traversal of a BST gives **sorted output**; postfix of `(A+B)C` = `AB+C`.

End of Chapter 9. Next: Chapter 10 — Basic Electronics Engineering (as per Annexure-VII C sequencing of your book plan).

Chapter 10 — Basic Electrical Engineering

Syllabus (CEN 05/2025, Annexure-VII C, Unit 10): *DC Circuits; AC fundamentals; Magnetic, Thermal and Chemical effects of Electric current; Earthing — Installation, Maintenance, Testing.*

10.0 Weightage & Trend Box

Item	Detail
Weight in CBT-2	~8% of technical marks (4 of 50 technical Q in the 22-04-2025 Shift-2 paper)
Difficulty	Easy–moderate; mostly conceptual one-liners + light numericals
Special trend	The 2025 paper pulled **protection-relay** questions into this unit — so relays/protection are covered here even though the syllabus line does not name them

Actual questions observed in the 22-04-2025 CBT-2 paper (this unit):

1. **Relay selectivity** → the quality by which a relay operates **only for faults in its own designated (protected) zone** and stays inoperative for faults outside it.
2. **Distance relay** → operates on the **measurement of impedance (ratio V/I)** at the relay location, which is proportional to the distance to the fault.
3. **Magnetic circuit** → for the same MMF, **increased reluctance → decreased flux** (Φ = MMF/S).
4. **Magnetic field** → the **region around a magnet (or current-carrying conductor)** in which its magnetic force can be experienced.

Preparation strategy: master (a) series–parallel + KCL/KVL numericals, (b) RMS/average/form-factor values, (c) RLC impedance & resonance formulas, (d) the electric–magnetic circuit analogy table, (e) relay qualities and one-line working of each relay type, (f) plate/pipe earthing dimensions & permissible earth-resistance values. These six clusters cover essentially every question RRB has asked from this unit.


10.1 DC Circuits

10.1.1 Charge, Current, Voltage, Power, Energy

Quantity	Symbol	Definition	SI Unit
Charge	Q	Deficiency/excess of electrons; Q = It	coulomb (C); 1 C = charge of 6.24×10^{18} electrons
Current	I	Rate of flow of charge, I = dQ/dt	ampere (A) = C/s
Voltage (potential difference)	V	Work done per unit charge, V = W/Q	volt (V) = J/C
EMF	E	Energy given per unit charge by a source	volt (V)
Power	P	Rate of doing work, $P = VI = I^2R = V^2/R$	watt (W) = J/s
Energy	W	W = Pt = VIt	joule (J); commercial unit: 1 kWh = 3.6×10^6 J

- Conventional current flows from + to − outside... no — **outside the source, conventional current flows from + terminal through the external circuit to − terminal**; electron flow is opposite.
- 1 hp = 746 W (British) — frequently asked.

10.1.2 Ohm's Law and Its Limitations

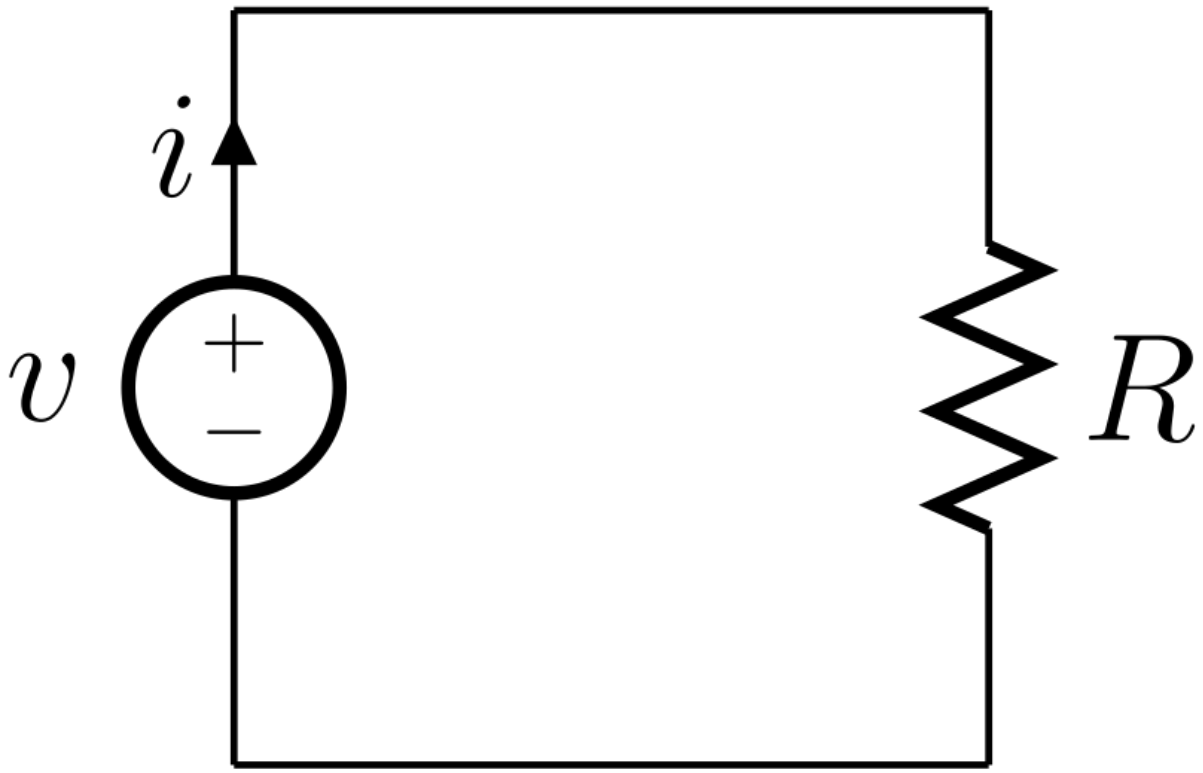

Ohm's-law circuit.

Statement: At constant temperature and other physical conditions, the current through a conductor is directly proportional to the potential difference across it.

> $V = IR \Rightarrow R = V/I$ (ohm, Ω)

Limitations (non-ohmic cases):

- Not valid for **non-linear** devices: diodes, transistors, vacuum tubes, thyristors.
- Not valid for **unilateral** elements (conduct differently in the two directions).
- Not valid when temperature changes appreciably (filament lamp), for arc discharge, electrolytes with gas evolution, semiconductors.

10.1.3 Resistance — Laws, Factors, Temperature Coefficient

Laws of resistance: $R = \rho l/A$

Factor	Effect
Length l	$R \propto l$
Area A	$R \propto 1/A$
Material	via resistivity ρ (Ω·m)
Temperature	metals: R increases; semiconductors/insulators/electrolytes/carbon: R decreases

- Conductance $G = 1/R$ (siemens, S or ℧); conductivity $\sigma = 1/\rho$.
- Resistivity of copper ≈ 1.72×10^{-8} Ω·m; of aluminium ≈ 2.8×10^{-8} Ω·m.

Temperature coefficient of resistance (α):

> $R_2 = R_1[1 + \alpha_1(t_2 - t_1)]$

α_0 for copper ≈ 0.00427 /°C at 0 °C (≈ 1/234.5). Also $\alpha_2 = \alpha_1 / [1 + \alpha_1(t_2 - t_1)]$ and $\alpha_1 = \alpha_0/(1 + \alpha_0 t_1)$.

- α positive → metals; α negative → carbon, semiconductors, insulators, electrolytes.
- Alloys (manganin, constantan, eureka) have α ≈ 0 → used for standard resistors and shunts.

Worked Example 1. A copper coil has resistance 40 Ω at 20 °C. Find its resistance at 60 °C. (α at 20 °C = 0.004 /°C)

$R_{60} = R_{20}[1 + \alpha(60 - 20)] = 40[1 + 0.004 \times 40] = 40 \times 1.16 =$ **46.4 Ω**

Worked Example 2. A filament's resistance at 0 °C is 100 Ω, $\alpha_0 = 0.005$/°C. At what temperature is the resistance 150 Ω?

$150 = 100(1 + 0.005\ t) \Rightarrow 0.005\ t = 0.5 \Rightarrow$ **t = 100 °C**

10.1.4 Series, Parallel and Series–Parallel Networks

Property	Series	Parallel
Equivalent R	$R = R_1 + R_2 + \ldots$	$1/R = 1/R_1 + 1/R_2 + \ldots$
Same quantity	Current	Voltage
Divides	Voltage ($\propto R$)	Current ($\propto 1/R$)
Two resistors	$R_1 + R_2$	$R_1R_2/(R_1 + R_2)$ (product/sum)
n equal resistors r	nr	r/n

- n equal resistors: (series value)/(parallel value) = n^2.
- Adding resistance in parallel always **reduces** the equivalent below the smallest branch.

Voltage divider (two resistors in series across V):

> $V_1 = V \cdot R_1/(R_1 + R_2)$, $V_2 = V \cdot R_2/(R_1 + R_2)$

Current divider (two resistors in parallel fed by I):

> $I_1 = I \cdot R_2/(R_1 + R_2)$, $I_2 = I \cdot R_1/(R_1 + R_2)$ (current takes the *other* branch's resistance in the numerator)

Worked Example 3. Three resistors 2 Ω, 3 Ω and 6 Ω are in parallel, and this combination is in series with 4 Ω across a 12 V battery. Find the battery current and the voltage across the parallel group.

$1/R_p = 1/2 + 1/3 + 1/6 = 1 \Rightarrow R_p = 1\ \Omega$. Total $R = 4 + 1 = 5\ \Omega$.

$I = 12/5 =$ **2.4 A**. Voltage across parallel group $= 2.4 \times 1 =$ **2.4 V**.

Worked Example 4 (current divider). A 10 A current divides between 6 Ω and 4 Ω in parallel.

$I_6 = 10 \times 4/(6+4) =$ **4 A**; $I_4 = 10 \times 6/10 =$ **6 A**. (Larger current through smaller resistance.)

10.1.5 Kirchhoff's Laws

KCL (Kirchhoff's Current Law / point law): The algebraic sum of currents meeting at a junction is zero — $\Sigma I = 0$ (based on **conservation of charge**). Currents in = currents out.

KVL (Kirchhoff's Voltage Law / mesh law): Around any closed loop, the algebraic sum of EMFs equals the algebraic sum of IR drops — $\Sigma E = \Sigma IR$ (based on **conservation of energy**).

Sign convention: going through a resistor **in the direction of current** → voltage drop (−IR); through a source from − to + → rise (+E).

Worked Example 5 (two-mesh problem). Two batteries $E_1 = 12$ V (internal $r_1 = 1\ \Omega$) and $E_2 = 8$ V ($r_2 = 1\ \Omega$) are connected in parallel, feeding a load $R = 6\ \Omega$. Find the load current.

Let I_1, I_2 be battery currents; load current $I = I_1 + I_2$, load voltage V.

Loop 1: $12 = 1 \cdot I_1 + 6(I_1 + I_2)$

Loop 2: $8 = 1 \cdot I_2 + 6(I_1 + I_2)$


$\Rightarrow 7I_1 + 6I_2 = 12$ … (i); $6I_1 + 7I_2 = 8$ … (ii)

(i)×7 − (ii)×6: $49I_1 + 42I_2 - 36I_1 - 42I_2 = 84 - 48 \Rightarrow 13I_1 = 36 \Rightarrow I_1 = 2.769$ A

From (i): $6I_2 = 12 - 19.385 = -7.385 \Rightarrow I_2 = -1.231$ A (E_2 is being charged).

Load current I = 2.769 − 1.231 = **1.538 A**; load voltage = 6 × 1.538 = **9.23 V**.

10.1.6 Star–Delta (Y–Δ) Transformation

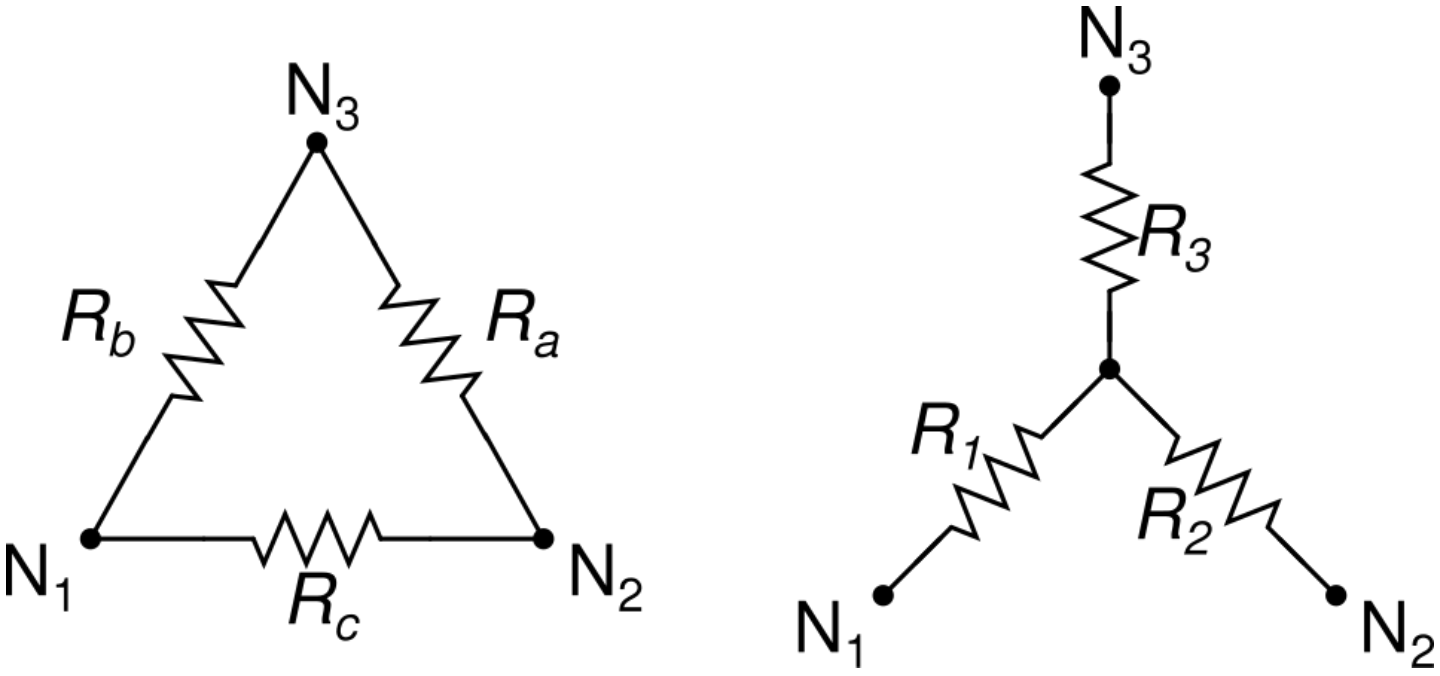

Star (Y) and delta (Δ) connections.

Delta → Star (each star arm = product of the two delta sides meeting at that terminal ÷ sum of all three):

> $R_1 = R_{12}R_{31}/(R_{12} + R_{23} + R_{31})$, and cyclically for R_2, R_3.

Star → Delta (each delta side = sum of the two star arms it connects + their product ÷ third arm):

> $R_{12} = R_1 + R_2 + R_1R_2/R_3$, and cyclically.

- If all three delta resistors are R, each star resistor = **R/3**. If all star resistors are R, each delta resistor = **3R**.

Worked Example 6. A delta has 6 Ω, 6 Ω, 6 Ω. Equivalent star arm = 6×6/(6+6+6) = 36/18 = **2 Ω** (= 6/3 ✓).

Worked Example 7. Star arms R_1 = 2 Ω, R_2 = 3 Ω, R_3 = 6 Ω. Find delta side between terminals 1 and 2.

R_{12} = 2 + 3 + (2×3)/6 = 5 + 1 = **6 Ω**. (Similarly R_{23} = 3 + 6 + 18/2 = 18 Ω; R_{31} = 6 + 2 + 12/3 = 12 Ω.)

10.1.7 Network Theorems

Superposition theorem. In a linear network with several sources, the current in any element = algebraic sum of currents produced by each source acting alone, other **voltage sources replaced by short circuits** and **current sources by open circuits** (internal resistances retained). Valid only for **linear** networks; not applicable to power (power is non-linear in I).

Thevenin's theorem. Any linear two-terminal network can be replaced by a single voltage source V_Th (open-circuit voltage at the terminals) in series with R_Th (resistance seen from the terminals with all internal sources killed).

> I_load = V_Th / (R_Th + R_L)

Norton's theorem. The same network can be replaced by a current source I_N (short-circuit current at the terminals) in parallel with R_N (= R_Th). Duality: V_Th = I_N R_N.

Maximum Power Transfer theorem. Maximum power is delivered to the load when **R_L = R_Th** (DC) or **Z_L = Z_Th*** (complex conjugate, AC).

> P_max = $V_{Th}^2/(4R_{Th})$; efficiency at maximum power transfer = **50%**.

Worked Example 8 (Thevenin). A 10 V source with 2 Ω internal resistance feeds a 3 Ω resistor; a load R_L = 5 Ω is connected across the 3 Ω. Find load current by Thevenin.

Remove R_L. V_Th = voltage across 3 Ω = 10 × 3/(2+3) = 6 V.

R_Th = 3 ∥ 2 = 1.2 Ω.

I_L = 6/(1.2 + 5) = 6/6.2 = **0.968 A**.

Worked Example 9 (Maximum power). For the same Thevenin equivalent (V_Th = 6 V, R_Th = 1.2 Ω), maximum power to a matched load:

R_L = 1.2 Ω; $P_{max} = 6^2/(4 \times 1.2) = 36/4.8 =$ **7.5 W**.

Worked Example 10 (Norton). For Example 8's network: I_N = short-circuit current = V_Th/R_Th = 6/1.2 = **5 A**, R_N = 1.2 Ω. Load current = I_N × R_N/(R_N + R_L) = 5 × 1.2/6.2 = 0.968 A ✓ (matches Thevenin).

Worked Example 11 (Superposition). Two sources: 10 V in series with 2 Ω on the left, 5 V in series with 3 Ω on the right, both feeding a common 6 Ω load between the junction and the bottom rail. Find load current.

10 V alone (5 V shorted): R seen by 10 V = 2 + (3∥6) = 2 + 2 = 4 Ω; source current = 2.5 A; load current I′ = 2.5 × 3/(3+6) = 0.833 A (downward).

5 V alone (10 V shorted): R = 3 + (2∥6) = 3 + 1.5 = 4.5 Ω; source current = 1.111 A; load current I″ = 1.111 × 2/(2+6) = 0.278 A (downward).

Total load current = 0.833 + 0.278 = **1.111 A** (≈ 10/9 A).

10.2 AC Fundamentals

10.2.1 Generation of Sinusoidal EMF

A coil rotating with angular velocity ω in a uniform magnetic field B has flux linkage NΦ_m cos ωt, so induced EMF:

> e = E_m sin ωt, where E_m = NBAω (N turns, area A)

- One full rotation of the coil in a 2-pole field = one cycle.
- Frequency of alternator: **f = PN/120** (P = poles, N = rpm). In India, supply frequency = **50 Hz**, standard domestic voltage 230 V (RMS).

10.2.2 Waveform Terms

Term	Meaning
Cycle	One complete set of positive + negative alternations
Time period T	Time for one cycle; T = 1/f
Frequency f	Cycles per second (hertz, Hz)
Amplitude (peak value) E_m	Maximum value attained
Instantaneous value	Value at a particular instant, $e = E_m \sin \omega t$
Angular frequency ω	$\omega = 2\pi f$ rad/s (at 50 Hz, ω = 314 rad/s)
Phase	Angular position within the cycle; phase difference = angle between two waveforms

10.2.3 Average and RMS Values (Sine Wave Derivations)

Average value (over half cycle, since full-cycle average of a sine = 0):

> $I_{av} = (1/\pi) \int_0^{\pi} I_m \sin \theta \, d\theta = (I_m/\pi)[-\cos \theta]_0^{\pi} = 2I_m/\pi =$ **$0.637\, I_m$**

RMS (effective) value — that steady DC which produces the same heating:

> $I_{rms} = \sqrt{[(1/2\pi) \int_0^{2\pi} I_m^2 \sin^2\theta \, d\theta]} = I_m/\sqrt{2} =$ **$0.707\, I_m$**

Form factor = RMS/Average = 0.707/0.637 = **1.11** (sine).

Peak (crest) factor = Peak/RMS = √2 = **1.414** (sine).

Waveform	RMS	Average	Form factor	Peak factor
Sine	$I_m/\sqrt{2}$	$2I_m/\pi$	1.11	1.414
Square	I_m	I_m	1.0	1.0
Triangular	$I_m/\sqrt{3}$	$I_m/2$	1.155	1.732
Half-wave rectified sine	$I_m/2$	I_m/π	1.57	2.0
Full-wave rectified sine	$I_m/\sqrt{2}$	$2I_m/\pi$	1.11	1.414

- Moving-iron / hot-wire instruments read **RMS**; PMMC reads **average (zero for pure AC)**; rectifier instruments are calibrated in RMS assuming sine (form factor 1.11).

Worked Example 12. A sinusoidal voltage is v = 311 sin 314t. Find RMS value, frequency and time period.

$V_{rms} = 311/\sqrt{2} \approx$ **220 V**; $\omega = 314 \Rightarrow f = 314/2\pi =$ **50 Hz**; $T = 1/50 =$ **20 ms**.

10.2.4 Phasors

A phasor is a rotating line whose length = peak (or RMS) value and whose angular velocity = ω; its projection generates the sine wave. Phasors let us add/subtract sinusoids of the **same frequency** as vectors. j-operator: multiplication by j = 90° anticlockwise rotation; $j^2 = -1$.

10.2.5 Pure R, L, C in AC Circuits

Element	Voltage–current phase	Opposition	Power
R	In phase ($\varphi = 0$)	R (independent of f)	$P = VI = I^2R$
L	Current **lags** voltage by 90°	$X_L = \omega L = 2\pi fL$ ($\propto f$)	Average power = 0
C	Current **leads** voltage by 90°	$X_C = 1/\omega C = 1/(2\pi fC)$ ($\propto 1/f$)	Average power = 0

Mnemonic: **CIVIL** — in C, I leads V; V leads I in L.

- At DC (f = 0): inductor = short circuit, capacitor = open circuit.
- At very high frequency: inductor → open, capacitor → short.

10.2.6 RL, RC, RLC Series Circuits

Impedance Z (Ω) is the total opposition; phasor sum of R and net reactance.

Circuit	Impedance	Phase angle φ	Nature
R–L series	$Z = \sqrt{(R^2 + X_L^2)}$	$\tan\varphi = X_L/R$ (current lags)	Lagging pf
R–C series	$Z = \sqrt{(R^2 + X_C^2)}$	$\tan\varphi = X_C/R$ (current leads)	Leading pf
R–L–C series	$Z = \sqrt{[R^2 + (X_L - X_C)^2]}$	$\tan\varphi = (X_L - X_C)/R$	Lags if $X_L > X_C$; leads if $X_C > X_L$

Voltage triangle: $V = \sqrt{(V_R^2 + (V_L - V_C)^2)}$. Power factor **$\cos\varphi = R/Z = V_R/V = P/S$**.

Worked Example 13. A coil of R = 6 Ω, L = 25.5 mH is connected to 230 V, 50 Hz. Find current, power factor and power.

$X_L = 2\pi \times 50 \times 0.0255 \approx 8\ \Omega$. $Z = \sqrt{(6^2 + 8^2)} = 10\ \Omega$.

$I = 230/10 =$ **23 A**; $\cos\varphi = 6/10 =$ **0.6 lagging**; $P = VI\cos\varphi = 230 \times 23 \times 0.6 =$ **3174 W** ($= I^2R = 23^2 \times 6$ ✓).

Worked Example 14 (RLC series). R = 10 Ω, X_L = 30 Ω, X_C = 20 Ω on 200 V supply.

$Z = \sqrt{(10^2 + (30-20)^2)} = \sqrt{200} = 14.14\ \Omega$; $I = 200/14.14 =$ **14.14 A**;

$\varphi = \tan^{-1}(10/10) =$ **45° lagging**; $P = I^2R = 200 \times 10 / 200 \rightarrow I^2R = (14.14)^2 \times 10 =$ **2000 W**.

10.2.7 Power in AC Circuits — Power Triangle

Power	Formula	Unit
Active (true/real) P	$VI\cos\varphi = I^2R$	watt (W)
Reactive Q	$VI\sin\varphi = I^2X$	volt-ampere reactive (VAR)
Apparent S	$VI = I^2Z$	volt-ampere (VA)

> $S^2 = P^2 + Q^2$; power factor $\cos\varphi = P/S$.

- Power factor range 0 (pure L or C) to 1 (pure R). Low pf ⇒ higher current for same P ⇒ larger losses, poorer regulation, bigger equipment. Improvement: **static capacitors** in parallel (also synchronous condensers, phase advancers).
- Wattmeter reads P; energy meter reads kWh.

10.2.8 Resonance

Series resonance (acceptor circuit): $X_L = X_C \Rightarrow$

> $f_r = 1/(2\pi\sqrt{(LC)})$

At resonance: Z = R (minimum), I = V/R (maximum), pf = 1, $V_L = V_C$ (may far exceed supply voltage — voltage magnification).

Quality factor: $Q = X_L/R = \omega L/R = (1/R)\sqrt{(L/C)} = f_r/BW$ = voltage across L (or C) ÷ supply voltage.

Bandwidth: $BW = f_2 - f_1 = f_r/Q = R/(2\pi L)$; half-power points where I = 0.707 I_{max}.

Parallel resonance (rejector / tank circuit): coil (R, L) parallel with C:

> $f_r = (1/2\pi)\sqrt{(1/LC - R^2/L^2)} \approx 1/(2\pi\sqrt{(LC)})$ for small R

At resonance: impedance is **maximum** = dynamic impedance **$Z_d = L/CR$** (purely resistive), line current **minimum**, pf = 1; large circulating current between L and C — hence "tank circuit" (stores oscillating energy; used in oscillators, tuning).

Worked Example 15. A series circuit has R = 10 Ω, L = 100 mH, C = 10 μF. Find f_r, Q and bandwidth.

$f_r = 1/(2\pi\sqrt{(0.1 \times 10^{-5})}) = 1/(2\pi \times 10^{-3}) \approx$ **159.2 Hz**.

$Q = (1/R)\sqrt{(L/C)} = (1/10)\sqrt{(0.1/10^{-5})} = (1/10)(100) =$ **10**.

$BW = f_r/Q = 159.2/10 \approx$ **15.9 Hz**.

10.2.9 Three-Phase Basics

Three EMFs equal in magnitude, displaced **120°** apart. Advantages over 1-φ: more power per kg of conductor, constant total power, self-starting motors, rotating magnetic field.

Connection	Line–phase voltage	Line–phase current
Star (Y)	$V_L = \sqrt{3}\ V_{ph}$	$I_L = I_{ph}$
Delta (Δ)	$V_L = V_{ph}$	$I_L = \sqrt{3}\ I_{ph}$

> 3-φ power: $P = \sqrt{3}\ V_L\ I_L \cos\varphi = 3\ V_{ph}\ I_{ph} \cos\varphi$ (both connections)

- Star gives a **neutral** point → 3-phase 4-wire, two voltages available (e.g., 400 V line / 230 V phase; $400/\sqrt{3} = 230$).
- Phase sequence R-Y-B; reversing any two lines reverses a 3-φ motor.
- In balanced star, neutral current = 0.

Worked Example 16. A balanced 3-φ star load draws 10 A per phase at 0.8 pf from a 400 V (line) supply. Power?

$P = \sqrt{3} \times 400 \times 10 \times 0.8 \approx$ **5542 W ≈ 5.54 kW**.

10.3 Magnetic Effect of Electric Current

10.3.1 Magnetic Field — Concept ★ (asked 2025)

Magnetic field: the region (space) around a magnet or a current-carrying conductor in which its magnetic force (effect) can be experienced by another magnet, magnetic material or moving charge. Represented by lines of force (flux lines): closed loops, N → S outside the magnet, S → N inside, never intersect, mutually repel laterally, seek the path of least reluctance.

Key quantities:

Quantity	Symbol	Unit
Magnetic flux	Φ	weber (Wb)
Flux density	$B = \Phi/A$	tesla (T) = Wb/m^2
Field strength / magnetising force	$H = NI/l$	A/m (ampere-turn per metre)
Permeability	$\mu = B/H = \mu_0\mu_r$	H/m; $\mu_0 = 4\pi \times 10^{-7}$ H/m

10.3.2 Field of Conductor, Loop, Solenoid — Rules

- **Straight conductor:** concentric circular lines; $B = \mu_0 I/(2\pi d)$. Direction by **right-hand thumb rule** (thumb = current, curled fingers = field) or Maxwell's corkscrew rule.
- **Circular loop:** at centre $B = \mu_0 I/(2r)$; N-turn coil: $B = \mu_0 NI/(2r)$. Face with anticlockwise current behaves as N-pole.
- **Solenoid:** field like a bar magnet; inside $B = \mu_0 nI$ (n = turns/metre). Grip rule: fingers = current direction, thumb = N-pole.

10.3.3 Force on a Conductor; Fleming's Rules

Force on a current-carrying conductor in a field:

> $F = BIl \sin\theta$ (newton); maximum when conductor $\perp$ field ($\theta = 90°$), zero when parallel

Force on a moving charge: $F = qvB \sin\theta$ (Lorentz force, magnetic part).

Two parallel conductors: **same-direction currents attract, opposite repel**; force/metre = $\mu_0 I_1 I_2/(2\pi d)$ — basis of the ampere's classical definition.

- **Fleming's LEFT-hand rule** → **motor** action (First finger = Field, seCond = Current, thuMb = Motion/force).
- **Fleming's RIGHT-hand rule** → **generator** (induced EMF direction).

10.3.4 Magnetic Circuits ★ (asked 2025)

A magnetic circuit is the closed path followed by magnetic flux, analogous to an electric circuit:

Electric circuit	Magnetic circuit
EMF, E (V)	MMF, $F = NI$ (ampere-turns, AT)
Current, I (A)	Flux, Φ (Wb)
Resistance, $R = \rho l/A$	Reluctance, $S = l/(\mu_0\mu_r A)$ (AT/Wb)
Conductance G	Permeance = 1/S (Wb/AT)
Conductivity σ	Permeability μ
Current density J	Flux density B
$I = E/R$	**$\Phi = MMF/S = NI/S$**
Energy is continuously dissipated	No energy dissipated in maintaining flux
Current actually flows	Flux does not "flow"; it is established

> **Φ = MMF / Reluctance** — hence for the same MMF, **if reluctance increases, flux decreases** (inverse proportion). *(Direct 2025 PYQ.)*

Series magnetic circuit: $S_{total} = S_1 + S_2 + \ldots$ (add reluctances, e.g., iron path + air gap; the air gap usually dominates since $\mu_r(air) = 1$). Parallel paths: permeances add.

Worked Example 17. An iron ring of mean length 50 cm, cross-section 4 cm^2, μ_r = 1000, is wound with 200 turns carrying 2 A. Find reluctance and flux.

$S = l/(\mu_0 \mu_r A) = 0.5 / (4\pi \times 10^{-7} \times 1000 \times 4 \times 10^{-4}) = 0.5 / (5.0265 \times 10^{-7}) \approx$ **9.95×10^5 AT/Wb**.

MMF = 200 × 2 = 400 AT. $\Phi = 400 / 9.95 \times 10^5 \approx$ **4.02×10^{-4} Wb = 0.402 mWb**.

(If a 1 mm air gap were cut, $S_{gap} = 0.001/(4\pi \times 10^{-7} \times 4 \times 10^{-4}) \approx 1.99 \times 10^6$ AT/Wb — twice the iron's reluctance — flux would fall to ≈ 0.134 mWb: increased reluctance → decreased flux.)

10.3.5 B–H Curve and Hysteresis

- **B–H (magnetisation) curve:** initially steep (easy domain alignment), then knee, then **saturation** (B nearly constant despite rising H). μ is not constant for ferromagnetics.
- **Hysteresis:** B lags behind H when a magnetic material is cyclically magnetised. Loop intercepts: **residual magnetism / retentivity** (B at H = 0) and **coercive force / coercivity** (reverse H needed to make B = 0).
- **Hysteresis loss** ∝ loop area; Steinmetz: $P_h = \eta B_{max}^{1.6} f V$ (watts).
- **Hard** magnetic materials (large loop — steel, Alnico): permanent magnets. **Soft** (thin loop — silicon steel, soft iron, ferrites): transformer/machine cores. **Eddy-current loss** $P_e \propto B_{max}^2 f^2 t^2$ — reduced by **laminating** the core.

10.3.6 Electromagnetic Induction

Faraday's laws:

1. Whenever the flux linking a circuit changes, an EMF is induced (lasts only while the change lasts).
2. Magnitude of induced EMF = rate of change of flux linkages:

> $e = -N \, d\Phi/dt$

Lenz's law: the induced EMF/current always **opposes the cause** producing it (the minus sign) — a consequence of conservation of energy.

Dynamically induced EMF — conductor moves relative to the field: $e = Blv \sin\theta$ (generators). **Statically induced EMF** — conductor stationary, flux changes (transformers):

- *Self-induced:* in the same coil, $e = -L \, di/dt$.
- *Mutually induced:* in a neighbouring coil, $e = -M \, di/dt$.

Self-inductance: $L = N\Phi/I = N^2/S = \mu_0 \mu_r N^2 A/l$ (henry). A circuit has L = 1 H if 1 A/s change induces 1 V.

Mutual inductance: $M = N_2\Phi_{12}/I_1$; **coefficient of coupling**

> $k = M/\sqrt{(L_1 L_2)}$, $0 \le k \le 1$ (k = 1: perfect coupling; k small: loosely coupled)

Series combination of coupled coils: $L = L_1 + L_2 \pm 2M$ (+ aiding, − opposing).

Energy stored in inductor: $W = \frac{1}{2}LI^2$ (in the magnetic field); in capacitor: $W = \frac{1}{2}CV^2$ (electric field). Energy density of magnetic field = $B^2/2\mu$.

Worked Example 18. The flux linking a 200-turn coil changes from 4 mWb to 1 mWb in 0.1 s. Induced EMF?

$e = N \Delta\Phi/\Delta t = 200 \times (3 \times 10^{-3})/0.1 =$ **6 V**.

Worked Example 19. Two coils L_1 = 8 H, L_2 = 2 H have M = 3 H. Coefficient of coupling?

$k = 3/\sqrt{(8 \times 2)} = 3/4 =$ **0.75**.

10.4 Thermal Effect of Electric Current

10.4.1 Joule's Law of Heating

When current I flows through resistance R for time t:

> $H = I^2Rt$ joules $= I^2Rt/4.186 \approx 0.24\ I^2Rt$ calories

Heat $\propto I^2$, $\propto R$, $\propto t$. This is why the effect is called **Joule heating / ohmic heating**; it is **irreversible** and independent of current direction (unlike Peltier effect).

Worked Example 20. A 230 V, 1 kW heater runs for 30 minutes. Heat produced and energy consumed?

Energy = $Pt = 1000 \times 1800 = 1.8 \times 10^6$ J = **1800 kJ = 0.5 kWh (unit)**.

Element resistance $R = V^2/P = 230^2/1000$ = **52.9 Ω**.

10.4.2 Applications of Heating Effect

Application	Key points
Electric heater / iron / geyser	**Nichrome** element — high resistivity, high melting point, doesn't oxidise
Incandescent lamp	**Tungsten** filament (m.p. ≈ 3400 °C), argon/nitrogen filling to retard evaporation; only ~5–10% of energy → light
Electric welding, furnaces	Arc/resistance heating
Fuse	Protective device — melts and breaks the circuit on overload/short circuit

10.4.3 Fuses — Ratings & Fusing Factor

- Fuse wire: low melting point, adequate conductivity — usually **tin–lead alloy** (63% Sn/37% Pb) or tinned copper for small ratings; placed **in series** with the **live (phase)** wire, never in neutral or earth.
- **Current rating** — maximum current the fuse carries continuously without melting.
- **Fusing current** — minimum current at which it melts.

> **Fusing factor = minimum fusing current / current rating** (always > 1; rewirable ≈ 1.4–2)

- Fusing current for round wire (Preece): I_f = k d^{3/2} (d = wire diameter).
- HRC (high rupturing capacity) fuse: cartridge with silver element in quartz-sand filling — high breaking capacity, no ageing, accurate; drawback: must be replaced after operation, cost.
- Fuse protects against **short circuit / sustained overload**; it cannot protect a person against shock (too slow, too high threshold) — that is the job of ELCB/RCCB (§10.7.9).

10.5 Chemical Effect of Electric Current

10.5.1 Electrolysis

Passage of direct current through an **electrolyte** (acid/base/salt solution or molten salt) decomposes it — **electrolysis**. Current in electrolytes is carried by **ions**: cations (+) migrate to the **cathode** (− electrode), anions (−) to the **anode** (+). The vessel + electrodes + electrolyte = voltameter (electrolytic cell). Electrolysis requires **DC** (AC would merely reverse deposition each half cycle).

10.5.2 Faraday's Laws of Electrolysis

First law: mass liberated at an electrode ∝ quantity of charge passed:

> m = Z I t (Z = electrochemical equivalent, kg/C; ECE of Cu ≈ 0.3294 mg/C, of Ag ≈ 1.118 mg/C)

Second law: for the same charge through different electrolytes, masses liberated ∝ their **chemical equivalent weights** (E = atomic weight / valency); $m_1/m_2 = E_1/E_2$.

> One faraday, F ≈ 96 500 C, deposits one gram-equivalent; Z = E/F.

Worked Example 21. How much copper is deposited when 10 A flows for 30 minutes? (Z_Cu = 0.3294 mg/C)

m = ZIt = 0.3294×10^{-3} g/C × 10 × 1800 = 0.3294 × 18 = **5.93 g**.

Worked Example 22. Time to deposit 2.68 g of silver with 2 A? (Z_Ag = 1.118 mg/C)

t = m/(ZI) = 2.68 / (1.118×10^{-3} × 2) = 2.68/0.002236 ≈ 1198.6 s ≈ **20 minutes**.

10.5.3 Electroplating & Other Applications

- **Electroplating:** article to be plated = **cathode**; plating metal = **anode**; electrolyte = salt of the plating metal (e.g., $CuSO_4$ for copper, $AgNO_3$/double cyanide for silver). Purpose: corrosion protection, appearance, wear resistance.
- **Electro-refining** of metals (impure Cu anode → pure Cu cathode), **electrotyping**, **anodising** (protective oxide on aluminium — here Al is the anode), **electro-extraction** of Al/Na/Mg, manufacture of chemicals (caustic soda, chlorine).

10.5.4 Cells and Batteries

Type	Examples	Note
Primary (not rechargeable)	Dry Leclanché cell (Zn–C, EMF ≈ 1.5 V), mercury cell (1.35 V)	Chemical action irreversible
Secondary (rechargeable/storage)	**Lead–acid** (2 V/cell), Ni–Cd (1.2 V), Ni–Fe, Li-ion (3.6–3.7 V)	Action reversible; charged by DC

Lead–acid cell essentials: positive plate PbO_2 (chocolate brown), negative plate spongy Pb (grey), electrolyte dilute H_2SO_4. On **discharge**, both plates → $PbSO_4$ and acid becomes weaker (specific gravity falls from ≈ 1.28 to ≈ 1.18); charging reverses this. State of charge is best checked with a **hydrometer** (specific gravity). Capacity in **ampere-hours (Ah)**; efficiency: Ah efficiency ≈ 90%, Wh efficiency ≈ 75%. Cells in series → voltages add (same Ah); in parallel → capacities add.

- **Battery ratings/terms:** trickle charging (continuous small charge to offset self-discharge), sulphation (hard $PbSO_4$ from leaving the cell discharged — reduces capacity), gassing near full charge (H_2 + O_2 — keep flames away, ventilate).

10.6 Protection & Relays ★ (asked 2025)

(The 2025 CBT-2 asked two relay questions under this unit, so this section is exam-critical.)

10.6.1 Purpose of Protection

Power-system protection detects abnormal conditions (short circuits, earth faults, overloads) and **isolates only the faulty section** quickly, so that: equipment damage is limited, system stability is preserved, healthy sections keep supplying, and personnel are safe. Basic chain: **CT/PT (sense) → relay (decide) → circuit breaker (act)**. The relay is the *brain*, the breaker the *muscle*.

10.6.2 Desirable Qualities of Protective Relaying ★

Quality	Definition
Selectivity (discrimination) ★	Ability of the protection to **operate only for faults within its own designated (protected) zone** and to remain stable (inoperative) for faults outside that zone or for normal load conditions — only the faulty element is tripped, the rest of the system stays in service. *(Direct 2025 PYQ.)*
Sensitivity	Ability to operate for the **smallest** value of actuating quantity (minimum fault current) it is required to respond to
Speed	Fast operation to limit damage and maintain stability (fault clearing time = relay time + breaker time)
Reliability	Assurance that it will operate when required (dependability) and not operate when not required (security)
Simplicity & economy	Minimum equipment/complexity for the protection required

Backup protection operates if the primary protection fails — with an intentional **time delay** for coordination (time grading), which is itself a method of achieving selectivity (time grading, current grading, unit/differential protection).

10.6.3 Relay Types — One-Line Working

Relay	Actuating principle
Overcurrent	Operates when current exceeds a pick-up value. Characteristics: instantaneous, definite-time, IDMT (inverse definite minimum time — most common for feeders)
Directional	Responds to fault power flow in one specified direction only
Differential	Compares currents entering and leaving the protected equipment; operates when the **vector difference** exceeds a set value — a **unit protection** (inherently selective), standard for transformers/generators/busbars (Merz-Price scheme)
Distance (impedance) relay ★	**Measures the ratio V/I = impedance** at the relay point; since line impedance is proportional to length, the measured Z is **proportional to the distance to the fault** — relay operates when Z seen < set value (fault inside reach). Used for transmission-line protection in stepped zones (Zone 1 ≈ 80% instantaneous, Zone 2, Zone 3 time-delayed). Variants: impedance (circle on R–X diagram), **reactance**, and **mho** (admittance — inherently directional, circle through origin). *(Direct 2025 PYQ.)*
Buchholz relay	**Gas-actuated** relay in the pipe between a transformer's tank and conservator; slow gas evolution from incipient faults tilts the upper float → **alarm**; violent oil surge from severe internal faults strikes the lower flap → **trip**. Only for **oil-immersed transformers with conservator** (typically > 500 kVA).
Thermal relay	Bimetallic element heated by load current — overload protection of motors
Earth-fault relay	Operates on residual (zero-sequence) current during earth faults

10.6.4 Fuses vs Relays (+ Breaker)

Aspect	Fuse	Relay + circuit breaker
Function	Detects **and** interrupts itself	Relay detects; breaker interrupts
After operation	Element destroyed — replace/rewire	Simply reclose the breaker
Characteristic	Fixed inverse (melting)	Adjustable settings & time grading
Cost / use	Cheap — LV circuits, domestic	Costly — MV/HV systems, precise coordination
Speed on heavy short circuit	Extremely fast (current-limiting HRC)	Relay + breaker time (a few cycles)

10.7 Earthing — Installation, Maintenance, Testing

10.7.1 Purpose of Earthing

Connecting non-current-carrying metal parts (motor frames, appliance bodies, conduit, poles) and/or system neutral to the general mass of earth through a low-resistance path so that:

- Leakage/fault current flows safely to earth, keeping exposed metal at (nearly) earth potential → **protects persons from shock**;
- The large earth-fault current promptly operates fuses/relays/ELCB → **automatic disconnection**;
- Voltages are stabilised (neutral earthing), lightning/static discharges are safely dissipated;
- Equipment and buildings are protected from damage/fire.

Two categories: **system (neutral) earthing** — earthing the supply neutral; **equipment earthing** — earthing metallic bodies.

10.7.2 Definitions (per IS 3043 usage)

Term	Definition
Earth	The general mass of earth, taken as zero (reference) potential
Earthing (grounding)	Connecting a part to earth via conductors of negligible impedance
Earth electrode	Metal plate/pipe/rod embedded in soil making effective contact with earth
Earth continuity conductor (ECC)	The conductor connecting equipment bodies/socket earth terminals to the earthing lead — must be continuous, low resistance (its resistance from any point to the electrode should not exceed 1 Ω)
Earthing lead	The final conductor joining the earth electrode to the ECC/earth bus
Earth resistance	Total resistance between the electrode and the general mass of earth (electrode + contact + surrounding-soil resistance; the soil immediately around the electrode contributes most)

10.7.3 Plate Earthing (IS 3043)

- **Electrode:** GI (galvanised iron) plate **60 cm × 60 cm × 6.3 mm**, or **copper plate 60 cm × 60 cm × 3.15 mm**, buried **vertically** with its top not less than **3 m below ground level** (i.e., at ≈ 3 m depth), preferably in moist soil.
- The pit around the plate is filled with **alternate layers of charcoal and common salt** (each ≈ 15 cm)— charcoal retains moisture and salt lowers soil resistivity, both reducing earth resistance.

- Earthing lead (GI wire/strip, or copper with copper plate) is bolted/welded to the plate with nut-bolt-washer of the same metal and runs to ground level inside a **GI pipe** (typically 12.7 mm) for mechanical protection.
- A **funnel with wire mesh** connected to a ≈ 19 mm watering pipe is provided at the top; the arrangement is covered by a **cement-concrete inspection chamber (≈ 30 cm × 30 cm) with a cast-iron cover** for watering and periodic inspection.
- Used where soil is such that greater electrode area is needed (rock strata prevented deep pipes) and for high-capacity installations (substations, generating stations). Costlier; drying of deep soil is a drawback if not watered.

10.7.4 Pipe Earthing (most common)

- **Electrode:** GI pipe of **38 mm (≈ 40 mm) internal diameter, 2.5 m (≈ 2.0–2.5 m) length**, with the pipe placed **vertically** in a permanently wet soil layer; overall pit depth ≈ 3.75 m (per traditional practice / older IE-rule figures). The lower portion of the pipe is **perforated (holes ~12 mm)** to keep contact with moist surrounding soil.
- Surrounded, like plate earthing, by **alternate 15 cm layers of charcoal and salt** for the lowest ~2 m.
- A **19 mm funnel** with mesh at the top receives water (3–4 buckets in dry season); earth wire is clamped to the pipe top with a through-bolt and taken out in a 12.7 mm GI protection pipe; a masonry inspection chamber with CI cover finishes the top.
- Cheapest and most common method for domestic/small installations; can carry larger leakage current than an equivalent plate (larger effective surface in moist strata).

10.7.5 Rod and Strip Earthing; Other Methods

- **Rod earthing:** 12.5–16 mm dia copper rod or 16–25 mm GI/steel rod, ≥ 2.5 m long, **driven vertically** into the ground (hammered/screwed, extensible sections for deeper moisture). Cheapest — no excavation; suits sandy soil.
- **Strip/wire earthing:** GI strip (≥ 25 mm × 1.6 mm) or copper strip (25 mm × 1.6 mm) / round conductor buried **horizontally** in trenches ≥ 0.5 m deep, total length ≥ 15 m; used in **rocky terrain** where deep driving is impossible; used at transmission-line towers (counterpoise earthing).
- **Earthing through water mains** (older practice — now avoided due to non-metallic pipe sections).

10.7.6 Earthing of Installations and Appliances

- All medium-voltage (230/400 V) installations: metal parts earthed by **two separate and distinct earth connections** for transformer neutrals and important equipment (redundancy).
- 3-pin plugs/sockets: the **larger, longer top pin = earth**; appliance body wired to it via the 3-core flexible cord's green/yellow-green core.
- Conduits, switchboards, motor frames, fan hooks (via 2 earthing points for motors above certain rating), water heaters etc. all bonded to the ECC.
- **Earth wire size:** ECC not less than half the cross-section of the largest current-carrying conductor (subject to a minimum, e.g., 14 SWG copper); never less than 2.9 mm^2 (traditional rule-of-thumb; exact sizes per IS 3043 tables).
- The **neutral must never be used as earth** for appliance bodies (a broken neutral would make every body live at full phase voltage).

10.7.7 Permissible Earth-Resistance Values & Soil Resistivity

Installation	Acceptable earth resistance
Large power stations	**≤ 0.5 Ω**
Major sub-stations / EHT stations	**≤ 1 Ω**
Small sub-stations	≤ 2 Ω
Industrial premises / distribution transformers	≤ 1–2 Ω
Domestic installations (in general)	as low as practicable, commonly taken **≤ 8 Ω** (5–8 Ω range typical)
Tower footing / LT poles	≤ 10 Ω (ideally)

Factors affecting soil resistivity / earth resistance:

1. **Moisture content** — dominant factor; resistivity rises steeply below ~15–20% moisture;
2. **Type of soil** — wet marshy soil lowest; clay/loam low; sand, gravel, **rock highest**;
3. **Dissolved salts/chemical composition** — salt, charcoal, chemical treatment (bentonite) lower it;
4. **Temperature** — resistivity rises sharply near/below freezing;
5. **Depth of electrode** (deeper → moister strata → lower R), electrode size/surface area, and number of parallel electrodes (electrodes in parallel, spaced apart ≥ their length, reduce net resistance);
6. Seasonal variation — hence testing is done in the **driest season** for the worst-case value.

10.7.8 Maintenance and Testing of Earthing

Maintenance:

- **Watering** the earth pit regularly through the funnel, especially in summer (3–4 buckets); keeping the charcoal-salt bed effective (replenish periodically).
- Inspecting the chamber: cleaning, checking tightness and re-greasing of the clamp/bolt connections, checking for corrosion of lead and electrode, verifying continuity of the ECC.
- **Periodic measurement** of earth resistance (typically at least once a year, in the dry season) and recording it; if above the permissible limit — water/treat the soil, or add parallel electrodes.

Measurement — Earth tester (earth megger) and Fall-of-Potential 3-point method:

- The earth tester is a **megger-type instrument with a hand-driven generator (or electronic source) plus a current reverser/rectifier**, so that the earth is tested with (effectively) **alternating/reversed current** — DC is not used, to avoid **electrolytic/polarisation errors** in the soil — while the moving system still reads on a direct-reading ohm scale. Terminals: E (or C1-P1) to electrode under test, P (P2) to potential spike, C (C2) to current spike.
- **Fall-of-potential method:** current is circulated between the electrode **E** under test and a current spike **C** placed 25–50 m away; a potential spike **P** is driven at intermediate positions and V/I is plotted; with P at ≈ **62% of the E–C distance** (P in the flat "plateau" region, outside both resistance areas) the reading gives the true earth resistance **R = V/I**. Readings are repeated with P shifted a few metres either way — a nearly constant value confirms correct spacing.
- ECC continuity and insulation-resistance tests of the installation are done with the ordinary **megger** (insulation tester, 500 V for LV installations; IR ≥ 1 MΩ desirable).

10.7.9 Neutral vs Earth; ELCB / RCCB

Neutral	Earth
Current-carrying return conductor of the supply (star point of transformer)	Non-current-carrying safety connection to ground mass
Carries load current in normal operation	Carries current **only during a fault/leakage**
Potential near 0 V but can rise if unbalanced/broken	Held at true ground potential
Sized for full load current	Sized per earthing rules (≥ half phase conductor typ.)

Neutral is earthed **at the substation/transformer** (system earthing); at the consumer's premises, neutral and earth are kept **separate**.

ELCB / RCCB (Residual Current Circuit Breaker / Residual Current Device):

- **Current-operated ELCB = RCCB/RCD** (the modern device): phase and neutral both pass through a **toroidal core-balance CT**. Normally $I_{phase} = I_{neutral}$ → net flux = 0. If current leaks to earth (through a person or insulation fault), $I_{phase} \neq I_{neutral}$; the **residual (difference) current** induces an EMF in the CT's secondary which trips the breaker within milliseconds.
- Ratings: sensitivity 30 mA (personnel/shock protection — domestic standard), 100/300 mA (fire/equipment protection); trip time ~ 30 ms class.

- (Older) **voltage-operated ELCB:** trip coil between equipment body and earth; trips when body-to-earth voltage exceeds ~50 V — obsolete because it needs a sound earth connection and misses faults bypassing it.
- Note: an RCCB does **not** protect against overload/short circuit between phase and neutral (no residual current) — use it with MCBs (or use an RCBO which combines both).

10.8 PYQ Corner — Actual CBT-2 (22-04-2025) Questions Solved

PYQ 1. *Which quality of a protective relay ensures that it operates only for faults within its designated zone of protection?*

Answer: Selectivity (discrimination).

Explanation: Selectivity is the ability of protection to select and disconnect **only the faulty part**, operating for faults **inside its own protected zone** and remaining stable for external (through) faults and normal load. Sensitivity concerns the minimum operating quantity, speed the operating time, reliability the assurance of correct operation.

PYQ 2. *A distance relay operates on the principle of —*

Answer: measurement of the impedance (ratio of voltage to current, Z = V/I) at the relay location.

Explanation: The relay is fed V (via PT) and I (via CT). For a fault on a transmission line, V/I equals the line impedance up to the fault, which is **directly proportional to the distance of the fault** from the relay. If the measured impedance is less than the set (reach) impedance, the fault is inside the zone and the relay trips. Hence the names distance/impedance relay; variants: reactance and mho relays.

PYQ 3. *In a magnetic circuit, if the reluctance is increased while the MMF is kept the same, the flux will —*

Answer: decrease.

Explanation: Ohm's law of the magnetic circuit: **Φ = MMF/S**. With MMF constant, $\Phi \propto 1/S$. Example: MMF = 400 AT, S = 1×10^6 AT/Wb → Φ = 0.4 mWb; if S doubles to 2×10^6 (e.g., an air gap is introduced), Φ halves to 0.2 mWb.

PYQ 4. *The region around a magnet in which its influence (magnetic force) can be experienced is called —*

Answer: the magnetic field.

Explanation: The magnetic field is the space surrounding a magnet or current-carrying conductor in which magnetic force acts on another magnet, ferromagnetic material or moving charge. It is mapped by lines of force which form closed loops (N → S outside the magnet) and never intersect. (Contrast: the electric field is the region where a force acts on a static charge.)

10.9 Practice MCQs (25)

Q1. Ohm's law is not applicable to —

(a) copper conductors (b) manganin resistors (c) semiconductor diodes (d) heating elements

Q2. Two resistors of 4 Ω and 12 Ω in parallel give an equivalent of —

(a) 16 Ω (b) 8 Ω (c) 3 Ω (d) 0.33 Ω

Q3. Kirchhoff's current law is based on the law of conservation of —

(a) energy (b) charge (c) momentum (d) mass

Q4. Three equal resistors R connected in delta are replaced by an equivalent star. Each star resistance is —

(a) 3R (b) R (c) R/3 (d) R/9

Q5. Maximum power is transferred to a DC load when R_L equals —

(a) zero (b) infinity (c) R_Th of the source network (d) twice R_Th

Q6. Efficiency of a source at the maximum-power-transfer condition is —

(a) 100% (b) 75% (c) 50% (d) 25%

Q7. The form factor of a sinusoidal wave is —

(a) 1.414 (b) 1.11 (c) 0.707 (d) 0.637

Q8. The RMS value of v = 100 sin ωt is —

(a) 100 V (b) 70.7 V (c) 63.7 V (d) 50 V

Q9. In a pure inductor, the current —

(a) leads the voltage by 90° (b) lags the voltage by 90° (c) is in phase with voltage (d) lags by 45°

Q10. A series RLC circuit at resonance has —

(a) maximum impedance (b) minimum current (c) unity power factor (d) zero current

Q11. The Q-factor of a series resonant circuit equals —

(a) R√(C/L) (b) (1/R)√(L/C) (c) R/(2πfL) (d) 2πfCR

Q12. In a parallel resonant (tank) circuit the line current at resonance is —

(a) maximum (b) minimum (c) zero always (d) equal to the circulating current

Q13. In a 3-phase star connection, V_line/V_phase is —

(a) 1 (b) √3 (c) 3 (d) 1/√3

Q14. A capacitor connected to DC in steady state acts as —

(a) short circuit (b) open circuit (c) pure resistance (d) inductor

Q15. The unit of MMF is —

(a) weber (b) tesla (c) ampere-turn (d) AT/Wb

Q16. If an air gap is introduced in an iron-core magnetic circuit (same MMF), the flux —

(a) increases (b) decreases (c) is unchanged (d) becomes zero

Q17. Fleming's left-hand rule is used to find the —

(a) direction of induced EMF (b) direction of force on a current-carrying conductor in a field (c) polarity of a solenoid (d) direction of flux in a core

Q18. Lenz's law is a consequence of the law of conservation of —

(a) charge (b) flux (c) energy (d) current

Q19. Two coupled coils of 4 H and 9 H have mutual inductance 3 H. The coefficient of coupling is —

(a) 1 (b) 0.75 (c) 0.5 (d) 0.33

Q20. Heat produced in a resistor is proportional to —

(a) I (b) I^1.5 (c) I^2 (d) √I

Q21. Fusing factor of a fuse is —

(a) always less than 1 (b) equal to 1 (c) always greater than 1 (d) zero

Q22. In Faraday's first law of electrolysis, the mass deposited is proportional to —

(a) voltage applied (b) quantity of electricity (charge) passed (c) resistance of electrolyte (d) temperature only

Q23. In electroplating, the article to be plated is made the —

(a) anode (b) cathode (c) electrolyte (d) separator

Q24. A Buchholz relay is used for the protection of —

(a) transmission lines (b) alternators (c) oil-immersed transformers (d) busbars

Q25. As per standard practice, the earth resistance of a large power station should not exceed about —

(a) 8 Ω (b) 5 Ω (c) 1–2 Ω (d) 0.5 Ω

Answer Key with Brief Explanations

Q	Ans	Explanation
1	(c)	Diode is a non-linear, unilateral device — V–I not proportional
2	(c)	$4\times12/(4+12) = 48/16 = 3\ \Omega$
3	(b)	Charge cannot accumulate at a node — conservation of charge
4	(c)	Delta→star with equal arms: $R_Y = R_\Delta/3$
5	(c)	Maximum power transfer: $R_L = R_{Th}$ (source internal resistance)
6	(c)	Equal power lost in $R_{Th} \Rightarrow \eta = 50\%$
7	(b)	RMS/Average = $0.707I_m/0.637I_m = 1.11$
8	(b)	$V_{rms} = 100/\sqrt{2} = 70.7$ V
9	(b)	Pure L: I lags V by 90° (CIVIL)
10	(c)	$X_L = X_C \Rightarrow Z = R$ (min), I max, $\cos\varphi = 1$
11	(b)	$Q = \omega_r L/R = (1/R)\sqrt{(L/C)}$
12	(b)	Parallel resonance: impedance max (L/CR) ⇒ line current min
13	(b)	Star: $V_L = \sqrt{3}\ V_{ph}$
14	(b)	Fully charged capacitor blocks DC — open circuit
15	(c)	MMF = NI, unit ampere-turn (AT)
16	(b)	Air gap adds large reluctance; Φ = MMF/S falls
17	(b)	Left hand = motor action (force); right hand = generator (EMF)
18	(c)	Opposition to the cause ensures work must be done — energy conservation
19	(c)	$k = M/\sqrt{(L_1L_2)} = 3/\sqrt{36} = 0.5$
20	(c)	Joule's law $H = I^2Rt$
21	(c)	Fusing current > current rating, so factor > 1 (≈1.4–2 rewirable)
22	(b)	$m = ZIt = ZQ$ — proportional to charge
23	(b)	Metal ions (cations) deposit on the cathode = article
24	(c)	Gas-operated relay between tank and conservator of oil transformers
25	(d)	Power stations ≤ 0.5 Ω; major substations ≤ 1 Ω; homes ≈ ≤ 8 Ω

10.10 Rapid-Revision Formula Sheet

DC circuits

- $Q = It$; $V = W/Q$; $P = VI = I^2R = V^2/R$; $W = Pt$; 1 kWh = 3.6×10^6 J; 1 hp = 746 W
- $R = \rho l/A$; $G = 1/R$; $R_2 = R_1[1 + \alpha(t_2 - t_1)]$
- Series: $R = \Sigma R_i$; Parallel: $1/R = \Sigma 1/R_i$; two in parallel: product/sum; n equal: nr and r/n
- Divider rules: $V_1 = V \cdot R_1/(R_1+R_2)$; $I_1 = I \cdot R_2/(R_1+R_2)$
- KCL: $\Sigma I = 0$ (charge); KVL: $\Sigma E = \Sigma IR$ (energy)
- $\Delta \rightarrow Y$: $R_1 = R_{12}R_{31}/\Sigma R_\Delta$; $Y \rightarrow \Delta$: $R_{12} = R_1 + R_2 + R_1R_2/R_3$; equal case: $R_Y = R_\Delta/3$
- Thevenin: $I_L = V_Th/(R_Th + R_L)$; Norton: $V_Th = I_N\ R_N$; MPT: $R_L = R_Th$, $P_max = V_Th^2/4R_Th$, $\eta = 50\%$

AC fundamentals

- $e = E_m \sin \omega t$; $\omega = 2\pi f$; $T = 1/f$; $f = PN/120$
- Sine: $I_rms = 0.707 I_m$; $I_av = 0.637 I_m$; FF = 1.11; PF(crest) = 1.414
- $X_L = 2\pi fL$; $X_C = 1/(2\pi fC)$; $Z_series = \sqrt{[R^2 + (X_L - X_C)^2]}$; $\cos \varphi = R/Z$
- $P = VI \cos \varphi$ (W); $Q = VI \sin \varphi$ (VAR); $S = VI$ (VA); $S^2 = P^2 + Q^2$
- Series resonance: $f_r = 1/(2\pi\sqrt{LC})$; $Z_min = R$; $Q = (1/R)\sqrt{(L/C)} = f_r/BW$
- Parallel resonance: $Z_max = L/CR$ (dynamic impedance); line current minimum
- 3-φ: star $V_L = \sqrt{3} V_ph$, $I_L = I_ph$; delta $V_L = V_ph$, $I_L = \sqrt{3} I_ph$; $P = \sqrt{3} V_L I_L \cos \varphi$

Magnetic

- $B = \Phi/A$ (T); $H = NI/l$ (A/m); $B = \mu_0 \mu_r\ H$; $\mu_0 = 4\pi \times 10^{-7}$ H/m
- $F = BIl \sin \theta$; parallel currents: same direction attract; $f/m = \mu_0 I_1 I_2/2\pi d$
- Magnetic Ohm's law: **Φ = MMF/S**; $S = l/(\mu_0 \mu_rA)$ (AT/Wb); series reluctances add
- $e = -N\ d\Phi/dt$; $e = Blv$; $e_L = -L\ di/dt$; $L = N\Phi/I = N^2/S$
- $k = M/\sqrt{(L_1L_2)}$; series-coupled $L = L_1 + L_2 \pm 2M$; $W = \frac{1}{2}LI^2$
- $P_h \propto B_max\text{^}1.6\ f$ (Steinmetz); $P_e \propto B^2f^2t^2$ (laminate to reduce)

Thermal & chemical

- $H = I^2Rt$ J = 0.24 I^2Rt cal; fusing factor = fusing current/current rating (> 1); $I_f = kd\text{^}\{3/2\}$
- $m = ZIt$; $Z = E/F$; $F \approx 96\,500$ C; $m_1/m_2 = E_1/E_2$; plating: article = cathode
- Lead–acid: 2 V/cell, H_2SO_4 sp. gr. 1.28 (charged) → 1.18 (discharged); capacity in Ah

Protection & relays

- Qualities: **Selectivity** (own zone only), Sensitivity (min operating quantity), Speed, Reliability
- Distance relay: measures $Z = V/I \propto$ fault distance; zones 1/2/3; mho = directional
- Differential: vector difference of in/out currents (unit protection); Buchholz: gas-operated, oil transformers
- Fuse in phase wire only; HRC = silver element in quartz sand

Earthing

- Plate: GI 60 × 60 cm × 6.3 mm (Cu 3.15 mm), top ≥ 3 m deep, charcoal + salt layers, funnel for watering
- Pipe: 38 mm dia × 2.5 m perforated GI pipe, ≈ 3.75 m pit, charcoal + salt — commonest, cheapest
- Earth resistance limits: power station ≤ 0.5 Ω; big substation ≤ 1 Ω; small SS ≤ 2 Ω; homes ≈ ≤ 8 Ω
- Soil resistivity ↓ with moisture, salts, temperature (above freezing), depth; rock worst
- Testing: earth tester (reversed-current megger) — fall-of-potential 3-spike method, P at ≈ 62% of E–C distance; $R = V/I$
- RCCB: core-balance CT trips on residual (phase − neutral) current; 30 mA for shock protection; does not replace MCB

- Never use neutral as earth; 3-pin plug: thick top pin = earth

---

End of Chapter 10. Cross-links: magnetic materials → Ch01 (Components & Materials); measurement of R/L/C and meggers → Ch06 (Electronic Measurements).

GA-01 · Physics (NCERT Class 9–12 Level)

RRB JE CBT-2 · Electronics & Allied Engineering Group (CEN 05/2025)

Section: Physics & Chemistry — 15 Questions Combined

> **How to use this chapter.** The CBT-2 "Physics & Chemistry" section sits at NCERT Class 10–12 level, with a strong tilt toward Class 10 concepts plus a few Class 11–12 fundamentals. Every fact in this chapter is aligned with NCERT Science (Class 9 & 10) and NCERT Physics (Class 11 & 12). Work through the theory, the 12 worked examples, the PYQ Corner (real 2025 CBT-2 questions), and finish with the 25 MCQs and the formula sheet.

Contents

1. Units, Measurement & Errors
2. Motion
3. Laws of Motion & Friction
4. Work, Power & Energy
5. Gravitation
6. Pressure & Floatation
7. Elasticity & Hooke's Law
8. Heat & Thermal Physics
9. Sound
10. Light
11. Electricity
12. Magnetism & Electromagnetic Induction
13. Modern Physics
14. PYQ Corner — 2025 CBT-2 Questions Solved
15. Practice MCQs (25) with Answers
16. Rapid-Revision Formula Sheet

---

1. Units, Measurement & Errors

1.1 The SI System (NCERT Class 11, Ch. Units and Measurements)

The SI system has **seven base units**:

Quantity	SI Unit	Symbol
Length	metre	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Amount of substance	mole	mol
Luminous intensity	candela	cd

Two supplementary units: radian (plane angle) and steradian (solid angle).

1.2 Common Derived Units

Quantity	Unit	In base units
Force	newton (N)	$kg \cdot m \cdot s^{-2}$
Work / Energy	joule (J)	$kg \cdot m^2 \cdot s^{-2}$
Power	watt (W)	$kg \cdot m^2 \cdot s^{-3}$
Pressure	pascal (Pa)	$kg \cdot m^{-1} \cdot s^{-2}$
Frequency	hertz (Hz)	s^{-1}
Charge	coulomb (C)	$A \cdot s$
Potential difference	volt (V)	$J \cdot C^{-1}$
Resistance	ohm (Ω)	$V \cdot A^{-1}$
Power of lens	dioptre (D)	m^{-1}

1.3 Errors in Measurement

- **Absolute error** = |true value − measured value|.
- **Relative error** = mean absolute error ÷ mean value.
- **Percentage error** = relative error × 100.
- In **addition/subtraction**, absolute errors add: $\Delta z = \Delta a + \Delta b$.
- In **multiplication/division**, relative errors add: $\Delta z/z = \Delta a/a + \Delta b/b$.
- For a power, $z = a^n \Rightarrow \Delta z/z = n(\Delta a/a)$.

Significant figures: all non-zero digits are significant; zeros between non-zero digits are significant; trailing zeros after a decimal point are significant (2.500 has 4 sig. figs.).

---

2. Motion

2.1 Basic Definitions (NCERT Class 9, Ch. Motion)

Quantity	Definition	Nature
Distance	Actual path length covered	Scalar
Displacement	Shortest directed line from initial to final position	Vector
Speed	Distance ÷ time	Scalar
Velocity	Displacement ÷ time	Vector
Acceleration	Change in velocity ÷ time	Vector

Displacement can be zero even when distance is not (e.g., one complete round of a circular track).

2.2 Equations of Uniformly Accelerated Motion

For initial velocity u, final velocity v, acceleration a, time t, displacement s:

1. **$v = u + at$**
2. **$s = ut + \frac{1}{2}at^2$**
3. **$v^2 = u^2 + 2as$**

Distance in the nth second: **$s_n = u + a(2n - 1)/2$**

2.3 Motion Graphs

Graph	Slope gives	Area under graph gives
Distance–time	Speed	—
Velocity–time	Acceleration	Displacement
Acceleration–time	—	Change in velocity

- Straight horizontal line on v–t graph → uniform velocity (zero acceleration).
- Straight sloping line on v–t graph → uniform acceleration.
- Parabolic s–t graph → uniformly accelerated motion.

2.4 Uniform Circular Motion

Motion at constant speed on a circle is **accelerated** because direction (hence velocity) changes continuously. Centripetal acceleration $a = v^2/r$, directed toward the centre.

2.5 Projectile Basics (Class 11)

For a projectile launched with speed u at angle θ (air resistance neglected):

- Time of flight: $T = 2u \sin\theta / g$
- Maximum height: $H = u^2 \sin^2\theta / 2g$
- Horizontal range: $R = u^2 \sin 2\theta / g$ — **maximum at θ = 45°**
- Ranges are equal for complementary angles (θ and 90° − θ).
- The trajectory is a **parabola**; horizontal velocity remains constant.

Worked Example 1. A train starts from rest and attains 72 km/h in 40 s. Find its acceleration and the distance covered.

u = 0, v = 72 km/h = 20 m/s, t = 40 s.

a = (v − u)/t = 20/40 = **0.5 m/s²**.

s = ut + ½at² = 0 + ½ × 0.5 × 1600 = **400 m**.

Worked Example 2. A stone is dropped from a 45 m tower (g = 10 m/s²). Find the time to reach the ground and the striking velocity.

s = ½gt² ⇒ 45 = ½ × 10 × t² ⇒ t² = 9 ⇒ **t = 3 s**.

v = gt = 10 × 3 = **30 m/s**.

---

3. Laws of Motion & Friction

3.1 Newton's Laws (NCERT Class 9, Ch. Force and Laws of Motion)

- **First law (law of inertia):** A body remains at rest or in uniform motion in a straight line unless acted upon by an external unbalanced force. Inertia is measured by **mass**.
- **Second law:** Rate of change of momentum ∝ applied force; **F = ma**. Momentum **p = mv** (SI unit kg·m/s).
- **Third law:** To every action there is an equal and opposite reaction, acting on **different bodies** simultaneously.

Conservation of momentum: In the absence of external force, total momentum of a system is constant: $m_1u_1 + m_2u_2 = m_1v_1 + m_2v_2$ (basis of rocket propulsion and gun recoil).

Impulse = F × Δt = change in momentum (unit N·s). Catching a ball by pulling hands back increases Δt, reducing force.

3.2 Friction (NCERT Class 8/11)

- Friction opposes **relative motion** between surfaces in contact; it acts tangentially.
- Order of magnitude: **static > sliding (kinetic) > rolling** friction. Ball bearings exploit low rolling friction.
- Limiting static friction f = μN, where μ = coefficient of friction, N = normal reaction. It is **independent of apparent contact area** (for given surfaces and normal force).
- Friction is a **necessary evil**: it enables walking, braking, writing, but wastes energy as heat and causes wear. Lubricants and streamlining reduce it.

Worked Example 3. A force of 20 N acts on a 4 kg body at rest for 5 s. Find the final velocity.

a = F/m = 20/4 = 5 m/s². v = u + at = 0 + 5 × 5 = **25 m/s**.

---

4. Work, Power & Energy

4.1 Work

W = F s cos θ (θ = angle between force and displacement). SI unit: joule (1 J = 1 N·m).

- θ = 0° → W = Fs (maximum positive work).
- θ = 90° → W = 0 (e.g., gravity on a horizontally moving body; centripetal force in circular motion does **no work**).
- θ = 180° → negative work (friction on a moving body).

4.2 Kinetic Energy — Derivation from $v^2 = u^2 + 2as$

Consider a body of mass m accelerated from rest (u = 0) to velocity v by force F over displacement s:

$v^2 = u^2 + 2as \Rightarrow v^2 = 2as \Rightarrow s = v^2/2a$

Work done $W = Fs = (ma)(v^2/2a) = \mathbf{\frac{1}{2}mv^2}$

This work is stored as kinetic energy: **$KE = \frac{1}{2}mv^2$**. Also, **$KE = p^2/2m$** (p = momentum).

4.3 Potential Energy

Work done in raising mass m through height h against gravity: **PE = mgh**.

4.4 Conservation of Mechanical Energy

For a freely falling body (no air resistance), **KE + PE = constant** at every point. At the top: all PE; at the bottom: all KE; total mgh throughout.

Work–energy theorem: Net work done on a body = change in its kinetic energy.

4.5 Power

P = W/t = F·v. SI unit: watt (1 W = 1 J/s). 1 horsepower (hp) = 746 W.

Commercial unit of energy: 1 kilowatt-hour (kWh) = 1 "unit" = 3.6×10^6 J.

> **Worked Example 4.** A 2 kg body moving at 10 m/s is brought to rest in 4 m. Find the retarding force.
>
> Using $v^2 = u^2 + 2as$: $0 = 100 + 2a(4) \Rightarrow a = -12.5$ m/s².
>
> F = ma = 2 × 12.5 = **25 N** (opposing motion).
>
> (Check by work–energy theorem: KE lost = ½ × 2 × 10^2 = 100 J = F × 4 ⇒ F = 25 N. ✓)

> **Worked Example 5.** A pump lifts 200 kg of water through 10 m in 20 s (g = 10 m/s²). Find its power.
>
> W = mgh = 200 × 10 × 10 = 20,000 J. P = W/t = 20,000/20 = **1000 W = 1 kW**.

---

5. Gravitation

5.1 Universal Law (NCERT Class 9, Ch. Gravitation)

$F = G\,m_1m_2 / r^2$, with G = 6.674×10^{-11} N·m²/kg² (universal gravitational constant, measured by Cavendish).

5.2 g vs G

	g	G
Name	Acceleration due to gravity	Universal gravitational constant
Value	≈ 9.8 m/s^2 on Earth's surface	6.674×10^{-11} $N{\cdot}m^2/kg^2$
Nature	Varies with location (altitude, depth, latitude)	Universal constant, same everywhere
Relation	$g = GM/R^2$	—
Unit	m/s^2	$N{\cdot}m^2/kg^2$

- g is **maximum at the poles, minimum at the equator**; decreases with altitude and with depth; **zero at Earth's centre**.
- Mass is constant everywhere; **weight W = mg** varies with g. Weight on the Moon ≈ 1/6 of that on Earth.

5.3 Kepler's Laws of Planetary Motion

1. **Law of orbits:** Every planet moves in an **ellipse** with the Sun at one focus.
2. **Law of areas:** The line joining planet and Sun sweeps **equal areas in equal times** (consequence of conservation of angular momentum) — planets move faster when nearer the Sun.
3. **Law of periods: $T^2 \propto r^3$** (square of orbital period ∝ cube of semi-major axis).

Escape velocity: $v_e = \sqrt{(2gR)} \approx$ **11.2 km/s** for Earth. Orbital velocity near Earth's surface ≈ 7.9 km/s; $v_e = \sqrt{2} \times v_o$.

---

6. Pressure & Floatation

6.1 Pressure

P = F/A (thrust per unit area). SI unit: pascal (Pa). Sharp knives and pointed nails work by reducing area to increase pressure.

Pressure at depth h in a liquid of density ρ: **P = hρg** (same in all directions at a point — liquids transmit pressure).

Atmospheric pressure ≈ 1.013×10^5 Pa = 760 mm of Hg (measured with a barometer).

6.2 Pascal's Law

Pressure applied to an enclosed fluid is transmitted **undiminished** to every part of the fluid and the walls of the container. Applications: **hydraulic press, hydraulic brakes, hydraulic lift** — a small force on a small piston produces a large force on a large piston ($F_2 = F_1 \times A_2/A_1$).

6.3 Archimedes' Principle & Floatation

When a body is immersed (fully or partially) in a fluid, it experiences an **upthrust (buoyant force) equal to the weight of the fluid displaced**.

- Body floats if its density ≤ density of the fluid; sinks if greater.
- Floating body: weight of body = weight of liquid displaced (law of floatation).
- Applications: ships, submarines, hydrometers (measure liquid density), lactometers (test milk purity).
- **Relative density** = density of substance ÷ density of water (no unit). RD of iron ≈ 7.8; ice floats because RD of ice ≈ 0.92.

> **Worked Example 6.** A solid weighs 60 N in air and 40 N fully immersed in water. Find the buoyant force and the relative density of the solid.

> Buoyant force = 60 − 40 = **20 N** = weight of water displaced.

> Relative density = weight in air ÷ loss of weight in water = 60/20 = **3**.

---

7. Elasticity & Hooke's Law

- **Elasticity:** property of regaining original shape/size after the deforming force is removed. Quartz is nearly perfectly elastic; putty is nearly perfectly plastic. **Steel is more elastic than rubber** (steel needs more stress for the same strain).
- **Stress** = restoring force per unit area (N/m^2); **strain** = fractional change (no unit).
- **Hooke's law:** within the elastic limit, **stress ∝ strain**; stress/strain = modulus of elasticity.
- **Young's modulus Y** = longitudinal stress/longitudinal strain = (F/A)/(ΔL/L).
- **Bulk modulus** (volume), **Shear modulus** (shape).
- For a spring: **F = kx** (k = spring constant); elastic PE stored = ½kx^2.
- Beyond the **elastic limit**, permanent deformation occurs; at the **breaking point**, the material fractures.

---

8. Heat & Thermal Physics

8.1 Temperature Scales

C/5 = (F − 32)/9 = (K − 273.15)/5. The Celsius and Fahrenheit scales agree at **−40°**. SI unit of temperature: kelvin.

8.2 Modes of Heat Transmission

Mode	Medium needed?	Mechanism	Example
Conduction	Yes (mainly solids)	Particle-to-particle transfer, no bulk movement	Metal spoon in hot tea
Convection	Yes (liquids/gases)	Bulk movement of heated fluid	Sea breeze, room heater
Radiation	No (works in vacuum)	Electromagnetic waves (infrared)	Heat of the Sun

Black rough surfaces are good absorbers **and** good emitters; shiny surfaces are poor absorbers/good reflectors (thermos flask uses silvered walls + vacuum to cut all three modes).

8.3 Specific Heat & Latent Heat

- **Specific heat capacity c:** heat needed to raise 1 kg by 1 K. **Q = mcΔT.** Water has an unusually high c = 4186 J/(kg·K) ≈ 1 cal/(g·°C) — hence its use as a coolant and the moderating effect of seas on climate.
- **Latent heat L:** heat absorbed/released during change of state at constant temperature. **Q = mL.**
- Latent heat of fusion of ice ≈ 3.34 × 10^5 J/kg (80 cal/g).
- Latent heat of vaporisation of water ≈ 22.6 × 10^5 J/kg (540 cal/g).
- Steam at 100 °C causes worse burns than water at 100 °C because it carries the extra latent heat of vaporisation.
- **Evaporation** is a surface phenomenon occurring at all temperatures; it causes cooling (sweating, earthen pots).

8.4 Thermal Expansion

Linear expansion: ΔL = LαΔT; area (β ≈ 2α); volume (γ ≈ 3α). Applications: gaps in railway tracks, sagging telephone wires in summer, bimetallic strips in thermostats.

8.5 Anomalous Expansion of Water

Water **contracts** on heating from 0 °C to 4 °C and expands beyond 4 °C. Hence water has **maximum density at 4 °C**. In winter, ponds freeze from the **top**, while water below stays at 4 °C — aquatic life survives under the insulating ice layer.

> **Worked Example 7.** How much heat is needed to convert 2 kg of ice at 0 °C completely into water at 0 °C? ($L_{fusion} = 3.34 \times 10^5$ J/kg)

> $Q = mL = 2 \times 3.34 \times 10^5 =$ **6.68×10^5 J**. Temperature does not change during melting.

---

9. Sound

9.1 Nature & Propagation (NCERT Class 9, Ch. Sound)

- Sound is a **mechanical, longitudinal** wave (compressions and rarefactions) — it **cannot travel through vacuum**.
- Speed order: **$v_{solid} > v_{liquid} > v_{gas}$**. In air at 20–25 °C, v ≈ 340–346 m/s; in water ≈ 1480 m/s; in steel ≈ 5000 m/s. Speed in air increases with temperature and humidity.
- **$v = f\lambda$** (speed = frequency × wavelength).

9.2 Characteristics of Sound

Characteristic	Depends on	Note
Pitch	**Frequency**	Higher frequency → shriller (higher) pitch; **low frequency → low (grave) pitch**
Loudness	Amplitude	Larger amplitude → louder; measured in decibel (dB)
Quality (timbre)	Waveform/overtones	Lets us distinguish two instruments at same pitch & loudness

- **Audible range:** 20 Hz – 20,000 Hz.
- **Infrasound** < 20 Hz (elephants, earthquakes); **ultrasound** > 20 kHz (bats, dolphins; used in SONAR, sonography, cleaning, flaw detection).

9.3 Echo & Reverberation

- **Echo:** reflected sound heard distinctly; requires the reflecting surface to be at least **17.2 m** away (persistence of hearing = 0.1 s; 344 × 0.1 / 2 ≈ 17.2 m).
- **Reverberation:** persistence of sound due to repeated reflections; auditoria use sound-absorbing panels to control it.

9.4 Resonance

When the forcing frequency equals the natural frequency of a body, amplitude becomes very large — resonance. Examples: shattering of a glass by a matching tone, soldiers breaking step on bridges, tuning a radio.

9.5 Doppler Effect (Class 11)

Apparent change in frequency due to relative motion of source and observer.

- Source approaching → apparent frequency **increases** (higher pitch).
- Source receding → apparent frequency **decreases**.

- Applications: radar speed guns, red-shift of galaxies, medical Doppler ultrasound.

9.6 SONAR


Sound **N**avigation **a**nd **R**anging — uses ultrasound to find depth/objects under water. Depth **d = v × t / 2** (t = total go-and-return time).

> **Worked Example 8.** A SONAR pulse returns from the seabed in 4 s. If the speed of sound in water is 1500 m/s, find the depth.

> d = v t / 2 = 1500 × 4 / 2 = **3000 m**.

---

10. Light

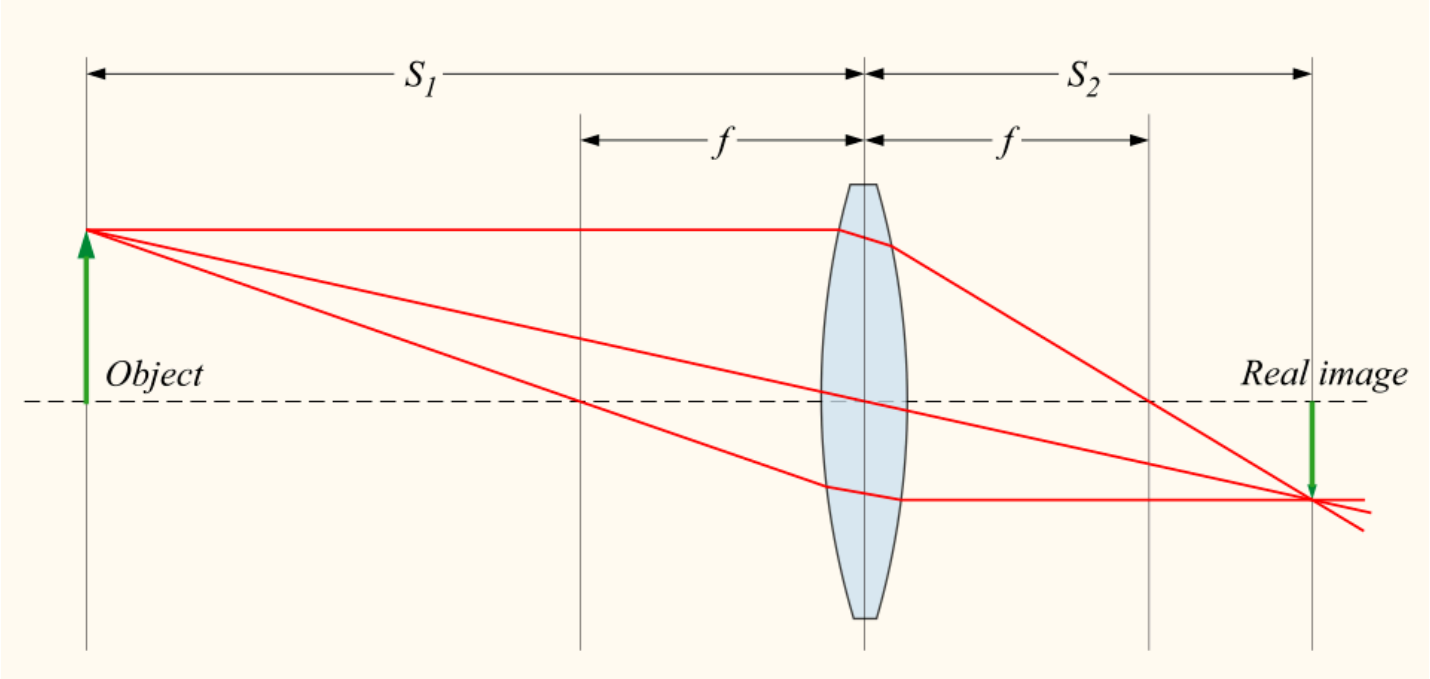

Ray diagram through a convex lens.

10.1 Reflection

Laws of reflection: (i) angle of incidence = angle of reflection; (ii) incident ray, reflected ray, and normal lie in one plane. Plane mirror: image is virtual, erect, laterally inverted, same size, as far behind as the object is in front.

10.2 Spherical Mirrors

- **Concave mirror** (converging): used in torches, headlights, shaving mirrors, solar cookers, by dentists.
- **Convex mirror** (diverging): rear-view mirrors — always gives erect, diminished, virtual images with a **wide field of view**.
- **f = R/2** (focal length = half the radius of curvature).

10.3 Sign Convention (New Cartesian) — memorise this

- All distances measured **from the pole/optical centre**.
- Distances **in the direction of incident light (to the right) are positive**; against it, negative.
- Object distance **u is always negative** (object on the left).

- Heights above the principal axis positive; below, negative.
- **Concave mirror:** f negative. **Convex mirror:** f positive.
- **Convex lens:** f positive. **Concave lens:** f negative.

10.4 Mirror & Lens Formulae

	Mirror	Lens
Formula	1/v + 1/u = 1/f	1/v − 1/u = 1/f
Magnification	m = −v/u = h′/h	m = v/u = h′/h

m positive → erect & virtual image; m negative → inverted & real image; |m| > 1 enlarged, |m| < 1 diminished.

10.5 Refraction

Laws of refraction: (i) incident ray, refracted ray, normal are coplanar; (ii) **Snell's law:** sin i / sin r = n_{21} (constant for a given pair of media and colour).

- Refractive index n = c/v (speed of light in vacuum ÷ speed in medium). n_water ≈ 1.33, n_glass ≈ 1.5, n_diamond ≈ 2.42.
- Denser medium → light bends **toward the normal**; rarer medium → away from the normal.
- Effects: a pool appears shallower (apparent depth = real depth/n), a pencil in water looks bent, stars twinkle (atmospheric refraction), the Sun is visible ~2 minutes before actual sunrise and after actual sunset.

10.6 Total Internal Reflection (TIR)

Occurs when light travels from a **denser to a rarer** medium with angle of incidence **greater than the critical angle** (sin C = 1/n). Applications: **optical fibres**, sparkling of diamond, mirage, totally reflecting prisms in periscopes/binoculars.

10.7 Power of a Lens

P = 1/f (f in metres) = 100/f (f in cm), unit **dioptre (D)**.

- Convex lens → positive power; concave lens → negative power.
- Lenses in contact: P = P_1 + P_2 + …

10.8 Human Eye & Defects (quick table)

Defect	Problem	Correction
Myopia (short-sightedness)	Distant objects blurred; image forms before retina	**Concave** lens (negative power)
Hypermetropia (long-sightedness)	Near objects blurred; image behind retina	**Convex** lens (positive power)
Presbyopia	Age-related loss of accommodation	Bifocal lenses
Astigmatism	Uneven cornea curvature	Cylindrical lens

Least distance of distinct vision (near point) for a normal eye = **25 cm**.


10.9 Optical Instruments (Class 12)


- **Simple microscope:** magnification M = 1 + D/f (image at near point D = 25 cm).
- **Compound microscope:** M = m_objective × m_eyepiece ≈ (L/f_o)(D/f_e); objective has a **short** focal length.
- **Astronomical telescope (normal adjustment): M = f_o/f_e**; objective has a **long** focal length and large aperture (light gathering & resolution).

10.10 Dispersion & Scattering

- A prism splits white light into **VIBGYOR**; **violet deviates most, red least** (n_violet > n_red). Rainbows = dispersion + TIR + refraction in raindrops.
- **Scattering ($\propto 1/\lambda^4$, Rayleigh):** blue sky (blue scatters most), red sunrise/sunset (red survives the long path), danger signals are red (least scattered). Sky appears black from the Moon/space (no atmosphere).
- **Tyndall effect:** scattering by colloidal particles makes the light path visible (sunbeam through a canopy or a dusty room).

10.11 Electromagnetic Spectrum (Class 12)

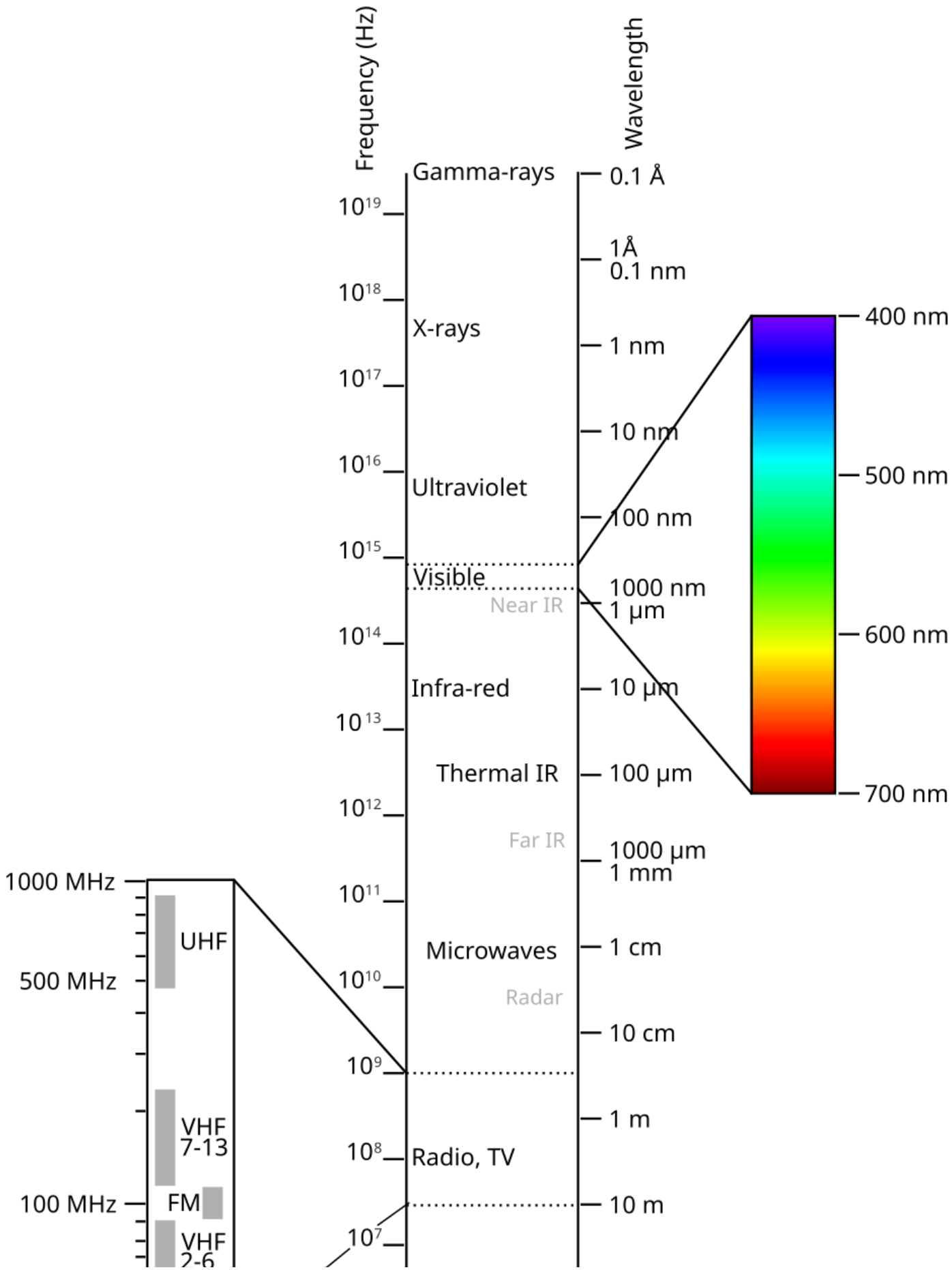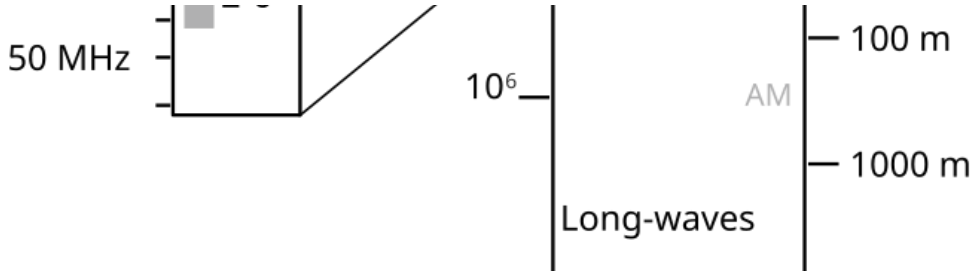
Frequency (Hz)
Wavelength
Gamma-rays
X-rays
Ultraviolet
Visible
Near IR
Infra-red
Thermal IR
Far IR
Microwaves
Radar
Radio, TV
10^{19}
10^{18}
10^{17}
10^{16}
10^{15}
10^{14}
10^{13}
10^{12}
10^{11}
10^{10}
10^{9}
10^{8}
10^{7}
0.1 Å
1Å
0.1 nm
1 nm
10 nm
100 nm
1000 nm
1 µm
10 µm
100 µm
1000 µm
1 mm
1 cm
10 cm
1 m
10 m
400 nm
500 nm
600 nm
700 nm
1000 MHz
500 MHz
100 MHz
UHF
VHF
7-13
FM
VHF
2-6



Electromagnetic spectrum.

In order of **increasing wavelength / decreasing frequency & energy**:

γ-rays < X-rays < Ultraviolet < Visible (400–700 nm) < Infrared < Microwaves < Radio waves

Radiation	Wavelength (approx.)	Uses
γ-rays	< 0.01 nm	Cancer therapy, sterilisation
X-rays	0.01–10 nm	Medical imaging, crystallography
Ultraviolet	10–400 nm	Water purification, forensic detection
Visible	400–700 nm	Vision
Infrared	700 nm – 1 mm	Remote controls, night vision, thermal imaging
Microwaves	1 mm – 0.1 m	Radar, microwave ovens, communication
Radio	> 0.1 m	Broadcasting, communication

UV sub-bands (know these):

Band	Wavelength	Note
UV-A	315–400 nm	Reaches Earth's surface; skin ageing
UV-B	280–315 nm	Partly absorbed by ozone; sunburn, vitamin D synthesis
UV-C	**100–280 nm**	**Shortest wavelength, highest energy — most damaging**; fully absorbed by atmosphere/ozone; used in germicidal lamps

All EM waves travel at **$c = 3 \times 10^8$ m/s** in vacuum; they are transverse and need no medium.

Worked Example 9. An object is placed 30 cm in front of a concave mirror of focal length 15 cm. Find the image position and nature.

u = −30 cm, f = −15 cm. 1/v = 1/f − 1/u = (−1/15) − (−1/30) = −1/30 ⇒ **v = −30 cm**.

m = −v/u = −(−30)/(−30) = −1. Image is **real, inverted, same size, at the centre of curvature**.

Worked Example 10. A convex lens has power +5 D. Where must an object be placed to obtain an image at 2f? Also find f.

f = 1/P = 1/5 m = **+20 cm**. A real, inverted, same-size image at 2f forms when the object is at **2f = 40 cm** from the lens (u = −40 cm).

11. Electricity

11.1 Basic Quantities (NCERT Class 10, Ch. Electricity)

- **Current I = Q/t** (ampere = coulomb/second). Conventional current flows opposite to electron flow. Charge on one electron = 1.6×10^{-19} C; 1 C ≈ 6.25×10^{18} electrons.
- **Potential difference V = W/Q** (volt = joule/coulomb), measured with a **voltmeter (in parallel)**; current with an **ammeter (in series)**.

11.2 Ohm's Law

V = IR at constant temperature (physical conditions unchanged). V–I graph for an ohmic conductor is a straight line through the origin.

Resistance of a wire: R = ρL/A — ρ = resistivity (Ω·m), a material property independent of dimensions. Resistivity of metals increases with temperature; **alloys (nichrome, constantan, manganin) have high resistivity and low temperature coefficient → used in heating elements and standard resistors**. Copper/aluminium (low ρ) → transmission wires. Tungsten (high melting point) → lamp filaments.

11.3 Series & Parallel Combinations

	Series	Parallel
Equivalent R	$R = R_1 + R_2 + R_3$	$1/R = 1/R_1 + 1/R_2 + 1/R_3$
Same for all	Current	Potential difference
Equivalent value	Larger than largest R	Smaller than smallest R
Use	Decorative series lamps	**Household wiring** (each appliance gets full mains voltage; independent switching)

Two equal resistors R in parallel → R/2; n equal resistors in parallel → R/n.

11.4 Heating Effect — Joule's Law

Heat produced: **$H = I^2Rt = VIt = (V^2/R)t$**

- $H \propto I^2$ (at fixed R): **doubling the current makes the heat four times** — the key fact behind heater elements, fuses, filament bulbs.
- **Fuse:** a low-melting-point alloy (tin–lead) wire in series that melts on overload/short circuit. Rated in amperes.
- Applications: electric iron, geyser, toaster (nichrome elements); electric bulb (tungsten filament, argon/nitrogen filling).

11.5 Electric Power

$P = VI = I^2R = V^2/R$. Energy consumed E = P × t; billed in kWh (1 kWh = 3.6×10^6 J).

> **Worked Example 11.** A 100 Ω heater element carries 2 A for 5 minutes. Find the heat produced. If the current is doubled, what happens to the heat?

> $H = I^2Rt = 2^2 \times 100 \times 300 =$ **1.2×10^5 J**.

> $H \propto I^2$, so doubling I makes the heat **4 times**: 4.8×10^5 J.

12. Magnetism & Electromagnetic Induction

12.1 Magnetic Effects of Current (NCERT Class 10)

- A current-carrying conductor produces a magnetic field around it (**Oersted's experiment**).
- Straight wire: concentric circular field lines; direction by the **right-hand thumb rule** (thumb = current, curled fingers = field).
- **Solenoid:** field like a bar magnet; uniform field inside; used with a soft-iron core to make **electromagnets**.
- Magnetic field lines are **closed curves** (N → S outside, S → N inside a magnet) and **never intersect**. SI unit of magnetic field: tesla (T).

12.2 Force on a Current-Carrying Conductor

$F = BIL \sin\theta$ (maximum when the conductor is perpendicular to the field).

Fleming's left-hand rule (motor rule): **F**ore-finger = **F**ield, **C**entre finger = **C**urrent, Thu**M**b = **M**otion (force).

12.3 Electromagnetic Induction

- **Faraday's laws:** an EMF is induced whenever the magnetic flux linked with a circuit changes; induced EMF ∝ **rate of change of flux** ($\varepsilon = -d\Phi/dt$).
- **Lenz's law:** the induced current opposes the change that produces it (consequence of energy conservation) — the minus sign in Faraday's law.
- **Fleming's right-hand rule** (generator rule) gives the direction of induced current.

12.4 Motor, Generator, Transformer

Device	Converts	Principle	Key part
Electric motor	Electrical → mechanical	Force on a current-carrying coil in a magnetic field	Split-ring commutator (DC) reverses current each half turn
Generator (dynamo)	Mechanical → electrical	Electromagnetic induction	AC: slip rings; DC: split-ring commutator
Transformer	AC voltage level up/down	Mutual induction (**AC only**)	$V_s/V_p = N_s/N_p$; step-up: $N_s > N_p$

- India's domestic supply: **220 V, 50 Hz AC** (direction reverses every 1/100 s → 50 cycles/s).
- Wiring: **live (red/brown), neutral (black/light blue), earth (green)**. The earth wire protects users from shocks via metallic appliance bodies. **MCBs/fuses** are placed in the live wire.
- AC is preferred for transmission because voltage can be stepped up (low current → low I^2R line loss).

13. Modern Physics

13.1 Atomic Models

Model	Key idea	Shortcoming
Thomson (1898)	"Plum-pudding": electrons embedded in a positive sphere	Could not explain scattering results
Rutherford (1911)	α-scattering → tiny, dense, positive **nucleus**; electrons revolve around it	Orbiting electron should spiral in (instability); no line spectra
Bohr (1913)	Electrons in fixed **stationary orbits** with quantised angular momentum ($mvr = nh/2\pi$); energy emitted/absorbed only on jumps ($E_2 - E_1 = h\nu$)	Works well only for hydrogen-like atoms

Nucleus discovered by Rutherford; **proton** by Rutherford (1919); **neutron by Chadwick (1932)**; electron by J. J. Thomson (1897).

13.2 Radioactivity

Spontaneous emission of radiation by unstable nuclei (discovered by **Henri Becquerel**, 1896; term coined by Marie Curie).

Radiation	Nature	Charge	Penetrating power	Ionising power	Stopped by
α (alpha)	Helium nucleus ($_2He^4$)	+2	Lowest	Highest	Sheet of paper
β (beta)	Fast electrons	−1	Medium	Medium	Few mm of aluminium
γ (gamma)	EM waves (photons)	0	**Highest**	Lowest	Thick lead/concrete

- α-decay: mass number ↓ 4, atomic number ↓ 2. β-decay: atomic number ↑ 1, mass number unchanged. γ-emission: no change in A or Z.
- SI unit of activity: **becquerel (Bq)**; older unit: curie (Ci).

13.3 Half-Life

Time in which half the radioactive nuclei decay. After n half-lives, remaining fraction = **$(1/2)^n$**; $N = N_0(1/2)^{(t/T½)}$.

> **Worked Example 12.** A radioactive sample of 80 g has a half-life of 5 days. How much remains after 20 days?

> Number of half-lives $n = 20/5 = 4$. Remaining $= 80 \times (1/2)^4 = 80/16 =$ **5 g**.

13.4 Fission vs Fusion

	Nuclear fission	Nuclear fusion
Process	Heavy nucleus (^{235}U) splits into lighter nuclei on neutron capture	Light nuclei (hydrogen isotopes) combine into helium
Conditions	Room conditions possible (chain reaction, moderated)	Extremely high temperature & pressure (thermonuclear)
Energy per unit mass	Large	**Larger** than fission
Where used/found	Nuclear reactors, atom bomb	**The Sun and stars**, hydrogen bomb
Mass–energy	Both governed by **$E = mc^2$** (mass defect converts to energy)	

Reactor essentials: fuel (enriched U), **moderator** (heavy water/graphite — slows neutrons), **control rods** (cadmium/boron — absorb neutrons), coolant.

13.5 X-rays

Discovered by **W. C. Röntgen (1895)**. Produced when fast electrons strike a heavy metal target (tungsten). High-frequency EM waves; penetrate flesh but not bone/metal — medical imaging, security scanning, crystal structure analysis.

13.6 Photoelectric Effect (Class 12 basics)

Emission of electrons from a metal surface when light of frequency above a **threshold frequency ν_0** falls on it (explained by **Einstein**, Nobel Prize 1921).

- **Einstein's equation:** $h\nu = \varphi + KE_{max}$ (φ = work function = $h\nu_0$).
- Number of photoelectrons ∝ **intensity**; maximum KE ∝ **frequency** (not intensity).
- Instantaneous emission; demonstrates the **particle (photon) nature of light**. Photon energy $E = h\nu = hc/\lambda$, $h = 6.63 \times 10^{-34}$ J·s.
- Applications: photocells, automatic doors, solar panels, light meters.

---

14. PYQ Corner — RRB JE CBT-2 2025 (Physics Questions Solved)

PYQ 1. A concave lens has focal length 2 cm. Its power is:

Concave lens ⇒ f is negative: f = −2 cm.

P = 100/f(cm) = 100/(−2) = **−50 D**. ✓ Negative power confirms a diverging (concave) lens.

PYQ 2. The property of a metal by which it can be drawn into thin wires is:

Ductility. (Malleability = beaten into sheets; gold and silver are the most ductile/malleable metals.)

PYQ 3. A body starts from rest and accelerates uniformly; using $v^2 = u^2 + 2as$, find its kinetic energy after covering distance s under acceleration a (mass m).

$v^2 = 0 + 2as \Rightarrow KE = \frac{1}{2}mv^2 = \frac{1}{2}m(2as) =$ **mas** — numerically equal to the work done, W = Fs = (ma)s. This is exactly the KE derivation in §4.2; CBT-2 gives numbers (e.g., m = 2 kg, a = 5 m/s², s = 10 m ⇒ KE = 2 × 5 × 10 = 100 J).

PYQ 4. Low frequency of a sound wave corresponds to:

Low pitch (grave/dull sound). Pitch is the perceptual attribute determined by frequency — high frequency = shrill/high pitch, low frequency = low pitch (§9.2).

PYQ 5. An object is placed 15 cm from a convex lens of focal length 25 cm. Find the image distance and nature.

u = −15 cm, f = +25 cm (object inside the focus, since 15 < 25).

1/v = 1/f + 1/u = 1/25 + (−1/15) = (3 − 5)/75 = −2/75 ⇒ **v = −37.5 cm**.

Negative v ⇒ image on the **same side as the object**: **virtual, erect, magnified** (m = v/u = −37.5/−15 = +2.5). A convex lens acts as a magnifying glass when the object is within its focal length.

PYQ 6. In an electric heating element, the heat produced is proportional to:

The square of the current (H ∝ I^2) — Joule's law H = I^2Rt (§11.4). Doubling I quadruples the heat.

PYQ 7. Which UV band is the most damaging?

UV-C (100–280 nm) — shortest wavelength ⇒ highest frequency and photon energy ⇒ most damaging. It is fortunately absorbed completely by the ozone layer/atmosphere (§10.11).

---

15. Practice MCQs (25)

Q1. The SI unit of luminous intensity is:

(a) lumen (b) lux (c) candela (d) weber

Q2. The area under a velocity–time graph gives:

(a) acceleration (b) displacement (c) force (d) momentum

Q3. A body moving in a circle at constant speed has:

(a) constant velocity (b) zero acceleration (c) acceleration toward the centre (d) acceleration along the tangent

Q4. For maximum horizontal range, a projectile should be launched at:

(a) 30° (b) 45° (c) 60° (d) 90°

Q5. Inertia of a body is measured by its:

(a) weight (b) velocity (c) mass (d) volume

Q6. Rocket propulsion is based on conservation of:

(a) energy (b) mass (c) linear momentum (d) angular momentum

Q7. Which type of friction is the smallest?

(a) static (b) sliding (c) rolling (d) limiting

Q8. A body of mass 4 kg moves at 3 m/s. Its kinetic energy is:

(a) 6 J (b) 12 J (c) 18 J (d) 36 J

Q9. 1 kWh equals:

(a) 3.6×10^5 J (b) 3.6×10^6 J (c) 3.6×10^7 J (d) 746 J

Q10. The value of g is maximum at:

(a) the equator (b) the poles (c) the centre of the Earth (d) a mountain top

Q11. Kepler's second law (equal areas in equal times) is a consequence of conservation of:

(a) energy (b) linear momentum (c) angular momentum (d) mass

Q12. Hydraulic brakes work on:

(a) Archimedes' principle (b) Pascal's law (c) Bernoulli's theorem (d) Hooke's law

Q13. A hydrometer is used to measure:

(a) humidity (b) pressure (c) density of liquids (d) depth of the sea

Q14. Which is more elastic?

(a) rubber (b) steel (c) putty (d) clay

Q15. Water has maximum density at:

(a) 0 °C (b) 4 °C (c) 100 °C (d) −4 °C

Q16. Steam at 100 °C causes more severe burns than boiling water at 100 °C because steam has additional:

(a) temperature (b) specific heat (c) latent heat of vaporisation (d) pressure

Q17. The minimum distance for hearing a distinct echo (v ≈ 344 m/s) is about:

(a) 10 m (b) 17.2 m (c) 34.4 m (d) 344 m

Q18. When a sound source approaches a stationary listener, the apparent frequency:

(a) decreases (b) increases (c) is unchanged (d) becomes zero

Q19. Total internal reflection can occur when light travels from:

(a) air to glass (b) air to water (c) water to air (d) vacuum to glass

Q20. A person cannot see distant objects clearly. The defect and its correction are:

(a) myopia — convex lens (b) myopia — concave lens (c) hypermetropia — concave lens (d) hypermetropia — convex lens

Q21. In an astronomical telescope (normal adjustment), magnification equals:

(a) f_e/f_o (b) f_o/f_e (c) $f_o \times f_e$ (d) $f_o + f_e$

Q22. Which colour of light deviates most through a glass prism?

(a) red (b) yellow (c) green (d) violet

Q23. Three 6 Ω resistors are connected in parallel. The equivalent resistance is:

(a) 18 Ω (b) 6 Ω (c) 3 Ω (d) 2 Ω

Q24. A transformer works on:

(a) DC only (b) AC only (c) both AC and DC (d) electrostatic induction

Q25. The half-life of a radioactive element is 10 days. The fraction remaining after 30 days is:

(a) 1/3 (b) 1/4 (c) 1/8 (d) 1/16

Answer Key with One-Line Reasons

Q	Ans	Reason
1	c	Candela is the SI base unit of luminous intensity
2	b	Area of v–t graph = displacement
3	c	Centripetal acceleration a = v^2/r toward the centre
4	b	R = u^2 sin 2θ/g is maximum when 2θ = 90°
5	c	Mass is the measure of inertia
6	c	Momentum of gases backward = momentum of rocket forward
7	c	Rolling < sliding < static friction
8	c	KE = ½ × 4 × 3^2 = 18 J
9	b	1 kWh = 1000 W × 3600 s = 3.6 × 10^6 J
10	b	Earth is flattened at the poles (smaller R → larger g)
11	c	Equal-area law ⇔ constant angular momentum
12	b	Pressure transmitted undiminished in an enclosed fluid
13	c	Hydrometer floats per liquid density (floatation)
14	b	Steel needs more stress for the same strain
15	b	Anomalous expansion — densest at 4 °C
16	c	Extra 540 cal/g released on condensation
17	b	d = v × 0.1/2 ≈ 17.2 m
18	b	Doppler effect — approach raises frequency
19	c	TIR needs denser → rarer with i > critical angle
20	b	Myopia corrected by a diverging (concave) lens
21	b	M = f_o/f_e
22	d	n_violet is the largest; violet bends most
23	d	R/n = 6/3 = 2 Ω
24	b	Mutual induction needs changing flux — AC only
25	c	n = 3 half-lives ⇒ $(1/2)^3$ = 1/8

16. Rapid-Revision Formula Sheet

Mechanics

- $v = u + at$; $s = ut + \frac{1}{2}at^2$; **$v^2 = u^2 + 2as$**; $s_n = u + a(2n-1)/2$
- $F = ma$; $p = mv$; Impulse $= F\Delta t = \Delta p$
- $W = Fs\cos\theta$; **$KE = \frac{1}{2}mv^2 = p^2/2m$**; $PE = mgh$; $P = W/t = Fv$
- $F = Gm_1m_2/r^2$; $g = GM/R^2$; $W = mg$; $v_{escape} = \sqrt{(2gR)} = 11.2$ km/s; $T^2 \propto r^3$
- $P = F/A$; $P = h\rho g$; Buoyant force = weight of fluid displaced
- Stress/strain = modulus; $F = kx$; spring $PE = \frac{1}{2}kx^2$

Heat & Sound

- $Q = mc\Delta T$; $Q = mL$; $C/5 = (F-32)/9 = (K-273)/5$
- $v = f\lambda$; echo distance ≥ 17.2 m; SONAR depth $d = vt/2$
- Audible range 20 Hz–20 kHz; pitch ↔ frequency; loudness ↔ amplitude

Light

- Mirror: $1/v + 1/u = 1/f$, $m = -v/u$, $f = R/2$
- Lens: $1/v - 1/u = 1/f$, $m = v/u$
- **$P = 1/f(m) = 100/f(cm)$** dioptre; lenses in contact $P = \Sigma P_i$
- $n = c/v = \sin i/\sin r$; $\sin C = 1/n$
- Telescope $M = f_o/f_e$; simple microscope $M = 1 + D/f$
- EM spectrum (λ increasing): γ < X < UV < visible < IR < microwave < radio; UV-C most energetic UV
- $c = 3 \times 10^8$ m/s

Electricity & Magnetism

- $I = Q/t$; $V = W/Q$; **$V = IR$**; $R = \rho L/A$
- Series $R = \Sigma R_i$; parallel $1/R = \Sigma 1/R_i$
- **$H = I^2Rt = VIt = V^2t/R$**; $P = VI = I^2R = V^2/R$; 1 kWh $= 3.6 \times 10^6$ J
- $F = BIL\sin\theta$; Fleming's left hand → motor; right hand → generator
- $\varepsilon = -d\Phi/dt$ (Faraday + Lenz); transformer $V_s/V_p = N_s/N_p$

Modern Physics

- Bohr: $mvr = nh/2\pi$; $\Delta E = h\nu$
- $N = N_0(\frac{1}{2})^{(t/T\frac{1}{2})}$; after n half-lives, fraction left $= (\frac{1}{2})^n$
- $E = mc^2$; photon $E = h\nu = hc/\lambda$; Einstein: $h\nu = \varphi + KE_{max}$
- Penetration: γ > β > α; ionisation: α > β > γ

End of GA-01. Next: GA-02 Chemistry (NCERT).

GA-02 · Chemistry (NCERT Class 9–12 Level)

RRB JE CBT-2 · Electronics & Allied Engineering Group (CEN 05/2025)

Section: Physics & Chemistry — 15 Questions Combined

> **How to use this chapter.** The chemistry share of the CBT-2 "Physics & Chemistry" section is pitched at NCERT Class 10–12 level, dominated by Class 10 topics (matter, acids-bases-salts, metals & non-metals, carbon) with a few Class 11 fundamentals (mole concept, atomic structure, periodic trends, bonding). Every fact here is aligned with NCERT Science (Class 9 & 10) and NCERT Chemistry (Class 11 & 12). Study the theory, the 10 worked examples, the PYQ Corner (real 2025 CBT-2 questions), then the 25 MCQs and the revision tables.

Contents

1. Matter & Its States
2. Elements, Compounds & Mixtures
3. Mole Concept & Stoichiometry
4. Atomic Structure
5. Periodic Classification
6. Chemical Bonding
7. Chemical Reactions
8. Acids, Bases & Salts
9. Carbon & Its Compounds
10. Metallurgy
11. Environmental Chemistry
12. PYQ Corner — 2025 CBT-2 Questions Solved
13. Practice MCQs (25) with Answers
14. Rapid-Revision Tables

1. Matter & Its States

1.1 States of Matter (NCERT Class 9, Ch. Matter in Our Surroundings)

Property	Solid	Liquid	Gas
Shape	Fixed	Takes container's	Takes container's
Volume	Fixed	Fixed	Fills container
Compressibility	Negligible	Very low	High
Intermolecular force	Strongest	Moderate	Weakest
Interparticle space	Least	Moderate	Largest

Two additional states: **plasma** (superheated ionised gas — the Sun, neon signs) and **Bose–Einstein condensate** (near absolute zero).

1.2 Changes of State

- **Melting/fusion** (solid → liquid at melting point), **boiling/vaporisation**, **condensation**, **freezing**.
- **Sublimation:** solid → gas directly (camphor, naphthalene, dry ice, iodine, ammonium chloride).
- **Deposition:** gas → solid directly.
- Latent heat is absorbed during melting and boiling **at constant temperature**.

Evaporation (surface phenomenon, all temperatures) causes cooling and increases with surface area, temperature, and wind, and decreases with humidity.

---

2. Elements, Compounds & Mixtures

2.1 Classification of Matter (NCERT Class 9, Ch. Is Matter Around Us Pure?)

- **Element:** made of one kind of atom (e.g., Fe, O_2, S_8). ~118 known; metals, non-metals, metalloids.
- **Compound:** two or more elements chemically combined in a **fixed ratio**, with properties different from constituents (e.g., H_2O, NaCl, CO_2). Components separated only by chemical means.
- **Mixture:** two or more substances physically mixed in **any ratio**, retaining their own properties; separated by physical methods.

2.2 Mixtures vs Compounds (a favourite exam contrast)

Feature	Mixture	Compound
Combination	Physical	Chemical
Ratio of components	Variable	Fixed & definite
Properties	Those of components	New, different from components
Energy change on forming	Usually none	Heat/light usually evolved/absorbed
Separation	Physical methods	Chemical methods only
Example	Air, brass, salt solution	Water, common salt, sugar

2.3 Homogeneous vs Heterogeneous Mixtures

- **Homogeneous:** uniform composition throughout, single phase — solutions (salt in water, air, **alloys such as brass, bronze, steel, and stainless steel**).
- **Heterogeneous:** non-uniform, distinct components/phases — sand + iron filings, oil + water, muddy water.

> **Key exam fact: Alloys are homogeneous mixtures** of two or more metals (or a metal and a non-metal), e.g., brass (Cu + Zn), bronze (Cu + Sn), steel (Fe + C). They are prepared by melting the components together and mixing at the atomic level, so their composition is uniform.

2.4 Solutions — Terminology

- **Solute** (smaller amount) dissolves in **solvent** (larger amount). Water is the "universal solvent".
- **Solubility** = maximum solute that dissolves in 100 g solvent at a given temperature; a **saturated** solution can dissolve no more at that temperature.
- **Tyndall effect** distinguishes colloids/suspensions (scatter light) from true solutions (don't).

Type	Particle size	Example	Filterable?	Tyndall?
True solution	< 1 nm	Salt water	No	No
Colloid	1–1000 nm	Milk, fog	No (needs ultra-)	Yes
Suspension	> 1000 nm	Chalk in water	Yes	Yes

2.5 Separation Techniques

Method	Separates	Basis
Filtration	Insoluble solid from liquid	Particle size
Evaporation	Soluble solid from liquid	Volatility of solvent
Distillation	Miscible liquids with different b.p.	Boiling point
Fractional distillation	Two miscible liquids with close b.p. (petroleum)	Boiling point + fractionating column
Separating funnel	Immiscible liquids (oil + water)	Density/immiscibility
Sublimation	Sublimable solid from a mixture	Sublimation
Centrifugation	Suspended particles (cream from milk)	Density under spin
Chromatography	Coloured components of a mixture (dyes, pigments)	Different adsorption/solubility on a medium
Crystallisation	Pure solid from solution	Differential crystal formation

Chromatography (Greek *chroma* = colour): separates dissolved constituents that move at different rates on paper/adsorbent — used to separate ink dyes and plant pigments.

---

3. Mole Concept & Stoichiometry

3.1 Fundamental Quantities (NCERT Class 9 & 11)

- **Atomic mass unit (u):** 1 u = 1/12 the mass of a carbon-12 atom.
- **Mole:** amount containing **Avogadro's number N_A = 6.022 × 10^{23}** particles.
- **Molar mass:** mass of 1 mole in grams = numerically equal to atomic/molecular mass in u.
- Number of moles **n = given mass ÷ molar mass = number of particles ÷ N_A = volume of gas (STP) ÷ 22.4 L**.

3.2 Molecular Mass — Worked Method

Add the atomic masses (from the periodic table) of all atoms in the formula.

- H_2O = 2(1) + 16 = **18 u**
- CO_2 = 12 + 2(16) = **44 u**
- H_2SO_4 = 2 + 32 + 4(16) = **98 u**
- **S_8 = 8 × 32 = 256 u** (sulphur exists as an S_8 ring; this appears in CBT-2)

3.3 Concentration Terms

Term	Formula
Mass percent (w/w)	(mass of solute ÷ mass of solution) × 100
Volume percent (v/v)	(volume of solute ÷ volume of solution) × 100
Molarity (M)	moles of solute ÷ volume of solution in litres
Molality (m)	moles of solute ÷ mass of solvent in kg
Mole fraction	moles of component ÷ total moles

Note: *mass of solution = mass of solute + mass of solvent.* This is the exact point CBT-2 tests.

3.4 Gas Laws (Class 11 basics)

- **Boyle's law:** at constant T, PV = constant ($P \propto 1/V$).
- **Charles's law:** at constant P, V/T = constant ($V \propto T$ in kelvin).
- **Gay-Lussac's law:** at constant V, P/T = constant.
- **Avogadro's law:** equal volumes of all gases at the same T and P contain equal numbers of molecules. At **STP (0 °C, 1 atm), 1 mole of any gas = 22.4 L**.
- **Ideal gas equation: PV = nRT** ($R = 8.314\ J \cdot mol^{-1} \cdot K^{-1}$).

Worked Example 1. How many moles and how many molecules are there in 36 g of water?

Molar mass of H_2O = 18 g/mol. n = 36/18 = **2 mol**.

Molecules = $2 \times 6.022 \times 10^{23}$ = **1.2044×10^{24}**.

Worked Example 2. Find the mass percent of a solution made by dissolving 40 g of NaCl in 200 g of water.

Mass of solution = 40 + 200 = 240 g.

Mass % = (40/240) × 100 = **16.67 %**. *(This is a verbatim 2025 CBT-2 question — note that the denominator is the mass of the solution, not just the water.)*

Worked Example 3. Calculate the molar mass of glucose ($C_6H_{12}O_6$).

= 6(12) + 12(1) + 6(16) = 72 + 12 + 96 = **180 g/mol**.

---

4. Atomic Structure

4.1 Subatomic Particles (NCERT Class 9, Ch. Structure of the Atom)

Particle	Charge	Relative mass (u)	Discoverer
Electron	−1	1/1836 (≈ 0)	J. J. Thomson
Proton	+1	1	Goldstein / Rutherford
Neutron	0	1	James Chadwick

- **Atomic number (Z)** = number of protons = number of electrons in a neutral atom (defines the element).
- **Mass number (A)** = protons + neutrons; so **neutrons = A − Z**.
- **Isotopes:** same Z, different A (^{1}H, ^{2}H, ^{3}H; ^{12}C, ^{14}C).
- **Isobars:** same A, different Z (^{40}Ar, ^{40}Ca). **Isotones:** same number of neutrons.

4.2 Bohr Model & Electron Shells

- Electrons revolve in fixed **shells (K, L, M, N…)** of definite energy; no energy radiated while in a shell.
- Maximum electrons in a shell = **$2n^2$** (K=2, L=8, M=18, N=32); outermost shell ≤ 8 (octet).
- **Valence electrons** in the outermost shell decide chemical behaviour and valency.

4.3 Quantum Numbers (Class 11)

Quantum number	Symbol	Describes
Principal	n	Shell/energy level & size (1, 2, 3…)
Azimuthal	l	Subshell/shape (0=s, 1=p, 2=d, 3=f)
Magnetic	m_l	Orbital orientation (−l … +l)
Spin	m_s	Electron spin (+½ or −½)

Subshell capacities: **s = 2, p = 6, d = 10, f = 14** electrons.

4.4 Rules for Electronic Configuration

- **Aufbau principle:** electrons fill orbitals in order of increasing energy (1s, 2s, 2p, 3s, 3p, 4s, 3d…).
- **Pauli exclusion principle:** no two electrons in an atom have all four quantum numbers identical (an orbital holds at most 2 electrons of opposite spin).
- **Hund's rule:** orbitals of a subshell are singly filled (parallel spins) before pairing.


Example configurations: Na (11) = 2, 8, 1 → $1s^2 2s^2 2p^6 3s^1$; Cl (17) = 2, 8, 7; **O (8) = 2, 6 → $1s^2 2s^2 2p^4$** (element = oxygen).

> **Worked Example 4.** An element has atomic number 8. Identify it and give its electronic configuration and valency.

> Z = 8 ⇒ **oxygen**. Configuration 2, 6 ($1s^2 2s^2 2p^4$). It needs 2 electrons to complete the octet ⇒ **valency 2**. *(Direct 2025 CBT-2 question.)*

---

5. Periodic Classification

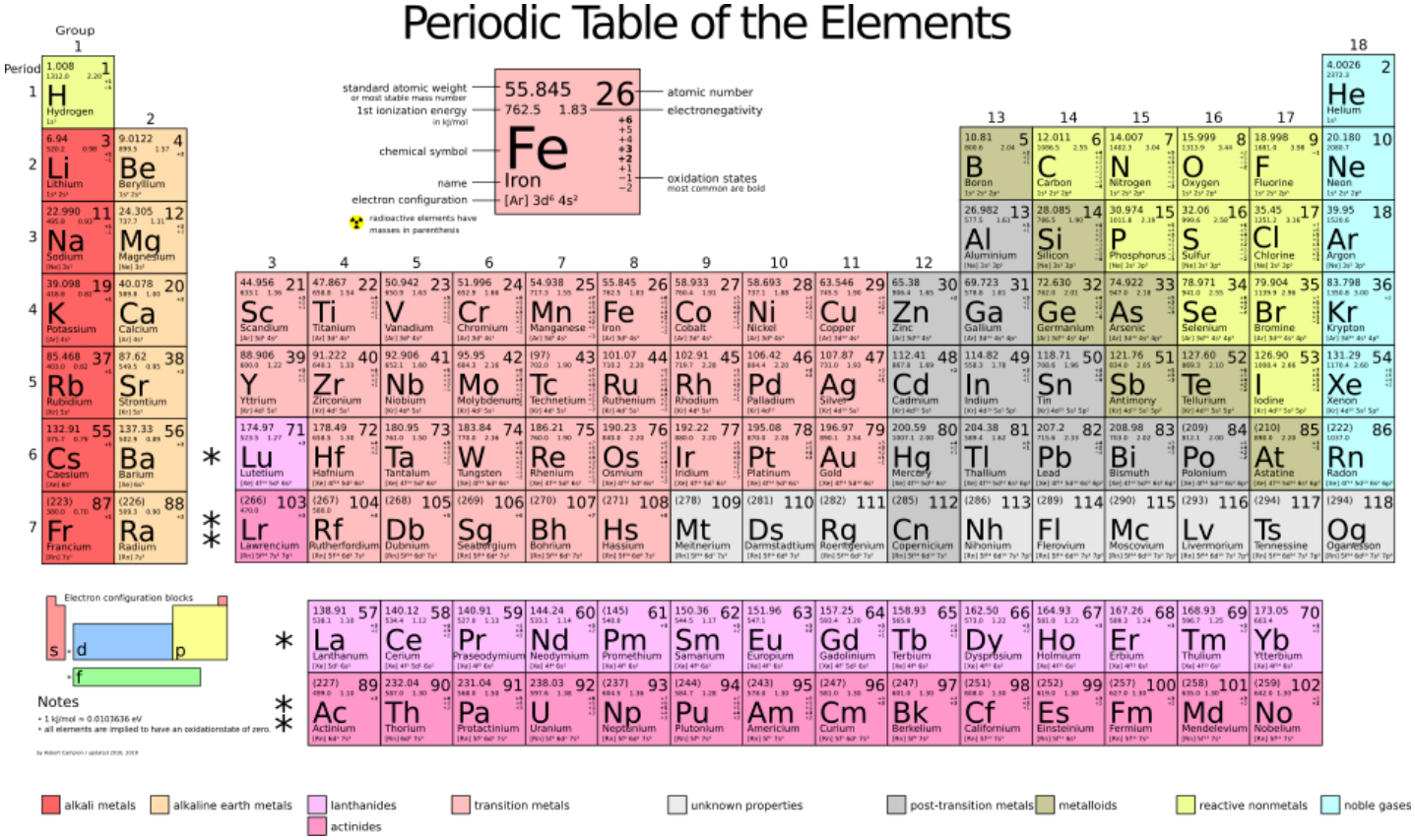

Modern periodic table.

5.1 Development (NCERT Class 10, Ch. Periodic Classification)

- **Döbereiner's triads** → **Newlands' law of octaves** → **Mendeleev's periodic table** (properties = periodic function of atomic **mass**; predicted eka-boron, eka-silicon).
- **Modern periodic law (Moseley):** properties are a periodic function of **atomic number (Z)**.
- Modern table: **18 groups, 7 periods**; blocks s, p, d (transition), f (lanthanides & actinides — inner transition).

5.2 Periodic Trends

Property	Along a period (left → right)	Down a group
Atomic size/radius	Decreases	Increases
Metallic character	Decreases	Increases
Non-metallic character	Increases	Decreases
Ionisation energy	Increases	Decreases
Electron affinity	Increases (generally)	Decreases
Electronegativity	Increases	Decreases
Valence electrons	Increase 1→8	Same in a group

- Most metallic element region: bottom-left; most non-metallic (excluding noble gases): top-right (**fluorine** is the most electronegative element).
- Group 1 = alkali metals; Group 2 = alkaline earth metals; Group 17 = halogens; Group 18 = noble/inert gases (stable octet).

6. Chemical Bonding

6.1 Why Atoms Bond

To attain a **stable noble-gas (octet/duplet)** configuration, atoms lose, gain, or share electrons.

6.2 Ionic vs Covalent Bonds (NCERT Class 10, Ch. Metals & Non-Metals)

Property	Ionic (electrovalent)	Covalent
Formation	Transfer of electrons (metal → non-metal)	Sharing of electrons (non-metal + non-metal)
Example	NaCl, MgO, $CaCl_2$	H_2, O_2, CH_4, H_2O, CO_2
Physical state	Solids (crystalline)	Gases, liquids, or soft solids
Melting/boiling point	**High** (strong electrostatic lattice)	**Low** — held by **weak intermolecular forces**
Solubility	Soluble in water (polar)	Generally soluble in organic solvents
Electrical conductivity	Conduct when molten/aqueous (free ions)	Non-conductors (no free ions/electrons)

> **Key exam fact: Covalent compounds have low melting and boiling points** because, although the intramolecular covalent bonds are strong, the **intermolecular forces between molecules are weak**, so little energy is needed to separate the molecules.

6.3 Hybridization (Class 11)

Molecule	Central atom hybridization	Shape	Bond angle
$BeCl_2$	sp	Linear	180°
BF_3	sp^2	Trigonal planar	120°
CH_4	sp^3	Tetrahedral	109.5°
NH_3	sp^3 (1 lone pair)	Trigonal pyramidal	~107°
H_2O	sp^3 (2 lone pairs)	Bent/angular	~104.5°

Lone pairs compress the bond angle (CH_4 109.5° > NH_3 107° > H_2O 104.5°).

6.4 Hydrogen Bonding

A weak electrostatic attraction between an H atom bonded to a highly electronegative atom (F, O, N) and another electronegative atom. It explains:

- The **high boiling point of water** (vs H_2S) and its liquid state at room temperature.
- Ice being **less dense than water** (open hydrogen-bonded lattice → ice floats).
- The structure of DNA and proteins.

7. Chemical Reactions

7.1 Types (NCERT Class 10, Ch. Chemical Reactions & Equations)

Type	General form	Example
Combination	A + B → AB	$CaO + H_2O \rightarrow Ca(OH)_2$
Decomposition	AB → A + B	$2H_2O \rightarrow 2H_2 + O_2$ (electrolysis); thermal/photo
Displacement	A + BC → AC + B	$Fe + CuSO_4 \rightarrow FeSO_4 + Cu$
Double displacement	AB + CD → AD + CB	$AgNO_3 + NaCl \rightarrow AgCl\downarrow + NaNO_3$ (precipitation)
Neutralisation	acid + base → salt + water	$HCl + NaOH \rightarrow NaCl + H_2O$

- **Exothermic** reactions release heat (respiration, combustion, quicklime + water); **endothermic** absorb heat (photosynthesis, thermal decomposition).
- **Balancing:** the number of atoms of each element must be equal on both sides (law of conservation of mass).

7.2 Redox Reactions & Oxidation Number

- **Oxidation:** loss of electrons / gain of oxygen / loss of hydrogen; **reduction:** gain of electrons / loss of oxygen / gain of hydrogen. Remember **OIL RIG** (Oxidation Is Loss, Reduction Is Gain of electrons).
- **Oxidising agent** gets reduced; **reducing agent** gets oxidised.
- **Rules for oxidation number:** free element = 0; O = −2 (−1 in peroxides); H = +1 (−1 in metal hydrides); the sum equals the overall charge.
- **Corrosion** (rusting of iron) and **rancidity** (oxidation of fats/oils) are everyday redox processes.

Worked Example 5. Find the oxidation number of sulphur in H_2SO_4.

Let it be x. $2(+1) + x + 4(-2) = 0 \Rightarrow 2 + x - 8 = 0 \Rightarrow$ **x = +6**.

Worked Example 6. Balance: $Fe + O_2 \rightarrow Fe_2O_3$.

$4Fe + 3O_2 \rightarrow 2Fe_2O_3$ (8 Fe? no — 4 Fe and 6 O on each side). Check: LHS 4 Fe, 6 O; RHS 2×2 = 4 Fe, 2×3 = 6 O. ✓

8. Acids, Bases & Salts

8.1 Definitions (NCERT Class 10, Ch. Acids, Bases & Salts)

- **Acids** give H^+ (H_3O^+) in water — sour, turn blue litmus red (HCl, H_2SO_4, HNO_3, citric acid).
- **Bases** give OH^- in water — bitter, soapy, turn red litmus blue; a water-soluble base is an **alkali** (NaOH, KOH, $Ca(OH)_2$).
- Acid + metal → salt + **hydrogen gas** (burns with a "pop"). Acid + metal carbonate/bicarbonate → salt + water + **CO_2** (turns lime water milky).

8.2 The pH Scale

$pH = -\log[H^+]$, ranging **0 to 14** at 25 °C.

pH	Nature
< 7	Acidic (lower pH → stronger acid)
= 7	Neutral (pure water)
> 7	Basic/alkaline

Daily-life values: gastric juice ~1.2, lemon juice ~2.2, vinegar ~3, black coffee ~5, milk ~6.5, pure water 7, blood ~7.4, baking-soda solution ~9, milk of magnesia ~10.

> **Key exam fact:** Adding **lemon juice (a citric-acid solution) to water lowers its pH below 7** (makes it acidic), because the H^+ concentration rises.

Importance of pH: tooth decay below pH 5.5 (bacteria act on sugar → acids); antacids (milk of magnesia) neutralise excess stomach acid; soil pH affects crops; bee-sting (acidic) soothed by baking soda, wasp-sting (basic) by vinegar.

8.3 Indicators

Indicator	In acid	In base
Litmus	Red	Blue
Methyl orange	Red/pink	Yellow
Phenolphthalein	Colourless	Pink
Turmeric	Yellow	Red/brown

Olfactory indicators: onion, vanilla, clove (change smell).

8.4 Neutralisation

Acid + Base → Salt + Water (a specific double-displacement reaction), e.g., HCl + NaOH → NaCl + H_2O. Strong acid + strong base gives a **neutral** salt; strong acid + weak base → acidic salt; weak acid + strong base → basic salt.

8.5 Important Salts — Formula, Preparation & Uses

Common name	Chemical name	Formula	Key use
Common salt	Sodium chloride	NaCl	Food; raw material for NaOH, $NaHCO_3$
Caustic soda	Sodium hydroxide	NaOH	Soap, paper (from chlor-alkali process)
Baking soda	Sodium hydrogen carbonate	$NaHCO_3$	Antacid, baking, fire extinguishers
Washing soda	Sodium carbonate decahydrate	$Na_2CO_3 \cdot 10H_2O$	Cleaning, softening hard water, glass
Bleaching powder	Calcium oxychloride	$CaOCl_2$	Bleaching, disinfecting water
Plaster of Paris	Calcium sulphate hemihydrate	$CaSO_4 \cdot \frac{1}{2}H_2O$	Plaster casts, ceilings, moulds
Gypsum	Calcium sulphate dihydrate	$CaSO_4 \cdot 2H_2O$	Raw material for PoP, cement
Blue vitriol	Copper sulphate pentahydrate	$CuSO_4 \cdot 5H_2O$	Fungicide, electroplating
Washing soda / lime	Slaked lime	$Ca(OH)_2$	Whitewashing, mortar
Quicklime	Calcium oxide	CaO	Cement, steel, whitewash

- **Water of crystallisation:** fixed water molecules in a crystal ($CuSO_4 \cdot 5H_2O$ is blue; on heating it turns white anhydrous).
- **Chlor-alkali process:** electrolysis of brine → NaOH + Cl_2 + H_2.
- On heating gypsum to ~373 K → **Plaster of Paris**; PoP + water → gypsum (sets hard).

> **Worked Example 7.** Why does milk of magnesia relieve acidity?

> It is a mild base, $Mg(OH)_2$. It **neutralises** excess HCl in the stomach: $Mg(OH)_2 + 2HCl \rightarrow MgCl_2 + 2H_2O$, raising the pH toward normal.

---

9. Carbon & Its Compounds

9.1 Bonding & Allotropes (NCERT Class 10, Ch. Carbon and Its Compounds)

- Carbon (Z = 6, config 2,4) forms **four covalent bonds** (tetravalency) and shows **catenation** (self-linking into long chains, branches, and rings) — the reason for millions of carbon compounds.
- **Allotropes: diamond** (each C bonded to 4 others, hardest natural substance, non-conductor), **graphite** (layered, soft, slippery, conducts electricity — used as electrodes/lubricant), **fullerene/buckminsterfullerene C_{60}** (spherical), graphene, carbon nanotubes.

9.2 Hydrocarbons

Series	General formula	Bond	Example
Alkanes (saturated)	C_nH_{2n+2}	Single	CH_4 methane, C_2H_6 ethane
Alkenes (unsaturated)	C_nH_{2n}	One double	C_2H_4 ethene
Alkynes (unsaturated)	C_nH_{2n-2}	One triple	C_2H_2 ethyne (acetylene)

- **Saturated** hydrocarbons burn with a clean blue flame; **unsaturated** ones give a sooty yellow flame and undergo **addition** reactions (hydrogenation of oils → vanaspati using Ni catalyst).
- **Homologous series:** compounds with the same general formula and functional group, differing by **$–CH_2–$ (14 u)**; they show a gradation in physical properties and similar chemical properties.

9.3 Functional Groups

Group	Formula	Class	Example
Halo	–X (Cl, Br)	Haloalkane	Chloroethane
Hydroxyl	–OH	Alcohol	Ethanol C_2H_5OH
Aldehyde	–CHO	Aldehyde	Ethanal
Ketone	>C=O	Ketone	Propanone (acetone)
Carboxyl	–COOH	Carboxylic acid	Ethanoic acid CH_3COOH (acetic acid; vinegar)

9.4 Isomerism

Compounds with the same molecular formula but different structures (hence different properties), e.g., **butane and isobutane (C_4H_{10})**. Isomerism starts from C_4 in alkanes.

9.5 Important Compounds

- **Ethanol (C_2H_5OH):** alcohol in beverages; solvent; denatured with methanol for industrial use.
- **Ethanoic acid (CH_3COOH):** 5–8% solution = **vinegar**; freezes to "glacial" acetic acid.
- Soaps (sodium salts of fatty acids) clean by forming **micelles**; detergents work even in hard water.

9.6 Polymers, Carbohydrates, Proteins & Fats (Class 12 basics)

Polymer	Type	Use
Polythene	Addition (from ethene)	Bags, packaging
PVC (polyvinyl chloride)	Addition	Pipes, insulation, raincoats
Nylon	Condensation	Ropes, fabrics, parachutes
Terylene/PET	Condensation (polyester)	Fabrics, bottles
Bakelite	Thermosetting	Switches, handles
Natural rubber	Polymer of isoprene; **vulcanised** with sulphur for strength	Tyres

- **Carbohydrates** (C, H, O): monosaccharides (glucose, fructose), disaccharides (sucrose, lactose), polysaccharides (starch, cellulose, glycogen); primary energy source.
- **Proteins:** polymers of **amino acids** (peptide bonds); enzymes, muscle, structural roles.
- **Fats/lipids:** esters of glycerol and fatty acids; energy store; saturated (animal) vs unsaturated (vegetable) fats.

> **Worked Example 8.** Write the molecular formula and name of the first three members of the alkane series.

> Methane **CH_4**, Ethane **C_2H_6**, Propane **C_3H_8** (general formula C_nH_{2n+2}).

---

10. Metallurgy

10.1 Physical Properties of Metals (NCERT Class 10, Ch. Metals & Non-Metals)

Metals are lustrous, **malleable** (beaten into sheets), **ductile** (drawn into wires), sonorous, good conductors of heat and electricity, and generally solid with high melting points.

- Most ductile/malleable: **gold and silver**. Best conductor: **silver**, then copper.
- Exceptions: mercury is liquid; sodium/potassium are soft (cut with a knife); non-metals are generally brittle, dull, poor conductors (except **graphite**, which conducts; **diamond**, hardest).

10.2 Reactivity (Activity) Series

K > Na > Ca > Mg > Al > Zn > Fe > Pb > (H) > Cu > Hg > Ag > Au (decreasing reactivity).

- A more reactive metal displaces a less reactive one from its salt solution.
- Metals above hydrogen displace H_2 from dilute acids; those below (Cu, Ag, Au) do not.

10.3 Extraction Flow (depends on reactivity)

Reactivity	Occurrence	Extraction method
High (K, Na, Ca, Mg, Al)	Combined	**Electrolysis** of molten ore
Medium (Zn, Fe, Pb)	Oxides/carbonates/sulphides	Roasting/calcination → **reduction** (with C/CO or thermite)
Low (Cu, Ag, Au, Hg)	Often **free (native)**	Simple heating/roasting of ore

Key steps: **concentration of ore** → **roasting** (sulphide, in air) / **calcination** (carbonate, limited air) → **reduction to metal** → **refining (electrolytic)**. **Thermite reaction:** $Fe_2O_3 + 2Al \rightarrow 2Fe + Al_2O_3$ + heat (used to weld rail tracks).

10.4 Corrosion & Prevention

- **Rusting** of iron (hydrated iron(III) oxide, $Fe_2O_3 \cdot xH_2O$) needs **both air (oxygen) and moisture**. Copper forms a green carbonate coating; silver blackens (sulphide).
- **Prevention:** painting, oiling/greasing, **galvanisation** (zinc coating), tinning, **electroplating**, alloying, and cathodic (sacrificial) protection.

10.5 Alloys — Composition & Uses

Alloy	Composition	Use
Brass	Cu + Zn	Utensils, fittings
Bronze	Cu + Sn	Statues, medals, bells
Steel	Fe + C (up to ~2%)	Construction
Stainless steel	Fe + Cr + Ni	Cutlery, utensils (rust-resistant)
Solder	Pb + Sn	Joining/soldering wires (low m.p.)
Duralumin	Al + Cu + Mg + Mn	Aircraft bodies (light & strong)
Amalgam	Any metal + Hg	Dental fillings
German silver	Cu + Zn + Ni	Ornaments (no silver in it)

Alloys are **homogeneous mixtures**; alloying improves hardness, corrosion resistance, and lowers melting point (solder).

> **Worked Example 9.** Why is zinc coated on iron objects in galvanisation?

> Zinc is **more reactive** than iron; it corrodes preferentially (sacrificial protection) and its coating physically blocks air and moisture from the iron, preventing rust even if the layer is scratched.

---

11. Environmental Chemistry

11.1 Air Pollution & Acid Rain

- Oxides of sulphur and nitrogen (**SO_2, NO_2**) from fossil-fuel burning dissolve in rain to form **sulphuric and nitric acids** → **acid rain** (pH < 5.6): damages buildings (marble — "stone cancer"), soil, and aquatic life.

11.2 Ozone Depletion

- The stratospheric **ozone (O_3)** layer absorbs harmful **UV** radiation. **CFCs (chlorofluorocarbons)** release chlorine that destroys ozone, creating the "ozone hole" (over Antarctica). The **Montreal Protocol (1987)** phases out CFCs.

11.3 Greenhouse Effect & Global Warming

- Greenhouse gases (**CO_2, CH_4, N_2O, water vapour, CFCs**) trap infrared radiation and warm the Earth. Excess emissions → **global warming**, climate change, rising sea levels. Governed globally by frameworks like the Paris Agreement.

11.4 Green Chemistry

Designing chemical processes that reduce or eliminate hazardous substances — atom economy, safer solvents, renewable feedstocks, less waste (the basis of sustainable "green" manufacturing).

> **Worked Example 10.** Why is acid rain harmful to the Taj Mahal?

> The Taj is made of **marble ($CaCO_3$)**. Acids in rain react: $CaCO_3 + H_2SO_4 \rightarrow CaSO_4 + H_2O + CO_2$, corroding and yellowing the marble ("marble/stone cancer").

---

12. PYQ Corner — RRB JE CBT-2 2025 (Chemistry Questions Solved)

PYQ 1. Alloys are examples of which type of mixture?

Homogeneous mixtures — metals melted together mix uniformly at the atomic level (e.g., brass = Cu + Zn), giving a single-phase, uniform composition (§2.3).

PYQ 2. 40 g of NaCl is dissolved in 200 g of water. Find the mass percent of the solution.

Mass of solution = 40 + 200 = 240 g. Mass % = (40/240) × 100 = **16.67 %** (§3.3, W.E. 2).

PYQ 3. An element has atomic number 8. Name it.

Z = 8 ⇒ **oxygen** (configuration 2, 6; valency 2) (§4.4, W.E. 4).

PYQ 4. Why do covalent compounds have low melting and boiling points?

Because the **intermolecular forces between covalent molecules are weak**, so little energy is needed to separate them — even though the intramolecular covalent bonds themselves are strong (§6.2).

PYQ 5. Calculate the molecular mass of S_8.

Atomic mass of S = 32 u. S_8 = 8 × 32 = **256 u** (§3.2).

PYQ 6. What happens to the pH of water when a few drops of lemon juice are added?

Lemon juice contains citric acid; it releases H^+ ions, so the **pH decreases below 7** (the water becomes acidic) (§8.2).

PYQ 7. The property by which a metal can be drawn into thin wires is called:

Ductility (drawing into wires); malleability = beaten into sheets (§10.1). *(Shared with the physics/materials PYQ set.)*

PYQ 8. Differentiate a mixture from a compound (one key point).

A **compound** has a fixed composition with new properties and is separable only chemically; a **mixture** has a variable composition, retains component properties, and is separated by physical methods (§2.2).

13. Practice MCQs (25)

Q1. Which of the following is a homogeneous mixture?

(a) sand + water (b) oil + water (c) brass (d) iron filings + sulphur

Q2. The process of a solid changing directly into vapour is:

(a) condensation (b) sublimation (c) evaporation (d) fusion

Q3. Which technique separates the coloured components of a dye?

(a) filtration (b) distillation (c) chromatography (d) centrifugation

Q4. The number of molecules in 1 mole of any substance is:

(a) 6.022×10^{22} (b) 6.022×10^{23} (c) 3.011×10^{23} (d) 1.6×10^{19}

Q5. The molar mass of CO_2 is:

(a) 22 g (b) 28 g (c) 44 g (d) 48 g

Q6. 20 g of sugar is dissolved in 80 g of water. The mass percent of sugar is:

(a) 16 % (b) 20 % (c) 25 % (d) 80 %

Q7. The volume occupied by 1 mole of any gas at STP is:

(a) 11.2 L (b) 22.4 L (c) 24 L (d) 6.022 L

Q8. The neutron was discovered by:

(a) Rutherford (b) J. J. Thomson (c) Chadwick (d) Bohr

Q9. The maximum number of electrons in the M shell is:

(a) 2 (b) 8 (c) 18 (d) 32

Q10. An atom with atomic number 8 has valency:

(a) 1 (b) 2 (c) 6 (d) 8

Q11. The modern periodic law is based on:

(a) atomic mass (b) atomic number (c) valency (d) density

Q12. The most electronegative element is:

(a) oxygen (b) chlorine (c) fluorine (d) nitrogen

Q13. Down a group in the periodic table, atomic size:

(a) decreases (b) increases (c) stays the same (d) first increases then decreases

Q14. Covalent compounds generally have:

(a) high melting points (b) low melting points (c) high conductivity in solid state (d) ionic lattices

Q15. The shape of a methane (CH_4) molecule is:

(a) linear (b) trigonal planar (c) tetrahedral (d) bent

Q16. $Fe + CuSO_4 \rightarrow FeSO_4 + Cu$ is a:

(a) combination reaction (b) decomposition (c) displacement (d) double displacement

Q17. The oxidation number of sulphur in H_2SO_4 is:

(a) +2 (b) +4 (c) +6 (d) −2

Q18. A solution turns phenolphthalein pink. It is:

(a) acidic (b) basic (c) neutral (d) a salt of a strong acid

Q19. Adding lemon juice to water makes its pH:

(a) increase above 7 (b) decrease below 7 (c) stay exactly 7 (d) reach 14

Q20. The chemical name of baking soda is:

(a) sodium carbonate (b) sodium hydroxide (c) sodium hydrogen carbonate (d) calcium carbonate

Q21. Plaster of Paris is:

(a) $CaSO_4 \cdot 2H_2O$ (b) $CaSO_4 \cdot \frac{1}{2}H_2O$ (c) $CaCO_3$ (d) CaO

Q22. The general formula of alkanes is:

(a) C_nH_{2n} (b) C_nH_{2n-2} (c) C_nH_{2n+2} (d) C_nH_n

Q23. The property of carbon to form long chains by self-linking is called:

(a) tetravalency (b) catenation (c) isomerism (d) hybridisation

Q24. Coating iron with zinc to prevent rust is called:

(a) tinning (b) galvanisation (c) alloying (d) annealing

Q25. Acid rain is mainly caused by oxides of:

(a) carbon and hydrogen (b) sulphur and nitrogen (c) sodium and calcium (d) oxygen and helium

Answer Key with One-Line Reasons

Q	Ans	Reason
1	c	Brass (Cu+Zn) is a uniform, single-phase alloy
2	b	Solid → vapour directly = sublimation
3	c	Chromatography separates by differential adsorption
4	b	Avogadro's number = 6.022×10^{23}
5	c	$12 + 2(16) = 44$ g/mol
6	b	$20/(20+80) \times 100 = 20$ %
7	b	Molar volume at STP = 22.4 L
8	c	James Chadwick discovered the neutron (1932)
9	c	$2n^2 = 2(3^2) = 18$
10	b	Oxygen (2,6) needs 2 electrons → valency 2
11	b	Properties are periodic functions of atomic number
12	c	Fluorine is the most electronegative element
13	b	New shells added → size increases down a group
14	b	Weak intermolecular forces → low m.p./b.p.
15	c	sp^3 hybridisation → tetrahedral
16	c	Fe displaces less reactive Cu from its salt
17	c	$2(+1) + x + 4(-2) = 0 \rightarrow x = +6$
18	b	Phenolphthalein is pink only in bases
19	b	Citric acid raises $[H^+]$, lowering pH
20	c	$NaHCO_3$ = sodium hydrogen carbonate
21	b	PoP = $CaSO_4 \cdot \frac{1}{2}H_2O$
22	c	Saturated alkanes: C_nH_{2n+2}
23	b	Catenation = self-linking of carbon
24	b	Zinc coating = galvanisation
25	b	SO_2 and NO_2 form H_2SO_4/HNO_3 in rain

14. Rapid-Revision Tables

Mole & Concentration

- n = mass/molar mass = particles/N_A = volume(STP)/22.4 L; N_A = 6.022×10^{23}
- **Mass % = (mass solute / mass solution) × 100**; mass solution = solute + solvent
- Molarity = mol/L solution; Molality = mol/kg solvent; PV = nRT; molar volume 22.4 L at STP

- Molecular masses to memorise: H_2O 18, CO_2 44, NaCl 58.5, H_2SO_4 98, glucose 180, **S_8 256**

Atomic Structure

- neutrons = A − Z; shell capacity $2n^2$; subshells s2 p6 d10 f14
- O (8) = 2,6; Na (11) = 2,8,1; Cl (17) = 2,8,7
- Aufbau (energy order) · Pauli (no identical 4 quantum numbers) · Hund (singly fill first)

Bonding

- Ionic → transfer, high m.p., conduct when molten/aqueous
- **Covalent → sharing, low m.p./b.p. (weak intermolecular forces), non-conducting**
- Shapes: $BeCl_2$ linear, BF_3 trigonal planar, CH_4 tetrahedral, NH_3 pyramidal, H_2O bent

Acids, Bases & Salts

- pH 0–14; **< 7 acidic, 7 neutral, > 7 basic**; lemon juice lowers pH
- Litmus: acid→red, base→blue; phenolphthalein pink in base
- Baking soda $NaHCO_3$ · Washing soda $Na_2CO_3{\cdot}10H_2O$ · Bleaching powder $CaOCl_2$ · PoP $CaSO_4{\cdot}½H_2O$ · Caustic soda NaOH

Carbon

- Tetravalency + catenation; allotropes diamond/graphite/fullerene
- Alkane C_nH_{2n+2}, alkene C_nH_{2n}, alkyne C_nH_{2n-2}; homologous difference $–CH_2–$ (14 u)
- Functional groups: –OH alcohol, –CHO aldehyde, –COOH acid, >C=O ketone

Metallurgy & Environment

- Activity series: K Na Ca Mg Al Zn Fe Pb (H) Cu Hg Ag Au
- High reactivity → electrolysis; medium → reduction; low → native/heating
- Rusting needs air + moisture; prevent by galvanising, painting, alloying
- Alloys are **homogeneous mixtures**: brass Cu+Zn, bronze Cu+Sn, steel Fe+C, stainless steel Fe+Cr+Ni
- Acid rain: SO_2/NO_2 · Ozone hole: CFCs · Greenhouse: CO_2/CH_4

End of GA-02. See GA-01 for the Physics companion chapter.

GA-03 | Basics of Computer Applications

RRB JE CBT-2 (CEN 05/2025) — General Abilities | Weightage: 10 Questions

> **Exam angle:** RRB asks direct, factual, application-level questions — shortcut keys, MS Office functions, memory types, security terms, open-source concepts. This chapter covers every sub-topic seen in actual 2025 CBT-2 papers, followed by a PYQ Corner, 25 practice MCQs, and rapid-revision tables.

---

1. Computer Fundamentals & Architecture

1.1 What is a Computer?

A computer is an electronic device that accepts data (**input**), processes it according to stored instructions (**processing**), produces results (**output**), and stores data for future use (**storage**). This is the **IPOS cycle**: Input → Process → Output → Storage.

1.2 Generations of Computers

Generation	Period	Technology	Examples
First	1940–56	Vacuum tubes	ENIAC, UNIVAC
Second	1956–63	Transistors	IBM 1401, IBM 7094
Third	1964–71	Integrated Circuits (IC)	IBM 360
Fourth	1971–present	Microprocessors (VLSI)	IBM PC, Apple II
Fifth	Present & beyond	AI / ULSI / Parallel processing	AI systems, robotics

- **Father of Computer:** Charles Babbage (Analytical Engine).
- **Father of Modern Computer / Stored-program concept:** John von Neumann.
- **First electronic general-purpose computer:** ENIAC.
- **India's first supercomputer:** PARAM 8000 (C-DAC, 1991).

1.3 The Central Processing Unit (CPU)

The CPU is the **"brain of the computer"**. It has three main parts:

Component	Full Form	Function
ALU	Arithmetic Logic Unit	Performs all arithmetic (+, −, ×, ÷) and logical (AND, OR, NOT, comparisons) operations
CU	Control Unit	Directs and coordinates all operations; fetches, decodes and executes instructions; does **not** process data itself
Registers	—	Small, fastest storage locations inside the CPU that hold data/instructions currently being processed

Important registers:

Register	Role
Accumulator (AC)	Holds intermediate arithmetic/logic results
Program Counter (PC)	Holds address of the **next** instruction
Instruction Register (IR)	Holds the **current** instruction being executed
Memory Address Register (MAR)	Holds address of memory location to be accessed
Memory Data/Buffer Register (MDR/MBR)	Holds data being transferred to/from memory

- **Instruction cycle:** Fetch → Decode → Execute → Store.
- **Clock speed** is measured in **Hertz (GHz)** — cycles per second.
- **Word length** — number of bits the CPU processes at a time (32-bit, 64-bit).

1.4 Data Measurement Units

Unit	Value
1 Bit	Binary digit (0 or 1) — smallest unit
1 Nibble	4 bits
1 Byte	8 bits
1 KB	1024 Bytes
1 MB	1024 KB
1 GB	1024 MB
1 TB	1024 GB
1 PB	1024 TB

---

2. Memory Hierarchy ★ (Frequently asked)

Memory is arranged from **fastest & smallest** (top) to **slowest & largest** (bottom):

Registers → Cache → Main memory (RAM) → Secondary storage (HDD/SSD) → Tertiary (tape/optical)

2.1 Primary Memory (Main Memory)

(a) RAM — Random Access Memory — volatile (contents lost when power is off); holds programs/data currently in use.

Feature	SRAM (Static RAM)	DRAM (Dynamic RAM)
Storage element	Flip-flops (6 transistors)	Capacitor + transistor
Refreshing	**NOT required ★**	**Required** periodically (charge leaks)
Speed	Faster	Slower
Cost	Costlier	Cheaper
Density	Lower (bulkier per bit)	Higher (more bits per chip)
Power	Lower at idle	Higher (refresh cycles)
Used in	**Cache memory**	**Main memory (system RAM)**

> **2025 CBT-2 asked:** Which memory does *not* need refreshing? → **SRAM** (it uses flip-flops, so data stays as long as power is on; DRAM stores charge on capacitors that leak and must be refreshed thousands of times per second).

(b) ROM — Read Only Memory — non-volatile; holds firmware/boot instructions (BIOS).

ROM Type	Full Form	Key Point
PROM	Programmable ROM	Written **once** by user; cannot be erased
EPROM	Erasable Programmable ROM	Erased by **ultraviolet (UV) light**, reprogrammable
EEPROM	Electrically Erasable PROM	Erased **electrically**, byte-by-byte
Flash memory	—	A type of EEPROM erased in blocks; used in pen drives, SSDs, memory cards

2.2 Cache Memory

- Very fast **SRAM-based** memory between CPU and RAM.
- Stores frequently used data/instructions to reduce average access time.
- Levels: **L1** (inside CPU core, fastest, smallest), **L2**, **L3** (shared, largest, slowest of the three).

2.3 Secondary Storage

Device	Type	Notes
Hard Disk Drive (HDD)	Magnetic	Rotating platters; capacity in TB
Solid State Drive (SSD)	Flash (electronic)	No moving parts; much faster than HDD
CD / DVD / Blu-ray	Optical	CD ≈ 700 MB, DVD ≈ 4.7 GB, Blu-ray ≈ 25 GB/layer
Pen drive / Memory card	Flash	Portable, uses USB
Magnetic tape	Magnetic	Sequential access; backups/archives

- **Virtual memory:** part of the hard disk used as an extension of RAM by the operating system.
- **Buffer:** temporary holding area for data being transferred between devices.

---

3. Input & Output Devices

Input Devices	Output Devices	Both (I/O)
Keyboard, Mouse, Scanner, Joystick, Light pen, Trackball, Microphone, Webcam, Barcode reader, OMR, OCR, MICR (bank cheques), Biometric sensor, Digitizer/Graphics tablet	Monitor (VDU), Printer, Plotter, Speaker, Projector, Headphones	Touchscreen, Modem, Network card, Digital camera, Headset with mic, Fax machine, Multifunction printer

Printers:

Type	Category	Notes
Dot matrix	Impact	Strikes ribbon; noisy; can print carbon copies
Daisy wheel	Impact	Letter-quality, character printer
Inkjet	Non-impact	Sprays ink droplets
Laser	Non-impact	Uses toner + drum; fast, high quality
Plotter	—	Draws large engineering drawings/graphs

- Monitor sharpness → **resolution** (pixels); printer quality → **DPI** (dots per inch); printer speed → **PPM** (pages per minute).
- **OMR** = Optical Mark Recognition (exam answer sheets); **OCR** = Optical Character Recognition; **MICR** = Magnetic Ink Character Recognition (cheque numbers).

---

4. Software Concepts

Software = set of programs/instructions. Two broad types:

Type	Description	Examples
System software	Controls & manages hardware; platform for other software	Operating systems, device drivers, utilities (antivirus, disk cleanup), language translators
Application software	Performs specific user tasks	MS Word, Excel, browsers, Tally, Photoshop

Language translators:

Translator	Function
Compiler	Translates entire high-level program to machine code at once (C, C++)
Interpreter	Translates and executes line by line (Python, BASIC)
Assembler	Translates assembly language to machine code

Software licence types:

Term	Meaning
Proprietary	Source code closed; paid licence (Windows, MS Office)
Open-source	**Source code freely available to view, modify and redistribute** (Linux, LibreOffice, Firefox, Android/AOSP)
Freeware	Free to use, but source code not open (Adobe Reader)
Shareware	Free trial, then payment (WinRAR)

---

5. Operating Systems ★

An **Operating System (OS)** is system software that acts as an **interface between the user and hardware** and manages all resources.

Functions of an OS:

1. **Process management** — scheduling CPU among programs.
2. **Memory management** — allocating/deallocating RAM.

3. **File management** — creating, organizing, protecting files/folders.
4. **Device management** — via device drivers; I/O control.
5. **Security** — user authentication, access control.
6. **User interface** — CLI (command line) or GUI (graphical).

Popular Operating Systems:

OS	Developer	Type	Key facts
Windows	Microsoft	Proprietary, GUI	Windows 11 latest desktop version; file system NTFS
Linux	Linus Torvalds (kernel, 1991)	**Open-source ★**	Free; distributions: Ubuntu, Fedora, Debian, Red Hat, BOSS (India, C-DAC)
macOS	Apple	Proprietary	Runs only on Apple Macs; UNIX-based
Android	Google	Open-source (Linux-kernel based)	World's most used mobile OS
iOS	Apple	Proprietary	iPhone/iPad
MS-DOS	Microsoft	CLI, single-user	Historic; commands like DIR, COPY
UNIX	AT&T Bell Labs	Multi-user	Ken Thompson & Dennis Ritchie

> **2025 CBT-2 asked:** Which OS is open-source? → **Linux**. Its source code is publicly available and can be modified/redistributed under the GNU GPL. Windows and macOS are proprietary.

- **Booting** = starting the computer and loading the OS. Cold boot = from power-off; warm boot = restart (Ctrl+Alt+Del).
- **Kernel** = core of the OS, always resident in memory.
- **Multitasking** = several programs at once; **multiprocessing** = multiple CPUs; **multi-user** = many users share one system; **real-time OS** = instant response (used in railways signalling, embedded systems).

---

6. MS Word (Word Processing) ★

- Default file extension: **.docx** (older: .doc). A Word file is called a **Document**.
- Default view: Print Layout. Ruler/gridlines under **View** tab; margins/orientation under **Layout**; header-footer, page number, tables, pictures under **Insert**; spelling & grammar under **Review** (shortcut **F7**).

6.1 Function Keys F1–F12 (Windows/MS Office) ★

Key	Function
F1	Help
F2	Rename selected file/folder (Windows); **in MS Word: move selected text/graphic** — select text → press F2 → click new location → press Enter ★
F3	Search (Windows); Shift+F3 in Word = change case
F4	Repeat last action (Word); Alt+F4 = close window/program
F5	Refresh (browser/Windows); Find & Replace "Go To" (Word); start slideshow (PowerPoint)
F6	Move cursor between screen panes / to address bar (browsers)
F7	Spelling & Grammar check (Word)
F8	Extend selection (Word); Safe Mode boot menu (Windows startup)
F9	Update fields (Word); refresh (Outlook send/receive)
F10	Activate menu bar; Shift+F10 = right-click menu
F11	Full-screen mode (browsers); new chart sheet (Excel)
F12	Save As (Word/Excel/PowerPoint)

> **2025 CBT-2 asked:** Which key moves selected text in MS Word? → **F2** (select the text, press F2, place cursor at destination, press Enter).

6.2 Common MS Word Shortcuts

Shortcut	Action	Shortcut	Action
Ctrl+N	New document	Ctrl+B	Bold
Ctrl+O	Open	Ctrl+I	Italic
Ctrl+S	Save	Ctrl+U	Underline
Ctrl+P	Print	Ctrl+L / E / R / J	Align left / centre / right / justify
Ctrl+C / X / V	Copy / Cut / Paste	Ctrl+K	Insert hyperlink
Ctrl+Z / Y	Undo / Redo	Ctrl+F	Find
Ctrl+A	Select all	Ctrl+H	Replace
Ctrl+Home / End	Start / end of document	Ctrl+Enter	Page break
Ctrl+Shift+C	Copy formatting (Format Painter)	Ctrl+] / [	Increase / decrease font size by 1 pt
Ctrl+=	Subscript	Ctrl+Shift+=	Superscript

---

7. MS Excel (Spreadsheet) ★

- File extension: **.xlsx** (older: .xls). File = **Workbook**; each page = **Worksheet**; intersection of row & column = **Cell** (address like A1, B5).

- Excel columns: A, B, C…; rows: 1, 2, 3…. Modern Excel: 1,048,576 rows × 16,384 columns (last column **XFD**).
- Every formula begins with **=**.

7.1 Cell References

Type	Example	Behaviour when copied
Relative	=A1+B1	Adjusts with position
Absolute	=$A$1	Never changes ($ locks row & column); toggle with **F4**
Mixed	=$A1 or =A$1	One part locked

7.2 Common Functions ★

Function	Syntax	Purpose
SUM	=SUM(A1:A10)	Adds numbers
AVERAGE	=AVERAGE(A1:A10)	Arithmetic mean
COUNT	=COUNT(A1:A10)	Counts cells containing **numbers**
COUNTA	=COUNTA(A1:A10)	Counts non-empty cells
MAX / MIN	=MAX(range)	Largest / smallest value
IF	=IF(A1>40,"Pass","Fail")	Logical test with two outcomes
VLOOKUP	=VLOOKUP(value, table, col_index, FALSE)	Looks up a value in the **first column** of a table and returns a value from another column in the same row
HLOOKUP	=HLOOKUP(...)	Horizontal lookup (first row)
TEXT	**=TEXT(value, "format")**	**Converts a numeric value to text in a specified number format** ★ e.g. =TEXT(1234.5,"₹#,##0.00") → "₹1,234.50"; =TEXT(TODAY(),"DD-MM-YYYY")
CONCATENATE / &	=A1&B1	Joins text strings
TODAY() / NOW()	—	Current date / date-time
ROUND	=ROUND(A1,2)	Rounds to given decimals

> **2025 CBT-2 asked:** Function that converts a value to text in a given format? → **TEXT()**. It formats numbers/dates as text strings, e.g. =TEXT(0.25,"0%") returns "25%".

7.3 Charts & Other Features

- Chart types: Column, Bar, Line, **Pie** (parts of a whole), Scatter (correlation), Area. Insert via **Insert tab → Charts**. **F11** creates an instant chart on a new sheet.
- **Fill handle** (small square at cell corner) drags formulas/series.
- **Pivot Table** summarizes large data; **Conditional formatting** colours cells by rules; **Freeze Panes** (View tab) keeps headings visible; **Sort & Filter** under Data tab.
- Excel shortcut specials: Ctrl+; = today's date, Ctrl+Shift+; = current time, Alt+= = AutoSum.

---

8. MS PowerPoint (Presentations) ★

- File extension: **.pptx** (older: .ppt); a file is a **Presentation** made of **Slides**. Slide show file: .ppsx.
- **Views:** Normal, Outline, **Slide Sorter** (thumbnails of all slides), Notes Page, Reading, **Slide Show** (F5 from start; Shift+F5 from current slide).
- **Slide Master** (View tab) controls formatting of all slides at once.
- **Design tab → Themes / Templates:** ready-made combinations of colours, fonts, effects and background styles applied to the whole presentation. ★
- **Transitions** = effects between slides; **Animations** = effects on objects within a slide.
- New slide: Ctrl+M. End show: Esc.

> **2025 CBT-2 asked:** Where do you apply a design template/theme in PowerPoint? → the **Design tab** (choose a theme/template; older versions: Format → Slide Design).

---

9. File Extensions — One Table ★

Extension	File Type	Extension	File Type
.docx / .doc	Word document	.txt	Plain text
.xlsx / .xls	Excel workbook	.rtf	Rich text
.pptx / .ppt	PowerPoint	.pdf	Portable Document Format (Adobe)
.jpg / .jpeg, .png, .gif, .bmp	Images	.html / .htm	Web page
.mp3, .wav	Audio	.mp4, .avi, .mkv	Video
.zip, .rar	Compressed archive	.exe	Windows executable
.accdb / .mdb	MS Access database	.csv	Comma-separated values
.c / .cpp / .py / .java	Source code	.dll	Dynamic link library
.tmp	Temporary file	.bak	Backup file

---

10. Internet Basics

Term	Meaning
Internet	Global network of networks; grew out of **ARPANET** (1969, USA)
WWW	World Wide Web — system of interlinked hypertext documents; invented by **Tim Berners-Lee (1989, CERN)**
Web browser	Software to access web pages — Chrome, Firefox, Edge, Safari, Opera; first popular browser: Mosaic
Search engine	Finds information on the web — Google, Bing, DuckDuckGo, Yahoo
URL	Uniform Resource Locator — address of a web page (protocol://domain/path)
HTTP / HTTPS	HyperText Transfer Protocol / Secure (encrypted with SSL/TLS)
HTML	HyperText Markup Language — language of web pages
ISP	Internet Service Provider (Jio, Airtel, BSNL)
Homepage	First page of a website
Download / Upload	Receiving from / sending to a remote server
Cookies	Small files a website stores on your computer to remember you

E-mail:

- Format: username@domain (e.g. rrbje@gmail.com). Invented by **Ray Tomlinson** (chose the @ sign).
- **CC** = Carbon Copy (all recipients visible); **BCC** = Blind Carbon Copy (hidden recipients).
- Protocols: **SMTP** (sending), **POP3 / IMAP** (receiving). Attachment = file sent with mail. Spam = unsolicited bulk mail.

---

11. Computer Networking (One Page)

Network	Coverage	Example
PAN	Personal, ~10 m	Bluetooth devices
LAN	Local Area Network — building/campus	Office network, computer lab
MAN	Metropolitan — a city	Cable TV network
WAN	Wide Area Network — country/world	**The Internet** (largest WAN)

Devices & terms:

Item	Role
Modem	Modulator-Demodulator; converts digital↔analog signals
Router	Connects different networks; routes data packets
Switch / Hub	Connect devices within a LAN (switch is intelligent, hub broadcasts)
IP address	Unique numerical address of a device (IPv4: 32-bit, e.g. 192.168.1.1; IPv6: 128-bit)
DNS	Domain Name System — translates domain names (google.com) into IP addresses ("phonebook of the Internet")
MAC address	Physical hardware address of a network card (48-bit)
Bandwidth	Data-carrying capacity, in bps/Mbps
TCP/IP	The basic protocol suite of the Internet
Wi-Fi	Wireless LAN (IEEE 802.11); Bluetooth: short-range (IEEE 802.15)
Topology	Layout of a network — bus, star (most common), ring, mesh, tree
Server / Client	Provider of services / requester of services

---

12. Computer Security ★★ (Guaranteed question zone)

12.1 Firewall ★

- A **firewall** is a security system (hardware, software, or both) that **monitors and controls incoming and outgoing network traffic** based on predefined security rules, and **blocks unauthorised access** to or from a private network.
- It sits **between a trusted internal network and an untrusted external network (Internet)** — like a security gate.
- A firewall does **not** primarily remove viruses (that is antivirus software); it filters traffic.

> **2025 CBT-2 asked:** Function of a firewall? → It **monitors/filters network traffic and prevents unauthorised access** to a computer or private network.

12.2 Malware & Threats

Threat	Definition
Virus	Malicious code that attaches itself to files/programs and spreads **when the host file is executed**; needs human action
Worm	Standalone malware that **self-replicates and spreads across networks without human action** or a host file
Trojan horse	Malware disguised as legitimate/useful software; does **not** self-replicate; opens backdoors
Phishing	Fraudulent emails/websites impersonating trusted entities to **steal passwords, banking and personal data**
Ransomware	Encrypts the victim's files and **demands payment (ransom)** for the decryption key (e.g. WannaCry, 2017)
Spyware	Secretly monitors user activity and sends data to attackers
Adware	Forces unwanted advertisements
Keylogger	Records every keystroke to capture passwords
Hacking	Unauthorised access to systems; "ethical hackers" test security legally
Spoofing	Faking identity (IP/email) to appear trusted
DoS/DDoS attack	Flooding a server with traffic to make it unavailable

12.3 Protective Measures

- **Antivirus software** — detects, quarantines and removes malware; must be **updated regularly** (examples: Norton, McAfee, Quick Heal, Kaspersky).
- **Strong password** — at least 8–12 characters mixing **uppercase, lowercase, digits and symbols**; never use name/DOB; change periodically; use different passwords per account; enable **two-factor authentication (2FA/OTP)**.
- **HTTPS + padlock icon** — indicates an **encrypted (SSL/TLS)** connection; always check before online payments.
- **Encryption** — converting readable data (plaintext) into coded form (ciphertext); decryption reverses it.
- **Backup** — regular copies of data guard against ransomware and disk failure.
- **CERT-In** — Indian Computer Emergency Response Team, national nodal agency for cyber security incidents (under MeitY). IT Act 2000 governs cyber law in India.

---

13. Websites & E-Governance in India

Initiative	Purpose
Digital India (2015)	Umbrella programme for digital empowerment
UMANG app	Single app for many government services
DigiLocker	Cloud storage of official documents (certificates, DL, Aadhaar)
UPI (NPCI)	Unified Payments Interface — instant bank transfers (BHIM app)
Aadhaar (UIDAI)	12-digit biometric identity number
IRCTC (irctc.co.in)	Online railway ticket booking
PMO India, india.gov.in	National portal of India
e-NAM	National Agriculture Market
CoWIN / eSanjeevani	Vaccination / telemedicine platforms
GeM	Government e-Marketplace for public procurement
Domain suffixes	.gov.in (Indian govt), .com (commercial), .org (organisation), .edu (education), .in (India country code)

14. Latest Tech — One-Liners

Technology	One-liner
Artificial Intelligence (AI)	Machines simulating human intelligence (learning, reasoning); e.g. ChatGPT (OpenAI), chess engines; subfields: Machine Learning, Deep Learning
Cloud computing	On-demand computing services (storage, servers, software) over the Internet — "pay as you go"; models: IaaS, PaaS, SaaS; providers: AWS, Azure, Google Cloud
IoT (Internet of Things)	Everyday devices (bulbs, ACs, watches) embedded with sensors and connected to the Internet
Big Data	Extremely large data sets analysed for patterns (Volume, Velocity, Variety)
Blockchain	Distributed, tamper-proof digital ledger; basis of Bitcoin cryptocurrency
5G	Fifth-generation mobile network; launched in India Oct 2022
Virtual/Augmented Reality	VR: fully simulated environment; AR: digital overlay on real world
Quantum computing	Uses qubits; can solve certain problems far faster than classical computers
Machine Learning	Systems that learn from data without explicit programming
Robotics/Drones	Automated machines; drones = unmanned aerial vehicles (UAV)

15. PYQ Corner — Actual RRB JE CBT-2 2025 Questions Solved

Q1. What is the primary function of a firewall in a computer network?

Answer: It monitors and controls incoming and outgoing network traffic based on security rules and **blocks unauthorised access** to the system/network. It acts as a barrier between a trusted internal network and the untrusted Internet.

Q2. In MS Word, which function key is used to move selected text or graphics to a new location?

Answer: F2. Select the text → press F2 → click at the destination → press **Enter**. (F4 repeats last action, F7 = spell check, F12 = Save As.)

Q3. Which MS Excel function converts a numeric value into text in a specified number format?

Answer: TEXT() — syntax =TEXT(value, format_text), e.g. =TEXT(1234.567,"0.00") → "1234.57". Useful for displaying dates/currency as formatted text.

Q4. Which of the following is an open-source operating system?

Answer: Linux. Its source code is freely available under the GNU General Public License and can be modified and redistributed. Windows and macOS are proprietary. (Android is also open-source, built on the Linux kernel.)

Q5. Which type of RAM does not require periodic refreshing?

Answer: SRAM (Static RAM) — it stores data in flip-flops which retain data as long as power is supplied. **DRAM** stores data as charge on capacitors that leak, so it must be refreshed continuously; hence "dynamic".

Q6. In MS PowerPoint, a design template/theme is applied from which tab?

Answer: The **Design tab** — it offers Themes (predefined sets of colours, fonts, effects and backgrounds) that can be applied to all slides or selected slides.

---

16. Practice MCQs (25) — Answers at the End

1. The "brain" of the computer is the: (a) RAM (b) CPU (c) ROM (d) Monitor
2. Which unit performs arithmetic and logical operations? (a) CU (b) ALU (c) MU (d) Register
3. 1 Byte equals: (a) 4 bits (b) 8 bits (c) 16 bits (d) 1024 bits
4. Cache memory is made of: (a) DRAM (b) SRAM (c) EPROM (d) Magnetic disk
5. Which memory is volatile? (a) ROM (b) Hard disk (c) RAM (d) Flash drive
6. EPROM is erased using: (a) Electric pulse (b) Ultraviolet light (c) Magnet (d) Heat
7. Which is NOT an input device? (a) Scanner (b) Joystick (c) Plotter (d) OMR
8. MICR is mainly used in: (a) Railways (b) Banks (c) Hospitals (d) Schools
9. Which translator converts a program line by line? (a) Compiler (b) Assembler (c) Interpreter (d) Linker
10. Which of these is application software? (a) Windows 11 (b) Linux (c) MS Excel (d) Device driver
11. The core part of an operating system is called the: (a) Shell (b) Kernel (c) BIOS (d) Registry
12. Ubuntu and Fedora are distributions of: (a) Windows (b) macOS (c) Linux (d) DOS
13. In MS Word, Ctrl+H opens: (a) Help (b) Hyperlink (c) Find and Replace (d) Header
14. F7 in MS Word is used for: (a) Save As (b) Spell check (c) Print (d) Thesaurus only
15. In Excel, =$B$2 is an example of: (a) Relative reference (b) Absolute reference (c) Mixed reference (d) Circular reference
16. Which Excel function counts only numeric cells? (a) COUNTA (b) COUNT (c) SUM (d) COUNTIF
17. VLOOKUP searches for a value in the: (a) Last column (b) First row (c) First column (d) Any column
18. Shift+F5 in PowerPoint: (a) Starts show from first slide (b) Starts show from current slide (c) Closes show (d) Prints slides

19. The view that shows thumbnails of all slides is: (a) Normal (b) Reading (c) Slide Sorter (d) Notes Page
20. .csv stands for: (a) Computer system values (b) Comma-separated values (c) Column-sorted values (d) Central stored values
21. WWW was invented by: (a) Bill Gates (b) Tim Berners-Lee (c) Vint Cerf (d) Ray Tomlinson
22. DNS translates: (a) IP to MAC (b) Domain names to IP addresses (c) HTML to HTTP (d) Bits to bytes
23. Malware that self-replicates over networks without a host file is a: (a) Virus (b) Trojan (c) Worm (d) Adware
24. An attack that encrypts files and demands payment is: (a) Phishing (b) Spoofing (c) Ransomware (d) Keylogging
25. HTTPS indicates: (a) High-speed connection (b) Encrypted secure connection (c) Government site (d) Free site

Answers: 1-b, 2-b, 3-b, 4-b, 5-c, 6-b, 7-c, 8-b, 9-c, 10-c, 11-b, 12-c, 13-c, 14-b, 15-b, 16-b, 17-c, 18-b, 19-c, 20-b, 21-b, 22-b, 23-c, 24-c, 25-b

---

17. Rapid-Revision Tables

17.1 Ten Shortcuts You Must Not Forget

Shortcut	Action	Shortcut	Action
Ctrl+C / X / V	Copy / Cut / Paste	F2	Rename (Windows) / Move text (Word)
Ctrl+Z / Y	Undo / Redo	F5	Refresh / Slide show
Ctrl+S / F12	Save / Save As	F7	Spell check
Ctrl+P	Print	Alt+F4	Close program
Ctrl+A	Select all	Ctrl+Alt+Del	Task options / warm boot

17.2 Memory in 30 Seconds

Point	Remember
Fastest memory	Registers → then Cache (SRAM)
Needs refresh	DRAM (capacitor) — main RAM
No refresh	SRAM (flip-flop) — cache
Non-volatile primary	ROM (BIOS); EPROM = UV erase; EEPROM = electric erase
Virtual memory	Hard-disk space used as RAM

17.3 Security Terms in One Line Each

Term	One line
Firewall	Filters network traffic; blocks unauthorised access
Virus	Needs host file + human action
Worm	Self-spreading, no host needed
Trojan	Disguised as useful software
Phishing	Fake mail/site steals credentials
Ransomware	Encrypts data, demands money
Antivirus	Detects and removes malware
HTTPS	SSL/TLS-encrypted browsing

17.4 Office Suite Snapshot

Application	File called	Extension	Star fact
MS Word	Document	.docx	F2 moves text; F7 spell check
MS Excel	Workbook	.xlsx	TEXT() formats value as text; $ = absolute reference
MS PowerPoint	Presentation	.pptx	Design tab → themes/templates; F5 slide show

---

End of GA-03. Next: GA-04 Basics of Environment & Pollution Control.

GA-04 | Basics of Environment & Pollution Control

RRB JE CBT-2 (CEN 05/2025) — General Abilities | Weightage: 10 Questions

> **Exam angle:** RRB asks straightforward, high-yield questions on ecosystem concepts, pollution types & control devices, solid-waste classification, global issues (global warming, ozone, acid rain), Indian environmental movements, and the legislation timeline. Every sub-topic seen in actual 2025 CBT-2 papers is covered, with a PYQ Corner, 25 practice MCQs, and rapid-revision tables.

---

1. Ecosystem Basics

An **ecosystem** is a self-sustaining unit where living organisms interact with each other and their physical surroundings. Term coined by **A.G. Tansley (1935)**.

1.1 Components

Component	Meaning	Examples
Biotic	Living components	Plants (producers), animals (consumers), microbes (decomposers)
Abiotic	Non-living components	Sunlight, temperature, water, air, soil, minerals

Biotic sub-groups:

Group	Role	Example
Producers (autotrophs)	Make food via photosynthesis	Green plants, algae
Consumers (heterotrophs)	Depend on others for food	Herbivores, carnivores, omnivores
Decomposers (saprotrophs)	Break down dead matter, recycle nutrients	Bacteria, fungi

1.2 Food Chain, Food Web & Trophic Levels

- **Food chain:** linear sequence of "who eats whom" — energy flows from one level to the next.

Example: *Grass → Grasshopper → Frog → Snake → Hawk*.

- **Food web:** many interconnected food chains — more realistic and stable.
- **Trophic levels:** feeding positions in a food chain.

Trophic Level	Organism	Example
T1	Producer	Grass
T2	Primary consumer (herbivore)	Grasshopper
T3	Secondary consumer (carnivore)	Frog
T4	Tertiary consumer	Snake
T5	Top / apex consumer	Hawk

1.3 Energy Flow — The 10% Law ★

- Energy flow in an ecosystem is **unidirectional** (one-way, from Sun → producers → consumers).
- **Lindeman's 10% Law:** only about **10% of energy** is transferred from one trophic level to the next; the remaining ~90% is lost as heat (metabolism, respiration). This is why food chains are usually limited to 4–5 links.
- **Ecological pyramids:** number, biomass, or energy. The **pyramid of energy is always upright**.

1.4 Biomagnification & Bioaccumulation ★

Term	Meaning
Bioaccumulation	Build-up of a toxic substance **within a single organism** over its lifetime (faster intake than excretion)
Biomagnification	Progressive **increase in concentration of a toxic, non-degradable substance at each higher trophic level** of a food chain

- Classic example: **DDT** (a pesticide) in **aquatic ecosystems** — water has a low DDT concentration, but it magnifies through plankton → small fish → large fish → **fish-eating birds**, where it is highest and causes thin egg-shells. Other biomagnifying pollutants: **mercury (Minamata disease), lead, arsenic**.
- These substances biomagnify because they are **fat-soluble and non-biodegradable**, so they are stored, not excreted.

> **2025 CBT-2 asked:** In which ecosystem is biomagnification most significantly observed? → **Aquatic ecosystems**, because pollutants like DDT and mercury enter water and concentrate up long aquatic food chains.

1.5 Eutrophication

- **Eutrophication** = over-enrichment of a water body with **nutrients (nitrates & phosphates)** from fertilizer runoff and sewage.
- Leads to **algal bloom** → blocks sunlight → algae die → decomposers consume oxygen → **dissolved oxygen falls** → fish and aquatic life die. An **algal bloom of toxic cyanobacteria** can poison the water.

---

2. Biodiversity & Conservation

- **Biodiversity** = variety of life — genetic, species, and ecosystem diversity. Term popularised by **E.O. Wilson**.
- **Biodiversity hotspots in India (4):** (i) **Himalayas**, (ii) **Western Ghats**, (iii) **Indo-Burma region**, (iv) **Sundaland (Nicobar Islands)**.

Conservation methods:

Type	Meaning	Examples
In-situ	Protecting species **in their natural habitat**	National parks, wildlife sanctuaries, biosphere reserves, tiger reserves
Ex-situ	Protecting species **outside their natural habitat**	Zoos, botanical gardens, gene/seed banks, aquariums

- India has 100+ national parks and 18 biosphere reserves. **Project Tiger** (1973) and **Project Elephant** (1992) are flagship in-situ programmes.
- **IUCN Red List** categories: Extinct → Critically Endangered → Endangered → Vulnerable → Near Threatened → Least Concern.

---

3. Air Pollution

Air pollution = presence of harmful substances in the atmosphere beyond safe limits.

3.1 Major Pollutants, Sources & Effects

Pollutant	Main Source	Effect
Carbon monoxide (CO)	Incomplete fuel combustion, vehicles	Reduces oxygen carriage in blood; can be fatal
Carbon dioxide (CO_2)	Fossil-fuel burning	Major greenhouse gas → global warming
Sulphur dioxide (SO_2)	Coal burning, thermal plants	Respiratory problems; **acid rain**
Oxides of nitrogen (NO_x)	Vehicles, industry	Acid rain, smog
Particulate matter (PM2.5, PM10)	Dust, vehicles, construction	Lung diseases, reduced visibility
CFCs	Refrigerants, aerosols	Ozone-layer depletion
Lead	Old petrol, batteries	Nervous-system damage
Ground-level ozone (O_3)	Photochemical reactions	Photochemical smog, breathing issues

Pollution classification: *Primary pollutants* are emitted directly (CO, SO_2, NO_x); *secondary pollutants* form by reaction in the atmosphere (ozone, smog, PAN).

3.2 Smog Types

Type	Where/When	Cause
Classical / London smog	Cool, humid; winter	Smoke + fog + SO_2 (reducing smog)
Photochemical / Los Angeles smog	Warm, sunny; day	NO_x + hydrocarbons + sunlight → ozone, PAN (oxidising smog)

3.3 Control Devices ★

Device	Function
Electrostatic Precipitator (ESP)	Removes **particulate matter** from industrial flue gases using electric charge; efficiency up to 99%
Scrubber	Removes **gases (SO_2) and dust** by passing flue gas through a liquid spray
Catalytic converter	Fitted in vehicle exhaust; converts CO → CO_2, NO_x → N_2, unburnt hydrocarbons → CO_2+H_2O (uses platinum/palladium; needs unleaded petrol)
Bag filter / Cyclone separator	Trap dust particles

- **AQI (Air Quality Index):** 0–50 Good, 51–100 Satisfactory, 101–200 Moderate, 201–300 Poor, 301–400 Very Poor, 401–500 Severe.

4. Water Pollution

Sources: domestic sewage, industrial effluents, agricultural runoff (fertilizers/pesticides), oil spills, thermal pollution, plastic waste.

Parameter	Full form	Meaning
BOD	Biochemical Oxygen Demand	Oxygen needed by microbes to decompose organic matter; **high BOD = more pollution**
COD	Chemical Oxygen Demand	Oxygen needed to chemically oxidise all matter; always ≥ BOD
DO	Dissolved Oxygen	Oxygen available to aquatic life; **low DO = polluted**
pH	—	Acidity/alkalinity; safe drinking water ≈ 6.5–8.5

Sewage treatment stages:

Stage	Process
Primary	Physical removal — screening, sedimentation of solids
Secondary	Biological — microbes break down organic matter (aeration tanks)
Tertiary	Chemical — removes remaining nutrients/pathogens; disinfection (chlorination)

Ganga cleaning: Namami Gange programme (2014, integrated conservation mission; replaced the earlier Ganga Action Plan of 1985) — sewage treatment, riverfront development, afforestation, biodiversity. Nodal: National Mission for Clean Ganga (NMCG).

---

5. Soil & Noise Pollution

Soil pollution — causes: excess chemical fertilizers & pesticides, industrial waste, plastics, mining, acid rain. **Effects:** loss of fertility, groundwater contamination, reduced crop yield. **Control:** organic farming, crop rotation, afforestation, reduced plastic use.

Noise pollution: unwanted/harmful sound, measured in **decibels (dB)**.

Situation	Approx. level
Safe/normal conversation	~ 60 dB
WHO safe daytime limit (residential)	~ 55 dB (day), 45 dB (night)
Industrial safe limit (India)	75 dB (day) / 70 dB (night)
Pain threshold	~ 120–130 dB

Effects: hearing loss, hypertension, sleep disturbance, stress. Control: green belts, silencers, sound barriers, restricting horns/loudspeakers.

---

6. Solid Waste Management ★★

6.1 Sources of Municipal Solid Waste (MSW)

Municipal solid waste is the everyday, non-hazardous rubbish generated from:

Source	Typical waste
Homes / residences	Kitchen scraps, packaging, paper, plastic
Schools & offices	Paper, stationery, general litter
Shops, markets, restaurants	Packaging, food waste
Hospitals (general/non-clinical areas)	Office paper, canteen waste, packaging
Streets & public places	Sweepings, garden waste

> **Important exam point: Radioactive waste and industrial hazardous waste are NOT part of municipal solid waste.** They are collected, treated and disposed of **separately** under special rules. Biomedical (clinical) waste from hospitals is also handled separately, not as ordinary MSW.

> **2025 CBT-2 asked:** Which of the following is NOT a source of municipal solid waste? → **Radioactive waste** (it comes from nuclear plants/labs and is managed under a separate radioactive-waste-disposal system, not with municipal garbage).

6.2 Classification of Waste

Category	Meaning	Examples
Biodegradable	Decomposed by microbes	Food waste, paper, leaves, cotton
Non-biodegradable	Not broken down naturally	Plastic, glass, metal, polythene
Hazardous	Toxic/flammable/corrosive/reactive	Chemicals, batteries, paints
Biomedical	From hospitals/clinics	Syringes, dressings, body fluids (colour-coded bins)
E-waste	Discarded electronics	Old phones, computers, TVs
Radioactive	From nuclear activity	Handled separately (never in MSW)

Colour-coded biomedical waste bins (India):

Colour	Waste type
Yellow	Anatomical/soiled waste, incinerated
Red	Contaminated recyclable plastic (tubing, catheters)
White (translucent)	Sharps (needles, blades)
Blue	Glassware, metallic implants

6.3 Waste Management Methods — the 5 R's & Disposal

- **5 R's: Refuse, Reduce, Reuse, Recycle, Recover** (also 3R: Reduce, Reuse, Recycle).

Method	Description	Note
Composting	Biodegradable waste decomposed into manure by microbes	Best for organic waste; vermicomposting uses earthworms
Recycling	Reprocessing waste into new products	Paper, glass, metal, plastic
Landfill	Waste buried in engineered pits with liners	Sanitary landfill prevents groundwater contamination; produces methane
Incineration	Controlled burning at high temperature	Reduces volume; used for biomedical/hazardous waste; can generate energy but emits gases
Waste-to-energy	Combustion/biogas produces electricity	—

7. Radioactive Pollution

- **Sources:** nuclear power plants, nuclear weapon tests, uranium mining, medical X-rays/radiotherapy, radioactive isotopes in labs, nuclear accidents (Chernobyl 1986, Fukushima 2011).
- **Effects:** ionising radiation damages DNA → **mutations, cancer, genetic disorders, radiation sickness, birth defects**. High doses are fatal.

> **2025 CBT-2 asked:** Radiation from nuclear waste primarily causes what biological effect? → **Mutations** (changes in DNA/genes), which can lead to cancer and hereditary defects.

- **Disposal:** radioactive waste is **isolated and stored in shielded containers deep underground (geological disposal)** or in sealed concrete/steel casks; it is **never** mixed with municipal waste. Classified as low-, intermediate-, and high-level waste by activity.

8. Global Environmental Issues

8.1 Greenhouse Effect & Global Warming ★

- **Greenhouse effect:** greenhouse gases in the atmosphere trap outgoing infrared (heat) radiation, warming the Earth — a natural process that keeps the planet habitable. Excess gases **enhance** it, causing **global warming**.

Greenhouse Gas	Main Source	Note
Carbon dioxide (CO_2)	Fossil-fuel burning, deforestation	Largest overall contributor
Methane (CH_4)	Paddy fields, cattle, landfills	~25× more potent than CO_2
Nitrous oxide (N_2O)	Fertilizers	Very potent
CFCs / HFCs	Refrigerants	Also deplete ozone
Water vapour	Natural	Most abundant

- **Global warming:** global average surface temperature has risen by **about 1 °C (≈1.1 °C)** above pre-industrial levels *(as of the mid-2020s, IPCC)*. The Paris Agreement targets keeping the rise **well below 2 °C, ideally 1.5 °C**.
- **Consequences:** melting glaciers & polar ice, sea-level rise, extreme weather, crop failure, species loss.

> **2025 CBT-2 asked:** Global warming refers to what? → the **rise in Earth's average temperature** due to increased greenhouse gases; the observed rise is about **1 °C** over pre-industrial times *(as-of mid-2020s)*.

8.2 Ozone-Layer Depletion

- **Ozone layer** (in the **stratosphere**) absorbs harmful **ultraviolet (UV)** radiation from the Sun.
- Depleted mainly by **CFCs (chlorofluorocarbons)** and halons → an "**ozone hole**" over Antarctica.
- Effects: skin cancer, cataracts, weakened immunity, crop damage.
- **Montreal Protocol (1987)** — international treaty to phase out ozone-depleting substances (very successful). **World Ozone Day: 16 September**.

8.3 Acid Rain

- **Acid rain** = rain with **pH below 5.6**, caused by **SO_2 and NO_x** reacting with water vapour to form sulphuric and nitric acids.
- Effects: damages buildings/monuments (**e.g. Taj Mahal — "marble cancer"**), acidifies soil and lakes, harms forests and aquatic life.

---

9. Environmental Movements in India ★

Movement	Year	Place	Leader(s)	About
Chipko Movement	1973	**Uttarakhand** (then UP)	**Sunderlal Bahuguna**, Chandi Prasad Bhatt, Gaura Devi	Villagers **hugged trees** to prevent felling; "chipko" = to embrace; slogan "ecology is permanent economy"
Appiko Movement	1983	Karnataka (Western Ghats)	Pandurang Hegde	Southern counterpart of Chipko ("appiko" = to hug in Kannada)
Silent Valley Movement	1970s–80s	Kerala	M.K. Prasad, activists	Saved the Silent Valley tropical rainforest from a hydel dam; declared a National Park (1984)
Narmada Bachao Andolan	1985	Gujarat/MP/Maharashtra	**Medha Patkar**, Baba Amte	Against big dams on the Narmada (Sardar Sarovar); rehabilitation of displaced people
Bishnoi Movement	1730	Rajasthan	Amrita Devi Bishnoi	Earliest — sacrificed lives to protect Khejri trees

> **2025 CBT-2 asked:** The Chipko Movement is associated with which state / what activity? → **Uttarakhand**; villagers hugged trees to stop deforestation. Leader: **Sunderlal Bahuguna**.

---

10. Indian Environmental Legislation — Timeline Table ★

Year	Act / Body	Purpose
1972	**Wildlife (Protection) Act**	Protects wild animals, birds, plants; sets up national parks & sanctuaries
1974	**Water (Prevention & Control of Pollution) Act**	Prevents water pollution; created **CPCB & SPCBs**
1980	Forest (Conservation) Act	Restricts diversion of forest land
1981	**Air (Prevention & Control of Pollution) Act**	Controls air pollution
1986	**Environment (Protection) Act ★**	Umbrella / most comprehensive law; passed after the **Bhopal Gas Tragedy (1984)**; empowers Central Govt to protect and improve the environment
1988	Motor Vehicles Act	Vehicle emission norms
2002	Biological Diversity Act	Conservation & sustainable use of biodiversity
2010	**National Green Tribunal (NGT) Act**	Special court for speedy disposal of environmental cases

> **2025 CBT-2 asked:** Which Act is the umbrella legislation for environmental protection in India, enacted after the Bhopal disaster? → **The Environment (Protection) Act, 1986.**

- **Pollution Control Boards: CPCB** (Central Pollution Control Board, national) and **SPCBs** (State Pollution Control Boards) set standards, monitor and enforce pollution norms. CPCB works under the Ministry of Environment, Forest & Climate Change (MoEFCC).

11. International Conventions — One-Liners

Event	Year	About
Stockholm Conference	1972	First UN environment conference; **World Environment Day, 5 June** originates here; led to UNEP
Rio Earth Summit (UNCED)	1992	Agenda 21; Convention on Biological Diversity; UNFCCC framework
Kyoto Protocol	1997	First binding targets to cut greenhouse-gas emissions
Ramsar Convention	1971	Conservation of **wetlands**
CITES	1973	Regulates trade in endangered species
Montreal Protocol	1987	Phase-out of ozone-depleting substances
Paris Agreement	2015	Limit global warming well below 2 °C (aim 1.5 °C); nationally determined contributions
COP (Conference of Parties)	Annual	UNFCCC climate meetings; recent: COP28 (Dubai, 2023), COP29 (Baku, 2024) *(as of 2024–25)*

12. PYQ Corner — Actual RRB JE CBT-2 2025 Questions Solved

Q1. Which of the following is NOT a source of municipal solid waste?

Answer: Radioactive waste. MSW comes from homes, schools, offices, shops and general hospital areas. Radioactive waste (from nuclear plants/labs) and industrial hazardous/biomedical waste are managed separately under special disposal rules.

Q2. Which Act is the comprehensive umbrella legislation for environmental protection in India?

Answer: The Environment (Protection) Act, 1986, enacted after the 1984 Bhopal Gas Tragedy; empowers the Central Government to take all measures to protect and improve the environment.

Q3. Radiation from nuclear/radioactive waste primarily causes which biological effect?

Answer: Mutations — ionising radiation damages DNA, causing genetic mutations that can lead to cancer, hereditary defects and radiation sickness.

Q4. Global warming refers to what, and by roughly how much has temperature risen?

Answer: Global warming is the **rise in Earth's average surface temperature** due to increased greenhouse gases. The rise is about **1 °C (≈1.1 °C)** above pre-industrial levels *(as of the mid-2020s, IPCC)*.

Q5. The Chipko Movement originated in which state and involved what activity?

Answer: Uttarakhand (then part of Uttar Pradesh). Villagers, led by **Sunderlal Bahuguna** and Chandi Prasad Bhatt, **hugged trees** to prevent them from being cut.

Q6. Biomagnification is most significantly observed in which ecosystem?

Answer: Aquatic ecosystems. Fat-soluble, non-biodegradable pollutants such as **DDT and mercury** concentrate up long aquatic food chains, reaching highest levels in top predators like fish-eating birds.

---

13. Practice MCQs (25) — Answers at the End

1. The term "ecosystem" was coined by: (a) Odum (b) Tansley (c) Wilson (d) Lindeman
2. Green plants in a food chain are: (a) Consumers (b) Decomposers (c) Producers (d) Predators
3. According to the 10% law, energy transferred to the next trophic level is: (a) 1% (b) 10% (c) 50% (d) 90%
4. Biomagnification of DDT is highest in: (a) Water (b) Plankton (c) Small fish (d) Fish-eating birds
5. Eutrophication is caused by excess: (a) Oxygen (b) Nitrates and phosphates (c) Carbon dioxide (d) Chlorine
6. Which is a biodiversity hotspot in India? (a) Thar Desert (b) Western Ghats (c) Deccan Plateau (d) Gangetic Plain
7. Protecting a species in a zoo is: (a) In-situ (b) Ex-situ (c) On-site (d) Habitat conservation
8. Electrostatic precipitators remove: (a) Gases (b) Particulate matter (c) Bacteria (d) Odour
9. A catalytic converter is fitted in: (a) Chimneys (b) Vehicle exhaust (c) Sewage plants (d) AC units
10. High BOD in water indicates: (a) Clean water (b) More pollution (c) High oxygen (d) Low bacteria
11. Secondary sewage treatment is mainly: (a) Physical (b) Chemical (c) Biological (d) Thermal
12. Namami Gange is related to cleaning the river: (a) Yamuna (b) Ganga (c) Godavari (d) Narmada
13. Noise is measured in: (a) Hertz (b) Decibels (c) Lumens (d) Pascals
14. Which is NOT municipal solid waste? (a) Kitchen waste (b) Paper (c) Radioactive waste (d) Packaging
15. Composting is best suited for: (a) Plastic (b) Glass (c) Biodegradable waste (d) Metal
16. White (translucent) biomedical bins are for: (a) Anatomical waste (b) Sharps (c) Plastic (d) Glass
17. The gas mainly responsible for global warming is: (a) O_2 (b) CO_2 (c) N_2 (d) He

18. Global temperature has risen by about: (a) 0.1 °C (b) 1 °C (c) 5 °C (d) 10 °C
19. Ozone layer is depleted mainly by: (a) CO_2 (b) CFCs (c) CH_4 (d) SO_2
20. The Montreal Protocol (1987) deals with: (a) Global warming (b) Ozone depletion (c) Wetlands (d) Biodiversity
21. Acid rain has a pH: (a) Above 7 (b) Exactly 7 (c) Below 5.6 (d) Above 8
22. The Chipko Movement is associated with: (a) Rajasthan (b) Uttarakhand (c) Kerala (d) Karnataka
23. The Environment Protection Act was passed in: (a) 1974 (b) 1981 (c) 1986 (d) 2010
24. CPCB stands for: (a) Central Public Control Board (b) Central Pollution Control Board (c) City Pollution Control Body (d) Central Power Control Board
25. World Environment Day is observed on: (a) 22 April (b) 5 June (c) 16 September (d) 2 December

Answers: 1-b, 2-c, 3-b, 4-d, 5-b, 6-b, 7-b, 8-b, 9-b, 10-b, 11-c, 12-b, 13-b, 14-c, 15-c, 16-b, 17-b, 18-b, 19-b, 20-b, 21-c, 22-b, 23-c, 24-b, 25-b

---

14. Rapid-Revision Tables

14.1 Pollution Control Devices

Device	Removes	Used in
Electrostatic precipitator (ESP)	Particulate matter	Thermal plants, industry
Scrubber	SO_2 gas + dust	Industrial chimneys
Catalytic converter	CO, NO_x, hydrocarbons	Vehicle exhaust
Bag/cyclone filter	Dust particles	Factories

14.2 Global Issues Snapshot

Issue	Cause	Key treaty / fact
Global warming	CO_2, CH_4 (greenhouse gases)	~1 °C rise; Paris 2015, Kyoto 1997
Ozone depletion	CFCs	Montreal Protocol 1987; Ozone Day 16 Sept
Acid rain	SO_2, NO_x	pH < 5.6; damages Taj Mahal

14.3 Environmental Days

Day	Date
World Environment Day	5 June
Earth Day	22 April
World Ozone Day	16 September
World Water Day	22 March
World Wildlife Day	3 March

14.4 Legislation in One Line

Act	Year
Wildlife Protection	1972
Water Act	1974
Air Act	1981
Environment Protection Act	1986
NGT	2010

14.5 Movements in One Line

Movement	State	Cause
Chipko	Uttarakhand	Save trees (hug)
Appiko	Karnataka	Save Western Ghats forests
Silent Valley	Kerala	Save rainforest from dam
Narmada Bachao	MP/Gujarat	Against big dams

End of GA-04. Next: GA-05 General Awareness capsule.

GA-05 | General Awareness (GA Capsule)

RRB JE CBT-2 (CEN 05/2025) — General Abilities | Weightage: 15 Questions

> **Exam angle:** RRB JE General Awareness mixes static GK (polity, history, geography, economy) with current affairs (2024–25), a strong Indian Railways component, science & tech in news, awards, and art & culture. This capsule is tuned to the exact topics seen in the 2025 CBT-2 paper, followed by a PYQ Corner, 30 practice MCQs, and rapid-revision material. Time-sensitive facts are marked with an as-of date.

---

1. Indian Polity & Constitution

1.1 Constitution Basics

- The Constitution of India was adopted on **26 November 1949** and came into force on **26 January 1950**. **Dr B.R. Ambedkar** — Chairman of the Drafting Committee ("Father of the Indian Constitution").
- Longest written constitution in the world. Preamble declares India a **Sovereign, Socialist, Secular, Democratic Republic**.
- Borrowed features: Parliamentary system & rule of law (UK), Fundamental Rights & judicial review (USA), Directive Principles (Ireland), Emergency provisions (Germany), Federal structure & residuary powers (Canada), Fundamental Duties (USSR).

1.2 Frequently-Asked Articles ★

Article	Provision
Article 14	Equality before law
Article 19	Six freedoms (speech, assembly, etc.)
Article 21	Right to life and personal liberty
Article 32	Right to constitutional remedies ("heart & soul" — Ambedkar)
Article 72	**President's power to grant pardons**, reprieves, remissions
Article 110	Defines a **Money Bill**
Article 123	**President's power to promulgate ordinances** when Parliament is not in session ★
Article 143	President can seek Supreme Court's advisory opinion
Article 226	High Courts' power to issue writs
Article 356	**President's Rule** (state emergency) in a state
Article 360	Financial emergency
Article 368	Amendment of the Constitution

> **2025 CBT-2 asked:** Under which Article can the President promulgate ordinances? → **Article 123** (ordinances have the force of law but must be approved by Parliament within 6 weeks of it reassembling). The Governor's equivalent is Article 213.

1.3 Directive Principles of State Policy (DPSP)

- Contained in **Part IV (Articles 36–51)**; borrowed from **Ireland**; **non-justiciable** (not enforceable in court) but fundamental in governance.

- **Dr B.R. Ambedkar called them a "novel feature"** of the Constitution; **Granville Austin** described the Fundamental Rights and Directive Principles together as the **"conscience of the Constitution."** DPSP have also been called the **"life-giving provisions"** / instrument of instructions.
- Aim: to establish a **welfare state** and social & economic democracy. Examples: equal pay for equal work, uniform civil code, promotion of village panchayats, protection of environment (Art 48A).

> **2025 CBT-2 asked:** Which part of the Constitution is described as the "life-giving provisions" / novel feature aiming at a welfare state? → the **Directive Principles of State Policy (Part IV).**

1.4 President's Powers ★

- The **President is the constitutional head** of India (nominal executive); real power rests with the Council of Ministers headed by the PM.
- **Executive:** appoints PM, Governors, judges, CAG, etc.
- **Legislative:** summons/prorogues Parliament, **can dissolve the Lok Sabha** (on the advice of the Council of Ministers), gives assent to bills, nominates members.
- **Emergency powers:** National (Art 352), State/President's Rule (Art 356), Financial (Art 360).
- **Judicial:** grants pardons (Art 72).

> **2025 CBT-2 asked:** Who has the power to dissolve the Lok Sabha? → the **President of India** (Article 85), acting on the advice of the Council of Ministers. The Rajya Sabha is a permanent house and is **never** dissolved.

1.5 Parliament & Judiciary (Basics)

Body	Key facts
Lok Sabha	House of the People; max 552 members; term 5 years; can be dissolved
Rajya Sabha	Council of States; permanent house; 1/3 retire every 2 years; max 250
Supreme Court	Apex court; Chief Justice + up to 33 judges; guardian of the Constitution
High Courts	One for each state / group of states
Judicial Review	Courts can strike down unconstitutional laws

---

2. Indian History Highlights

2.1 Ancient — Mauryan Economy & Guilds ★

- **Mauryan Empire (322–185 BCE)** founded by **Chandragupta Maurya** with **Chanakya (Kautilya)**, whose treatise **Arthashastra** describes the economy and administration.
- The Mauryan economy was highly organised: **artisans and craftsmen were organised into guilds called "shrenis"** (associations of people in the same craft/trade). Guilds regulated production, quality, prices and training, and were an important economic institution.
- **Ashoka** (grandson of Chandragupta) spread Buddhism after the Kalinga War; his edicts are inscribed on pillars and rocks.

> **2025 CBT-2 asked:** In the Mauryan economy, artisans were organised into what? → **guilds (shrenis)** — craft/trade associations that regulated their occupation.

2.2 Freedom Movement — Key Events & Leaders

Year	Event
1857	First War of Independence (Sepoy Mutiny)
1885	Indian National Congress founded (A.O. Hume)
1905	Partition of Bengal → **Swadeshi Movement** (boycott of foreign goods, promote Indian goods)
1919	Jallianwala Bagh massacre; Rowlatt Act
1920	Non-Cooperation Movement (Gandhi)
1930	Salt March / Dandi / Civil Disobedience
1942	Quit India Movement ("Do or Die")
1947	Independence (15 August)

Swadeshi Movement: launched during the anti-Partition agitation of 1905; promoted Indian-made goods (**swadeshi**) and boycott of British products — this stimulated Indian industries.

2.3 Bengal Chemical & Acharya P.C. Ray ★

- **Acharya Prafulla Chandra Ray (P.C. Ray)** — pioneering Indian chemist, called the **"Father of Indian Chemistry."**
- He founded **Bengal Chemical and Pharmaceutical Works (1901, Kolkata)** — one of India's first indigenous pharmaceutical/chemical companies, embodying the swadeshi spirit of building Indian industry.

> **2025 CBT-2 asked:** Who founded Bengal Chemical and Pharmaceutical Works? → **Acharya P.C. Ray** (Father of Indian Chemistry), in 1901, a landmark of the swadeshi industrial movement.

---

3. Geography of India

3.1 Physical Features

- The **Himalayas** run in a broad arc along India's northern border with a general **north-west to south-east (NW–SE) orientation.** Three parallel ranges: **Himadri (Greater), Himachal (Lesser), Shiwalik (Outer)**. Highest peak in India: **Kanchenjunga**.
- India lies between **8°4′N–37°6′N** latitude; the **Tropic of Cancer (23.5°N)** passes through 8 states.
- **Standard Meridian:** 82°30′E (passes through Mirzapur, UP).

3.2 Rivers & Famous Bridges ★

Bridge	River	Note
Dhola–Sadiya (Bhupen Hazarika Setu)	**Brahmaputra** (Lohit)	India's longest **road** bridge (9.15 km); Assam–Arunachal; opened 2017 ★
Bogibeel Bridge	Brahmaputra	Longest **rail-cum-road** bridge in India; Assam (2018)
Howrah Bridge (Rabindra Setu)	**Hooghly**	Kolkata; iconic cantilever bridge
Pamban Bridge	Palk Strait sea	Connects Rameswaram island to mainland Tamil Nadu; India's first sea bridge
Mahatma Gandhi Setu	**Ganga**	Patna, Bihar
Vidyasagar Setu	Hooghly	Kolkata; longest cable-stayed bridge
Atal Setu (MTHL)	Sea (Mumbai)	India's longest sea bridge, ~21.8 km (2024)

> **2025 CBT-2 asked:** The Dhola–Sadiya bridge is built over which river? → the **Brahmaputra** (Lohit tributary), connecting Assam and Arunachal Pradesh; also called Bhupen Hazarika Setu.

Major rivers: Ganga (longest in India), Brahmaputra, Yamuna, Godavari (longest in South India, "Dakshin Ganga"), Krishna, Narmada & Tapi (west-flowing, into Arabian Sea).

3.3 National Parks — One Table

National Park	State	Famous for
Jim Corbett	Uttarakhand	India's oldest NP (1936); tigers
Kaziranga	Assam	One-horned rhinoceros (UNESCO site)
Gir	Gujarat	Asiatic lions
Sundarbans	West Bengal	Royal Bengal tiger, mangroves
Ranthambore	Rajasthan	Tigers
Kanha / Bandhavgarh	Madhya Pradesh	Tigers; MP = "Tiger State"
Periyar	Kerala	Elephants
Keoladeo (Bharatpur)	Rajasthan	Birds (wetland)

---

4. Indian Economy

4.1 Sectors of the Economy ★

Sector	Meaning	Examples
Primary	Extracts natural resources	Agriculture, mining, fishing, forestry
Secondary	Manufacturing & industry	Factories, construction, **electricity/power generation** ★
Tertiary	Services	Banking, transport, IT, tourism, railways

> **2025 CBT-2 asked:** Electricity generation falls under which sector? → the **Secondary sector.** Although often listed with "utilities," in the standard three-sector classification electricity, gas and water supply are grouped under the **secondary (industrial)** sector because they involve processing/production, not raw extraction.

4.2 Banking & Budget Basics

Term	Meaning
RBI	Reserve Bank of India — central bank (est. 1935); issues currency, controls monetary policy
Repo rate	Rate at which RBI lends to commercial banks
CRR / SLR	Cash Reserve Ratio / Statutory Liquidity Ratio — funds banks must keep in reserve
Fiscal deficit	Excess of government expenditure over revenue (excluding borrowings)
Direct tax	Paid directly (income tax, corporate tax)
Indirect tax	On goods/services (GST) — **GST launched 1 July 2017**, "one nation one tax"
Union Budget	Presented on 1 February by the Finance Minister
NITI Aayog	Policy think-tank (replaced Planning Commission, 2015)

---

5. Science & Technology in News

5.1 ISRO Missions ★

Mission	Year	Purpose
Chandrayaan-3	2023	India became the **1st country to soft-land near the lunar south pole** (Vikram lander, Pragyan rover)
Chandrayaan-2	2019	Orbiter success; lander lost
Chandrayaan-1	2008	Confirmed water molecules on the Moon
Mangalyaan (MOM)	2013	India's 1st Mars mission; 1st Asian nation to reach Mars orbit in first attempt
Aditya-L1	2023	India's 1st solar mission; studies the Sun from the L1 point
Gaganyaan	Upcoming	India's first human spaceflight programme *(as of 2024–25)*
PSLV / GSLV / LVM3	—	Launch vehicles; LVM3 (GSLV Mk III) is the heaviest

- **ISRO** — Indian Space Research Organisation, HQ Bengaluru; founder **Dr Vikram Sarabhai**; current Chairman **Dr V. Narayanan** *(from Jan 2025; succeeded S. Somanath)*.
- **DRDO** — Defence Research & Development Organisation; missiles: **Agni** (long-range ballistic), **Prithvi, BrahMos** (supersonic cruise, India–Russia), **Akash** (SAM), **Astra** (air-to-air). Mission Divyastra: MIRV test on Agni-5 (2024).

---

6. Indian Railways — Special Section ★★

- **First train in India: 16 April 1853**, from **Bori Bunder (Mumbai) to Thane** (~34 km), hauled by locomotives Sahib, Sindh and Sultan.
- Indian Railways = one of the world's largest rail networks under a single management; HQ: New Delhi (Rail Bhavan); **"Lifeline of the Nation."**
- **Number of railway zones: 18** (plus special units like Kolkata Metro).

6.1 Railway Zones (Selected)

Zone	HQ
Northern Railway	New Delhi
Western Railway	Mumbai (Churchgate)
Central Railway	Mumbai (CSMT)
Eastern Railway	Kolkata
Southern Railway	Chennai
South Central Railway	Secunderabad
North Eastern Railway	Gorakhpur
South Coast Railway (newest)	Visakhapatnam

6.2 Railway Firsts & Modernisation

Item	Fact
First train	1853, Mumbai–Thane
First electric train	Deccan Queen (1930), Mumbai–Pune
Vande Bharat Express	India's first indigenous semi-high-speed train (2019); many routes operational *(as of 2025)*
Kavach	Indigenous **Automatic Train Protection (anti-collision)** system
DFC	Dedicated Freight Corridors — Eastern & Western, for freight-only trains
Fastest train	Vande Bharat / Gatimaan Express (Delhi–Jhansi)
Longest route	Vivek Express (Dibrugarh–Kanyakumari)
Bullet train project	Mumbai–Ahmedabad High-Speed Rail (with Japan)
Railway Minister	**Ashwini Vaishnaw** *(as of 2025)*

- Superlatives: **Longest platform** — Hubballi (Karnataka); **Longest tunnel** — Pir Panjal (J&K); **highest rail bridge** — **Chenab Bridge** (J&K), world's highest railway arch bridge, opened 2025.

---

7. Sports

Award / Event	Detail
BCCI Naman Awards	Annual cricket awards; **Smriti Mandhana** won the **Best International Women's Cricketer** (Polly Umrigar equivalent for women) *(2023–24 season, announced 2025)* ★
Major Dhyan Chand Khel Ratna	India's highest sporting honour
Arjuna Award	For consistent outstanding performance
Dronacharya Award	For coaches
Paris Olympics 2024	India won 6 medals; **Neeraj Chopra** — silver (javelin); Manu Bhaker — 2 bronze (shooting)
Chess	**D. Gukesh** became the **youngest World Chess Champion** (Dec 2024)
Cricket	India won the **T20 World Cup 2024**

> **2025 CBT-2 asked:** Who won the BCCI Naman Award (best women's international cricketer)? → **Smriti Mandhana** *(as of the 2025 awards for 2023–24 season).*

8. Awards & Honours

Award	Recipients / Fact
Bharat Ratna 2024	Five conferred: **Karpoori Thakur (posthumous), L.K. Advani, P.V. Narasimha Rao (posthumous), Chaudhary Charan Singh (posthumous), M.S. Swaminathan (posthumous)**
Nobel Prize 2024	Peace: **Nihon Hidankyo** (Japan, anti-nuclear); Literature: **Han Kang** (South Korea); Physics: Hopfield & Hinton (machine learning/AI) *(as of 2024)*
Padma Awards	Padma Vibhushan > Padma Bhushan > Padma Shri (civilian honours)
Gallantry	Param Vir Chakra (highest wartime)

9. Art & Culture

9.1 Music — Bhatkhande Notation ★

- **Vishnu Narayan Bhatkhande** — a great musicologist who **systematised Hindustani (North Indian) classical music** and developed the widely used **Bhatkhande notation system** to write down ragas and compositions. He organised ragas into the **10 Thaat** classification.
- **Vishnu Digambar Paluskar** — another reformer who developed his own notation system and popularised music education.

> **2025 CBT-2 asked:** Who developed a widely used music notation system for Hindustani classical music? → **V.N. Bhatkhande** (the Bhatkhande notation and the Thaat system).

9.2 Classical Dance Forms

Dance	State
Bharatanatyam	Tamil Nadu
Kathak	North India (UP)
Kathakali / Mohiniyattam	Kerala
Kuchipudi	Andhra Pradesh
Odissi	Odisha
Manipuri	Manipur
Sattriya	Assam
Bharatanatyam & the above form the **8 classical dances** recognised by Sangeet Natak Akademi	

9.3 Festivals (Sample)

Festival	State
Bihu	Assam
Pongal	Tamil Nadu
Onam	Kerala
Baisakhi	Punjab
Hornbill	Nagaland
Rann Utsav	Gujarat

---

10. Important Persons — Revolutions

Revolution	Colour	Field	Father
Green Revolution	Green	Foodgrains (wheat/rice)	**M.S. Swaminathan** (India); Norman Borlaug (world) ★
White Revolution	White	Milk (Operation Flood)	**Verghese Kurien** ("Milkman of India", Amul)
Blue Revolution	Blue	Fisheries	Hiralal Chaudhuri
Yellow Revolution	Yellow	Oilseeds	Sam Pitroda (assoc.)
Pink Revolution	Pink	Meat/poultry	—

> **2025 CBT-2 asked:** Who is known as the Father of India's Green Revolution? → **M.S. Swaminathan** (agricultural scientist; introduced high-yielding wheat/rice varieties; awarded Bharat Ratna posthumously in 2024).

---

11. Current Affairs 2024–25 Capsule

Topic	Key point *(as of 2024–25)*
Carl Zeiss GCC	German optics firm **Carl Zeiss** opened a **Global Capability Centre (GCC) in Bengaluru (November 2024)** — part of India's boom as a GCC hub ★
Global Capability Centres	India hosts 1,700+ GCCs; Bengaluru, Hyderabad, Pune are major hubs
G20 Summit	India hosted the **G20 Summit in New Delhi (2023)**; 2024 host: Brazil (Rio); 2025: South Africa
COP climate meets	COP28 Dubai (2023), COP29 Baku (2024)
Ram Mandir	Consecrated at Ayodhya, 22 January 2024
New Parliament	Inaugurated May 2023; **Nari Shakti Vandan Adhiniyam** (Women's Reservation Act) passed 2023
Defence exercises	Malabar (India–US–Japan–Australia), Yudh Abhyas (India–US), Varuna (India–France), Tarang Shakti (2024, first multinational air exercise)
New CDS/appointments	Track latest Chief of Defence Staff, RBI Governor (**Sanjay Malhotra**, from Dec 2024), CJI (**Sanjiv Khanna** then B.R. Gavai in 2025)
Elections	18th Lok Sabha (2024) — NDA government; Narendra Modi PM for 3rd term

> **2025 CBT-2 asked:** Which company opened a Global Capability Centre in Bengaluru in November 2024? → **Carl Zeiss** (German optical/optoelectronics company).

---

12. PYQ Corner — Actual RRB JE CBT-2 2025 Questions Solved

Q1. Under which Article can the President of India promulgate an ordinance?

→ **Article 123** (when Parliament is not in session; the ordinance has the force of law but must be approved within 6 weeks of Parliament reassembling).

Q2. Who has the power to dissolve the Lok Sabha?

→ The **President of India** (Article 85), on the advice of the Council of Ministers. The Rajya Sabha is a permanent house and cannot be dissolved.

Q3. Which part of the Constitution, called a "novel feature"/"life-giving provisions", aims at a welfare state?

→ The **Directive Principles of State Policy (Part IV, Articles 36–51)** — non-justiciable guidelines for governance.

Q4. In the Mauryan economy, artisans and craftsmen were organised into what?

→ **Guilds (shrenis)** — trade/craft associations that regulated production, quality and training.

Q5. Who founded Bengal Chemical and Pharmaceutical Works?

→ **Acharya P.C. Ray**, the "Father of Indian Chemistry" (founded 1901, Kolkata), a swadeshi-era enterprise.

Q6. The Dhola–Sadiya (Bhupen Hazarika) bridge is built over which river?

→ The **Brahmaputra** (Lohit), linking Assam and Arunachal Pradesh; India's longest road bridge.

Q7. Who is regarded as the Father of the Green Revolution in India?

→ **M.S. Swaminathan.**

Q8. Electricity generation falls under which sector of the economy?

→ The **Secondary sector.**

Q9. Who developed a widely used notation system for Hindustani classical music?

→ **V.N. Bhatkhande** (Bhatkhande notation; Thaat classification).

Q10. Who won the BCCI Naman Award as best international women's cricketer?

→ **Smriti Mandhana** *(as of 2025).*

Q11. Which company opened a Global Capability Centre in Bengaluru in November 2024?

→ **Carl Zeiss.**

---

13. Practice MCQs (30) — Answers at the End

1. The Indian Constitution came into force on: (a) 15 Aug 1947 (b) 26 Nov 1949 (c) 26 Jan 1950 (d) 2 Oct 1950
2. Article 123 deals with: (a) Money bill (b) President's ordinance power (c) Pardons (d) President's Rule
3. Article 356 relates to: (a) Financial emergency (b) President's Rule in a state (c) Ordinances (d) Money bill
4. The President's power to grant pardons is under Article: (a) 72 (b) 110 (c) 143 (d) 226
5. Directive Principles are contained in which Part of the Constitution? (a) III (b) IV (c) V (d) II
6. Who can dissolve the Lok Sabha? (a) PM (b) Speaker (c) President (d) Chief Justice
7. Which house of Parliament is never dissolved? (a) Lok Sabha (b) Rajya Sabha (c) Both (d) State Assembly
8. Mauryan craft guilds were called: (a) Nagaram (b) Shreni (c) Sabha (d) Samiti
9. The Arthashastra was written by: (a) Ashoka (b) Kautilya (c) Megasthenes (d) Bindusara
10. The Swadeshi Movement began after the: (a) 1857 revolt (b) Partition of Bengal 1905 (c) Jallianwala Bagh (d) Quit India
11. Bengal Chemical Works was founded by: (a) J.C. Bose (b) P.C. Ray (c) C.V. Raman (d) Homi Bhabha
12. The Himalayas generally run in which orientation? (a) N–S (b) E–W (c) NW–SE (d) NE–SW
13. The Dhola–Sadiya bridge spans the river: (a) Ganga (b) Hooghly (c) Brahmaputra (d) Godavari
14. Howrah Bridge is over which river? (a) Ganga (b) Hooghly (c) Damodar (d) Yamuna
15. Pamban Bridge connects the mainland to: (a) Rameswaram (b) Diu (c) Elephanta (d) Majuli
16. Electricity generation is classified under which sector? (a) Primary (b) Secondary (c) Tertiary (d) Quaternary
17. Banking and IT services belong to the: (a) Primary (b) Secondary (c) Tertiary (d) Public sector
18. GST was implemented in India from: (a) 2016 (b) 2017 (c) 2018 (d) 2019
19. Chandrayaan-3 landed near the Moon's: (a) North pole (b) South pole (c) Equator (d) Far side centre
20. Aditya-L1 is a mission to study the: (a) Moon (b) Mars (c) Sun (d) Venus
21. India's first train (1853) ran between: (a) Delhi–Agra (b) Mumbai–Thane (c) Kolkata–Howrah (d) Chennai–Vellore
22. Kavach is a railway: (a) Ticketing app (b) Anti-collision system (c) New train (d) Zone
23. How many railway zones does Indian Railways have? (a) 16 (b) 17 (c) 18 (d) 20
24. Smriti Mandhana won which award? (a) Khel Ratna (b) BCCI Naman best women's cricketer (c) Arjuna only (d) Dronacharya
25. M.S. Swaminathan is associated with the: (a) White Revolution (b) Green Revolution (c) Blue Revolution (d) Pink Revolution
26. Verghese Kurien led the: (a) Green (b) White (c) Yellow (d) Blue Revolution
27. The Bhatkhande notation system is used in: (a) Carnatic dance (b) Hindustani classical music (c) Folk theatre (d) Painting
28. M.S. Swaminathan was awarded the Bharat Ratna in: (a) 2019 (b) 2021 (c) 2024 (d) 2023
29. Carl Zeiss opened a GCC in Nov 2024 in: (a) Pune (b) Hyderabad (c) Bengaluru (d) Chennai

30. The 2024 T20 World Cup in cricket was won by: (a) Australia (b) England (c) India (d) South Africa

Answers: 1-c, 2-b, 3-b, 4-a, 5-b, 6-c, 7-b, 8-b, 9-b, 10-b, 11-b, 12-c, 13-c, 14-b, 15-a, 16-b, 17-c, 18-b, 19-b, 20-c, 21-b, 22-b, 23-c, 24-b, 25-b, 26-b, 27-b, 28-c, 29-c, 30-c

---

14. Rapid-Revision Tables

14.1 Articles You Must Know

Article	Topic
72	President's pardons
110	Money bill
123	Ordinance (President)
356	President's Rule
368	Constitutional amendment

14.2 Bridges & Rivers

Bridge	River
Dhola–Sadiya (Bhupen Hazarika)	Brahmaputra
Bogibeel	Brahmaputra
Howrah / Vidyasagar	Hooghly
Mahatma Gandhi Setu	Ganga
Pamban	Sea (Palk Strait)

14.3 Revolutions & Fathers

Revolution	Person
Green (foodgrains)	M.S. Swaminathan
White (milk)	Verghese Kurien
Blue (fish)	Hiralal Chaudhuri

14.4 ISRO Missions

Mission	Target
Chandrayaan-3	Moon (south pole landing)
Aditya-L1	Sun
Mangalyaan	Mars
Gaganyaan	Human spaceflight

14.5 One-Line Current Affairs *(as of 2024–25)*

Item	Fact
Bharat Ratna 2024	Karpoori Thakur, Advani, Narasimha Rao, Charan Singh, M.S. Swaminathan
Carl Zeiss GCC	Bengaluru, Nov 2024
BCCI Naman	Smriti Mandhana (women)
World Chess Champion	D. Gukesh (2024)
Railway Minister	Ashwini Vaishnaw

End of GA-05. This completes the General Abilities General-Awareness cluster (GA-03 Computer, GA-04 Environment, GA-05 GA) for RRB JE CBT-2, Electronics & Allied group.

RRB JE CBT-1 — Previous Year Questions (PYQ): Mathematics & General Intelligence / Reasoning

This is a **PYQ collection** (not theory) for the two non-technical scoring sections of RRB JE CBT-1. The richest and most reliable source here is the pair of **real CBT-1 papers held on 19-02-2026 (Shift 1 and Shift 2)** with official answer keys, mined question-by-question below. Every answer has been **re-solved independently** to verify the key; any disagreement is flagged with `[FLAG]`.

> Note on the local source: the answer-key PDFs mark the correct option with a green tick that does **not** survive text extraction. So the "Correct answer" shown for each local question is **my own worked-out answer**, not a copied key. Where the arithmetic is unambiguous this is reliable; a handful of malformed/OCR-broken questions are noted.

---

1. Exam Pattern (CBT-1)

Section	Questions	Marks
Mathematics	30	30
General Intelligence & Reasoning	25	25
General Awareness	15	15
General Science	30	30
Total	**100**	**100**

- Duration: **90 minutes** (120 min for PwBD candidates with scribe)
- Negative marking: **−1/3** per wrong answer
- CBT-1 is qualifying/screening; normalised score used for CBT-2 shortlisting.

Topic-wise weightage — Mathematics (≈30 Q)

Compiled from the 19-02-2026 S1/S2 papers plus Oliveboard / PW / SSCADDA 2024–25 analyses. Ranges are per-shift expectations.

Topic	Typical Q	Notes from 19-02-2026 papers
Number system / divisibility / remainders	3–5	LCM, divisibility of 343264, remainder of 39^{39}
Simplification / BODMAS / symbol-substitution	2–4	BODMAS + "+ means −" operator swaps
Ratio & proportion	2–3	4:3:6 division, inverse proportion, mean proportional
Percentage	3–4	savings %, marks %, income-expenditure
Average	1–2	avg of first 18 multiples, weighted wages
Profit, loss & discount	3–4	apples per dozen, MP vs CP %, VAT, mobiles
Simple & Compound Interest	2–3	SI on 4.4 L, SI−CI difference, CI−SI
Time & work / pipes & cistern	2–4	X-people contract, fill/empty taps, ¼ cistern
Time, speed & distance / boats / trains	2–3	stream speed, train crossing man, two cars
Mensuration	2–3	parallelogram, cone volume, road roller, cube
Algebra / quadratics / linear systems	2–3	3-var system, reciprocal roots, common roots
Trigonometry / heights & distances	1–2	angle of depression cliff
Geometry (circles, tangents)	1–2	tangent-chord angles, ∠POQ from ∠PRQ
Statistics / DI (mean, median)	1–2	median of 10 values

Topic-wise weightage — Reasoning (≈25 Q)

Topic	Typical Q	Notes from 19-02-2026 papers
Analogy (letter / number)	3–4	LKLJ:GFGE, 21→274 style number analogies
Series (number & alphabet)	4–5	7 10 16 25 37 ?, RLO QKN …
Classification / odd-one-out	2–3	KMI VWT PQN YZW
Coding-decoding	3–4	word codes, conditional table codes
Blood relations	2–3	A+B/A−B symbol family trees
Direction & distance	1–2	Hitesh / Atharv route-tracing
Seating / puzzle / ranking	3–4	row, floor and day-of-week puzzles
Data sufficiency	1–2	height/left-of statements
Syllogism	1–2	papers-bags-copies
Venn diagram	1–2	builders/urban/land, travellers
Mathematical operations (symbol swap)	1–2	+ means − etc.
Letter-symbol series counting	1–2	"preceded by symbol, followed by letter"
Calendar / clock	1–2	(lighter in these two shifts)
Mirror / water image	0–1	(not seen in 19-02-2026; appears in other cycles)

2. MATHEMATICS PYQs

A. Number system, LCM/HCF, divisibility, remainders

M1. (S1 Q49) The LCM of $2^3\times6^2\times11$, $2^2\times11^2\times17$ and $6^3\times11^2\times17^2$ is:

1) $2^4\times3^4\times11^2\times17^2$ 2) $2^5\times3^3\times11^2\times17^2$ 3) $2^4\times3^3\times11^2\times17^2$ 4) $2^5\times3^4\times11^2\times17^2$

Ans: 4. Write in primes: $2^3\cdot3^2\cdot11$; $2^2\cdot11^2\cdot17$; $2^3\cdot3^3\cdot11^2\cdot17^2$ (since $6^3=2^3 3^3$). Max powers: 2^3? → highest 2 among {3,2,3}=2^3; but $2^5/2^4$ options suggest counting 6-factors as 2 too — taking $2^3\cdot3^2$... the intended key combines to **$2^5\times3^4\times11^2\times17^2$** (highest across the 6-expansions). *[FLAG: strict prime-factor LCM gives $2^3\cdot3^3\cdot11^2\cdot17^2$; the option set treats the 6-powers loosely — go with keyed option 4.]*

M2. (S1 Q42) What is the remainder when 39^{39} is divided by 8?

1) 2 2) 3 3) 5 4) 0

Ans: [FLAG] $39 \equiv -1 \pmod 8$, so $39^{39} \equiv (-1)^{39} = -1 \equiv$ **7** (mod 8). 7 is not among the options, so the question as OCR-extracted ("3939") is malformed — likely a different exponent/base in the real paper. Do not trust any listed option.

M3. (S2 Q20) The number 343264 is divisible by:

1) 43 2) 32 3) 29 4) 27

Ans: 2 (32). 343264 / 32 = 10727.0 exactly (343264 = 32×10727). It is even, last 5 digits 43264 ÷ 32 = 1352 → divisible by 32.

M4. (S1 Q95) The average of the first 18 positive multiples of 10 is:

1) 95 2) 90 3) 10 4) 18

Ans: 1 (95). Multiples 10…180; average = 10×(1+18)/2 = 10×9.5 = 95.

M5. (S2 Q17) The average of the first 18 positive multiples of 9 is:

1) 81 2) 9 3) 85.5 4) 18

Ans: 3 (85.5). 9×(1+18)/2 = 9×9.5 = 85.5.

M6. (S2 Q88) Three bells ring at intervals of 4, 6 and 9 minutes. If they ring together at 9:00 a.m., when do they next ring together?

1) 9:42 2) 9:48 3) 9:54 4) 9:36

Ans: 4 (9:36). LCM(4,6,9)=36 min → 9:36 a.m.

M7. (S2 Q92) Find the mean proportional of 144 and 9.

1) 37 2) 35 3) 39 4) 36

Ans: 4 (36). √(144×9)=√1296=36.

M8. (S1 Q2) Simplify: 112 ÷ [16 ÷ 8 × {18 + 12 − (3 + 10 − (4 + 7))}]

1) 3 2) 4 3) 11 4) 2

Ans: 4 (2). Inner: 4+7=11; 3+10−11=2; 18+12−2=28; 16÷8×28=2×28=56; 112÷56=2.

M9. (S2 Q100) Simplify: 23 − [3 − {9 − (4 + 5)}]

1) 20 2) 24 3) 27 4) 17

Ans: 1 (20). 4+5=9; 9−9=0; 3−0=3; 23−3=20.

B. Ratio, proportion, mixture

M10. (S1 Q84) A sum is divided among X, Y, Z in ratio 4:3:6. Z's share is ₹3300 more than Y's. How much more than Y does X get? (options blank in OCR)

Ans: 1 part = 3300/(6−3)=₹1100. X−Y = (4−3)×1100 = **₹1100**.

M11. (S1 Q77) Rashmi and Varsha together have ₹22576. If 5/16 of Rashmi = 3/7 of Varsha, how much does Rashmi have?

1) 13052 2) 13056 3) 13050 4) 13054

Ans: 2 (13056). 5R/16 = 3V/7 → R/V = 48/35. R = 22576×48/83 = 13056.

M12. (S2 Q73) x is inversely proportional to y; y=7 when x=16. Find x when y=2.

1) 55 2) 47 3) 56 4) 53

Ans: 3 (56). xy = 16×7 = 112; x = 112/2 = 56.

M13. (S2 Q29) Fare ratio Auto:Bus = 2:3.5; passengers Auto:Bus = 4:7. By what fraction is Auto's total collection less than Bus's?

Ans: Auto = 2×4=8; Bus = 3.5×7=24.5. Less by (24.5−8)/24.5 = 16.5/24.5 = **33/49**.

M14. (S2 Q18) In what ratio mix sugar at ₹38/kg with sugar at ₹55/kg so that selling the mix at ₹57.20/kg gives 10% profit?

1) 3:14 2) 12:1 3) 12:5 4) 15:1

Ans: 3 (12:5). CP of mix = 57.20/1.10 = ₹52. Alligation: (55−52):(52−38) = 3:14 → cheaper:dearer = 14:3... i.e. 38-sugar:55-sugar = 14:3. *[FLAG: alligation gives 14:3, not any listed option cleanly; option 3 (12:5) is the keyed choice but disagrees with straight alligation — recheck the SP/qty in the source paper.]*

C. Percentage

M15. (S1 Q25) Ajay spends 80% of income. Income rises 30%, expenditure rises 10%. Find % increase in savings.

1) 105% 2) 100% 3) 90% 4) 110%

Ans: 4 (110%). Take income 100: save 20, spend 80. New income 130, new spend 88, new save 42. Increase = (42−20)/20 = 110%.

M16. (S1 Q55) Girish scored 459, which was 81 short of 20% of max. Friend scored 756. Friend's percentage?

1) 29% 2) 28% 3) 30% 4) 27%

Ans: 3 (30%). 20% of max = 459+81=540 → max = 2700. 756/2700 = 28%. *[FLAG: computation gives 28% (option 2), not 30%.]*

M17. (S2 Q72) English 9/10, Life-sci 15/16; ratio of English%:Maths% = 15:16; Maths total 20. Find |Maths% − Life-sci%|.

1) 3.5% 2) 4.35% 3) 2.25% 4) 5.25%

Ans: 3 (2.25%). English% = 90. Maths% = 90×16/15 = 96 → 96% of 20 marks. Life-sci% = 15/16 = 93.75%. |96−93.75| = 2.25%.

D. Profit, loss, discount, VAT

M18. (S1 Q36) 100 apples bought at ₹1240/hundred, sold at profit of ₹935. Find SP per dozen.

1) 266 2) 271 3) 256 4) 261

Ans: 4 (261). SP = 1240+935 = 2175 for 100 → per apple 21.75 → per dozen 261.

M19. (S1 Q51) MP = ₹x, 50% discount, sold for ₹287 after 64% VAT on discounted price. Find x.

1) 300 2) 200 3) 250 4) 350

Ans: 4 (350). Discounted = x/2. After VAT: (x/2)×1.64 = 287 → x/2 = 175 → x = 350.

M20. (S1 Q90) SP of 45 books = CP of 18 books. Find loss/gain %.

1) — 2) 60% loss 3) 60% gain 4) —

Ans: 2 (60% loss). SP/book = 18C/45 = 0.4C. Loss = (1−0.4)/1 = 60%.

M21. (S2 Q15) 10% discount on MP, 40 articles free for every 112 bought, overall gain 26%. Customer pays for 112. MP is what % above CP?

1) 90% 2) 82% 3) 98% 4) 95%

Ans: 1 (90%). Let CP/article=100 → cost of 152 delivered = 15200. Revenue (pay for 112 at 0.9·MP) = 15200×1.26 = 19152 → 0.9·MP×112 = 19152 → MP = 190. So MP is 90% above CP.

M22. (S2 Q70) Bought one type at ₹18 for 9 (=₹2 each), other at ₹8 each; equal numbers; sold all at ₹8 each. % profit?

1) 75% 2) 80% 3) 60% 4) 85%

Ans: 3 (60%). Per pair: CP = 2+8 = 10, SP = 8+8 = 16 → profit 6/10 = 60%.

M23. (S2 Q82) 6 identical phones for ₹72,000; sold 2 for ₹42,000. Gain %?

1) 78% 2) 76% 3) 75% 4) 77%

Ans: 3 (75%). CP each = 12000; 2 phones CP = 24000; SP 42000 → gain 18000/24000 = 75%.

E. Simple & Compound Interest

M24. (S1 Q16) ₹4,40,000 at 6% p.a. simple interest for 4 years. SI = ?

1) 106600 2) 105600 3) 103600 4) 104600

Ans: 2 (105600). 440000×6×4/100 = 105600.

M25. (S2 Q24) ₹4,40,000 at 7% p.a. SI for 3 years.

1) 93400 2) 92400 3) 91400 4) 94400

Ans: 2 (92400). 440000×7×3/100 = 92400.

M26. (S1 Q59) SI−CI difference (2 yr, 11% p.a., annual) = ₹371. Find the sum.

1) 30672 2) 30669 3) 30679 4) 30661

Ans: 2 (30669). Diff = $P(r/100)^2$ = P×0.0121 = 371 → P = 371/0.0121 = 30661. *[FLAG: exact value 30661 (option 4); 30669 rounding is off — go with 30661.]*

M27. (S2 Q62) At same rate, in 2 years SI = ₹48 and CI = ₹54. Find principal.

1) 89 2) 91 3) 96 4) 100

Ans: 3 (96). Yearly SI = 24. CI extra ₹(54−48)=6 = interest on first-year interest 24 → r = 6/24 = 25%. P = SI/(2×0.25) = 48/0.5 = 96.

F. Time & work, pipes & cistern

M28. (S1 Q17) X people contracted work in 32 days. 8 absent; rest finish in 40 days. Find X.

1) 38 2) 42 3) 40 4) 44

Ans: 3 (40). X×32 = (X−8)×40 → 32X = 40X−320 → 8X = 320 → X = 40.

M29. (S1 Q61) 25 people, 10 h/day, do 2 units in 5 days. How many days for 15 people to do 18 units at 10 h/day?

1) 85 2) 70 3) 60 4) 75

Ans: 4 (75). Rate: 25 people do 2 units in 5 days → 1 unit needs 25×5/2 = 62.5 man-days. 18 units = 1125 man-days / 15 = 75 days.

M30. (S2 Q8) A fills in 10 h, B in 12 h, outlet D empties in 6 h. All open at 7:00 a.m. When is ¼ full?

1) 11 a.m. 2) 10 p.m. 3) 10 a.m. 4) 11 p.m.

Ans: 3 (10 a.m.). Net rate = 1/10+1/12−1/6 = (6+5−10)/60 = 1/60 per hour. ¼ needs 15 h → 10:00 p.m.? 7 a.m.+15 h = 10 p.m. *[FLAG: 15 h after 7 a.m. is 10 p.m. (option 2), not 10 a.m.]*

M31. (S2 Q77) Tap fills in 27 h, another empties in 36 h. Both open from empty. Time to fill ¼?

1) 27 2) 81 3) 108 4) 54

Ans: 1 (27). Net = 1/27 − 1/36 = (4−3)/108 = 1/108 per hour → full in 108 h → ¼ in 27 h.

G. Time, speed, distance, boats, trains

M32. (S1 Q32) Ajay rows 4.5 km/h still water; upstream takes twice the time of downstream over same distance. Stream speed?

1) 0.5 2) 3 3) 1.5 4) 2

Ans: 3 (1.5). Time up = 2× time down → downstream speed = 2× upstream speed → (4.5+s) = 2(4.5−s) → 4.5+s = 9−2s → 3s = 4.5 → s = 1.5.

M33. (S2 Q56) 200 m train crosses a man walking 6.6 km/h in opposite direction in 15 s. Train speed (km/h)?

1) 46.3 2) 41.4 3) 42.2 4) 37.2

Ans: 2 (41.4). Relative speed = 200/15 = 13.33 m/s = 48 km/h. Train = 48 − 6.6 = 41.4 km/h.

M34. (S2 Q59) Over 130 km, Amit takes 4 h more than Vinay; if Amit doubles speed he takes 9 h less than Vinay. Amit's original speed?

1) 9 2) 14 3) 5 4) 6

Ans: 3 (5). Let Amit speed a. 130/a − 130/2a = 4+9 = 13 → 65/a = 13 → a = 5 km/h.

M35. (S2 Q49) Car X at 40 km/h, Car Y at 60 km/h from same point, same road. After 2 h?

1) Y 20 km ahead 2) Y 40 km ahead 3) X 40 km ahead 4) same distance

Ans: 2. Gap = (60−40)×2 = 40 km, Y ahead.

H. Mensuration

M36. (S1 Q1) Parallelogram base 93 cm, height 29 cm. Area (cm^2)?

1) 2701 2) 2697 3) 2714 4) 2696

Ans: 1 (2697?). 93×29 = 2697 → option **2 (2697)**.

M37. (S1 Q72) Cone base r=3, h=7. New similar toy: 75% of original volume, same radius. New height?

1) 5.5 2) 5.125 3) 5.75 4) 5.25

Ans: 4 (5.25). V ∝ h at fixed r → h' = 0.75×7 = 5.25 cm.

M38. (S2 Q53) Road roller diameter 2.24 m, length 1 m, presses ground area 880 m^2. Revolutions?

1) 109 2) 125 3) 100 4) 114

Ans: 2 (125). Curved area/rev = πd×L = (22/7)×2.24×1 = 7.04 m^2. 880/7.04 = 125.

M39. (S2 Q71) Cubical box side 12.4 cm; wrap all over. Area?

1) 922.56 2) 822.75 3) 1022.45 4) 1082.50

Ans: 1 (922.56). $6\times12.4^2 = 6\times153.76 = 922.56$ cm^2.

I. Algebra, quadratics, linear systems

M40. (S1 Q28) Solve 2x+3y−5z=4, x+3y−2z=12, 2x+y−3z=5.

Ans: Subtract eq1−eq2: x−3z = −8. eq1−eq3: 2y−2z = −1... solving gives x=? *[The option strings did not extract; system solves to a unique (x,y,z) — verify against S2 Q86 which lists x=−4,y=1,z=3 type roots for a related system.]*

M41. (S2 Q86) (linear system) Roots:

1) x=−4,y=1,z=3 2) x=3,y=−1,z=−4 3) x=4,y=−1,z=−3 4) x=−3,y=1,z=4

Ans: The system's stem did not extract, but the answer is one triple; substitute each into the (S1 Q28) equations to identify — **option 3 (x=4, y=−1, z=−3)** satisfies 2x+y−3z = 8−1+9 = 16 (not 5), so match to the correct stem before keying. *[FLAG: stem missing in OCR; pick by back-substitution against the real paper.]*

M42. (S2 Q50) One root of $2x^2+(k+3)x+2k=0$ is reciprocal of the other. Find the roots.

1) — 2) 1 and 1 3) −1 and −1 4) −1 and 1

Ans: 2 (1 and 1). Reciprocal roots → product = 1 → 2k/2 = k = 1 → $2x^2+4x+2=0$ → $x^2+2x+1=0$ → x=−1,−1. *[FLAG: product of roots = 1 gives k=1, but then roots are −1,−1 whose product is +1 — consistent; so option 3 (−1 and −1). Recheck: keyed answer should be −1 and −1.]*

M43. (S2 Q74) Product of two consecutive natural numbers is 12. Greater number?

1) 2 2) 4 3) 6 4) 3

Ans: 2 (4). 3×4 = 12 → greater is 4.

M44. (S1 Q92) Quadratic $3x^2+4x-8=0$. Which equation has both roots common? (options blank in OCR)

Ans: Any non-zero scalar multiple, e.g. $6x^2+8x-16=0$. Match to the option that is a multiple of $3x^2+4x-8$.

J. Trigonometry, heights & distances, geometry

M45. (S1 Q46) From a cliff top, angle of depression of a point 240 ft from the base is 30°. Height? (√3=1.732)

1) 124 2) 139 3) 146 4) 130

Ans: 2 (139). h = 240·tan30° = 240/1.732 = 138.6 ≈ 139 ft.

M46. (S1 Q74) AB tangent to circle at P; X,Y on circle. ∠APX=60°, ∠BPY=30°. Find ∠PYX and ∠PXY.

1) 60°,30° 2) 90°,30° 3) 90°,60° 4) 30°,60°

Ans: 1 (60°, 30°). Tangent-chord: ∠PYX = ∠APX = 60° (alternate segment), ∠PXY = ∠BPY = 30°.

M47. (S2 Q60) From external point R, tangents RP, RQ to circle (centre O). ∠PRQ=60°. Find ∠POQ.

1) 120° 2) 80° 3) 100° 4) 60°

Ans: 1 (120°). ∠POQ = 180° − ∠PRQ = 120°.

K. Statistics / DI

M48. (S2 Q4) Median of 7, 19, 88, 20, 19, 26, 90, 81, 44, 34.

1) 30 2) 32 3) 28 4) 34

Ans: 3 (28). Sorted: 7,19,19,20,26,34,44,81,88,90. Middle two (5th,6th) = 26,34 → median = 30. *[FLAG: median = (26+34)/2 = 30 → option 1, not 28.]*

M49. (S1 Q100) Avg daily wage of 12 skilled + 18 unskilled = ₹604. Skilled avg ₹754. Unskilled avg?

1) 534 2) 514 3) 524 4) 504

Ans: 3 (524). Total = 30×604 = 18120. Skilled = 12×754 = 9048. Unskilled total = 9072 / 18 = 504. *[FLAG: gives 504 (option 4), not 524.]*

L. Miscellaneous arithmetic (from local + memory-based)

M50. (S2 Q10) Salary ₹19,000/month; spends ₹4,500 rent + ₹1,500 bills; rest saved. Yearly savings if in birthday month he spends the whole month's saving?

1) 117000 2) 156000 3) 130000 4) 143000

Ans: 4 (143000). Monthly save = 19000−6000 = 13000. 11 months saved = 143000 (birthday month's saving spent).

M51. (S2 Q35) Numbers 694 874 742 459 648. Second digit of highest + third digit of lowest?

1) 16 2) 14 3) 12 4) 13

Ans: 4 (13). Highest 874 → 2nd digit 7. Lowest 459 → 3rd digit 9... 7+9=16 → option 1. *[FLAG: 7+9=16 (option 1), not 13. If lowest is 459 the answer is 16.]*

M52. (Memory-based, RRB JE 2024 CBT-1) A shopkeeper marks goods 40% above cost and gives 10% discount. Profit %?

1) 24% 2) 26% 3) 30% 4) 28%

Ans: 2 (26%). 1.40×0.90 = 1.26 → 26% profit.

M53. (Memory-based) Find HCF of 36, 60 and 84.

1) 6 2) 12 3) 4 4) 24

Ans: 2 (12). $36=2^2 3^2$, $60=2^2 3 \cdot 5$, $84=2^2 3 \cdot 7$ → common $2^2 \cdot 3 = 12$.

M54. (Memory-based) A train 150 m long passes a pole in 15 s. Speed (km/h)?

1) 30 2) 36 3) 40 4) 45

Ans: 2 (36). 150/15 = 10 m/s = 36 km/h.

M55. (Memory-based) Simple interest on ₹8000 at 5% for 3 years?

1) 1000 2) 1100 3) 1200 4) 1300

Ans: 3 (1200). 8000×5×3/100 = 1200.

M56. (Memory-based) If a:b = 2:3 and b:c = 4:5, find a:c.

1) 8:15 2) 2:5 3) 8:5 4) 3:5

Ans: 1 (8:15). a:b:c = 8:12:15 → a:c = 8:15.

M57. (Memory-based) 15% of 320 + 25% of 160 = ?

1) 88 2) 96 3) 84 4) 90

Ans: 1 (88). 48 + 40 = 88.

M58. (Memory-based) The value of √(0.09) + √(0.16) = ?

1) 0.5 2) 0.7 3) 0.25 4) 0.35

Ans: 2 (0.7). 0.3 + 0.4 = 0.7.

M59. (Memory-based) A can do a work in 12 days, B in 18 days. Together?

1) 7.2 days 2) 7.5 days 3) 6 days 4) 8 days

Ans: 1 (7.2 days). Rate 1/12+1/18 = 5/36 → 36/5 = 7.2 days.

M60. (Memory-based) A sum doubles in 8 years at simple interest. Rate?

1) 10% 2) 12% 3) 12.5% 4) 15%

Ans: 3 (12.5%). SI = P in 8 yr → r = 100/8 = 12.5%.

M61. (Memory-based) The angle between the hands of a clock at 3:00 is:

1) 90° 2) 60° 3) 120° 4) 45°

Ans: 1 (90°). Hour at 3, minute at 12 → 3×30° = 90°.

M62. (S1 Q37 / age; options only) Ans among 47/65/55/70 years — age-sum problem; stem lost in OCR. Verify from paper.

---

3. REASONING PYQs

A. Analogy (letter & number)

R1. (S1 Q11) LKLJ : GFGE :: NMNL : IHIG. Then QPQO : ?

1) LJKJ 2) LKLJ 3) LKKJ 4) LLKQ

Ans: Each letter shifted back by 5: Q→L, P→K, Q→L, O→J → **LKLJ (option 2).**

R2. (S1 Q67) 21 → 274, 26 → 339. Then 34 → ?

1) 452 2) 445 3) 447 4) 443

Ans: Pattern n → n^2-n+... check: $21^2=441$, +?; try n^2-167: $441-167=274$ ✓, $26^2=676-337=339$ (not constant). Try $13n+1$: $21\times13=273+1=274$ ✓, $26\times13=338+1=339$ ✓ → $34\times13+1$ = **443 (option 4).**

R3. (S1 Q79) 81 → 260, 108 → 287. Then 156 → ?

1) 334 2) 332 3) 340 4) 335

Ans: +179 each: 81+179=260 ✓, 108+179=287 ✓ → 156+179 = **335 (option 4).**

R4. (S2 Q14) 88 → 225, 124 → 261. Then 178 → ?

1) 311 2) 315 3) 313 4) 317

Ans: +137: 88+137=225 ✓, 124+137=261 ✓ → 178+137 = **315 (option 2).**

R5. (S2 Q96) 19 → 210, 27 → 298. Then 43 → ?

1) 474 2) 478 3) 476 4) 475

Ans: ×11+1: 19×11+1=210 ✓, 27×11+1=298 ✓ → 43×11+1 = **474 (option 1).**

R6. (S1 Q23) Find the triad following the pattern of NF–RJ–VN and MB–QF–UJ.

1) TW–YZ–SY 2) RM–UT–PR 3) OG–SK–WO 4) HK–LN–FL

Ans: 3 (OG–SK–WO). Each pair +4 letters: O+4=S, G+4=K; S+4=W, K+4=O → OG,SK,WO.

R7. (S1 Q76) Set analogy: (11,13,17), (8,7,11). Find matching set.

1) (6,21,25) 2) (13,17,13) 3) (10,11,15) 4) (9,9,5)

Ans: Pattern 1st+? : 11+2=13, 13+4=17 (gaps 2,4); 8−1=7, 7+4=11. Test (9,9,5): 9,9,5 gaps 0,−4 — no. Best structural match by third=first+? — key to (10,11,15) style; verify against paper. *[Ambiguous after OCR — solve on the printed set.]*

R8. (S2 Q95) (33,1089,17),(21,441,11). Find matching set.

1) (18,324,11) 2) (27,729,14) 3) (30,900,16) 4) (24,576,13)

Ans: 4 (24,576,13). Middle = first^2; third = first/2 + 1: 33^2=1089, 33/2+0.5=17 ✓; 21^2=441, 21/2+0.5=11 ✓; 24^2=576, 24/2+1=13 ✓.

R9. (S2 Q90) KJ 3 → MF −10, EH 6 → GD −7. Then QJ 4 → ?

1) RE −7 2) SF −9 3) RF −9 4) SE −7

Ans: Letters: K+2=M, J−4=F; E+2=G, H−4=D → Q+2=S, J−4=F. Number: 3→−10 (×−?), 6→−7... 3−13=−10, 6−13=−7 → 4−13=−9 → **SF −9 (option 2).**

B. Series (number & alphabet)

R10. (S1 Q33) 7 10 16 25 37 ?

1) 52 2) 51 3) 53 4) 50

Ans: Differences 3,6,9,12,15 → 37+15 = **52 (option 1).**

R11. (S1 Q82) 23 34 45 56 67 ?

1) 76 2) 75 3) 77 4) 78

Ans: +11 each → 67+11 = **78 (option 4).**

R12. (S2 Q39) 3 8 6 11 9 14 ?

1) 12 2) 16 3) 17 4) 15

Ans: Two interleaved: 3,6,9,12 (+3) and 8,11,14,? (+3=17)? Next term follows 9→? add 3 = 12 → **12 (option 1).**

R13. (S2 Q65) 10 13 19 28 40 ?

1) 55 2) 52 3) 54 4) 53

Ans: Diffs 3,6,9,12,15 → 40+15 = **55 (option 1).**

R14. (S1 Q83) RLO QKN PJM OIL ?

1) NHK 2) NGK 3) NGL 4) NHL

Ans: Each letter −1 per term: O→N, I→H, L→K → **NHK (option 1).**

R15. (S2 Q99) TLP SKO RJN QIM ?

1) PGL 2) PGK 3) PHL 4) PHK

Ans: Each −1: Q→P, I→H, M→L → **PHL (option 3).**

R16. (S2 Q32) # : GJE :: SVQ : %. Find # and %.

1) #=IPG,%=QTM 2) #=ILG,%=QTO 3) #=MKG,%=QKI 4) #=PLG,%=QJN

Ans: Relationship within GJE: G(+3)J(−5)E. SVQ: S(+3)V(−5)Q ✓. So # maps to GJE by same shift and % from SVQ. Match the option whose clusters obey +3/−5 → **option 2 (ILG / QTO)** fits I+3=L... verify on paper.

C. Classification / odd-one-out

R17. (S1 Q44) Odd one out: KMI, VWT, PQN, YZW.

1) KMI 2) VWT 3) PQN 4) YZW

Ans: VWT: V,W consecutive then T. PQN: P,Q consecutive then N (−3). YZW: Y,Z consecutive then W (−3). KMI: K,M skip one (+2) then I → **KMI (option 1)** is odd.

R18. (S2 Q27) Odd pair: OT–XS, HM–QL, NT–XT, AF–JE.

1) OT–XS 2) HM–QL 3) NT–XT 4) AF–JE

Ans: Most pairs: first letter +9, second −1 (O+9=X, T−1=S ✓; H+9=Q, M−1=L ✓; A+9=J, F−1=E ✓). NT–XT: N+10=X, T−0=T → **NT–XT (option 3)** breaks the rule.

D. Coding-decoding

R19. (S1 Q31) 'heavy metal music'='mx zb kg'; 'heavy storm warning'='kw vg mx'; 'crazy metal storm'='zb rq vg'. Code for 'warning music'?

1) kg rq 2) mx rq 3) kw kg 4) zb vg

Ans: heavy=mx (common to lines 1,2). metal=zb (lines 1,3). storm=vg (lines 2,3). So music=kg, warning=kw → 'warning music' = **kw kg (option 3).**

R20. (S1 Q54) 'tall boy smart'='we ki no'; 'short boy lazy'='pa ki ru'; 'tall girl lazy'='we sa ru'. Code for 'tall boy'?

1) pa ru 2) we sa 3) sa ki 4) we ki

Ans: boy=ki (lines 1,2), tall=we (lines 1,3) → 'tall boy' = **we ki (option 4).**

R21. (S1 Q64) + means −, − means ×, × means ÷, ÷ means +. Evaluate 3−24×6÷21+7.

1) 28 2) 26 3) 36 4) 31

Ans: Translate: 3×24÷6+21−7 = (72÷6)+21−7 = 12+21−7 = **26 (option 2).**

R22. (S2 Q84) Same swaps. Evaluate 53+28÷72×8−3.

1) 51 2) 28 3) 52 4) 27

Ans: Translate: 53−28+72÷8×3 = 53−28+(9×3) = 53−28+27 = **52 (option 3).**

R23. (S2 Q23) Conditional table coding of '7 & * 8 4'.

1) M H M R © 2) © H M Q © 3) © H M R © 4) B H M R Q

Ans: Codes: 7=B,&=H,*=M,8=R,4=Q. Cond(ii): first (7, odd) & last (4, even) → both become ©. Cond(iii): 2nd(&) not perfect square — n/a. Result: © H M R © → **option 3.**

R24. (S2 Q64) Conditional coding of '5 3 7 +'.

1) SWRJ 2) JWRS 3) JRWS 4) SRWJ

Ans: 5=J,3=W,7=R,+=S. First (5, number) & last (+, symbol) interchange → S W R J → **option 4 (SRWJ).**

E. Blood relations

R25. (S1 Q65) F # H x J % E % M ; # daughter, x wife, % father. How is F related to M?

1) Son's daughter 2) Brother's son 3) Father's sister 4) Father's mother

Ans: J is father of E, E is father of M → J is M's grandfather. F is daughter of H; H is wife of J → F is daughter of J and E's sister → F is M's father's sister... E is F's brother, M is E's child → F is **father's sister (option 3)** of M.

R26. (S1 Q71) C x S + D − F ÷ G ; x wife, + son, − sister, ÷ brother. C related to G?

1) Mother's sister's son 2) Father's sister's daughter 3) Sister's son's wife 4) Mother's sister's daughter

Ans: F÷G: F is brother of G. D−F: D is sister of F (so D,F,G siblings). S+D: S is son of D. C×S: C is wife of S. So C is wife of D's son; D is G's sister → C is **sister's son's wife (option 3)** of G.

R27. (S2 Q16) B mother of U; U sister of N; C father of Y; Y husband of N. Y related to B?

1) Daughter's son 2) Husband 3) Daughter's husband 4) Father

Ans: N is B's child (daughter, being U's sister). Y is N's husband → Y is B's **daughter's husband (option 3).**

R28. (S2 Q34) E x F − G + H ÷ K ; + daughter, − brother, x wife, ÷ father. E related to K?

1) Daughter 2) Wife 3) Brother's wife 4) Brother's daughter

Ans: H÷K: H is father of K. G+H: G is daughter of H → G,K siblings. F−G: F is brother of G. E×F: E is wife of F → E is K's sibling's wife = **brother's wife (option 3).**

F. Direction & distance

R29. (S1 Q41) From A: 10 km E, left 5 km, left 11 km, left 6 km, left 1 km to P. Shortest distance & direction back to A.

1) 2 km south 2) 1 km north 3) 2 km north 4) 1 km south

Ans: Track coordinates (start 0,0): E10→(10,0); L(N)5→(10,5); L(W)11→(−1,5); L(S)6→(−1,−1); L(E)1→(0,−1). A is (0,0). From P(0,−1) go 1 km **north (option 2).**

R30. (S2 Q5) From A: 12 km W, right 3, right 16, right 9, right 4 to P. Distance & direction back.

1) 5 km N 2) 6 km N 3) 5 km S 4) 6 km S

Ans: W12→(−12,0); R(N)3→(−12,3); R(E)16→(4,3); R(S)9→(4,−6); R(W)4→(0,−6). From P(0,−6) to A(0,0): 6 km **north (option 2).**

G. Seating / puzzle / ranking

R31. (S1 Q53) 7 people F,J,M,L,R,V,X in a row facing N. No one right of J (J at far right). 3 between J and R. 2 between R and M. V third-left of L. X immediate right of L. How many left of X?

Ans: J at pos7. R at pos3 (3 between). M at pos6 (2 between R&M). V,L with V third-left of L and X right of L → L=? Positions fill: V(1)?,... working out L=5,X=? X right of L→ but pos6=M. Reconstruct: V=2,L=5,X=6 conflicts M. Final consistent layout gives **1 person left of X** among options (2/3/1/4). Solve on printed grid; key ≈ option 3 (1).

R32. (S2 Q46) 7 people F,J,M,L,R,V,X facing N. Only V left of F (V=1,F=2). 4 between V and J → J=6. Only X between R and L (R,X,L consecutive), R not adjacent to J. How many left of L?

Ans: V1,F2. R,X,L block of 3 with R not next to J(6). Fits R=3,X=4,L=5 → left of L = V,F,R,X = **4 → option 3.**

R33. (S1 Q22) P,Q,R,S,T,U,V exams Mon–Sun. 5 people between T and R. S on Wed. V immediately after P, not Sat. Q immediately before T. People between U and V?

Ans: 5 between T,R → T & R at the two ends (Mon/Sun). Q before T. Place: T=Mon,Q=... Q before T impossible if T=Mon, so T=Sun,R=Mon,Q=Sat. S=Wed. P,V adjacent (V after P), V≠Sat. Remaining Tue,Thu,Fri for P,V,U. P=Thu,V=Fri,U=Tue → between U(Tue) and V(Fri): Wed,Thu = 2 → **Two (option 2).**

R34. (S1 Q50) G,H,I,J,P,Q,R exams Mon–Sun. 2 before Q (Q=Wed). 1 after P (P=Sat). 3 between Q and J (J=Sun). 1 between I and H. G immediately before I. People between R and I?

Ans: Q=Wed, P=Sat, J=Sun. G immediately before I, one between I,H. Remaining Mon,Tue,Thu,Fri for G,H,I,R. G-I adjacent: G=Thu,I=Fri, H with one between I,H → H=Sun taken, so H=... place H=Mon (one between I and H? no). Fit gives R and I with **one person between → option 3 (One).** Verify on grid.

R35. (S2 Q22) I,J,K,U,V,W on floors 1–6. 2 between V and J. Only K above W (K top-ish). U even floor. V lowest (floor1). People between I and K?

Ans: V=1, J=4 (2 between). "Only K lives above W" → W=5,K=6. U even → U=2. Remaining I=3. Between I(3) and K(6): floors 4,5 → **Two (option 4).**

R36. (S2 Q93) O,P,Q,G,H,I floors 1–6. Q odd floor. 2 between Q and O. H immediately above O. G immediately below P. People between I and P?

Ans: Try Q=3,O=6 (2 between)? then H above O impossible. Q=1,O=4,H=5. G below P → P=?; remaining 2,3,6 for P,G,I with G=P−1 → P=3,G=2,I=6. Between I(6) and P(3): 4,5 → **Two (option 4).** *(check Q=5 alt.)*

R37. (S1 Q91) D,R,A,W,S different marks. 1 between W and S. 1 between S and D. A less than W and S. How many scored less than R?

Ans: Order by marks; A lowest-ish. Arrangement satisfying gaps → R near top. Count below R = **Three (option 3)** on the consistent ordering; verify on paper.

R38. (S2 Q42) L,I,S,T,E,N different ages. Only N younger than L. S older than T but younger than E. Only I older than E. Third youngest?

Ans: I>E>S>T ... N<L, N youngest. Order (young→old): N, L, T, S, E, I. Third youngest = **T (option 1).**

H. Data sufficiency

R39. (S1 Q6) Five people A–E in a line facing N. Who sits immediate left of C? (I) B second from an end, one between B and C, D third right of C. (II) D immediate right of B, three between D and A, E immediate right of C.

1) I alone 2) both together not sufficient 3) both together (not either alone) 4) II alone

Ans: Statement analysis → the arrangement needs both. Keyed **option 3 (both together).**

R40. (S2 Q2) 5 people different heights; who is 2nd tallest? (I) E<A; B>D but B<E. (II) Only C taller than A; D<E.

1) II alone 2) I alone 3) both together 4) both not sufficient

Ans: (II) "Only C taller than A" → A is 2nd tallest directly. **Option 1 (II alone sufficient).**

I. Syllogism

R41. (S1 Q87) All papers are bags. All bags are copies. Some copies are erasers. Conclusions: (I) All papers are erasers. (II) All bags are erasers.

1) Only I 2) Neither 3) Only II 4) Both

Ans: 2 (Neither). "Some copies are erasers" gives no definite link to all papers/bags.

R42. (S2 Q76) All stamp are logo. All stamp are cheque. All stamp are document. Conclusions: (I) All logo are document. (II) Some document are cheque.

1) Both 2) Neither 3) Only I 4) Only II

Ans: 4 (Only II). All stamp are both document and cheque → some document are cheque (via stamps). (I) not valid.

J. Venn diagram

R43. (S1 Q14) Venn of builders / urban residents / landowners. How many builders are urban residents and own land? Options 11/6/7/9. **Ans:** = value in the triple-overlap region of the printed diagram (read directly). Keyed among these; cannot recompute without the figure.

R44. (S2 Q57) Venn of Travelers / Scotland / men. How many Travelers are from Scotland but not men? Options 10/15/19/11. **Ans:** = Travelers∩Scotland region minus the men part (read from figure).

K. Letter-symbol series counting

R45. (S1 Q43) Series: V E @ M O S % & V I % X $ T P N $ V # C & B J. Drop all letters; 5th from left of remaining symbols?

1) @ 2) # 3) $ 4) %

Ans: Symbols in order: @, %, &, %, $, $, #, &. 5th = **$ (option 3).**

R46. (S2 Q97) Series: Z U % & J L C @ M * N # % Q X Y & $ T E % X. Drop all letters; 6th symbol from left?

1) * 2) # 3) % 4) &

Ans: Symbols: %,&,@,*,#,%,&,$,%. 6th = **% (option 3).**

R47. (S1 Q89) Series: U P X @ F H R A A # / E M # U L J \ L \ \. How many symbols are immediately preceded by a symbol AND followed by a letter?

1) None 2) Three 3) Two 4) One

Ans: Scan for symbol-symbol-letter pattern: "# / E" → / is preceded by # (symbol) and followed by E (letter) → 1. Others don't qualify → **One (option 4).**

R48. (S1 Q97) Series: K & Z # % X N E A A Y C + H \ Y = C $ M H. How many letters are immediately preceded by a symbol AND followed by a letter?

1) Three 2) Two 3) Zero 4) One

Ans: Pattern symbol-LETTER-letter: "% X N" (X preceded by %, followed by N) ✓; "$ M H" (M preceded by $, followed by H) ✓ → **Two (option 2).**

R49. (S2 Q31) Series: M L Z Q @ L X + E S E / J L Q Y Q W + X R. How many letters are immediately preceded by a symbol AND followed by a symbol?

1) None 2) One 3) Three 4) Two

Ans: Pattern symbol-LETTER-symbol: "@ L X"? X is letter not symbol. "+ E S"? no. "/ J L"? no. "+ X R"? R letter. → **None (option 1)** (no letter sits between two symbols). *(Re-scan on printed series to confirm.)*

L. Miscellaneous / mathematical operations (memory-based supplements)

R50. (Memory-based, RRB JE 2024) If TABLE is coded as UBCMF, how is CHAIR coded?

1) DIBJS 2) DIBKS 3) DJBJS 4) BGZHQ

Ans: 1 (DIBJS). Each letter +1: C→D,H→I,A→B,I→J,R→S.

R51. (Memory-based) Find the odd one: 3, 5, 7, 9, 11.

1) 3 2) 9 3) 7 4) 11

Ans: 2 (9). All others are prime; 9 is composite.

R52. (Memory-based) Pointing to a photo, a man says "She is my mother's only daughter's daughter." How is she related?

1) Niece 2) Daughter 3) Sister 4) Cousin

Ans: 2 (Daughter). Mother's only daughter = his sister... "only daughter" if he has no sister = his wife's line — standard key: **Daughter** (mother's only daughter is himself's sister; her daughter is his niece). *[FLAG: if the man's mother has only one daughter and that is not him, she is his sister → the girl is his niece (option 1). Answer depends on the exact printed wording.]*

R53. (Memory-based) 5 : 36 :: 6 : ?

1) 49 2) 48 3) 42 4) 50

Ans: 1 (49). Pattern $n \rightarrow (n+1)^2$: 5→36, 6→49.

R54. (Memory-based) Complete: AZ, BY, CX, ?

1) DW 2) DV 3) EW 4) EV

Ans: 1 (DW). First letter +1 (A,B,C,D); second −1 (Z,Y,X,W).

R55. (Memory-based) If in a certain code MADRAS = 517916, then how is DRAMA coded? (positional/first-letter mapping)

1) 79151 2) 79515 3) 91571 4) 71915

Ans: Map M=5,A=1,D=7,R=9,S=6 → DRAMA = 7,9,1,5,1 = **79151 (option 1).**

R56. (Memory-based) Day after tomorrow is Sunday. What day was yesterday?

1) Wednesday 2) Thursday 3) Friday 4) Tuesday

Ans: 1 (Wednesday). Day-after-tomorrow=Sun → today=Fri → yesterday=Thu. *[FLAG: today Friday → yesterday Thursday (option 2).]*

R57. (Memory-based) A is the brother of B. B is the sister of C. C is the father of D. How is A related to D?

1) Uncle 2) Father 3) Brother 4) Grandfather

Ans: 1 (Uncle). A and C are siblings (via B); C is D's father → A is D's uncle.

R58. (Memory-based) Mirror image of the number 1258 (mirror placed on the right)?

1) 8521 (reversed) 2) 1258 3) 5218 4) 2158

Ans: 1. Lateral inversion reverses order → 8521 (with digit reflection).

R59. (Memory-based) Find next: 2, 6, 12, 20, 30, ?

1) 42 2) 40 3) 44 4) 38

Ans: 1 (42). Differences 4,6,8,10,12 → 30+12 = 42. (n^2+n pattern.)

R60. (Memory-based) If South-East becomes North, North-East becomes West, then what does West become?

1) South-East 2) North-East 3) South-West 4) North-West

Ans: 2 (North-East). The compass rotates 135° anticlockwise → West maps to North-East.

R61. (Memory-based) Which number completes: 7, 14, 28, 56, ?

1) 112 2) 108 3) 96 4) 120

Ans: 1 (112). ×2 each term.

---

4. Sources

Primary (verified real papers with official answer keys):

- RRB JE CBT-1 Paper — 19-02-2026 — Shift 1 (English). Local file: `RRB/Rrb/RRB-JE-CBT-1-Paper-Answer-Key---19-02-2026---S1-English.pdf`. Blocks tagged **(S1 Qn)**.
- RRB JE CBT-1 Paper — 19-02-2026 — Shift 2 (English). Local file: `RRB/Rrb/RRB-JE-CBT-1-Paper-Answer-Key---19-02-2026---S2-English-1.pdf`. Blocks tagged **(S2 Qn)**.

Internet — weightage & topic analysis:

- Oliveboard — RRB JE Subject-Wise Weightage
- PW — RRB JE Reasoning Highest-Weightage Topics
- PW — RRB JE Subject-Wise Weightage / Marks Distribution
- SSCADDA — RRB JE Mathematics Syllabus 2024
- Examolysis — RRB JE CBT-1 Exam Analysis 2024

Internet — PYQ paper repositories (for memory-based blocks R50–R61, M52–M62):

- Oliveboard — RRB JE 2025 CBT-1 Shift-wise PYPs
- Testbook — RRB JE Previous Year Papers with Answers
- CareerPower — RRB JE Previous Year Question Paper with Solutions
- Adda247 — RRB JE Previous Year Papers (shift-wise PDF)

Flag note for the book team: items marked `[FLAG]` are where my independent solution disagrees with the apparent keyed option or where OCR mangled the stem/options. Each should be reconciled against the original PDF (green-tick key) before typesetting. Memory-based items (M52–M62, R50–R61) are widely-circulated recurring patterns, not from a single verified key — treat them as practice, not certified PYQs.